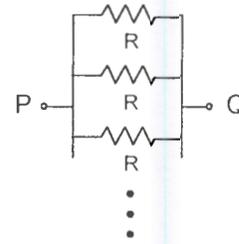


Short Answer Questions (15 pts):

1. As more identical resistors R are added to the parallel circuit shown here, what happens to value of the equivalent resistance, R_{eq} , between terminals P and Q? (4 pts)



- a. R_{eq} increases
- b. R_{eq} remains the same
- c. R_{eq} decreases

$$\frac{1}{R_{eq}} = \sum_i^n \left(\frac{1}{R_i} \right)$$


IF THIS GETS BIGGER AS $n \uparrow$, $R_{eq} \downarrow$

2. Circle T (true) or F (false) for the following statements (3 pts):

- T F Decreasing the diameter of a conductor increases its resistance. $R = \rho L/A$
- T F kWh and Joules are both measures of energy.
- T F Voltmeters are connected in ~~series~~ parallel to measure the voltage across an element.

3. The circuit below consists of two identical light bulbs and a single 12 V battery. The light bulbs can be modeled as resistors each with equal resistance. When the switch is closed, what happens at bulb A? (4 pts)

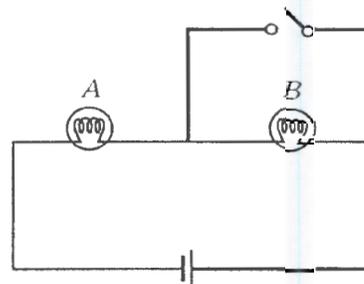
- a. current through bulb A increases and it glows more brightly
- b. current through bulb A remains unchanged and its brightness remains unchanged
- c. current through bulb A decreases and it glows more dimly



$R \downarrow$ so $I \uparrow$

4. An ideal ammeter A is connected between points a and b in the bridge circuit below, in which the four resistors are identical. The value of the total current supplied by the battery is I . What value of current will be measured through the ammeter? (4 pts)

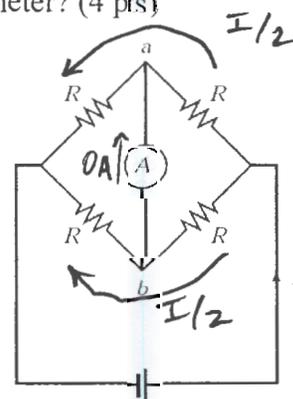- a. $I/2$
- b. $I/4$
- c. zero
- d. need more information to answer the question




2R IN EACH BRANCH, CURRENT SPLITS EVENLY

Short Answer Problems (20 pts):


1. In the linear DC circuit below, the output voltage across a $500\ \Omega$ load is 2.0V . Using the same circuit, maximum power is delivered to the load when $R_L = 1500\ \Omega$. What is the value of the maximum power that is delivered to a load resistor of $R_L = 1500\ \Omega$? (10 pts)

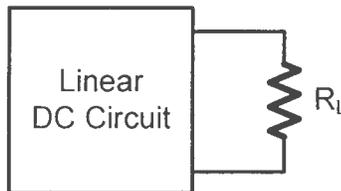- a. $0.5\ \text{mW}$
- b. $0.67\ \text{mW}$
- c. $2\ \text{mW}$
- d. $10.67\ \text{mW}$**
- e. Cannot be determined



$R_{TH} = 1500\ \Omega$

THEV EQ

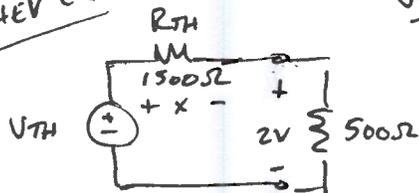

V-DIV

$$\frac{x}{1500} = \frac{2\text{V}}{500}$$



$$x = 6\text{V}$$

$$V_{TH} = 6 + 2 = 8\text{V}$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

$$= \frac{(8)^2}{4(1500)} = 10.67\ \text{mW}$$

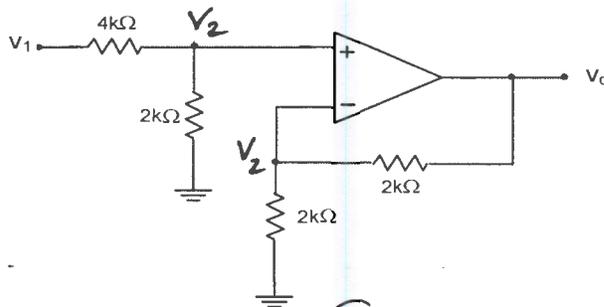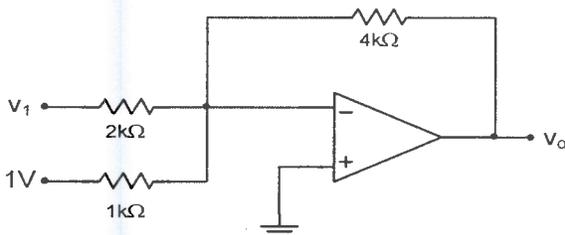2. Answer the following for the two circuits below. (10 pts)



A

OR

B

a) (Fill in the blanks with the best answer.) Circuits A and B are configured as _____ and _____ amplifiers, respectively. (4 pts)

- I. inverting, non-inverting
- II. inverting, summing
- III. non-inverting, inverting
- IV. non-inverting, summing
- V. summing, inverting
- VI. summing, non-inverting**

b) If $v_o = 6\text{V}$ in each of the circuits, solve for v_1 in only ONE of the circuits A or B above. Clearly indicate which circuit was chosen by circling either letter A or letter B for that circuit. (6 pts)

CKT A

$$v_o = 6 = v_1 \left(\frac{-4\text{k}}{2\text{k}} \right) + 1 \left(\frac{-4\text{k}}{1\text{k}} \right)$$

$$= -2v_1 - 4$$

$$10 = -2v_1$$

$$\boxed{v_1 = -5\text{V}}$$

CKT B


$$v_2 = v_o \cdot \frac{2\text{k}}{4\text{k}} = \frac{1}{2} v_o = \frac{1}{2} 6 = 3\text{V}$$

$$\text{Also } v_2 = v_1 \cdot \frac{2\text{k}}{6\text{k}} = 3 \text{ so } v_1 = 3 \cdot 3$$

$$\text{OR } \boxed{v_1 = 9\text{V}}$$


Problems (65 pts):

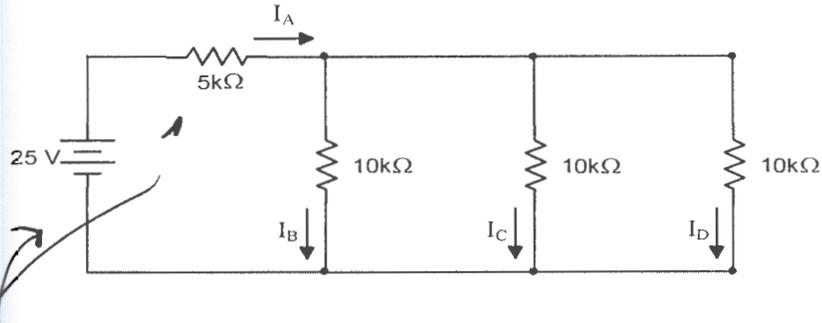1. In the circuit shown below, use **source transformation** and **current dividers** to determine the currents I_A , I_B , I_C and I_D . (20 pts)



$$\frac{25V}{5k\Omega} = 5mA$$

NOTE: $I_A = I_B + I_C + I_D$

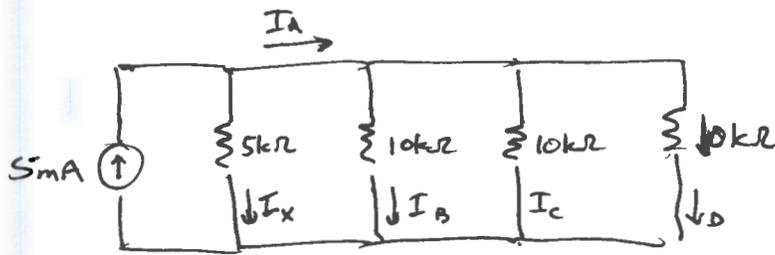

I-DIV $I_B = I_C = I_D$ AND $I_x = 2I_B$

SINCE $5mA = I_x + I_B + I_C + I_D$

$$I_B = I_C = I_D = \underline{1mA} \rightarrow I_A = I_B + I_C + I_D = \underline{\underline{3mA}}$$

$$I_x = 2mA$$


$I_A = \underline{3mA}$

$I_B = \underline{1mA}$


$I_C = \underline{1mA}$

$I_D = \underline{1mA}$

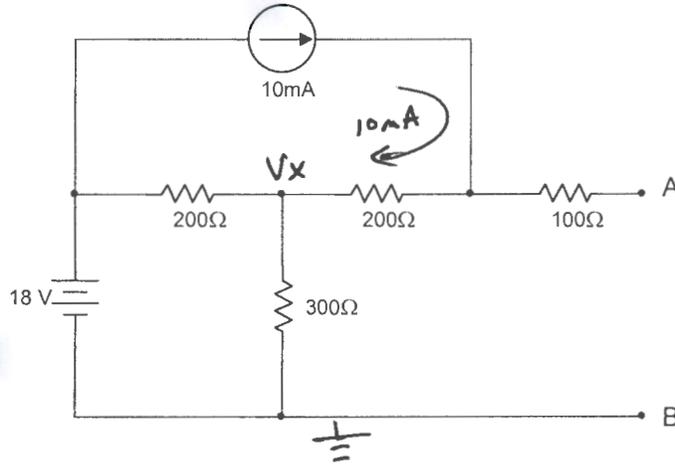2. For the circuit shown below, **determine and draw** the Thevenin equivalent circuit between terminals A and B. (Hint: Use superposition or nodal analysis to solve for V_{TH} .) (20 pts)





R_{TH}

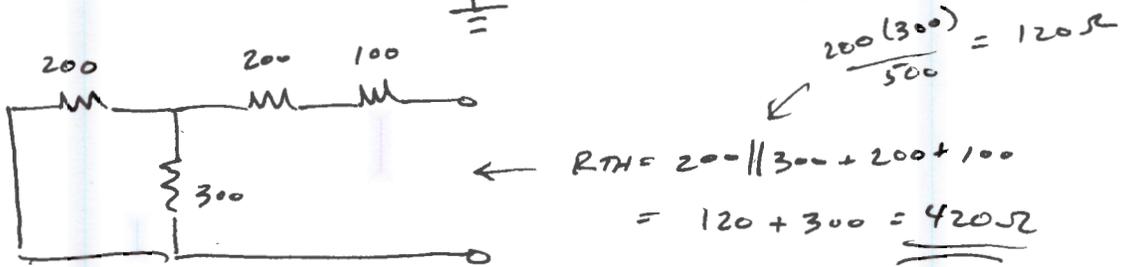

V_{TH}

SUPERPOSITION

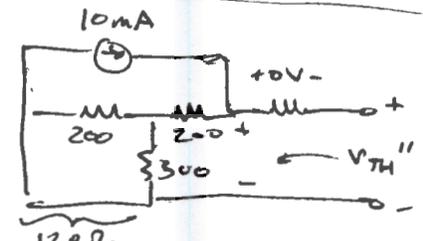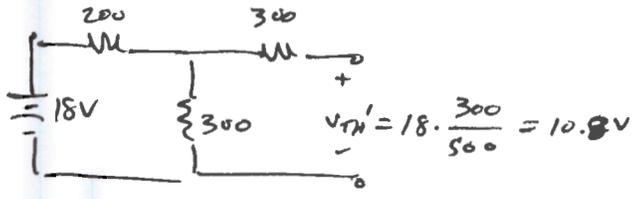

$V_{TH} = V_{TH}' + V_{TH}'' = 10.8 + 3.2 = 14V$


OR NODAL - SEE LABELS ON ORIGINAL CKT

$\left(\frac{18 - V_x}{200} + 10mA = \frac{V_x}{300} \right) 600$

$54 - 3V_x + 6 = 2V_x$

$60 = 5V_x \quad V_x = 12V$


$V_{TH} = 12 + 0.01(200) = 14V$

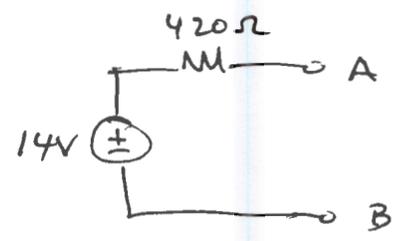

$V_{TH} = 14V$

$R_{TH} = 420 \Omega$

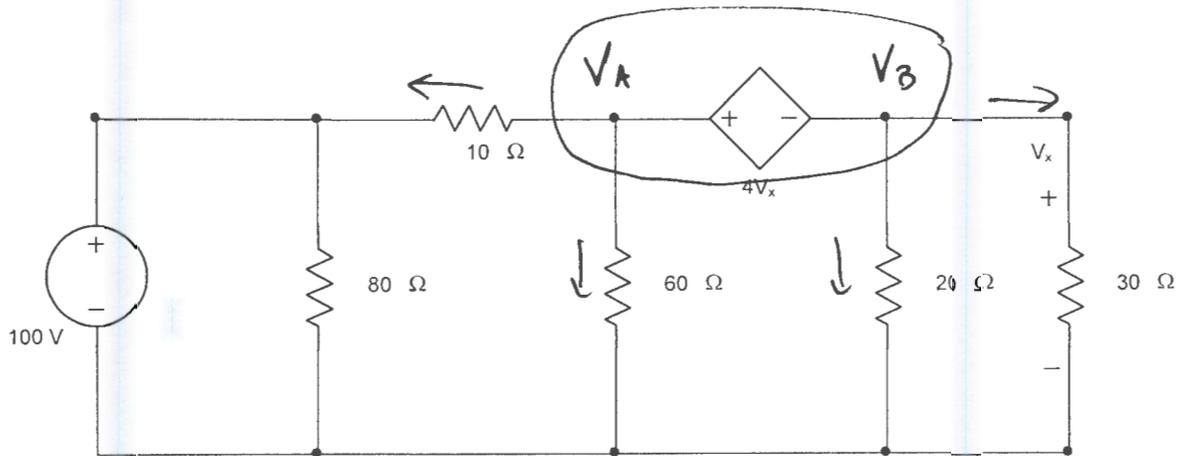3. Use the **node-voltage** method (aka "nodal analysis") to **determine the value of V_x** in the following circuit. (25 pts)



$$\left. \begin{array}{l} V_B = V_x \\ V_A - V_B = 4V_x \end{array} \right\} V_A = 5V_x$$

So

$$\frac{V_A - 100}{10} + \frac{V_A}{60} + \frac{V_B}{20} + \frac{V_B}{30} = 0$$

$$\left(\frac{5V_x - 100}{10} + \frac{5V_x}{60} + \frac{V_x}{20} + \frac{V_x}{30} = 0 \right) 60$$

$$36V_x - 600 + 5V_x + 3V_x + 2V_x = 0$$

$$40V_x = 600$$

$$V_x = \frac{600}{40} = \underline{\underline{15V}}$$

$$V_x = \underline{\underline{15V}}$$