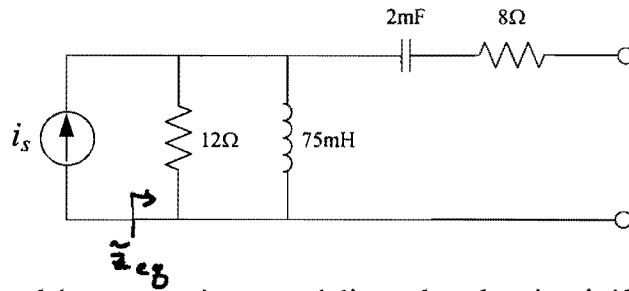


Consider the circuit shown below. The source current is given by $i_s = 5\cos(40t + 20^\circ)$ A. $\omega = 40 \text{ rad/s}$



$$j\omega L = j40(75\text{m}) = j3\Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j40(2\text{m})} = -j12.5\Omega$$

1) Solve for the real (or average) power delivered to the circuit if no load is attached.

$$\tilde{I}_s = 5 \angle 20^\circ \text{ A}$$

$$\tilde{Z}_{eq} = 12 \parallel j3 = \frac{12(j3)}{12 + j3} = 0.706 + j2.82 \Omega$$

$$P = \frac{|\tilde{I}_s|^2 R_{eq}}{2} = \frac{(5)^2 (0.706)}{2} = \boxed{8.8 \text{ W}}$$


2) Solve for the load impedance that will draw maximum real (or average) power when placed across the output terminals.

$$\tilde{Z}_{TH} = \tilde{Z}_{eq} + 8 - j12.5 = 0.706 + 8 + j(2.82 - 12.5)$$

$$= 8.706 - j9.68 \Omega$$

$$\tilde{Z}_L = \tilde{Z}_{TH}^* = \boxed{8.706 + j9.68 \Omega}$$

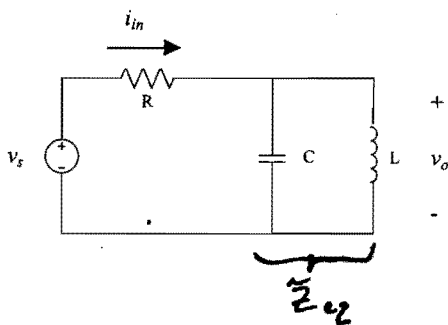3) Solve for the transfer function $H(\omega) = V_o/I_{in}$ in the circuit below.



$$H = \frac{V_o}{I_{in}} = \tilde{Z}_{eq} \text{ for } \parallel C, L, \text{ so...}$$

$$H = \frac{j\omega L \left(\frac{1}{j\omega C}\right)}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$$