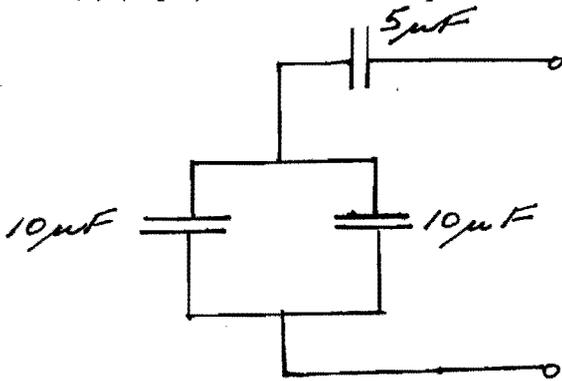




(1) (5 pts) Determine the equivalent capacitance of the capacitor network shown below.



$$20\ \mu\text{F} \parallel 5\ \mu\text{F} = 4\ \mu\text{F}$$

$$C_{EQ} = \underline{4\ \mu\text{F}}$$


(2) (5 pts) State the i-v characteristic for an inductor.

$$v = L \frac{di}{dt}$$


(3) (5 pts) In lab, how might you prevent a DC signal from entering a device while permitting an AC signal to pass through the device?

*Put a capacitor before the entrance of the device*

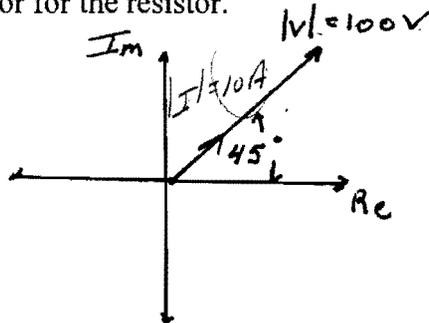(4) (5 pts) Given the voltage phasor for a  $10\ \Omega$  resistor sketched below on the polar graph, sketch the expected current phasor for the resistor.




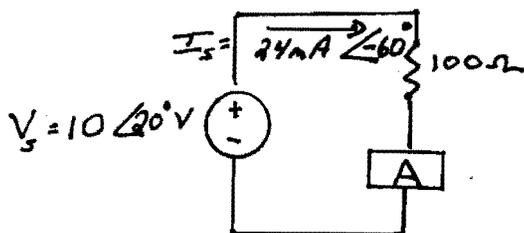(5) (5pts) What circuit element is element A?



*↑ ahead  
ELI  
Inductor*

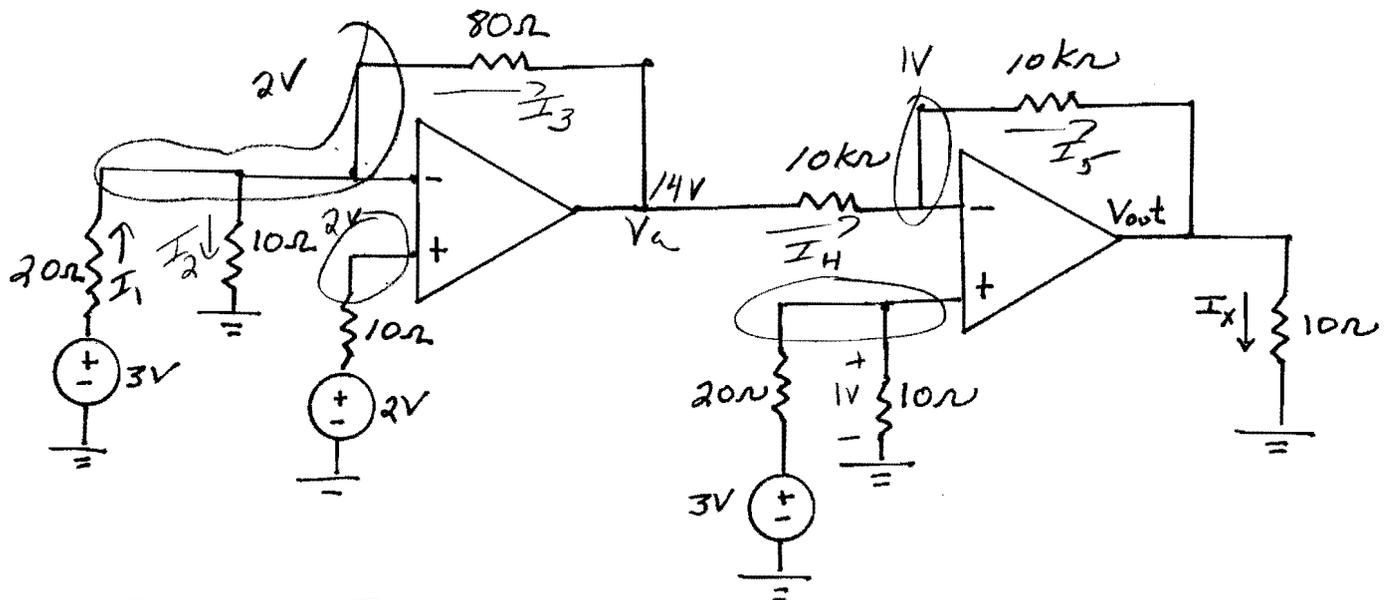(6) (25 points) Given the circuit shown below, determine the values of  $V_{out}$  and  $I_x$ .



$$I_1 = I_2 + I_3$$

$$\frac{3-2}{20} = \frac{2}{10} + \frac{2-V_a}{80}$$

$$\frac{1}{20} = \frac{2}{10} + \frac{2-V_a}{80}$$

$$4 = 16 + 2 - V_a$$

$$-14V = -V_a$$

$$14V = V_a$$

$$I_4 = I_5$$

$$\frac{14-1}{10k} = \frac{1-V_{out}}{10k}$$

$$13 = 1 - V_{out}$$

$$12 = -V_{out}$$


$$-12V = V_{out}$$

$$I_x = \frac{12}{10} = -1.2A$$

$$V_{out} = \underline{-12V}$$


$$I_x = \underline{-1.2A}$$

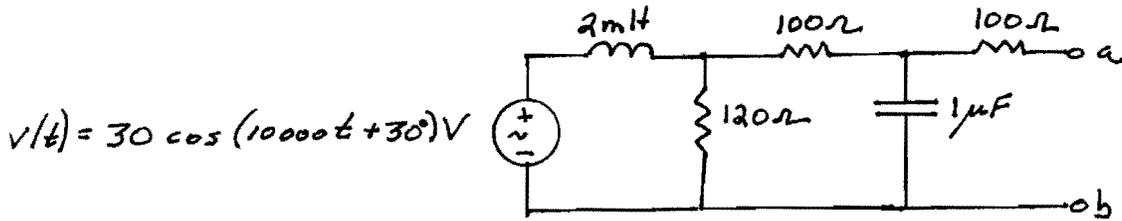(7) (25 points) Find the Thevenin Equivalent of the circuit shown below from the point of view of terminals a-b. **DRAW THE THEVENIN'S CIRCUIT.**



$$Z_L = j\omega L = j(10000)(2 \times 10^{-3}) = j20 \Omega$$
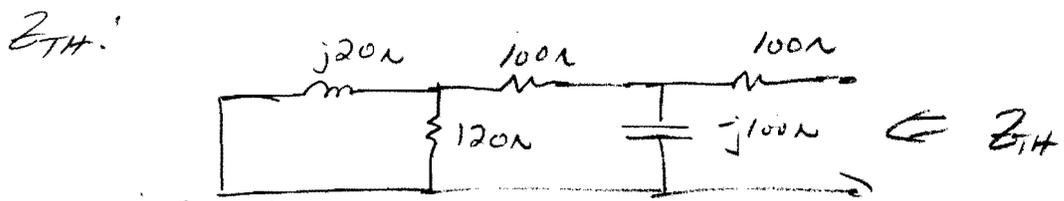
$$Z_C = -j\left(\frac{1}{\omega C}\right) = -j\left(\frac{1}{10000}\right)\left(\frac{1}{1 \times 10^{-6}}\right) = -j100 \Omega$$



$$Z_{TH} = \left\{ \left[ (j20 \parallel 120) + 100 \right] \parallel -j100 \right\} + 100$$


$$Z_{TH} = \left\{ \left[ 19.73 \angle 20.5^\circ + 100 \right] \parallel -j100 \right\} + 100$$

$$Z_{TH} = \left\{ (105.06 \angle 10.67^\circ) \parallel -j100 \right\} + 100$$

$$Z_{TH} = (80.23 \angle -41.37^\circ) + 100$$

$$Z_{TH} = 160.76 \angle -18.3^\circ$$

$$Z_{TH} = 160.21 - j53.02 \Omega$$

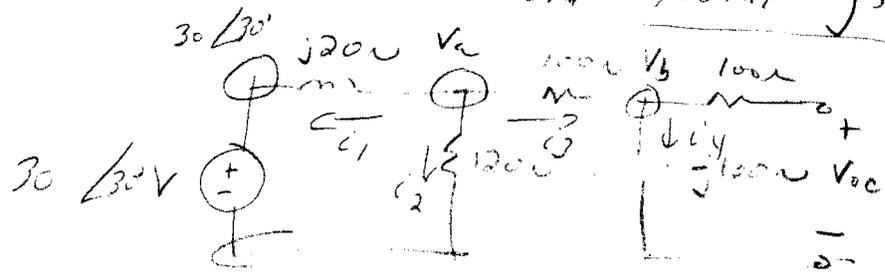

$$i_1 + i_2 + i_3 = 0$$


$$i_3 = i_4$$

$$\frac{V_a - 30 \angle 30^\circ}{20j} + \frac{V_a}{120} + \frac{V_a - V_b}{100} = 0$$

$$\frac{V_a - V_b}{100} = \frac{V_b}{-100j}$$

$$V_a = 31.08 + 7.46j$$
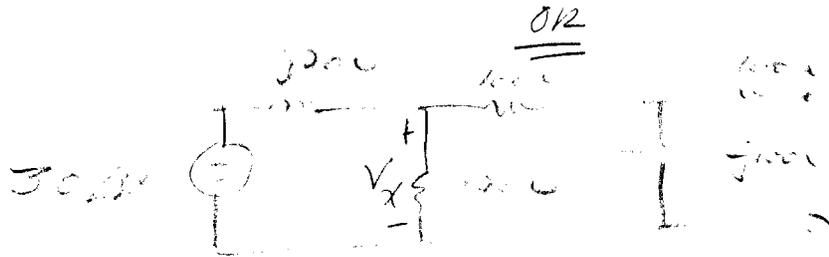
$$V_b = 19.27 - j11.81 = 22.6 \angle -31.5^\circ \text{ V}$$




$$Z_{TH} = 120 \parallel (100 - j100)$$

$$V_x = \left( \frac{120}{120 + 100 - j100} \right) 30 \angle 30^\circ$$



$$V_{oc} = \left( \frac{j100}{100 - j100} \right) V_x$$
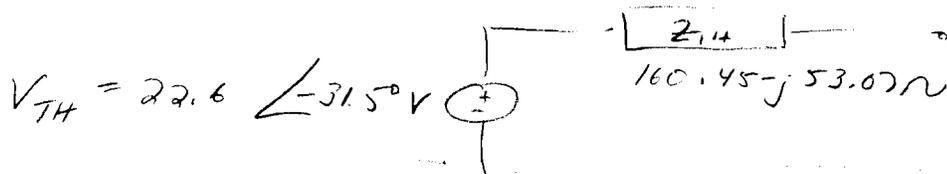
$$V_{TH} = 22.6 \angle -31.5^\circ \text{ V}$$



(8) (25 points) The switch in the circuit below has been closed for a long time. At  $t=0$  the switch opens. Find the following for  $t > 0$ .

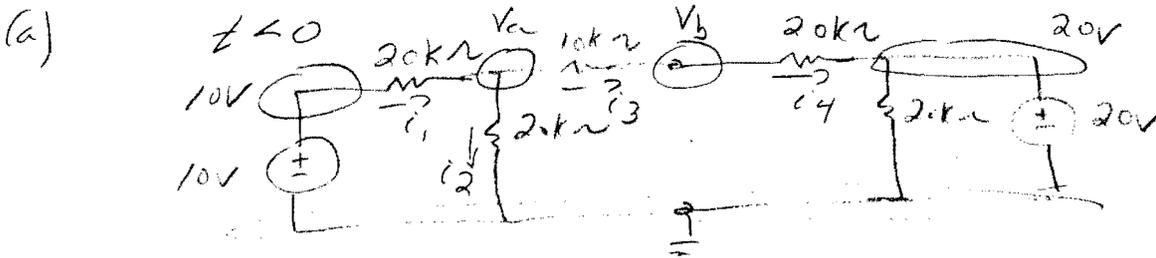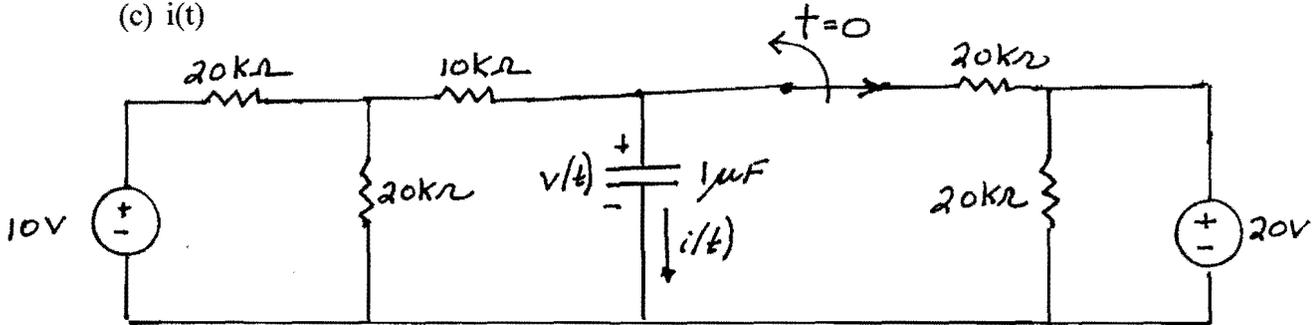- (a)  $v(t)$
- (b) Sketch  $V(t)$
- (c)  $i(t)$



$$i_1 = i_2 + i_3$$

$$\frac{10 - V_a}{20k} = \frac{V_a}{20k} + \frac{V_a - V_b}{70k}$$

$$i_3 = i_4$$

$$\frac{V_a - V_b}{70k} = \frac{V_b - 20}{20k}$$



$$V_a = 8.75 \text{ V}$$

$$V_b = 12.5 \text{ V}$$

(c)  $i = C \frac{dv}{dt}$


$$i = (1\mu)(-50)(7.5)e^{-50t}$$

$$i = -375 e^{-50t} \mu\text{A}$$

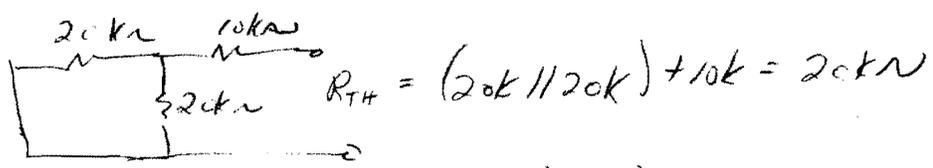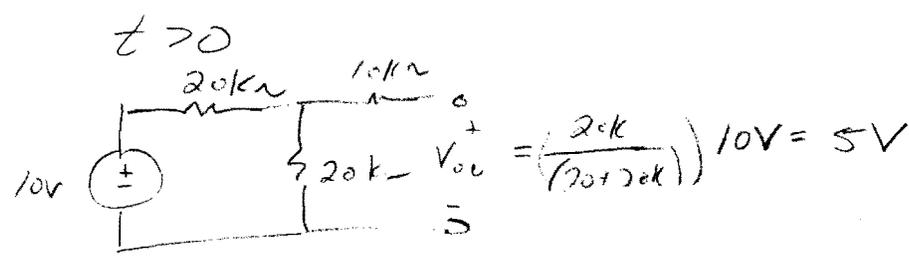

$$T = RC = (20k)(1\mu) = 20ms$$

$$\frac{1}{T} = 50$$

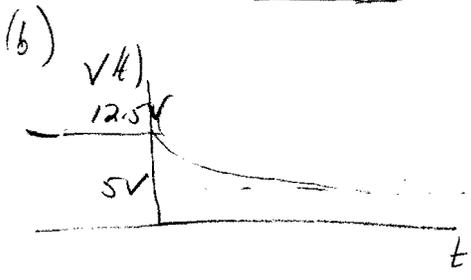

$$v(t) = \frac{5 + (12.5 - 5)e^{-50t}}{1} \text{ V}$$

$$i(t) = \frac{-375 e^{-50t}}{1} \mu\text{A}$$