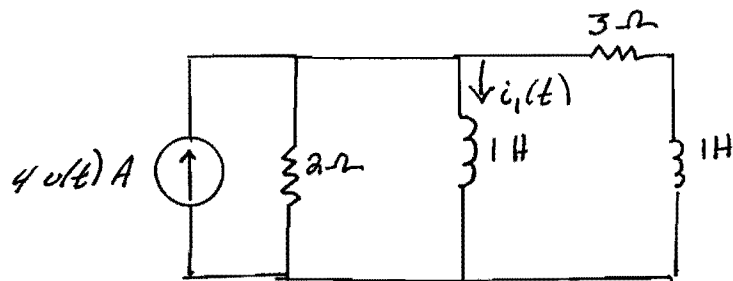




For the circuit below find $i(t)$ for $t \geq 0$ using the Laplace transform.



No aid given, received, or observed: _____

Practice Quiz Solution

$$i_1 = ? \quad t > 0$$

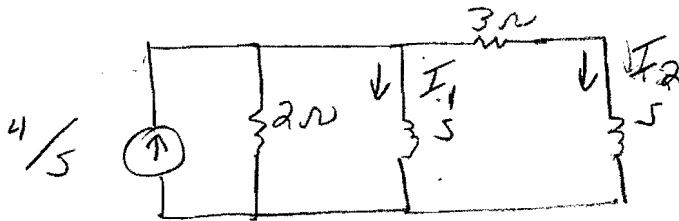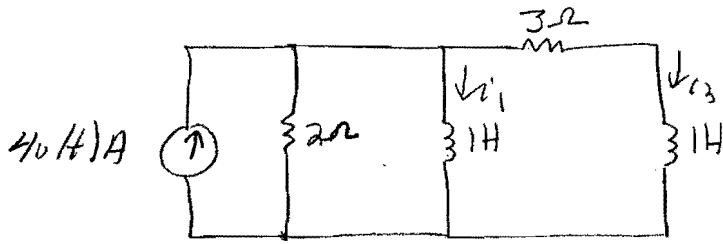

$$I_1 = \frac{4}{5} \left(\frac{1}{\frac{1}{2} + \frac{1}{5} + \frac{1}{3+5}} \right)$$

$$= \frac{4}{5} \left(\frac{1}{\frac{5}{2} + 1 + \frac{5}{3+5}} \right)$$

$$= \frac{4}{5} \left(\frac{2(3+5)}{5^2 + 35 + 6 + 25 + 25} \right)$$

$$= \frac{4}{5} \left(\frac{6 + 2s}{5^2 + 7s + 6} \right)$$

$$= \frac{24 + 8s}{s(s+1)(s+6)}$$

$$= \frac{K_1}{s} + \frac{K_2}{(s+1)} + \frac{K_3}{(s+6)}$$

$$K_1 = \frac{24 + 8s}{(s+1)(s+6)} \Big|_{s=0} = 4$$

$$K_2 = \frac{24 + 8s}{(s)(s+6)} \Big|_{s=-1} = -3.2$$

$$K_3 = \frac{24 + 8s}{(s)(s+1)} \Big|_{s=-6} = -0.8$$

$$i_1(t) = 4u(t) - 3.2e^{-t}u(t) - 0.8e^{-6t}u(t) \text{ A}$$

