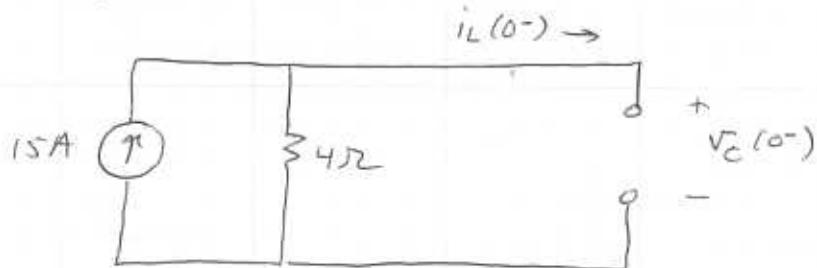


8.17


Step 1 Identify initial conditions (replace  $L \rightarrow$  short and  $C \rightarrow$  open)



$i_L(0^-) = 0$  because of the open, all current through  $4\Omega$  resistor so  $V_{4\Omega} = 15A(4\Omega) = 60V$ , Then by KVL  $V_C(0^-) = 60V$

Step 2 Flip switch, place circuit in s-domain

$$L_s = .25s$$

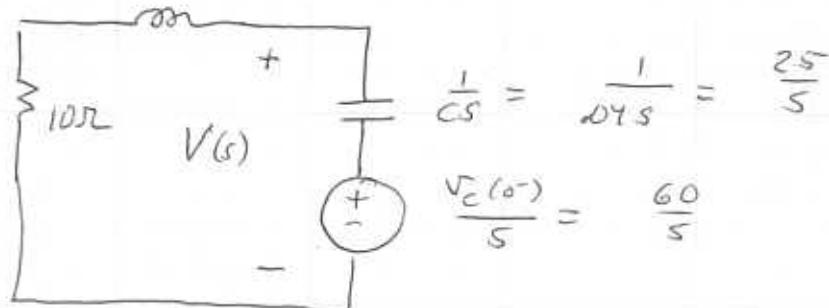

$V(s)$  is voltage across the RL part of circuit

$$\text{Voltage Divider} \rightarrow V = \frac{60}{s} \cdot \frac{\frac{0.25s+10}{s}}{\frac{0.25s+10}{s} + \frac{1}{s}} = \frac{15s + 600}{.25s^2 + 10s + 25}$$

$$\text{or } V = \frac{60s + 2400}{s^2 + 40s + 100} = \frac{A}{s+2.679} + \frac{B}{s+37.32}$$

$$A = \frac{60(-2.679) + 2400}{-2.679 + 37.32} = 64.64$$

$$B = \frac{60(-37.32) + 2400}{-37.32 + 2.679} = -4.64$$


$$V = \frac{64.64}{s+2.679} - \frac{4.64}{s+37.32}$$

$$v(t) = 64.64 e^{-2.679t} u(t) - 4.64 e^{-37.32t} u(t)$$

check  $v(0) = 64.64 - 4.64 = 60V \checkmark$

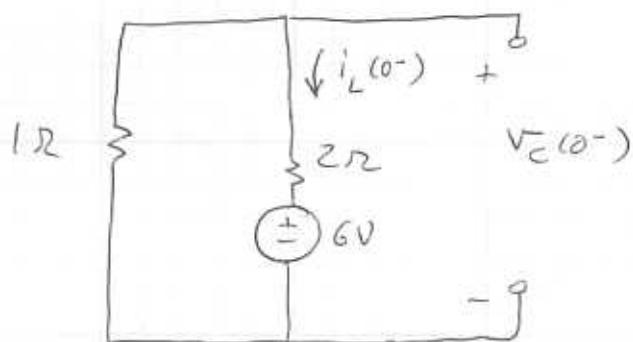8.48


Step 1 Find Initial Conditions :  $L \rightarrow$  short  $C \rightarrow$  open



$$v_C(0-) = V_{1\Omega} = 6V \quad \frac{1\Omega}{1\Omega + 2\Omega} = 2V$$

$$i_L(0-) = \frac{-6V}{1\Omega + 2\Omega} = -2A \quad (\text{current flows opposite direction})$$

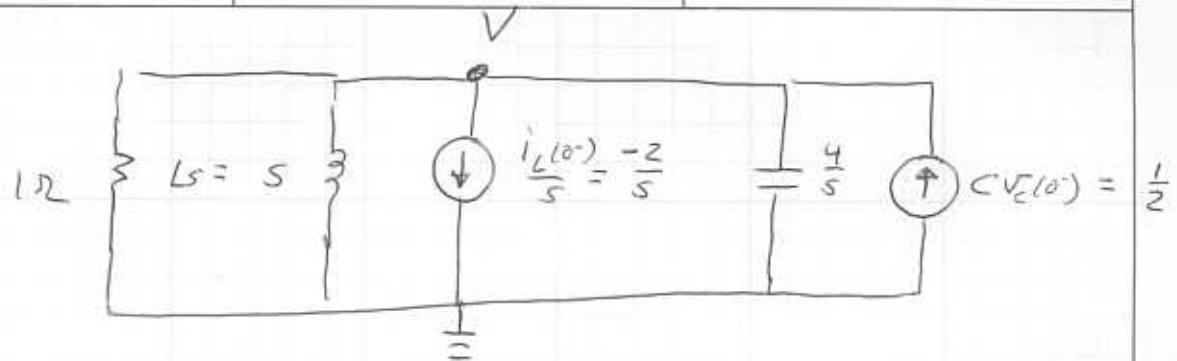Step 2 Place circuit in s-domain (all elements in parallel so use parallel models)



Step 3 Perform nodal to get parallel voltage

$$\frac{V}{1} + \frac{V}{s} - \frac{2}{s} + \frac{V}{4/s} - \frac{1}{2} = 0$$

Solving with calculator gives

$$V = \frac{2(s+4)}{s^2 + 4s + 4} = \frac{2(s+4)}{(s+2)(s+2)}$$


so expanding gives

$$V = \frac{2}{s+2} + \frac{4}{(s+2)^2}$$

Thus

$$v(t) = 2e^{-2t}u(t) + 4te^{-2t}u(t)$$

8.52

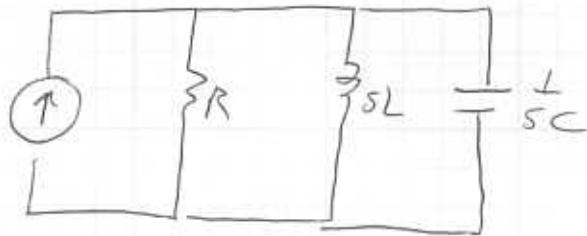

$$Z_p = \frac{1}{sC + \frac{1}{R} + \frac{1}{sL}} = \frac{sL}{s^2LC + \frac{L}{R}s + 1} = s^2 + \frac{1}{RC}s + \frac{1}{LC}$$

Thus the response has the quadratic term

$$s^2 + \frac{1}{RC}s + \frac{1}{LC}$$

The poles of the given response are at

$$\frac{s}{j\omega} = -300 \pm j400$$

which gives the polynomial

$$(s+300+j400)(s+300-j400) = s^2 + 600s + 250 \times 10^3$$

matching

$$\frac{1}{RC} = 600 \quad \frac{1}{LC} = 250 \times 10^3$$

$$\text{since } L = 50 \mu H \quad \text{Then} \quad C = \frac{1}{2\pi(250 \times 10^3)} = \underline{\underline{80 \mu F}}$$

~~R = 600~~ ~~(250)~~ ~~80~~ ~~μF~~

$$R = \frac{1}{600C} = \frac{1}{600(80 \times 10^{-6})} = \underline{\underline{20.83 \Omega}}$$