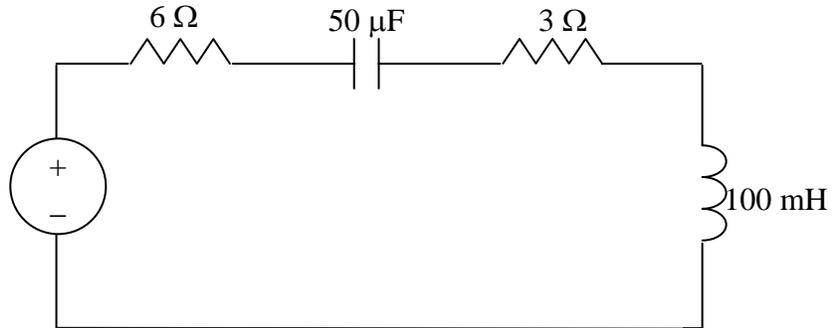


PS #19 Solutions

Chapter 14, Solution 26.

Consider the circuit as shown below. This is a series RLC resonant circuit.



$$R = 6 + 3 = 9 \Omega$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{100 \times 10^{-3} \times 50 \times 10^{-12}}} = \underline{447.21 \text{ krad/s}}$$

$$Q = \frac{\omega_o L}{R} = \frac{447.21 \times 10^3 \times 100 \times 10^{-3}}{9} = \underline{4969}$$

$$B = \frac{\omega_o}{Q} = \frac{447.21 \times 10^3}{4969} = \underline{90 \text{ rad/s}}$$

Chapter 14, Solution 28.

Let $R = 10 \Omega$.

$$L = \frac{R}{B} = \frac{10}{20} = 0.5 \text{ H}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(1000)^2 (0.5)} = 2 \mu\text{F}$$

$$Q = \frac{\omega_0}{B} = \frac{1000}{20} = 50$$

Therefore, if $R = 10 \Omega$ then

$$L = \underline{\mathbf{0.5 \text{ H}}}, \quad C = \underline{\mathbf{2 \mu\text{F}}}, \quad Q = \underline{\mathbf{50}}$$

Chapter 14, Solution 30.

$$\omega_o = 2\pi(15,000) = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(.01\text{H})C}}$$

$$C = 11.26\text{nF}$$

At resonance, the circuit appears purely resistive so $I = \frac{V}{R} = \frac{120\text{V}_{rms}}{20\Omega} = 6\text{A}_{rms}$

$$Q = \frac{\omega_o L}{R} = \frac{2\pi(15,000)(.01)}{20} = 47.12$$