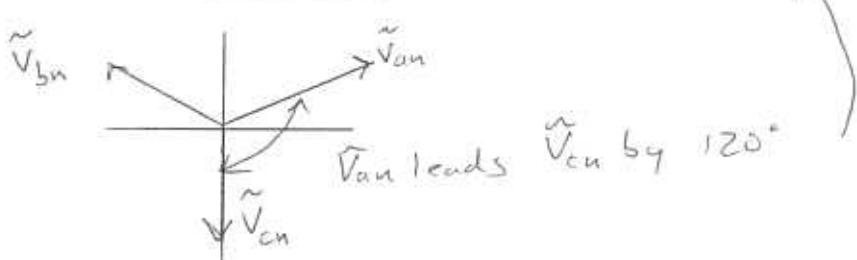


PROBLEM SET #27

Chapter 12, Solution 2.

Since phase c lags phase a by 120° , this is an acb sequence.

$$\tilde{V}_{ba} = 160 \angle (30^\circ + 120^\circ) = \underline{160 \angle 150^\circ \text{ V}}$$



Chapter 12, Solution 7.

This is a balanced Y-Y system.



Using the per-phase circuit shown above,


$$I_a = \frac{440 \angle 0^\circ}{6 - j8} = \underline{44 \angle 53.13^\circ \text{ A}}$$

$$I_b = I_a \angle -120^\circ = \underline{44 \angle -66.87^\circ \text{ A}}$$

$$I_c = I_a \angle 120^\circ = \underline{44 \angle 173.13^\circ \text{ A}}$$

Chapter 12, Solution 8.

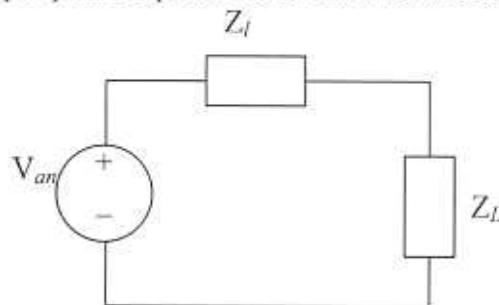Consider the per phase equivalent circuit shown below.



$$I_a = \frac{V_{an}}{Z_L + Z_t} = \frac{100 \angle 20^\circ}{10.6 + j15.2} = \underline{5.396 \angle -35.1^\circ \text{ A}}$$

$$I_b = I_a \angle -120^\circ = \underline{5.396 \angle -155.1^\circ \text{ A}}$$

$$I_c = I_a \angle +120^\circ = \underline{5.396 \angle 84.9^\circ \text{ A}}$$

$$V_{L_a} = I_a Z_L = (4.4141 - j3.1033)(10 + j14) = \underline{92.83 \angle 19.35^\circ \text{ A}}$$

$$V_{L_b} = V_{L_a} \angle -120^\circ = \underline{92.83 \angle -100.65^\circ \text{ A}}$$

$$V_{L_c} = V_{L_a} \angle +120^\circ = \underline{92.83 \angle 139.35^\circ \text{ A}}$$