

**PROBLEM SET #36**

- 36.1** A 3-phase, 60Hz, 4-pole, Y-connected synchronous motor has the following parameters:  $r_s = 12\Omega$ ,  $X_s = 120\Omega$ , and  $L_{SF} = 0.9H$ . The motor is connected to a balanced three-phase source that provides a line voltage of 208Vrms at 60Hz.
- a. If (using the two wattmeter method) we determine that the source delivers +150W and +75VAR (both are three-phase), calculate the following:
    - i. The source apparent power and the phase current (magnitude and angle)
    - ii. The excitation voltage
    - iii. The field current
    - iv. The mechanical power out (Hint: subtract the losses in the stator resistance from the input power) and the efficiency
  - b. Repeat part a if the source now delivers +150W and -75VAR (both three phase). Note, this means that the source absorbs reactive power from the motor