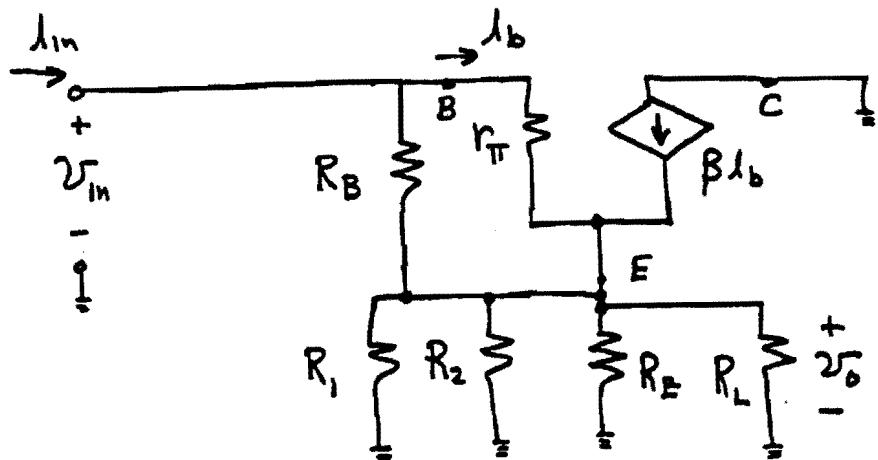


Problem 4.56




$$\text{Let } R'_L = R_1 \parallel R_2 \parallel R_E \parallel R_L$$

$$v_o = R'_L \left( i_b + \beta i_b + \frac{r_\pi i_b}{R_B} \right) \quad v_{in} = r_\pi i_b + v_o$$

$$A_v = \frac{v_o}{v_{in}} = \frac{R'_L \left( 1 + \beta + \frac{r_\pi}{R_B} \right)}{r_\pi + R'_L \left( 1 + \beta + \frac{r_\pi}{R_B} \right)}$$

$$i_{in} = \frac{v_{in} - v_o}{R_B \parallel r_\pi} = \frac{v_{in} - A_v v_{in}}{R_B \parallel r_\pi} \quad z_{in} = \frac{v_{in}}{i_{in}} = \frac{R_B \parallel r_\pi}{1 - A_v}$$

ANOTHER VIEW OF THE SMALL SIGNAL MODEL THAT IS (PERHAPS)  
EASIER TO ANALYZE:

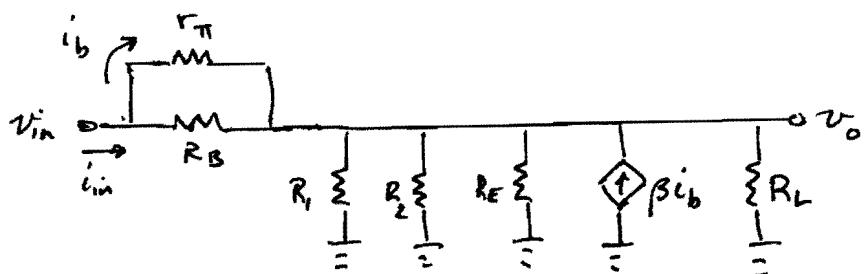


**Problem 4.57**

See the next page for the dc equivalent circuit from which we have:

$$I_{BQ} = (7.5 - V_{BEQ}) / [R'_B + (\beta + 1)R_E] = 3.21 \mu A$$
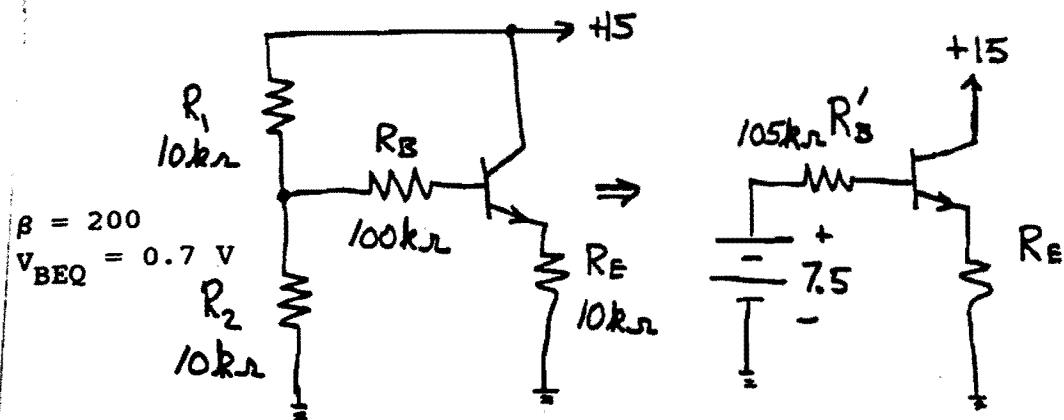
$$I_{CQ} = \beta I_{BQ} = 0.643 \text{ mA} \quad r_\pi = \beta V_T / I_{CQ} = 8.09 \text{ k}\Omega$$




Then using the formulas from Problem 4.56, we have:

$$R'_L = R_1 || R_2 || R_E || R_L = 1.95 \text{ k}\Omega$$

$$A_v = 0.9798 \quad Z_{in} = 370 \text{ k}\Omega$$

**Problem 4.55**

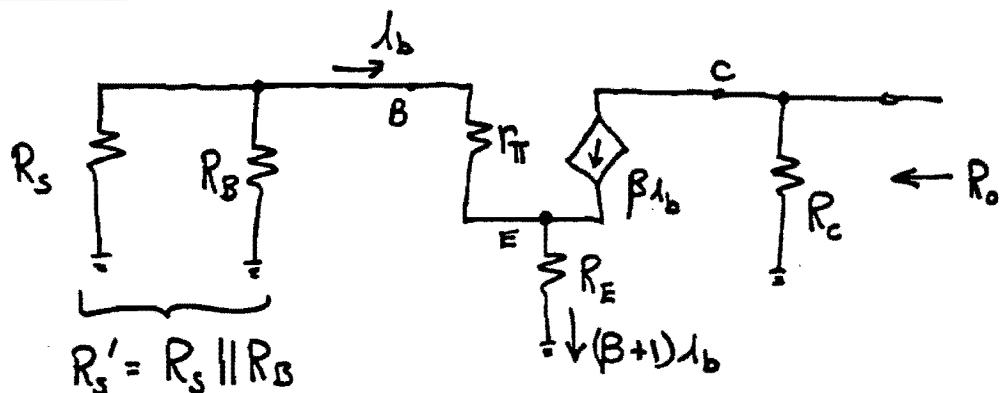

$$R'_s i_b + r_\pi i_b + (\beta + 1)R_E i_b = 0 \Rightarrow i_b = 0$$

Therefore we conclude that the  $\beta i_b$  acts as an open circuit and we have  $R_o = R_c$ .