

Name: _____ Section: _____

EE241: Electronics I
Problem Set 3
(Due 1/26/09)

These problems are based on Hambley, sections 2.6-2.8, and 2.10-2.11. Please complete the problems in pencil on engineering paper and attach them by staple to this cover sheet.

1. Hambley Problem 2.75
2. Hambley Problem 2.76
3. Hambley Problem D2.77
4. Hambley Problem 2.42
5. Hambley Problem 2.44
6. Hambley Problem 2.47
7. Hambley Problem 2.50
8. Hambley Problem 2.51
9. Hambley Problem 2.52
10. Hambley Problem 2.56
11. Hambley Problem 2.60
12. Hambley Problem D2.74, but use Multisim instead of PSPICE for the simulation.