

Homework 16 Solutions

1.


b)

x	A	B	A*	B*	z	S _A	R _A	S _B	R _B	T _A	T _B
0	0	0	1	0	0	1	0	0	X	1	0
0	0	1	0	0	0	0	X	0	1	0	1
0	1	0	0	1	1	0	1	1	0	1	1
0	1	1	0	0	1	0	1	0	1	1	1
1	0	0	1	1	0	1	0	1	0	1	1
1	0	1	0	1	0	0	X	X	0	0	0
1	1	0	1	1	0	X	0	1	0	0	1
1	1	1	0	0	1	0	1	0	1	1	1

The output is

$$z = x' A + A B$$

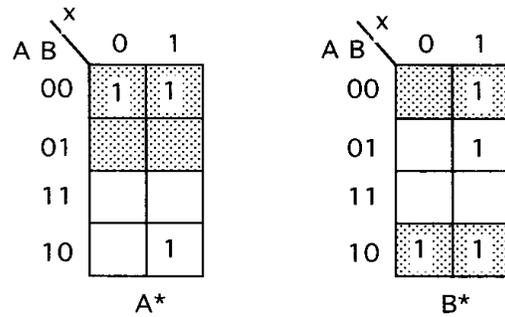To obtain the D and J K inputs, we map A* and B* (using the quick method for the JK flip flops).



$$D_A = A' B' + x B' \quad D_B = x A' + A B'$$


$$J_A = B' \quad K_A = x' + B \quad J_B = x + A \quad K_B = x' + A$$

The SR and T inputs can be obtained from maps of the truth table above.

$$S_A = A' B' \quad R_A = x' A + B \quad S_B = x A' + A B' \quad R_B = A B + \{x' B \text{ or } x' A'\}$$

$$T_A = A' B' + A B + \{x' A \text{ or } x' B'\} \quad T_B = A + x' B + x B'$$

The circuit for the JK design is

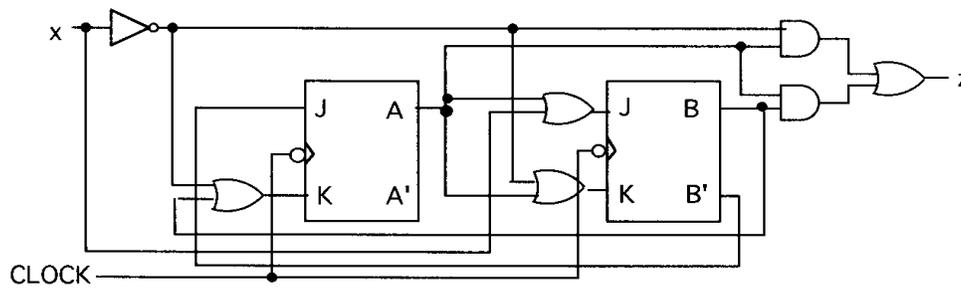

Homework 16 Solutions

2. a)

	x	q ₁	q ₂	q ₁ *	q ₂ *	z	J ₁	K ₁	J ₂	K ₂
-	0	0	0	X	X	X	X	X	X	X
B	0	0	1	1	0	0	1	X	X	1
C	0	1	0	1	1	0	X	0	1	X
A	0	1	1	1	0	0	X	0	X	1
-	1	0	0	X	X	X	X	X	X	X
B	1	0	1	1	1	1	1	X	X	0
C	1	1	0	1	0	0	X	0	0	X
A	1	1	1	0	1	1	X	1	X	0

Without drawing the maps, we can see that

$$D_1 = x' + q_1' + q_2'$$

$$J_1 = 1$$

$$J_2 = K_2 = x'$$

Thus, we show maps only for D₂ (q₂*), z, and K₁.

		x	
		0	1
q ₁ q ₂	00	X	X
	01		1
	11		1
	10	1	
		q ₂ *	

		x	
		0	1
q ₁ q ₂	00	X	X
	01		1
	11		1
	10		
		z	

		x	
		0	1
c ₁ q ₂	00	X	X
	01	X	X
	11		1
	10		
		K ₁	

$$D_2 = x' q_2' + x q_2$$

$$K_1 = x q_2$$

$$Z = q_2$$