

Homework 22 Solutions

12. We need to build a standard binary counter (four bits) and clear it when it reaches 10.

