

EE301 FALL 2009 EQUATION SHEET

Voltage, Current, Resistance	Ohm's Law and Power	KVL & KCL	VDR & CDR
$V = \frac{W}{Q} \quad \left(V = \frac{J}{C} \right)$ $I = \frac{Q}{t} \quad \left(A = \frac{C}{\text{sec}} \right)$ $Q = 1.602 \times 10^{-19} \text{ C} / e^-$ $R = \frac{\rho l}{A} (\Omega)$ battery life = $\frac{\text{capacity (Amp}\cdot\text{hr)}}{\text{discharge rate (A)}}$	$V = IR [V] \rightarrow I = \frac{V}{R} [A]$ $P = IV = I^2 R = \frac{V^2}{R} [W]$ $\eta = \frac{P_{out}}{P_{in}} \times 100\%$ 1 Hp = 746 W	KVL (Closed Loop) $\sum V = 0$ or $\sum E_{RISE} = \sum V_{DROP}$ KCL (In and Out of a Node) $\sum I = 0$ or $\sum I_{IN} = \sum I_{OUT}$	VDR: series resistors $V_x = E \left(\frac{R_x}{R_T} \right)$ CDR: parallel resistors $I_x = I_T \left(\frac{R_{EQ}}{R_x} \right)$ CDR: two parallel resistors $I_1 = I_T \left(\frac{R_2}{R_1 + R_2} \right)$
Series and Parallel Resistances $R_T = R_1 + R_2 + \dots R_n$ (series) $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \frac{1}{R_n}$ (parallel) $R_T = \frac{R_1 R_2}{R_1 + R_2}$ (2 parallel)	Capacitors $C = \frac{Q}{V} = \epsilon_r \epsilon_0 \frac{A}{d}$ (F) $\epsilon_0 = 8.854 \times 10^{-12}$ F/m $i_c = \frac{dq}{dt} = C \frac{dv_c}{dt} = C \frac{\Delta v_c}{\Delta t}$ $v = v(t_0) + \frac{1}{C} \int_{t_0}^t i dt = v_0 + \frac{1}{C} i \Delta t$ $W = \frac{1}{2} C v^2$ (J) Dielectric breakdown: $V = Kd$ (kV/mm)	Inductors $v = N \frac{d\phi}{dt}$ $v = L \frac{di}{dt} = L \frac{\Delta i}{\Delta t}$ $i_L = i(t_0) + \frac{1}{L} \int_{t_0}^t v dt = i_0 + \frac{1}{L} v \Delta t$ $W = \frac{1}{2} L i^2$ (J)	Max Power Transfer $P_{MAX} = \frac{V_{TH}^2}{4R_{TH}}$ $Z_{LD} = Z_{TH}^*$
			Linear Motors $\vec{F}_d = I \vec{L} \times \vec{B}$ (N) $E_{induced} = (\vec{v} \times \vec{B}) L$ $I = \frac{V_B - E_{induced}}{R}$ $v = \frac{V_B - IR_{rail}}{BL}$ (m/sec) $P_{out} = F_{load} v = E_{ind} I$ $P_{IN} = V_B I$ $1 T = \frac{V \cdot \text{sec}}{m^2} = \frac{N}{A \cdot m}$
DC Motors			
$P_{in} = P_{out} + P_a + P_{loss}$ $P_{in} = V_{DC} I_a$ $P_{out} = T_{LOAD} \omega = 746 * hp$ $P_a = I^2 R_a$ Electrical Loss (W) $P_{loss} = T_{loss} \omega$ Mechanical Loss (W) $P_d = P_{in} - P_a = P_{out} + P_{loss}$ $P_d = E_a I_a = T_d \omega = K_v I_a \omega$ Power Developed (W) $T_d = K_v I_a$ Torque Developed (N · m) $\omega = 2\pi (\text{RPM} / 60)$ Angular Velocity (rad/sec)			
AC Real and Reactive Power $Z = R + Xj$ $S = VI$ (VA) $P = \frac{V^2}{R} = I^2 R = VI \cos \theta$ (W) $Q = \frac{V^2}{X} = I^2 X = VI \sin \theta$ (VAR) $S^2 = P^2 + Q^2$ $F_p = \cos(\theta) = P / S$	Sinusoidal Eqns $e(t) = E_m \sin(\omega t + \theta)$ $e(t) = E_m \sin(2\pi f t + \theta)$ $e(t) = E_m \sin(2\pi \frac{t}{T} + \theta)$ $\omega = 2\pi f \quad f = 1/T$ $\Delta \theta = \frac{\Delta t}{T} (360^\circ)$ $E_{RMS} = 0.707 * E_{PK}$ $E_{PK} = 1.41 * E_{RMS}$	AC Impedance $Z_R = R + 0j = R \angle 0^\circ$ $Z_L = jX_L = X_L \angle 90^\circ$ $Z_C = -jX_C = X_C \angle -90^\circ$ $X_L = \omega L = 2\pi f L$ $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$	Transformers $a = \frac{N_p}{N_s} = \frac{e_{pri}}{e_{sec}} = \frac{i_{sec}}{i_{pri}}$ $E_{sec} = \frac{1}{a} E_{pri}$ $I_{sec} = a I_{pri}$ $Z_{P-reflected} = a^2 Z_{LD}$
3 Phase AC Power $Q_T = \sqrt{3} V_L I_L \sin \theta_\phi = 3Q_\phi$ (VAR) $P_T = \sqrt{3} V_L I_L \cos \theta_\phi = 3P_\phi$ (W) $S_T = \sqrt{3} V_L I_L = 3S_\phi$ (VA) Y Generator or Y LOAD $V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$ Δ LOAD $I_a = \sqrt{3} I_{ab} \angle -30^\circ$	AC Generator $\omega_{rotor} = \left(\frac{2}{\text{Poles}} \right) 2\pi f$ (rad/sec) $N_p = \frac{120f}{\text{Poles}}$ (RPM) $P_{IN} = \tau \omega_{rotor} = 746 * hp$ $P_{ELEC-LOSS} = 3I_L^2 R_{armature}$ $P_{OUT} = \sqrt{3} I_L V_L \cos \theta$		
		$P_{IN} = P_{OUT} + P_{MECH-LOSS} + P_{ELEC-LOSS}$	