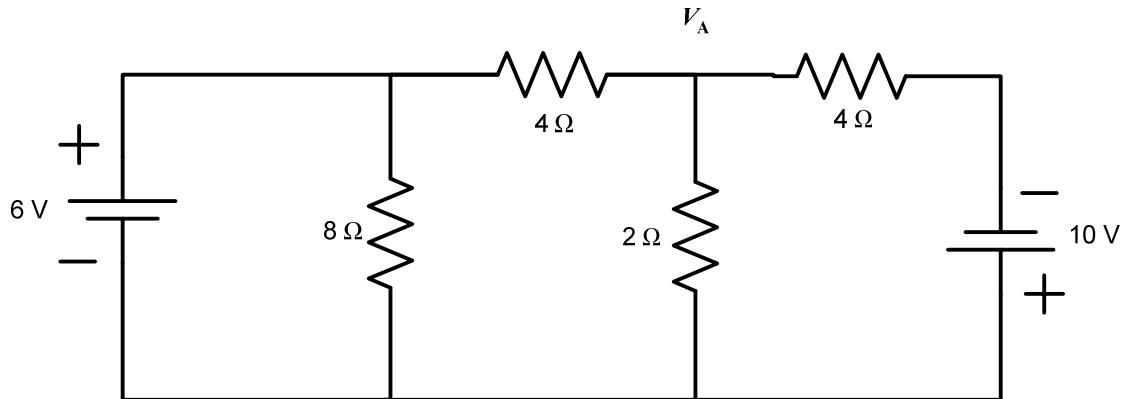
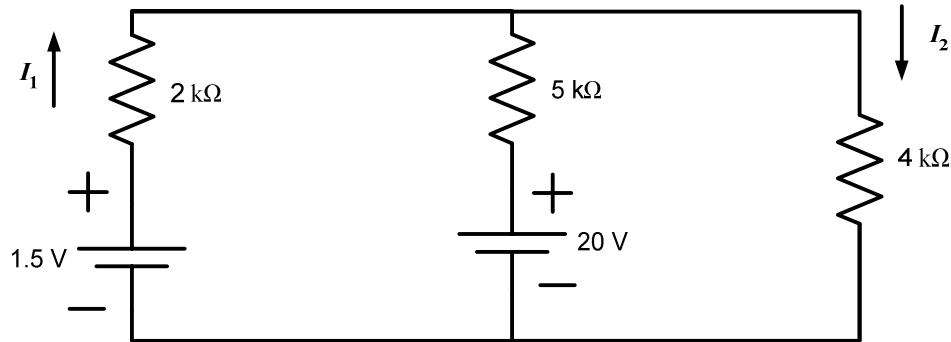


(1) Find the nodal voltage V_A using nodal analysis.



(2) Using nodal analysis, find I_1 and I_2 .



(3) Using nodal analysis find V_1 , V_2 , I_1 and I_2 .

