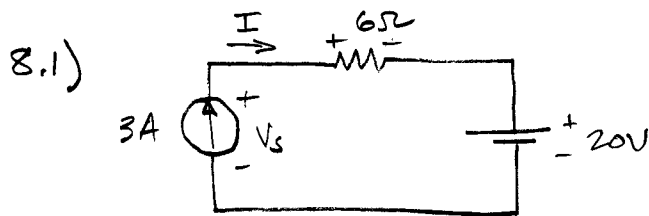


HW #10 Solutions EE301

Ch. 8 #1, 5, 9b, 10b, 11, 15




$$V_{6\Omega} = IR = (3A)(6\Omega) = 18V$$

Using KVL,  $\sum V = 0$

$$V_s - V_{6\Omega} - 20V = 0$$

$$V_s - 18V - 20V = 0$$

$$\boxed{V_s = 38V}$$

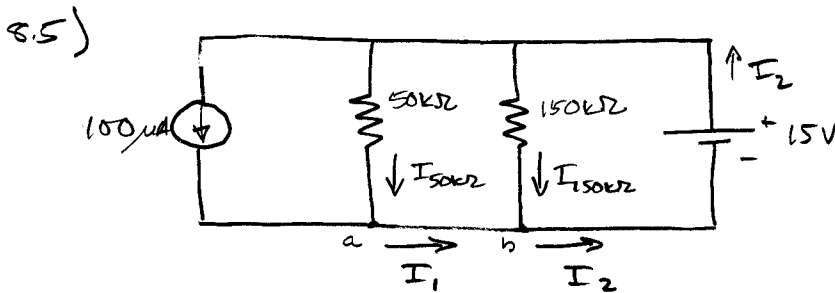

Recognizing 15V potential exists across all parallel branches,

$$I_{50k\Omega} = \frac{E}{R} = \frac{15V}{50k\Omega} = 300\mu A$$

Using KCL at node a,

$$I_{50k\Omega} + 100\mu A = I_1$$




$$I_1 = 100\mu A + 300\mu A = \boxed{400\mu A}$$

Using KCL at node b,

$$I_{150k\Omega} + I_1 = I_2$$

$$I_2 = 100\mu A + 400\mu A = \boxed{500\mu A}$$


8.9) b.

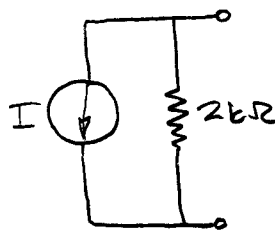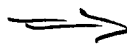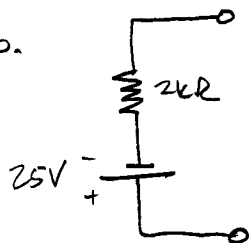


$$I = \frac{E}{R} = \frac{25V}{2k\Omega}$$

$$\boxed{I = 12.5mA}$$

8.10) b.

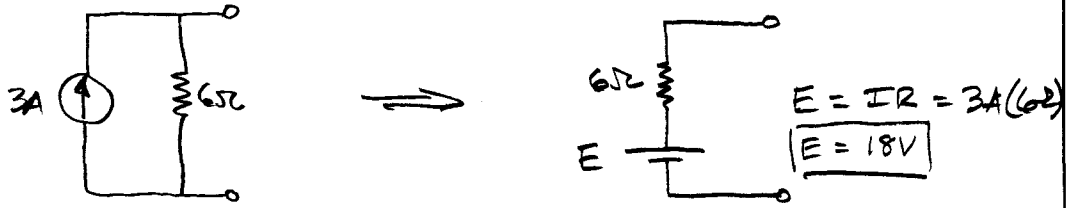

8.11)

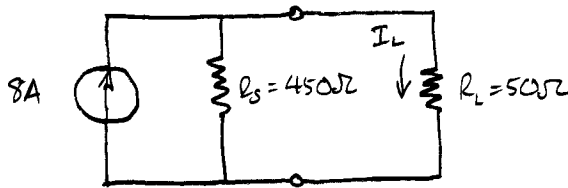


a) Solve for  $I_L$  using Current Divider Rule

$$I_L = \frac{R_s}{R_s + R_L} I_T \text{ for 2 parallel resistors}$$


$$I_L = \frac{450\Omega}{450\Omega + 50\Omega} (8A) = \boxed{7.2A}$$

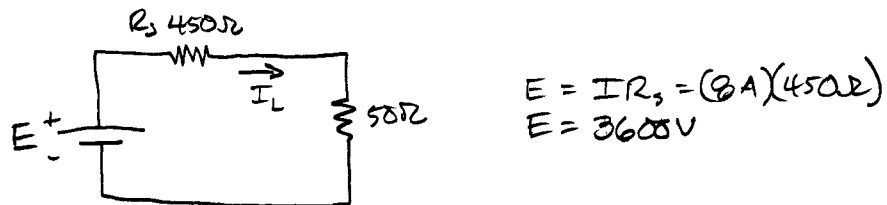b) Convert current source into equivalent voltage source and solve for  $I_L$ .




$$I_L = \frac{E}{R_T} = \frac{3600V}{450\Omega + 50\Omega} = \boxed{7.2A}$$

8.15)

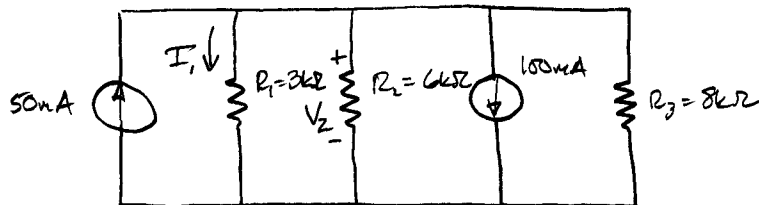

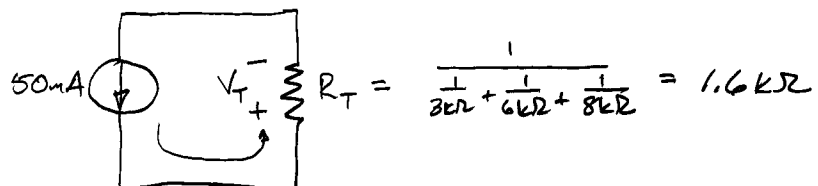
Simplify circuit by combining current sources and parallel resistors.



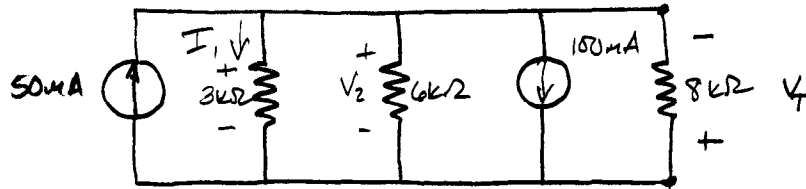8.15) Continued

We can determine  $V_T = I_T R_T = (50 \text{ mA})(1.6 \text{ k}\Omega) = 80 \text{ V}$

So, the voltage potential of the circuit is



Note the polarity of  $V_T$  is with the negative on top.

Since this is a parallel circuit,  $V_2 = -V_T = \boxed{-80 \text{ V}}$ .  
The negative sign is due to the polarity convention assigned to  $V_2$ .

Use Ohm's Law to find  $I_1$ ,

$$I_1 = \frac{-V_T}{3 \text{ k}\Omega} = \frac{-80 \text{ V}}{3 \text{ k}\Omega} = \boxed{-26.7 \text{ mA}}$$

Again, the negative current direction comes from the assigned direction for  $I_1$ .