

HW #17 Solutions EE301

1) 125 VDC Motor rated for 32A

$$R_a = 0.135 \Omega \text{ (armature resistance)}$$

a)  $P_{in} = V_T I_a$       $V_T = \text{terminal voltage}$   
 $= (125V)(32A)$

$$P_{in} = 4000W$$

b)  $P_{elec\ loss} = I_a^2 R_a = (32A)^2 (0.135\Omega)$

$$P_{elec\ loss} = 138.2W$$

c) From  $P_{in} = P_{out} + P_{loss} + P_{elec\ loss}$   
 $P_d$      assume no mechanical loss

$$P_d = P_{in} - P_{elec\ loss} = 4000W - 138.2W$$

$$P_d = 3862W$$


d) From  $P_d = E_g I_a$

$$E_g = \frac{P_d}{I_a} = \frac{3862W}{32A}$$

$$E_g = 121V$$

e)  $\eta = \frac{E_g}{V_T} = \frac{121V}{125V}$

$$\eta = 96.8\%$$

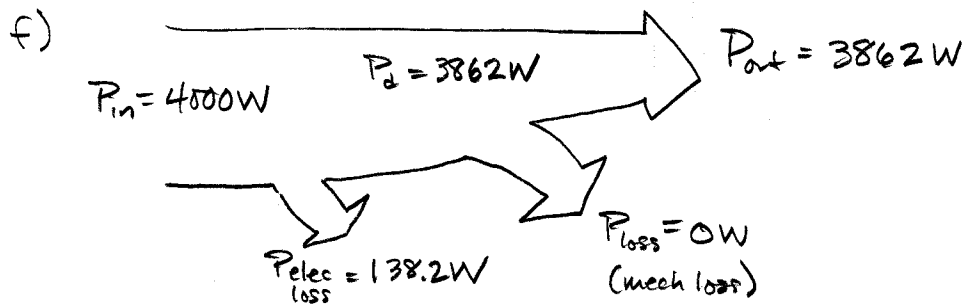

2) Design 5 hp, 120 VDC motor,  $\eta = 95\%$

$$K_v = 0.138 \text{ V}\cdot\text{s}, P_{\text{loss}} = 0 \text{ (no mechanical losses)}$$

To determine current draw, let's first find  $P_{\text{in}}$

$$P_{\text{in}} = \frac{P_{\text{out}}}{\eta} = \frac{5 \text{ hp}}{0.95} \left( \frac{746 \text{ W}}{1 \text{ hp}} \right) = 3926 \text{ W}$$

$$\text{From } P = I E$$

$$I_a = \frac{P_{\text{in}}}{V_T} = \frac{3926 \text{ W}}{120 \text{ V}} = \boxed{32.7 \text{ A}}$$

$$\text{From } P_{\text{out}} = T_{\text{load}} \omega = K_v I_a \omega$$

$$T_{\text{load}} = K_v I_a = (0.138 \text{ V}\cdot\text{s})(32.7 \text{ A}) \left[ \left( \frac{\text{W}}{\text{V}\cdot\text{A}} \right) \left( \frac{\text{N}\cdot\text{m/s}}{\text{W}} \right) \right]$$

$$\boxed{T_{\text{load}} = 4.52 \text{ N}\cdot\text{m}}$$

$$\text{From } P_{\text{out}} = T_{\text{load}} \omega$$

$$\omega = \frac{P_{\text{out}}}{T_{\text{load}}} = \frac{(5 \text{ hp}) \left( \frac{746 \text{ W}}{1 \text{ hp}} \right)}{4.52 \text{ N}\cdot\text{m}} \left[ \frac{\text{N}\cdot\text{m/s}}{\text{W}} \right] \left[ \left( \frac{\text{rev}}{2\pi \text{ rad}} \right) \left( \frac{60 \text{ sec}}{\text{min}} \right) \right]$$

$$\boxed{\omega = 7880 \text{ rpm}}$$


3) DC Motor rated for 120 V, 2 A

$$R_a = 0.175 \Omega, K_v = 0.175 \text{ V}\cdot\text{s}$$

$$\text{a) } I_a = \frac{V_T - E_g}{R_a}$$

Solving for  $E_g$ ,
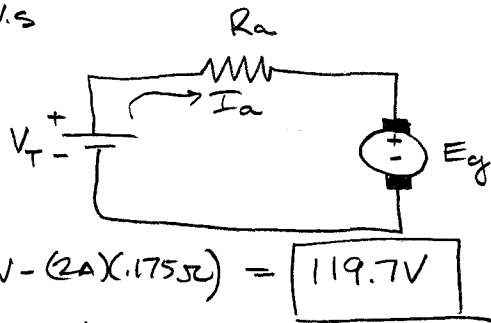
$$E_g = V_T - I_a R_a = 120 \text{ V} - (2 \text{ A})(0.175 \Omega) = \boxed{119.7 \text{ V}}$$



$$\text{b) } T_d = K_v I_a = (0.175 \text{ V}\cdot\text{s})(2 \text{ A})$$

$$\boxed{T_d = 0.35 \text{ N}\cdot\text{m}}$$

$$\text{c) From } E_g = K_v \omega$$

$$\omega = \frac{E_g}{K_v} = \frac{119.7 \text{ V}}{0.175 \text{ V}\cdot\text{s}} \left( \frac{60 \text{ sec}}{\text{min}} \right) \left( \frac{\text{rev}}{2\pi \text{ rad}} \right)$$

$$\boxed{\omega = 6530 \text{ rpm}}$$