


HW #23 Solutions EE301

Ch. 16 #s 20, 24a, 28b, 29a, 33

16.20)

$$v = 120V \sin(\omega t + 55^\circ)$$

$$i = -18mA \cos(\omega t + 145^\circ)$$

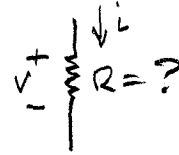

Show component is resistor and find its resistance.

If we can show that v and i are in phase, the component must be a resistor.

In terms of phasors, voltage can be expressed as

$$V = V_{eff} \angle 55^\circ = (0.707)(120V) \angle 55^\circ = 84.8V \angle 55^\circ$$

For current, convert the cosine function into a sine function by a phase shift of 270° from

$$\cos \alpha = \sin(\alpha - 270^\circ)$$


Therefore,

$$i = -18mA \sin(\omega t + 145^\circ - 270^\circ)$$

$$i = -18mA \sin(\omega t - 125^\circ)$$

Drawing this as a phasor, $i = (0.707)(-18mA) \angle -125^\circ$

$$i = -12.7mA \angle -125^\circ$$

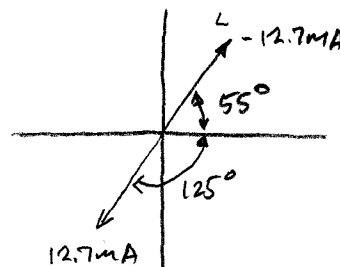

We then see that $i = -12.7mA \angle -125^\circ$ is the same as $i = 12.7mA \angle 55^\circ$. Since both v and i are in phase, the component is a resistor.

$$R = \frac{V_m}{I_m} = \frac{120V}{18 \times 10^{-3}A} = \boxed{6.7k\Omega}$$

16.24) a. $v_L = 100V \sin 377t$, $L = 200mH$

$$\text{Inductive reactance } X_L = \omega L = (377 \text{ rad/s})(200 \times 10^{-3}H) = 75.4\Omega$$

$$I_m = \frac{V_m}{X_L} = \frac{100V}{75.4\Omega} = 1.33A$$

Since current lags voltage by 90° for an inductor,

$$i = \boxed{1.33A \sin(377t - 90^\circ)}$$

16.28) b. $e = 100 \text{ V} \sin \omega t$
 $C = 5 \mu\text{F}$
 $f = 1000 \text{ Hz}$

$i_c = I_m \sin(\omega t + 90^\circ)$ for Capacitors, current always leads voltage by 90°

$\omega = 2\pi f = \frac{2\pi \text{ rad}}{\text{cycle}} (1000 \frac{\text{cycles}}{\text{sec}}) = 6283 \text{ rad/s}$

Capacitive Reactance $X_c = \frac{1}{\omega C}$

$X_c = \frac{1}{(6283 \text{ rad/s})(5 \times 10^{-6} \text{ F})} = 31.8 \Omega$

$I_m = \frac{V_m}{X_c} = \frac{100 \text{ V}}{31.8 \Omega} = 3.14 \text{ A}$

Therefore,

$i_c = 3.14 \text{ A} \sin[(6283 \text{ rad/s})t + 90^\circ]$




16.29) a. $C = 50 \mu\text{F}$
 $v_c = 100 \text{ V} \sin 377t$

$X_c = \frac{1}{\omega C} = \frac{1}{(377 \text{ rad/s})(50 \times 10^{-6} \text{ F})} = 53.1 \Omega$

$I_m = \frac{V_m}{X_c} = \frac{100 \text{ V}}{53.1 \Omega} = 1.88 \text{ A}$

$i_c = 1.88 \text{ A} \sin[(377 \text{ rad/s})t + 90^\circ]$

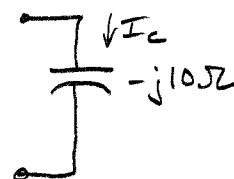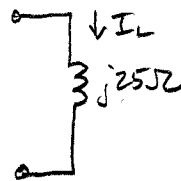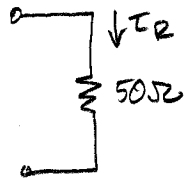16.33) $I = 0.5 \text{ A} \angle 0^\circ$ for each component below.




a) In Phasor Form, voltages are for

Resistor: $V_R = I_R Z_R = (0.5 \text{ A} \angle 0^\circ)(50 \Omega)$

where Z_R is impedance

for resistor.

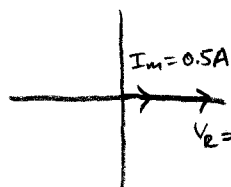


$V_R = (0.5 \text{ A} \cos 0^\circ + 0.5 \text{ A} \sin 0^\circ)j(50 \Omega + 0j)$

$V_R = 25 \text{ V} \angle \tan^{-1} \frac{0}{25} = 25 \text{ V} \angle 0^\circ$

same phase as current.

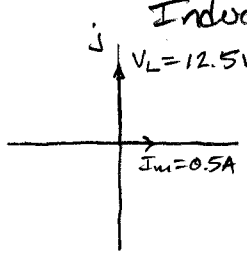
16.33) a. cont'd

Inductor: $V_L = I_L Z_L = (0.5 \angle 0^\circ)(25 \angle j)$
 $= (0.50 \angle 0^\circ + 0.50 \angle 10^\circ j)(25 \angle j)$
 $= 12.5 \angle j$



$V_L = 12.5 \angle 90^\circ$

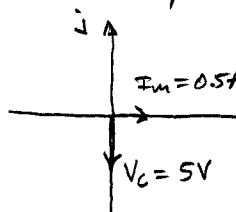Capacitor: $V_C = I_C Z_C = (0.5 \angle 0^\circ)(-10 \angle j)$
 $= (0.50 \angle 0^\circ + 0.50 \angle 10^\circ j)(-10 \angle j)$
 $= -5 \angle j$



$V_C = 5 \angle -90^\circ$

b. In time domain, voltages are

$$V_R = V_{Rm} \sin(\omega t + \theta_R)$$

$$= \sqrt{2}(25) \sin(\omega t + 0^\circ)$$

$V_R = 35.4 \text{ V} \sin \omega t$

$$V_L = V_{Lm} \sin(\omega t + \theta_L)$$

$$= \sqrt{2}(12.5) \sin(\omega t + 90^\circ)$$

$V_L = 17.7 \text{ V} \sin(\omega t + 90^\circ)$

$$V_C = V_{Cm} \sin(\omega t + \theta_C)$$

$$= \sqrt{2}(5) \sin(\omega t - 90^\circ)$$

$V_C = 7.07 \text{ V} \sin(\omega t - 90^\circ)$