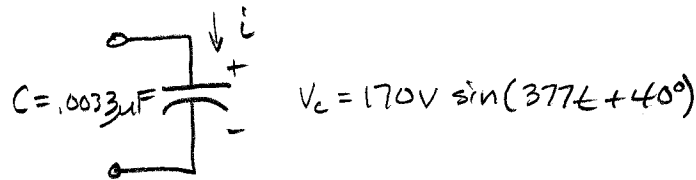


HW #24 Solutions EE301

Ch. 18 #'s 12, 13, 19, 25, 27

18.12)



a. Phasor Form

$$V_c = \frac{170\text{V}}{\sqrt{2}} \angle 40^\circ = \boxed{120\text{V} \angle 40^\circ}$$



b/c. Sinusoidal waveforms and Phasor Diagram

$$Z_c = \frac{-j}{\omega C} = \frac{-j}{(377 \text{ rad/s})(0.0033 \times 10^{-6} \text{ F})} = -804 \text{ k}\Omega j = 804 \text{ k}\Omega \angle -90^\circ$$

$$I_c = \frac{V_c}{Z_c} = \frac{120\text{V} \angle 40^\circ}{804 \text{ k}\Omega \angle -90^\circ} = 149 \mu\text{A} \angle 130^\circ$$


$$I_m = \sqrt{2} I_{\text{rms}} = \sqrt{2} (149 \mu\text{A}) = 211 \mu\text{A}$$
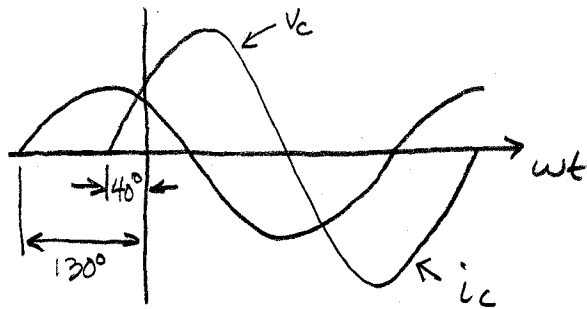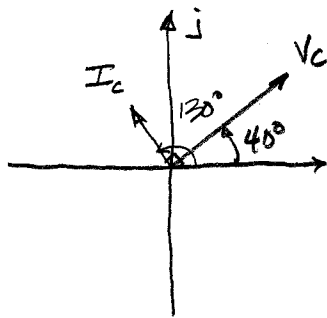
$$i_c = 211 \mu\text{A} \sin(377 \text{ rad/s} t + 130^\circ)$$



Note: Current leads voltage by 90°

18.13) Find Z_T

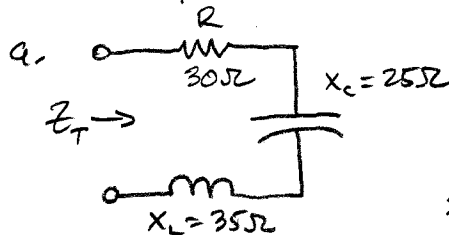

$$Z_R = 30 \Omega$$

$$Z_c = -25 \Omega j$$

$$Z_L = 35 \Omega j$$


$$Z_T = Z_R + Z_c + Z_L = 30 \Omega - 25 \Omega j + 35 \Omega j$$

$$\sqrt{(30 \Omega)^2 + (10 \Omega)^2} = 31.6 \Omega$$

$$\theta = \tan^{-1} \frac{10 \Omega}{30 \Omega} = 18.4^\circ$$

$$\boxed{Z_T = 30 \Omega + 10 \Omega j \text{ rectangular}} \\ \boxed{Z_T = 31.6 \Omega \angle 18.4^\circ \text{ polar}}$$

18.12) b.

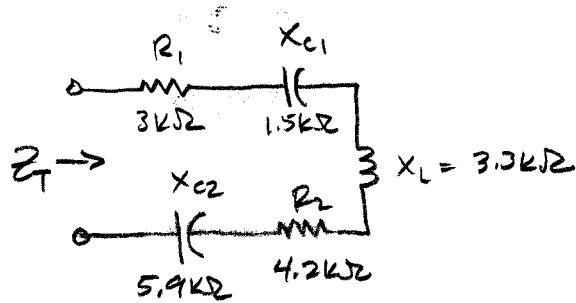

$$Z_{R1} = 3k\Omega, Z_{C1} = -1.5k\Omega j, Z_L = 3.3k\Omega j$$

$$Z_{R2} = 4.2k\Omega, Z_{C2} = -5.9k\Omega j$$

$$Z_T = Z_{R1} + Z_{C1} + Z_L + Z_{R2} + Z_{C2}$$


$$= 3k\Omega - 1.5k\Omega j + 3.3k\Omega j + 4.2k\Omega - 5.9k\Omega j$$

$$= 7.2k\Omega - 4.1k\Omega j$$

$$= \sqrt{(7.2k\Omega)^2 + (-4.1k\Omega)^2} \angle \tan^{-1}\left(\frac{-4.1k\Omega}{7.2k\Omega}\right)$$

$$\boxed{Z_T = 8.3k\Omega \angle -29.7^\circ}$$

18.19)

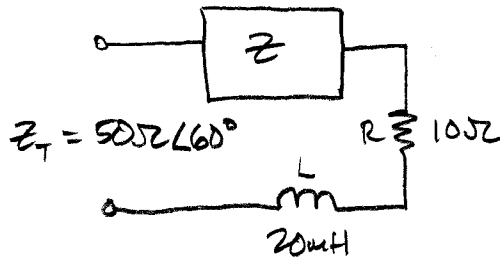

$$f = 1kHz$$

What RLC components are in Z to give ZT?

$$Z_R = 10\Omega, Z_L = \omega L j = (2\pi \frac{rad}{sec} \times 1000 \frac{cycles}{sec} \times 20 \times 10^{-3} H) j$$

$$Z_L = 126\Omega j$$

$$\omega = (2\pi \frac{rad}{s} \times 1000 \frac{cycles}{sec}) = 6283 \frac{rad}{s}$$

$$Z_T = Z + Z_R + Z_L = 50\Omega \angle 60^\circ$$

$$Z = 50\Omega \angle 60^\circ - Z_R - Z_L$$

$$= 50\Omega \cos 60^\circ + 50\Omega \sin 60^\circ j - 10\Omega - 126\Omega j$$

$$= 25\Omega + 43.3\Omega j - 10\Omega - 126\Omega j$$

$$Z = 15\Omega - 82.7\Omega j$$

↑ resistor


↑ Capacitor

$$C = \frac{1}{\omega X_C} = \frac{1}{(6283 \frac{rad}{s})(82.7\Omega)}$$

$$C = 1.92 \times 10^{-6} F$$

Z is a 15Ω resistor in series with a 1.92μF Capacitor

18.25)

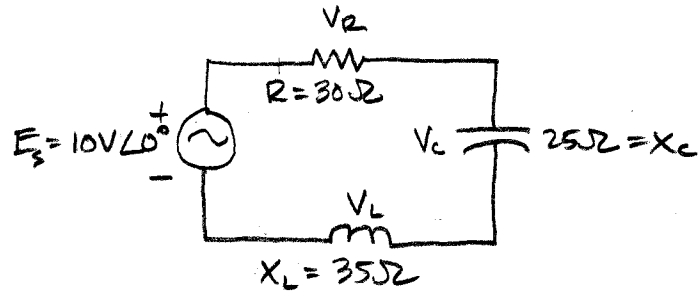

a. Use voltage divider rule to find V_R , V_C , V_L .

From 18.13, we already solved for $Z_T = 31.6\Omega \angle 18.4^\circ$

$$V_R = \frac{Z_R}{Z_T} E_s = \frac{30\Omega \angle 0^\circ}{31.6\Omega \angle 18.4^\circ} (10V \angle 0^\circ) = (0.95 \angle -18.4^\circ) (10V \angle 0^\circ)$$

$$\boxed{V_R = 9.5V \angle -18.4^\circ}$$

$$V_C = \frac{Z_C}{Z_T} E = \frac{25\Omega \angle -90^\circ}{31.6\Omega \angle 18.4^\circ} (10V \angle 0^\circ) = (0.79 \angle -108.4^\circ) (10V \angle 0^\circ)$$

$$\boxed{V_C = 7.9V \angle -108.4^\circ}$$

$$V_L = \frac{Z_L}{Z_T} E = \frac{35\Omega \angle 90^\circ}{31.6\Omega \angle 18.4^\circ} (10V \angle 0^\circ) = (1.11 \angle 71.6^\circ) (10V \angle 0^\circ)$$

$$\boxed{V_L = 11.1V \angle 71.6^\circ}$$

b. $\sum E - \sum V = 0$ Kirchhoff's Voltage Law

$$E_s - V_R - V_C - V_L = 0$$

$$10V \angle 0^\circ - 9.5V \angle -18.4^\circ - 7.9V \angle -108.4^\circ - 11.1V \angle 71.6^\circ = 0$$


$$10V - [9.5V \cos(-18.4^\circ) + 9.5V \sin(-18.4^\circ)j] - [7.9V \cos(-108.4^\circ) + 7.9V \sin(-108.4^\circ)j] - [11.1V \cos(71.6^\circ) + 11.1V \sin(71.6^\circ)j] = 0$$

$$10V - 9.0V + 3.0Vj + 2.5V + 7.5Vj - 3.5V - 10.5Vj = 0$$

$$(10V - 9.0V + 2.5V - 3.5V) + (3.0V + 7.5V - 10.5V)j = 0$$

$$\boxed{0 + 0j = 0}$$

18.27)

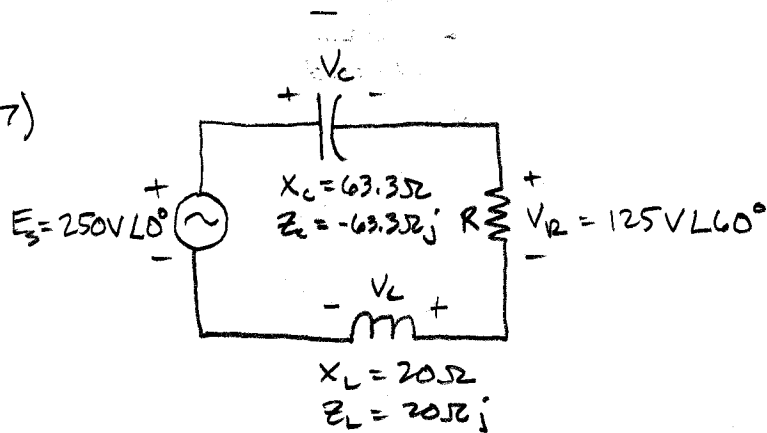a. Find V_C and V_L .

Using KVL,

$$E_s - V_C - V_R - V_L = 0$$

$$\begin{aligned} V_C + V_L &= E_s - V_R \\ &= 250V \angle 0^\circ - 125V \angle 60^\circ \\ &= 250V - 62.5V - 108.2Vj \\ &= 187.5V - 108.2Vj \\ V_C + V_L &= 216V \angle -30^\circ \end{aligned}$$

Then using the voltage divider rule,

$$\begin{aligned} V_C &= \frac{Z_C}{Z_C + Z_L} V_{C+L} = \frac{-63.3\Omega j}{-63.3\Omega j + 20\Omega} (216V \angle -30^\circ) \\ &= (1.46\Omega) (216V \angle -30^\circ) \end{aligned}$$

$$\boxed{V_C = 316V \angle -30^\circ}$$

$$\begin{aligned} V_L &= \frac{Z_L}{Z_C + Z_L} V_{C+L} = \frac{20\Omega j}{-63.3\Omega j + 20\Omega} (216V \angle -30^\circ) \\ &= (-0.46\Omega) (216V \angle -30^\circ) \\ &= -99.8V \angle -30^\circ \end{aligned}$$

$$\boxed{V_L = 99.8V \angle 150^\circ}$$

b. Find R .

$$I_s = \frac{V_L}{Z_L} = \frac{99.8V \angle 150^\circ}{20\Omega \angle 90^\circ} = 5.0A \angle 60^\circ$$

$$Z_R = \frac{V_R}{I_s} = \frac{125V \angle 60^\circ}{5.0A \angle 60^\circ} = 25\Omega \angle 0^\circ$$

$$\boxed{R = 25\Omega}$$

18.27 can be solved another way by using Z_T and Ohm's Law to find I_s and V_R to solve for R . Then, V_C and V_L can be found using Ohm's Law.

$$Z_T = Z_C + Z_R + Z_L = -63.3\Omega j + R + 20\Omega j = R - 43.3\Omega j$$

$$I_s = \frac{E_s}{Z_T} = \frac{250V \angle 0^\circ}{R - 43.3\Omega j} = \frac{250V}{R - 43.3\Omega j}$$

$$Z_R = \frac{V_R}{I_s} = \frac{125V \angle 60^\circ}{250V / (R - 43.3\Omega j)} = \frac{1}{250V} [(125V \angle 60^\circ)(R - 43.3\Omega j)]$$

$$R = Z_R = \frac{1}{250V} [(62.5V + 108.3Vj)(R - 43.3\Omega j)]$$

$$250V(R) = 62.5V(R) - 2706V\Omega j + 108.3V(R)j + 4689V\Omega$$

$$250V(R) = 62.5V(R) + 4689V\Omega + (108.3V(R) - 2706V\Omega j)j$$

The real components on both sides of the equal sign are equal and the same applies to the imaginary components.

$$\text{Real: } 250V(R) = 62.5V(R) + 4689V\Omega$$

$$187.5V(R) = 4689V\Omega$$

$$R = \frac{4689V\Omega}{187.5V} = \boxed{25\Omega}$$

$$\text{Imaginary: } 108.3V(R) - 2706V\Omega = 0$$

$$R = \frac{2706V\Omega}{108.3V} = 25\Omega \checkmark$$

$$\text{So, } I_s = \frac{250V \angle 0^\circ}{25\Omega - 43.3\Omega j} = \frac{250V \angle 0^\circ}{50\Omega \angle -60^\circ} = 5A \angle 60^\circ$$

$$\text{And, } V_C = Z_C I_s = (63.3\Omega \angle -90^\circ)(5A \angle 60^\circ)$$

$$\boxed{V_C = 317V \angle -30^\circ}$$

$$V_L = Z_L I_s = (20\Omega \angle 90^\circ)(5A \angle 60^\circ)$$

$$\boxed{V_L = 100V \angle 150^\circ}$$