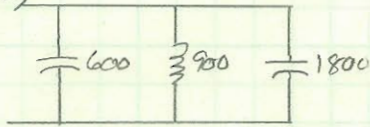


Chap 18 (32, 33a, 36, 41)

18-32REQD: CALCULATE Z_T SOLN:

a)



$$Z_{L1} = -600j$$

$$Z_L = 900j$$


$$Z_{C2} = -1800j$$

$$Z_T = (-600j) \parallel (900j) \parallel (-1800j)$$

$$= \left[\frac{1}{-600j} + \frac{1}{900j} + \frac{1}{-1800j} \right]^{-1}$$

$$= \boxed{900 \angle -90^\circ = Z_T}$$

b)

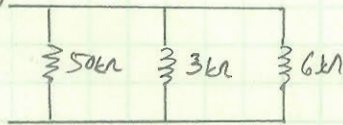

$$Z_R = 50 \angle 0^\circ \text{ k}\Omega$$


$$Z_L = 3 \angle 90^\circ \text{ k}\Omega$$

$$Z_{L2} = 6 \angle 90^\circ \text{ k}\Omega$$

$$Z_T = (50 \angle 0^\circ) \parallel (3 \angle 90^\circ) \parallel (6 \angle 90^\circ) \text{ k}\Omega$$

$$= \left[\frac{1}{50 \angle 0^\circ} + \frac{1}{3 \angle 90^\circ} + \frac{1}{6 \angle 90^\circ} \right]^{-1} \text{ k}\Omega$$

$$= \boxed{2 \angle 87.7^\circ \text{ k}\Omega = Z_T}$$

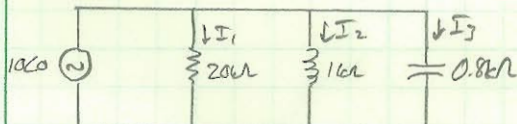18-33aGIVENREQD: Z_T , I_T , I_1 , I_2 , I_3 SOLN

$$Z_T = (20 \text{ k}\Omega) \parallel (1 \text{ k}\Omega \angle 90^\circ) \parallel (0.8 \text{ k}\Omega \angle -90^\circ) = \left[\frac{1}{20 \angle 0^\circ} + \frac{1}{1 \angle 90^\circ} + \frac{1}{0.8 \angle -90^\circ} \right]^{-1} \text{ k}\Omega = \boxed{3.92 \angle -78.7^\circ \text{ k}\Omega = Z_T}$$

$$\vec{I}_T = \frac{\vec{E}}{Z_T} = \frac{10 \angle 0^\circ \text{ V}}{3.92 \angle -78.7^\circ \text{ k}\Omega} = \boxed{2.55 \angle 78.7^\circ \text{ mA} = \vec{I}_T}$$

$$\vec{I}_1 = \frac{\vec{E}}{Z_R} = \frac{10 \angle 0^\circ \text{ V}}{20 \angle 0^\circ \text{ k}\Omega} = 0.5 \angle 0^\circ \text{ mA} = \boxed{500 \angle 0^\circ \mu\text{A} = \vec{I}_1}$$


$$\vec{I}_2 = \frac{\vec{E}}{Z_L} = \frac{10 \angle 0^\circ \text{ V}}{1 \angle 90^\circ \text{ k}\Omega} = \boxed{10 \angle -90^\circ \text{ mA} = \vec{I}_2}$$

$$\vec{I}_3 = \frac{\vec{E}}{Z_C} = \frac{10 \angle 0^\circ \text{ V}}{0.8 \angle -90^\circ \text{ k}\Omega} = \boxed{12.5 \angle 90^\circ \text{ mA} = \vec{I}_3}$$

$$\checkmark \text{ KCL} \rightarrow \vec{I}_T = \vec{I}_1 + \vec{I}_2 + \vec{I}_3 = 0.5 \angle 0^\circ + 10 \angle -90^\circ + 12.5 \angle 90^\circ = 2.55 \angle 78.7^\circ \checkmark$$

18-36

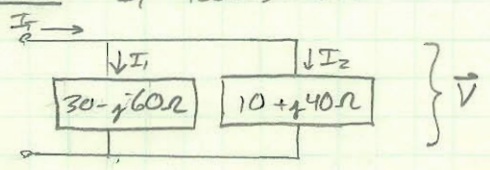GIVEN $I_1 = 100 \angle 30^\circ \text{ mA}$



READ: $Z_T, \bar{V}, \bar{I}_2, \bar{I}_T$

SOLN

$$\bar{V} = \bar{I}_1 \bar{Z}_1 = (100 \angle 30^\circ \text{ mA})(30 - j60) = \boxed{6.71 \angle -39^\circ \text{ V} = \bar{V}}$$


$$\bar{Z}_T = \bar{Z}_1 \parallel \bar{Z}_2 = (30 - j60) \parallel (10 + j40) = \left[\frac{1}{(30 - j60)} + \frac{1}{(10 + j40)} \right]^{-1} = \boxed{61.7 \angle 39^\circ \Omega = \bar{Z}_T}$$

$$\bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2} = \frac{6.71 \angle -39^\circ \text{ V}}{(10 + j40)} = \boxed{163 \angle -109^\circ \text{ mA} = \bar{I}_2}$$

$$\bar{I}_T = \bar{I}_1 + \bar{I}_2 = 100 \angle 30^\circ + 163 \angle -109^\circ \text{ mA} = \boxed{109 \angle -72.5^\circ \text{ mA} = \bar{I}_T}$$

18-41

GIVEN

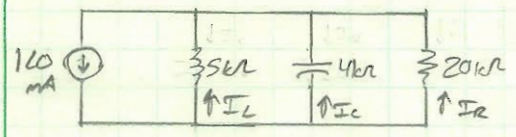

READ: USE CDR TO FIND $\bar{I}_L, \bar{I}_C, \bar{I}_R$. VERIFY KCL.

SOLN

$$\bar{Z}_T = (5000 \angle 90^\circ) \parallel (4000 \angle -90^\circ) \parallel (20000 \angle 0^\circ) = \left[\frac{1}{5290} + \frac{1}{4290} + \frac{1}{2020} \right]^{-1} \Omega = \boxed{14.1 \angle -45^\circ \Omega = \bar{Z}_T}$$

$$\bar{I}_L = \bar{I}_T \left(\frac{\bar{Z}_T}{\bar{Z}_L} \right) = (100 \text{ mA}) \left(\frac{14.1 \angle -45^\circ \Omega}{5290 \Omega} \right) = \boxed{2.82 \angle -135^\circ \text{ mA} = \bar{I}_L}$$

$$\bar{I}_C = \bar{I}_T \left(\frac{\bar{Z}_T}{\bar{Z}_C} \right) = (100 \text{ mA}) \left(\frac{14.1 \angle -45^\circ \Omega}{4290 \Omega} \right) = \boxed{3.53 \angle 45^\circ \text{ mA} = \bar{I}_C}$$

$$\bar{I}_R = \bar{I}_T \left(\frac{\bar{Z}_T}{\bar{Z}_R} \right) = (100 \text{ mA}) \left(\frac{14.1 \angle -45^\circ \Omega}{2020 \Omega} \right) = \boxed{0.705 \angle -45^\circ \text{ mA} = \bar{I}_R}$$

$$\text{KCL} \rightarrow \bar{I}_T = \bar{I}_L + \bar{I}_C + \bar{I}_R = 2.82 \angle -135^\circ + 3.53 \angle 45^\circ + 0.705 \angle -45^\circ \text{ mA} = 1.0 \angle 0^\circ \text{ mA}$$