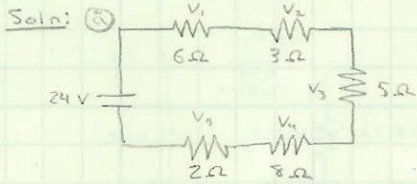


23. Given: resistance and voltage

Reqd: voltage across resistors



$$V_1 = 24V \left( \frac{6\Omega}{24\Omega} \right) \rightarrow V_1 = 6V$$

$$V_4 = 24V \left( \frac{2\Omega}{24\Omega} \right) \rightarrow V_4 = 2V$$

$$V_2 = 24V \left( \frac{3\Omega}{24\Omega} \right) \rightarrow V_2 = 3V$$


$$V_5 = 24V \left( \frac{8\Omega}{24\Omega} \right) \rightarrow V_5 = 8V$$

$$V_3 = 24V \left( \frac{5\Omega}{24\Omega} \right) \rightarrow V_3 = 5V$$

KVL  $\rightarrow 24 = 6 + 3 + 5 + 8 + 2 = 24 \checkmark$

24. Given: voltage and resistance

Reqd: voltage across resistors

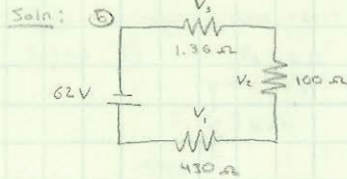

$$V_1 = 62V \left( \frac{430\Omega}{531.36\Omega} \right) \rightarrow V_1 = 50.2V$$


$$V_2 = 62V \left( \frac{100\Omega}{531.36\Omega} \right) \rightarrow V_2 = 11.7V$$

$$V_3 = 62V \left( \frac{1.36\Omega}{531.36\Omega} \right) \rightarrow V_3 = 158.7mV$$

KVL  $\rightarrow 62 \approx 50.2 + 11.7 + 0.16 = 61.86 \checkmark$

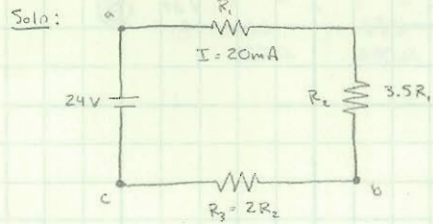25. Given: power, resistance and voltage

Reqd: unknown resistors, voltage across resistors, power dissipated by resistors



$$\textcircled{a} R_t = R_1 + 3.5R_1 + 7R_1 \rightarrow R_t = 11.5R_1$$

$$R_1 = \frac{V_1}{I} \rightarrow R_1 = \frac{2.09V}{.02A} \rightarrow R_1 = 104.5\Omega$$

$$R_2 = 3.5(104.5\Omega) \rightarrow R_2 = 365.8\Omega$$

$$\textcircled{b} V_1 = 24V \left( \frac{R_1}{11.5R_1} \right) \rightarrow V_1 = 2.09V$$

$$R_3 = 2(365.8\Omega) \rightarrow R_3 = 731.6\Omega$$

$$V_2 = 24V \left( \frac{365.8\Omega}{1201.9\Omega} \right) \rightarrow V_2 = 7.30V$$


$$\textcircled{c} P_1 = \frac{V_1^2}{R_1} \rightarrow P_1 = \frac{(2.09)^2}{104.5} \rightarrow P_1 = 41.8mW$$

$$P_2 = \frac{V_2^2}{R_2} \rightarrow P_2 = \frac{(7.30)^2}{365.8} \rightarrow P_2 = 146mW$$

$$P_3 = \frac{V_3^2}{R_3} \rightarrow P_3 = \frac{(14.6)^2}{731.6} \rightarrow P_3 = 291mW$$

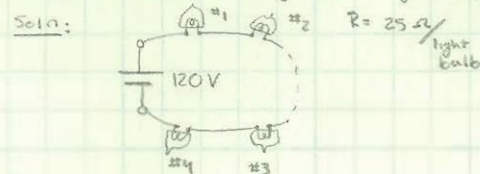27. Given: power, resistance

Reqd: current, voltage across lights, power dissipated



$$\textcircled{a} V = IR \rightarrow I = \frac{V}{R} \rightarrow I = \frac{120V}{600\Omega} \rightarrow I = 200mA$$

$$\textcircled{b} V = 120V \left( \frac{25\Omega}{600\Omega} \right) \rightarrow V = 5V$$

$$\textcircled{c} P = I^2 R \rightarrow P = (.2A)^2 (25\Omega) \rightarrow P = 1W$$

$$\textcircled{d} R_t = 22(25\Omega) \rightarrow R_t = 550\Omega$$

$$I = \frac{120V}{550\Omega} \rightarrow I = 218mA$$

$$P = (.218A)^2 (25\Omega) \rightarrow P = 1.2W$$

$\textcircled{e}$  life expectancy would decrease


$$V = 120V \left( \frac{25\Omega}{550\Omega} \right) \rightarrow V = 5.5V$$

# HW #6

29. Given: power, voltage, resistance, power dissipated

Reqd: voltages  $V_{ab}$  &  $V_{bc}$

Soln:

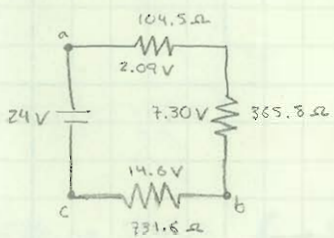

$$V_{ab} = 2.09 \text{ V} + 7.30 \text{ V}$$


$$\boxed{V_{ab} = 9.39 \text{ V}}$$

$$\boxed{V_{bc} = 14.6 \text{ V}}$$

31. Given: resistance

Reqd: voltage across resistors and  $V_a$

Soln: (a)

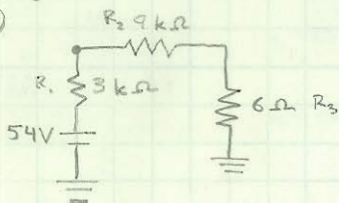


$$V_1 = 54 \text{ V} \left( \frac{3000 \Omega}{18000 \Omega} \right) \rightarrow \boxed{V_1 = 9 \text{ V}}$$

$$V_2 = 54 \text{ V} \left( \frac{9000 \Omega}{18000 \Omega} \right) \rightarrow \boxed{V_2 = 27 \text{ V}}$$

$$V_3 = 54 \text{ V} \left( \frac{6000 \Omega}{18000 \Omega} \right) \rightarrow \boxed{V_3 = 18 \text{ V}}$$
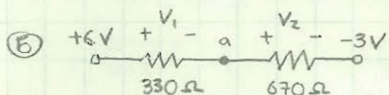
$$V_a = 54 \text{ V} - 9 \text{ V} \rightarrow \boxed{V_a = 45 \text{ V}}$$



$$V_1 = 9 \text{ V} \left( \frac{330 \Omega}{1000 \Omega} \right) \rightarrow \boxed{V_1 = 2.97 \text{ V}}$$

$$V_2 = 9 \text{ V} \left( \frac{670 \Omega}{1000 \Omega} \right) \rightarrow \boxed{V_2 = 6.03 \text{ V}}$$

$$V_a = 6 \text{ V} - 2.97 \text{ V} \rightarrow \boxed{V_a = 3.03 \text{ V}}$$

3-0235 — 5 SQUARES  
 3-0236 — 100 SHEETS — 5 SQUARES  
 3-0237 — 200 SHEETS — 5 SQUARES  
 3-0137 — 200 SHEETS — FILLER

COMET