

HW #8

Solutions EE301

Ch 6 #29, 30, 37, 41

6.29) a.  $I_1 = \frac{R_2}{R_1 + R_2} I_T$  for 2 resistors in parallel

$$I_1 = \frac{2\Omega}{8\Omega + 2\Omega} (10A) = \boxed{2A}$$

$$I_2 = \frac{8\Omega}{8\Omega + 2\Omega} (10A) = \boxed{8A}$$

b.  $I_1 = \frac{R_2}{R_1 + R_2} I_T = \frac{1k\Omega}{3k\Omega + 1k\Omega} (16mA) = \boxed{4mA}$

$$I_2 = \frac{R_1}{R_1 + R_2} I_T = \frac{3k\Omega}{3k\Omega + 1k\Omega} (16mA) = \boxed{12mA}$$

6.30) a.  $I_1 = \frac{R_2}{R_1 + R_2} I_T = \frac{1M\Omega}{1k\Omega + 1M\Omega} (2mA) = \boxed{1.998mA}$


$$I_2 = \frac{R_1}{R_1 + R_2} I_T = \frac{1k\Omega}{1k\Omega + 1M\Omega} (2mA) = \boxed{1.998\mu A}$$

b. Same current divider rule, but variables rearranged.

$$I = 4\mu A = \frac{80\Omega}{16\Omega + 80\Omega} (I_1)$$

$$\boxed{I_1 = 4.8mA}$$
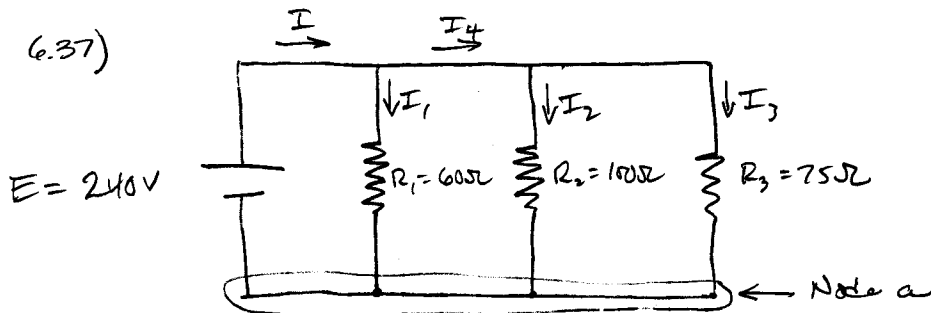
$$I_2 = \frac{16\Omega}{16\Omega + 80\Omega} (4.8mA) = \boxed{0.8mA}$$



a) Find  $R_T$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} = \frac{(60\Omega)(100\Omega)(75\Omega)}{(60\Omega)(100\Omega) + (100\Omega)(75\Omega) + (60\Omega)(75\Omega)}$$

$$R_T = \frac{450000\Omega^3}{6000\Omega^2 + 7500\Omega^2 + 4500\Omega^2} = \boxed{25\Omega}$$

6.37) b. Find  $I, I_1, I_2, I_3$

$$I = \frac{E}{R_T} = \frac{240V}{25\Omega} = \boxed{9.6A}$$

$$I_1 = \frac{E}{R_1} = \frac{240V}{60\Omega} = \boxed{4A}$$

$$I_2 = \frac{E}{R_2} = \frac{240V}{100\Omega} = \boxed{2.4A}$$

$$I_3 = \frac{E}{R_3} = \frac{240V}{75\Omega} = \boxed{3.2A}$$

Using KCL,

$$I = I_1 + I_4$$

$$I_4 = I - I_1 = 9.6A - 4A = \boxed{5.6A}$$

c. Verify KCL at node a

$$\sum I_{\text{entering } a} = \sum I_{\text{exiting } a}$$

$$I_1 + I_2 + I_3 = I$$

$$4A + 2.4A + 3.2A = 9.6A$$

$$9.6A = 9.6A \quad \checkmark$$

$$d. P_1 = I_1^2 R_1 = (4A)^2 (60\Omega) = \boxed{960W}$$

$$P_2 = I_2^2 R_2 = (2.4A)^2 (100\Omega) = \boxed{576W}$$


$$P_3 = I_3^2 R_3 = (3.2A)^2 (75\Omega) = \boxed{768W}$$

$$P_T = I^2 R_T = (9.6A)^2 (25\Omega) = \boxed{2304W}$$

$$P_1 + P_2 + P_3 = 960W + 576W + 768W = \boxed{2304W} \quad \checkmark$$

6.41)

$E = 48V$

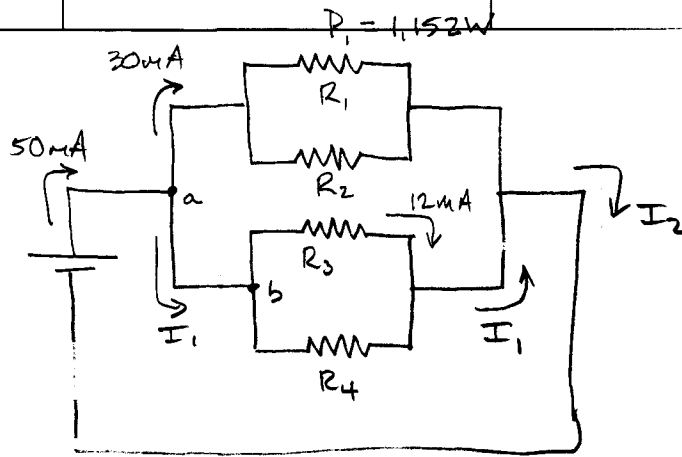

a. Find resistor values

From  $P_1$  and knowing that  $V_1 = E$  (parallel circuit), we can calculate  $R_1$ .

$$P_1 = \frac{V_1^2}{R_1} = \frac{E^2}{R_1} \Rightarrow R_1 = \frac{E^2}{P_1} = \frac{(48V)^2}{1.152W} = \boxed{2k\Omega}$$

After determining  $I_1$ , we can use KCL to calculate  $I_2$  then  $R_2$ .

$$P_1 = I_1^2 R_1 \Rightarrow I_1 = \sqrt{\frac{P_1}{R_1}} = \sqrt{\frac{1.152W}{2000\Omega}} = 0.024A$$

$$I_2 = 30mA - I_1 = 30mA - 24mA = 6mA$$

$$R_2 = \frac{V_2}{I_2} = \frac{E}{I_2} = \frac{48V}{6 \times 10^{-3}A} = \boxed{8k\Omega}$$

Using KCL at node a, we can find the current ( $I_1$ ) to  $R_3$  and  $R_4$  parallel resistors.

$$50mA = 30mA + I_1$$

$$I_1 = 20mA$$

Then, KCL at node b gives  $I_4$

$$I_1 = 12mA + I_4$$

$$20mA = 12mA + I_4$$

$$I_4 = 8mA$$

$$R_4 = \frac{V_4}{I_4} = \frac{E}{I_4} = \frac{48V}{8 \times 10^{-3}A} = \boxed{6k\Omega}$$

Use Ohm's Law to find  $R_3$

$$R_3 = \frac{V_3}{I_3} = \frac{E}{I_3} = \frac{48V}{12 \times 10^{-3}A}$$

$$\boxed{R_3 = 4k\Omega}$$

6.41) b. From part a,

$$\begin{aligned} I_{R_1} &= 24 \text{ mA} \\ I_2 &= 6 \text{ mA} \\ I_4 &= 8 \text{ mA} \end{aligned}$$

c.  $I_1 = 20 \text{ mA}$  from part a using KCL

$$I_2 = I_T = 50 \text{ mA}$$

$$d. P_2 = \frac{V_2^2}{R_2} = \frac{(48 \text{ V})^2}{8 \text{ k}\Omega} = \boxed{0.288 \text{ W}}$$

$$P_3 = \frac{V_3^2}{R_3} = \frac{(48 \text{ V})^2}{4 \text{ k}\Omega} = \boxed{0.576 \text{ W}}$$

$$P_4 = \frac{V_4^2}{R_4} = \frac{(48 \text{ V})^2}{6 \text{ k}\Omega} = \boxed{0.384 \text{ W}}$$