

I. Purpose.

1. Review the computation of the total impedance for AC series/parallel circuits.
2. Review the application of Kirchhoff's current law and the current divider rule to AC series/parallel circuits
3. Introduce the determination of real, reactive and apparent power to a load.

II. Equipment.

- Agilent 34401A Digital Multimeter (DMM)
- Oscilloscope
- Function Generator
- 220-Ω resistor
- 1-mH inductor
- 100-Ω resistor

III. Preparation.

IV. Lab Procedure.

You must read and complete each step.

Step One: Real and Reactive Power

- Compute the total impedance as seen by the ac power source, $e(t) = 5 \sin\{2\pi(20\text{kHz})t\}$, of the ac series/parallel circuit in Figure 1.

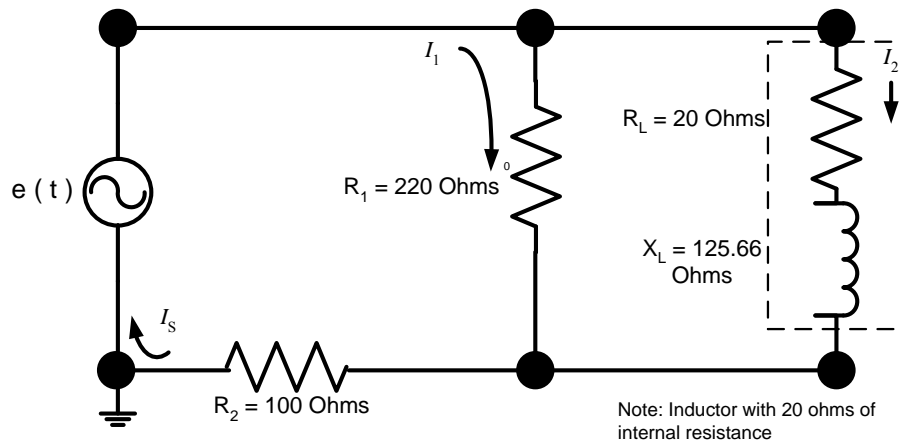


Figure 1

$Z_T =$ _____

- Using Ohm's law and your predicted total impedance (Z_T), calculate the current supplied by the ac power source for $e(t) = 5 \sin\{2\pi(20\text{kHz})t\}$.

$$I_S = \underline{\hspace{10cm}}$$

- Using the current divider rule calculate each branch current.

$$I_1 = \underline{\hspace{10cm}} \quad I_2 = \underline{\hspace{10cm}}$$

- Calculate the real and reactive power of the individual circuit elements in the AC circuit.

$$P_{R1} = \underline{\hspace{10cm}}$$

$$P_{R2} = \underline{\hspace{10cm}}$$

$$P_L = \underline{\hspace{10cm}}$$

$$Q_L = \underline{\hspace{10cm}}$$

Step Two: Power Triangle

- Determine the total apparent power (VA) delivered to this circuit.

$$S_T = \underline{\hspace{10cm}}$$

A Practical Exercise

- In the space provided below sketch the predicted power triangle.

Is the power factor leading or lagging? _____

Step Three: Construct an AC series/parallel circuit

- On a QUAD board construct the ac series/parallel circuit in Figure 1
- Set the function generator to be a sine wave with 10 V_{PP} at 20 kHz.
- Connect your oscilloscope so that CH 1 will measure the ac voltage source and CH 2 will measure the ac voltage across the 100-Ω resistor.
- Use a DMM to measure the output of the function generator. Adjust the function generator amplitude until the DMM displays 3.54 V_{RMS}.

Note:

The function generator voltage output decreases when it is attached to a circuit. The voltage indication on the function generator will not match the actual voltage output. You must adjust the function generator output based upon a DMM reading.

- Using your oscilloscope, determine the ac voltage across the 100-Ω resistor and express your answer in phasor form.

$$V_{100\Omega} = \underline{\hspace{2cm}}$$

- Use your measured value for V_{100Ω} to determine I_S.

$$I_S = \underline{\hspace{2cm}}$$

A Practical Exercise

Step Four: Calculating Real, Reactive, and Apparent power.

- Using your actual AC voltage source and the current that you determined in Step 3, calculate the measured real, reactive and apparent power dissipated by the circuit. Note that $S_T = V_{RMS} I_{RMS}$; θ_Z is the angle of your total impedance, as well as the angle between your source voltage and source current; $P_T = V_{RMS} I_{RMS} \cos(\theta_Z)$; and $Q_T = V_{RMS} I_{RMS} \sin(\theta_Z)$.

$$P_T = \underline{\hspace{2cm}}$$

$$Q_T = \underline{\hspace{2cm}}$$

$$S_T = \underline{\hspace{2cm}}$$