

A Practical Exercise

Name: _____

Section: _____

I. Purpose.

1. Review voltage subscript notation and the measurement of voltages as designated by their subscripts.
2. Introduce the concept of elements that are connected in parallel.
3. Introduce the construction of a DC parallel circuit.
4. Introduce voltage across parallel elements.
5. Introduce the calculation of total resistance of resistive elements connected in parallel.
6. Introduce the application of Kirchoff's Current Law in the analysis of a DC parallel circuit.
7. Introduce the application of the Current Divider Rule in the analysis of a DC parallel circuit.

II. Equipment.

Agilent 34401A Digital Multimeter (DMM)
Agilent E3620A Dual DC Power Supply
Quad Board and Test Leads
560 Ohm resistor
1000 Ohm resistor
220 Ohm resistor

III. Preparation.

Review procedures for measuring resistance, voltage, and current.

IV. Lab Procedure.

Step One: Construct a DC parallel circuit.

- On a QUAD board construct the DC parallel circuit in figure 1. Notice the suggested spacing of the layout allows you to easily measure current through each parallel branch without rebuilding your circuit following each measurement.

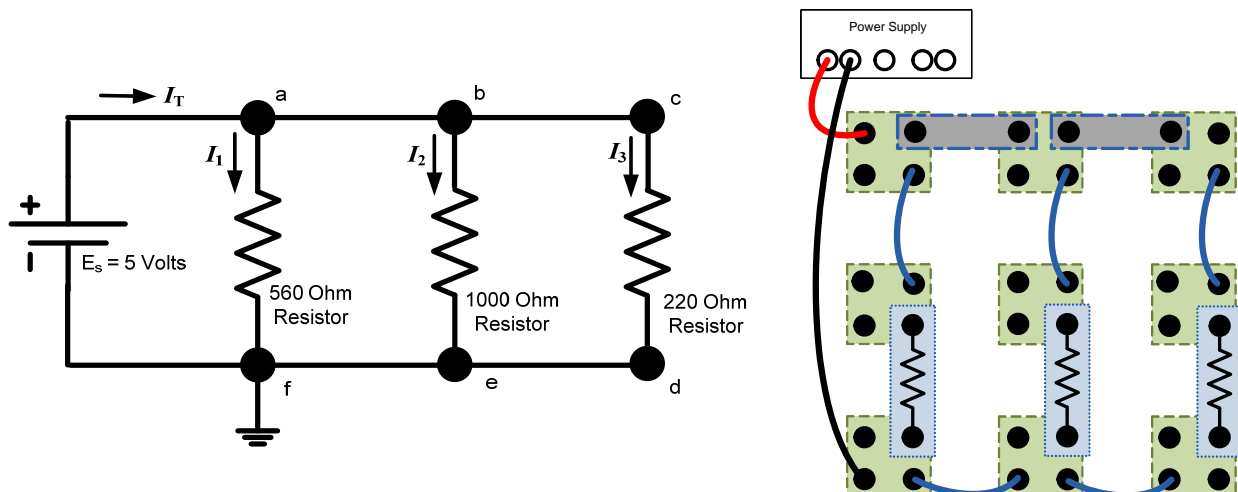


Figure 1
1 of 4

A Practical Exercise

Step Two: Verify voltages of parallel elements and Kirchhoff's current law.

Elements or branches are said to be connected in parallel when they have exactly two nodes in common, and therefore voltages across all parallel elements in a circuit will be the same. Kirchhoff's current law states that the summation of currents entering a node is equal to the summation of currents leaving that node.

Measure the voltages and currents indicated in the table below.

Remember the current that you wish to measure must pass through the DMM. It may be difficult to visualize how to measure the current through each resistor. Figure 2 depicts the measurement of current through the 2200 ohm resistor. Use this figure as a guide for your other current measurements.

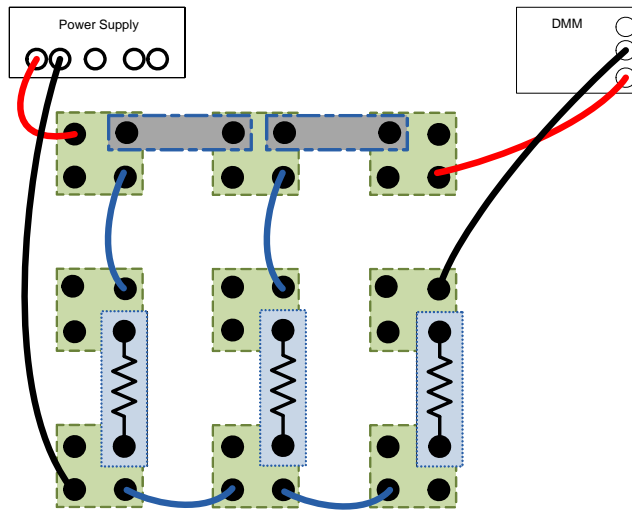


Figure 2

	Measured voltage values		Measured current values
E_s		I_T	
V_{af}		I_1	
V_{be}		I_2	
V_{cd}		I_3	

Are your measured DC voltage values the same? _____

Why? _____

A Practical Exercise

Step Four: Current Divider Rule.

The current divider rule can be used to determine how current entering a node is split between the various parallel resistors connected to the node.

$$I_x = I_T \left(\frac{R_{EQ}}{R_x} \right)$$

I_x is the current through R_x , R_{EQ} is the total resistance of parallel resistors, and I_T is the total source current entering the parallel circuit.

- Calculate the branch currents using the current divider rule, based upon your measured values of I_T and R_{EQ} , and the given resistor values.

$$I_1 = I_T \left(\frac{R_{EQ}}{R_1} \right) = \left(\text{—————} \right) =$$

$$I_2 = I_T \left(\frac{R_{EQ}}{R_2} \right) = \left(\text{—————} \right) =$$

$$I_3 = I_T \left(\frac{R_{EQ}}{R_3} \right) = \left(\text{—————} \right) =$$

For this parallel circuit, how does the measured value of branch currents compared to the calculated values? _____

From this practical exercise, what observation can we make about the relative values of resistance and the current flow through resistors? (Think of the phrase, “the path of least resistance”.) _____
