

I. Purpose.

1. Review the concept of Thevenin's Theorem for determining the Thevenin equivalent circuit of a DC series/parallel circuit from the standpoint of a two terminal load.
2. Review the use of nodal analysis to determine unknown voltages and branch currents in a DC series/parallel circuit.
3. Introduce the concept of the maximum power transfer theorem.

II. Equipment.

- Agilent 34401A Digital Multimeter (DMM)
- Agilent E3620A Dual DC Power Supply
- Quad Board and Test Leads
- Variable Ohm resistor
- 100 Ohm resistor
- 330 Ohm resistor
- 470 Ohm resistor
- 680 Ohm resistor
- 1000 Ohm resistor

III. Preparation.

Review procedures for measuring resistance, voltage, and current.

IV. Lab Procedure.

You must **read** and complete each step.

Step One: Circuit Analysis.

- Use any circuit analysis technique (preferably nodal analysis, etc.) determine I_L , V_{ab} , and P_{load} when R_{load} is 1000Ω in this DC series parallel network (Figure 1).

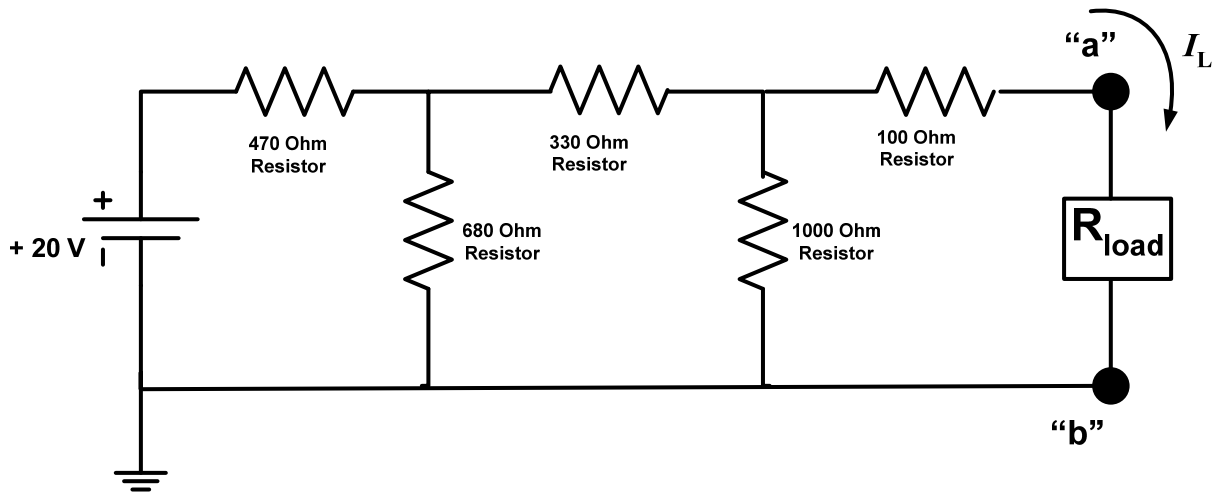


Figure 1

A Practical Exercise

Why or Why not? _____

Is this circuit supplying the maximum power to R_{load} ? _____

Why or Why not? _____

Step Four: Construct the DC series-parallel circuit.

- On a QUAD board construct the DC series-parallel circuit in Figure 2.

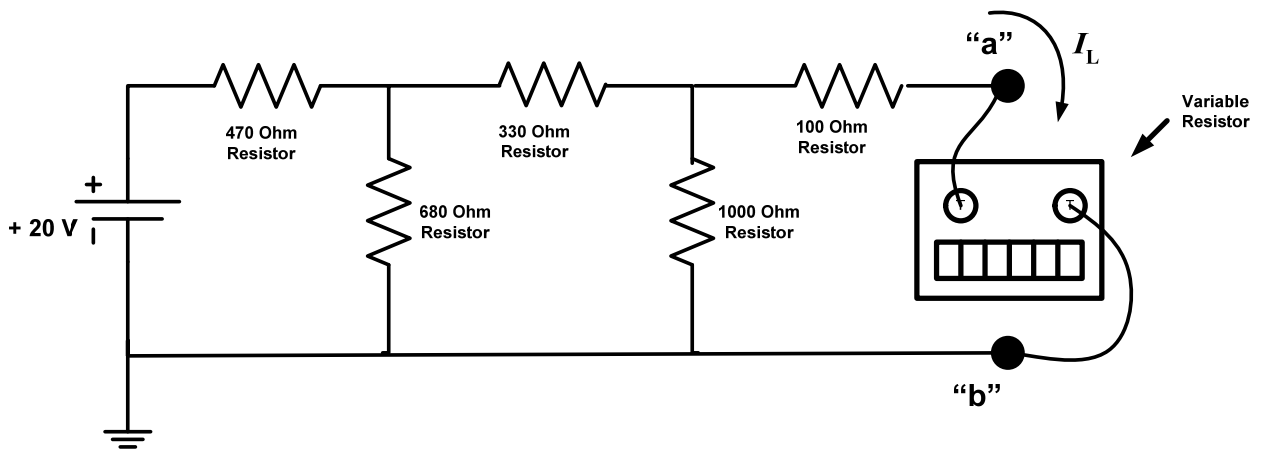


Figure 2

- Insert your DMM into your circuit such that it always displays the load current, I_L .
- Set the variable resistor to 2500 Ω .
- Record $I_{L2500\Omega}$
- Set the variable resistor to 200 Ω .
- Record $I_{L200\Omega}$
- Set the variable resistor to R_{th} .
- Record $I_{R(\text{Thevenin})}$

A Practical Exercise

	Measured current		Calculated power dissipated by the R_{load}
$I_{L2500\Omega}$		$P_{L2500\Omega}$	
$I_{L200\Omega}$		$P_{L200\Omega}$	
$I_{R(Thevenin)}$		$P_{R(Thevenin)}$	

Do your power values verify the Maximum Power Transfer theorem? _____

Explain. _____
