

I. Purpose.

1. Review the construction and analysis of AC circuits using a DMM and/or oscilloscope.
2. Introduce the determination of the Thevenin equivalent circuit for an AC circuit.
3. Introduce the Maximum Power Transfer Theorem for AC circuits.

II. Equipment.

- Agilent 34401A Digital Multimeter (DMM)
- Oscilloscope
- Function Generator
- 220 Ohm resistor
- 47 mH inductor
- Variable resistor
- Variable capacitor

III. Preparation.

IV. Lab Procedure.

You must read and complete each step.

Step One: Impedance for maximum power.

- Determine the value of load impedance required so that the load receives the maximum amount of power from the circuit (Figure 1). Note: Use a DMM and a inductor / capacitor analyzer to determine actual resistance and inductance values.

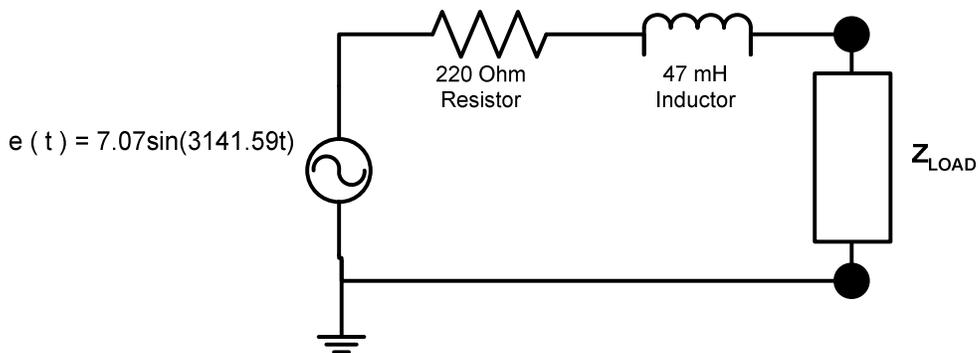


Figure 1

$Z_{Load} =$ _____

A Practical Exercise

- Determine the value of the Z_{LOAD} components (ohms, henries, and/or farads).

Step Two: Construct the AC Circuit.

- Construct this circuit (Figure 1) to include the components that you calculated for Z_{LOAD} .

- Using any meter or scope:

- Measure the **actual** voltage output of your function generator under this circuit's load and adjust your function generator as necessary to ensure that it is providing the voltage output specified in Figure 1.
- Measure the phase relationship between the source voltage and the current.

$$\Theta = \underline{\hspace{10em}}$$

- Calculate the total current I_S .

$$I_S = \underline{\hspace{10em}}$$

- Calculate the real power P_T dissipated in the circuit.

$$P_T = \underline{\hspace{10em}}$$

- Calculate the reactive power Q_T in the circuit.

$$Q_T = \underline{\hspace{10em}}$$

- Calculate the total apparent power S_T in the circuit.

$$S_T = \underline{\hspace{10em}}$$