

AC Thevenin and Maximum Power

A Practical Exercise

Name: _____

Section: _____

I. Purpose.

1. Review how to construct and analyze AC circuits with DMM and oscilloscope.
2. Introduce how to determine the Thevenin's equivalent for AC circuits.
3. Introduce the Maximum Power Transfer Theorem for AC circuits.

II. Equipment.

Agilent 34401A Digital Multimeter (DMM)

Oscilloscope

Function Generator

220 Ohm resistor

47 mH inductor

Variable resistor

Variable capacitor

III. Preparation.

IV. Lab Procedure.

You must **read** and complete each step.

Step One: Impedance for maximum power.

- Determine the value of load impedance required so that the load receives the maximum amount of power from the circuit (Figure 1). Note: Use a DMM and a inductor / capacitor analyzer to determine actual resistance and inductance values.

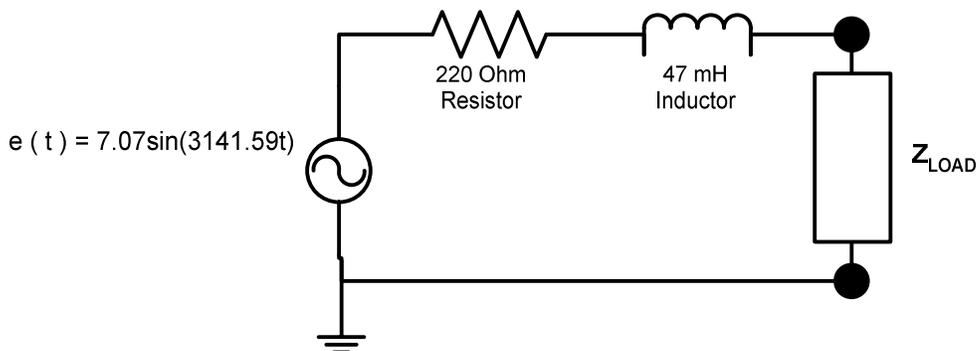


Figure 1

$$Z_{Load} = \underline{\hspace{10em}}$$

A Practical Exercise

- Determine the value of the Z_{LOAD} components (ohms, henries, and/or farads).

Step Two: Construct the AC Circuit.

- Construct this circuit (Figure 1) to include the components that you calculated for Z_{LOAD} .

- Using any meter or scope:

- Measure the **actual** voltage output of your function generator under this circuit's load and adjust your function generator as necessary to ensure that it is providing the voltage output specified in Figure 1.
- Measure the phase relationship between the source voltage and the current.

$$\Theta = \underline{\hspace{10em}}$$

- Calculate the total current I_S .

$$I_S = \underline{\hspace{10em}}$$

- Calculate the real power P_T dissipated in the circuit.

$$P_T = \underline{\hspace{10em}}$$

- Calculate the reactive power Q_T in the circuit.

$$Q_T = \underline{\hspace{10em}}$$

- Calculate the total apparent power S_T in the circuit.

$$S_T = \underline{\hspace{10em}}$$