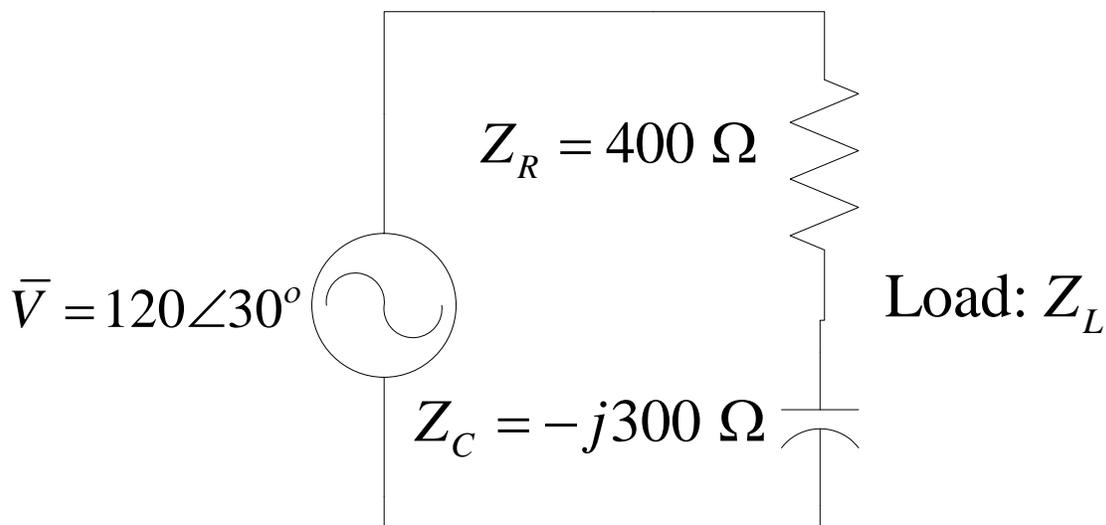


# Complex Power Calculations

AsstProf Jones -- Fall 2007

There are several techniques for calculating the real, reactive, and apparent powers of arbitrary impedances. Some common methods potentially require a large number of steps; however, in some cases, it may be desirable to use an alternate approach. Specifically, the approach presented here is widely applicable, and often requires fewer (*or less tedious*) calculations.

Now, let's agree on the notation we're going to use. In these problems, we'll be making use of voltage and current RMS phasors,  $\bar{V}$  and  $\bar{I}$ . The bar over the letters indicates that V and I are **phasored quantities**; i.e. they are expressed as complex numbers, typically in polar form. For example, the sinusoidal voltage,  $v(t) = 120\sqrt{2} \sin(120\pi t + 60^\circ)$ , has an RMS voltage phasor of  $\bar{V} = 120\angle 60^\circ$ . (*Note, the  $\sqrt{2}$  went away when converting from peak to RMS*) Next, we need to review the complex conjugate operator, “\*”. For example, the complex conjugate of  $\bar{I}$  is written  $\bar{I}^*$ . Mathematically, if  $\bar{I} = 15\angle 30^\circ$ , then  $\bar{I}^* = 15\angle -30^\circ$  (*just flip the sign on the angle*). Additionally, if the value is expressed in rectangular form, as is often the case for impedances, it's just as easy. Suppose that  $Z = 3 + j4$ , then  $Z^* = 3 - j4$  (*just flip the sign of the imaginary part*). Now, let's move to the actual calculations. Suppose that you have the following circuit (*you'll need to convert the R's, L's and C's to Z's and sources to phasors first*):



Now the question is, “*What are the real, reactive, and apparent powers in the load?*” Answering this question is simple with the alternative approach.


The equation you'll be using is:

$$S = P + jQ = \bar{V} \bar{I}^* = \frac{\bar{V}\bar{V}^*}{Z^*} = \bar{I} \bar{I}^* Z \quad (1.1)$$

So, in the circuit above, since we know the voltage across the entire load, and we know the impedance of the load, we have that:

$$\begin{aligned} S &= \frac{\bar{V}\bar{V}^*}{Z^*} = \frac{(120\angle 30^\circ)(120\angle 30^\circ)^*}{(400 - j300)^*} = \frac{(120\angle 30^\circ)(120^\circ \angle -30^\circ)}{(400 + j300)} \\ &= \frac{120^2}{400 + j300} \approx (23.0 - j17.3) \text{ VA} \end{aligned}$$

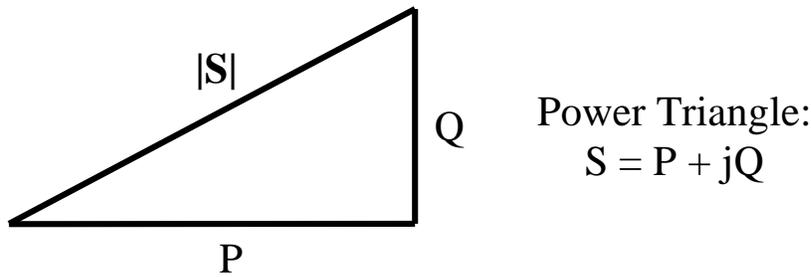This means that the **real power is 23.0 W** and the **reactive power is 17.3 VAR** capacitive. Since the apparent power is the hypotenuse of the power triangle: (*remember that S is a complex number, so its magnitude is the length of the hypotenuse*)



If we convert S into polar form using the calculator, we'll get that:

$$S = (23.0 - j17.3) = 28.8\angle 36.9^\circ \text{ VA}$$

This means that the **apparent power is 28.8 VA**.

*Although the complex power S can be expressed as a polar number, it IS NOT a phasor. Remember, phasors come from sinusoids in the time domain, and that's not what's going on here.*

That's it. We're done.