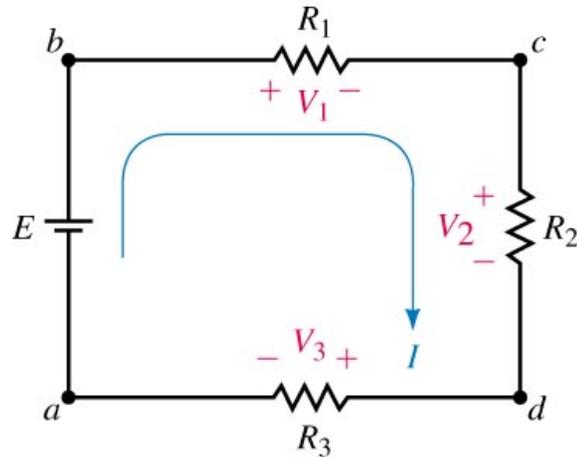


Series and Parallel Duality

Series



I is the same through E, R_1, R_2, R_3

Total Resistance: $R_T = R_1 + R_2 + R_3$

KVL: $\sum V_{\text{closed loop}} = 0$

$$\sum E_{\text{rise}} = \sum V_{\text{drop}}$$


$$E = V_1 + V_2 + V_3$$

Voltage Divider $V_x = E \frac{R_x}{R_T}$

R_T is the total resistance for the resistors/components that are in series.

E is the total voltage of the resistors/components that are in series.

Parallel

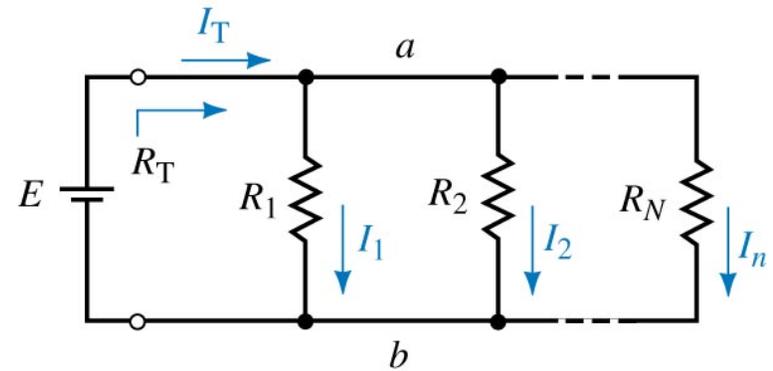

Voltage is the same across E, R_1, R_2, \dots, R_N

Total Resistance: $R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$

KCL: $\sum I_{\text{node}_a} = 0$

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

$$I_T = I_1 + I_2 + \dots + I_n$$

Current Divider $I_x = I_T \frac{R_T}{R_x}$

R_T is the total resistance for the resistors/components that are in parallel.

Series and Parallel Duality