



### What do we know?

R1 and R3 have the same current ( $I_T$ ) and are in series.

R4 and R5 have the same current ( $I_y$ ) and are in series.

R2 is in parallel with  $R_y$  ( $R_4 + R_5$ )

R2 has the same voltage drop as  $R_y$  ( $R_4 + R_5$ ) (KVL)

$$I_T = I_y + I_x \quad (\text{KCL})$$

$$I_T = \frac{E}{R_T} \quad (\text{Ohm's Law})$$

$$R_{\text{series}} = R_1 + R_3$$

$$R_{\text{parallel}} = \left[ R_2 \parallel (R_4 + R_5) \right] = \frac{1}{\frac{1}{R_2} + \frac{1}{(R_4 + R_5)}}$$

$$R_T = R_{\text{series}} + R_{\text{parallel}}$$

$$E = V_{R1} + V_{R2} + V_{R3} \quad \text{or} \quad E = V_{R1} + V_{R3} + V_{R4} + V_{R5} \quad (\text{KVL})$$

$$V_{R1} = I_T R_1, \quad V_{R3} = I_T R_3$$

$$I_y = I_T \frac{R_{\text{parallel}}}{R_y} = I_T \frac{R_2 \parallel (R_4 + R_5)}{R_4 + R_5} \quad (\text{Current Divider rule})$$

$$I_x = I_T \frac{R_{\text{parallel}}}{R_x} = I_T \frac{R_2 \parallel (R_4 + R_5)}{R_2} \quad (\text{Current Divider rule})$$

$$\text{or} \quad I_x = I_T - I_y$$

$$V_{R2} = V_{R4} + V_{R5} \quad \text{or} \quad V_{R2} = I_x R_2$$