

Review #2 - Major Topics

1. Capacitors & Transient Response
2. Inductors & Transient Response
3. Capacitor/ Inductor Thevenin Problems
4. Sinusoidal Waveforms, Peak & RMS Values
5. AC Response & Average Power
6. Power Factor
7. Complex Numbers & Phasors
8. AC Series & AC Parallel Circuits
9. Circuit Simplification Techniques
10. AC Thevenin Circuits - E_{TH} and Z_{TH}
11. Max Power Transfer in AC Circuits
12. AC Power & AC Power Triangle
13. Power Factor Correction
14. RLC Circuits & Resonance

Short Answer #2

1. The impedance of an Inductor at steady state when a DC voltage is applied across a series RL circuit is ∞ ohms.
2. The impedance of a Capacitor appears to be an (Short Open) Circuit at steady state when a DC voltage is applied across a series RC circuit.
3. To produce a transient response in an RL or RC series circuit, use a (DC AC) signal voltage applied through a switch.
4. Steady State conditions are achieved in response to a transient signal excitation in a series RC or RL circuit after (1τ 3τ 5τ) time constants.
5. Current in an RL series circuit (Leads Lags) the AC voltage applied across the terminals of the inductor.
6. The formula for calculating the time constant in an RL circuit that has a sudden voltage applied is ($\tau = L/R$ $\tau = L \cdot R$ $\tau = R/L$).
7. The formula for calculating the time constant in an RC circuit that has a sudden voltage applied is ($\tau = C/R$ $\tau = R \cdot C$ $\tau = R/C$).

8. The period for an AC sinusoidal voltage of frequency 20 KHZ is:

- (50 μ sec) 50 msec 5 msec).

9. $\pi/6$ radians converts to (30 deg) 60 deg 90 deg).

X 10. An AC waveform is expressed as $v(t) = 100 \sin 6283t$ in the time domain. This waveform has a frequency of (60 Hz 100 Hz 1000 KHz). 1000 Hz

11. The rectangular expression $(3 + j4)$ is equivalent to what in polar form:

- ($5 \angle 0^\circ$ $5 \angle 36.9^\circ$ $5 \angle 53.1^\circ$).

12. The Inductive reactance of a 5mH inductor at DC is: (0 Ω 5 Ω Open circuit).

13. Steady State conditions are achieved in response to a transient signal excitation in a series RC or RL circuit with a time constant of 5 seconds in:

- a. 5 seconds
- b. 10 seconds
- c. 20 seconds
- d. 25 seconds

14. $\pi/2$ radians converts to:

- a. 30 degrees
- b. 60 degrees
- c. 90 degrees
- d. 180 degrees

15. An AC waveform is expressed as $v(t) = 200 \sin 377t$ in the time domain. The RMS value of the voltage is:

- a. 141.4 volts
- b. 200 volts
- c. 70.7 volts
- d. 377 volts

16. The rectangular expression $(4 + j3)$ for Impedance is equivalent to what in polar form:

- a. $Z = 5$ at 0 degrees
- b. $\underline{Z = 5}$ at 36.9 degrees
- c. $Z = 5$ at 53.1 degrees
- d. $Z = 5$ at 90.0 degrees

17. True / False A lagging Power Factor means the circuit is inductive


18. True / False Adding a DC voltage to an AC waveform changes the period of the AC waveform.

19. True / False An AC waveform is applied to a purely capacitive load. The phase angle of the current through the inductor will be = + 90 degrees.

20. True / False At Resonance, the Impedance of an RLC circuit is purely inductive.

1) EE-301 REVIEW A - Exam #2

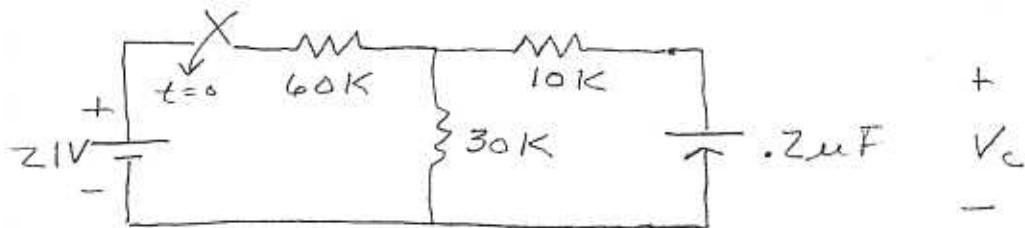1. GIVEN THE FOLLOWING CIRCUIT, CALCULATE THE CHARGING TIME CONSTANT τ_c



$$a) \tau_c = (30k)(0.2 \times 10^{-6}) \\ = 6 \times 10^{-3} = 6 \text{ msec}$$

$$R_{TH} = \frac{60k \parallel 30k + 7k}{20k + 10k} = 30k$$

$E_{TH} = 7V$
 $R_{TH} = 30k$

b) WRITE THE EXPRESSION FOR $V_c(t)$

$$V_c = V_f + (V_i - V_f) e^{-t/\tau} \\ = 7 + (0 - 7) e^{-t/6} = 7(1 - e^{-t/6}) \text{ VOLTS}$$

c) WRITE THE EXPRESSION FOR $I_c(t)$

$$I_c = A e^{-t/\tau} = \frac{7}{30k} = 0.233 \text{ mA } e^{-t/6}$$

d) THE SWITCH IS OPENED AT $t = 1$ SECOND,
WRITE THE EQUATION FOR $V_c(t)$ AFTER
1 SECOND.

$$R = 40k \quad C = 0.2 \mu F \\ \tau = (40k)(0.2 \mu F) = 8 \text{ msec}$$

$$V_c = V_f + (0 - V_f) e^{-t/\tau} \\ = 0 + (7 - 0) e^{-t/8} = 7 e^{-t/8}$$

2) EE-301 REVIEW A


2. FOR THE DIAGRAM BELOW, WHICH IS ALWAYS TRUE

A $I_s = I_3 \quad \times$

B $I_3 = I_4 + I_6 - I_4 + I_5 = \boxed{I_4 + I_6}$

C $I_3 = I_2 + I_5 \quad \times$

D $I_4 = I_6 \quad \times$

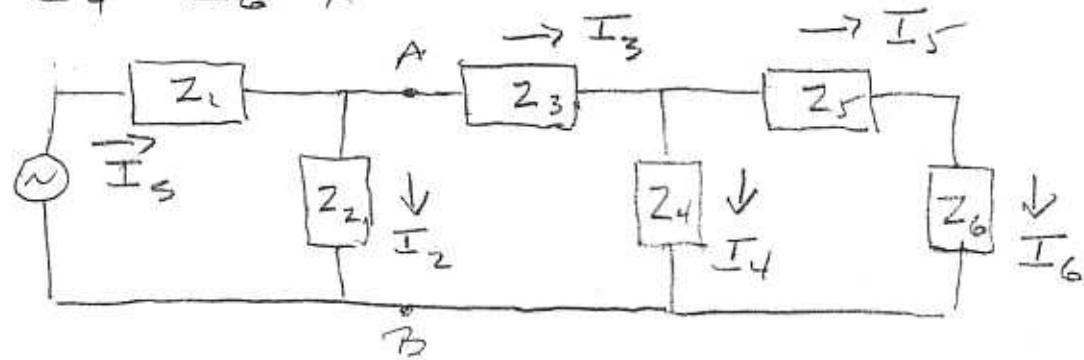

b) WRITE THE IMPEDANCE SEEN FROM TERMINALS AB AND LOOKING TO THE RIGHT

$$Z_{AB} = \underline{\underline{[(Z_5 + Z_6) \parallel Z_4] + Z_3}}$$

3. EE-301 REVIEW A

3. GIVEN THE CIRCUIT AND THE FOLLOWING INFORMATION, DETERMINE THE CIRCUIT COMPONENT OR COMPONENTS.



$$Z = \frac{16V \angle 65^\circ}{2mA \angle -25^\circ} = 8K \angle 90^\circ$$

$$V = 16V \angle 65^\circ$$

$$I = 2mA \angle -25^\circ$$

$$Z = \underline{8K \angle 90^\circ}$$

COMPONENT (R, L, C)
CIRCLE ONE

IF $\omega = 1000 \text{ RAD/SEC}$, DETERMINE THE VALUE OF THE ELEMENT IN R, H, OR F.

$$X_L = \omega L$$

$$\text{VALUE} = \underline{\underline{8H}}$$


$$8K = \omega L$$

$$= 10^3 L$$

$$L = \frac{8K}{10^3} = \underline{\underline{8H}}$$

4 EE-301 REVIEW A

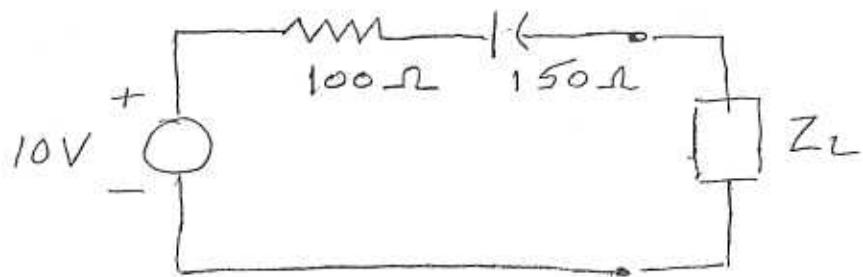4. A THEVENIN CIRCUIT IS SHOWN FOR A NETWORK WITH A LOAD.



- A) DETERMINE Z_L FOR MAX POWER TO LOAD

$$Z_L = \boxed{100 + 150}$$

- B) WHAT 2 ELEMENTS MAKE UP THIS LOAD

ELE #1 RESISTOR

ELE #2 INDUCTOR

- c) DETERMINE THE MAX POWER DELIVERED


$$P_{MAX} = \frac{E_{TH}^2}{4R_{TH}} = \frac{10^2}{4(100)} \quad P_{MAX} = \boxed{.25 \text{ WATTS}}$$

$$= \frac{100}{4(100)} = \frac{1}{4}$$

$$I = \frac{10}{200} = 50 \text{ mA}$$

$$P = I^2 R \\ = (50 \times 10^{-3})^2 (10^2) = \boxed{.25 \text{ WATTS}}$$

5 EE-301 REVIEW A

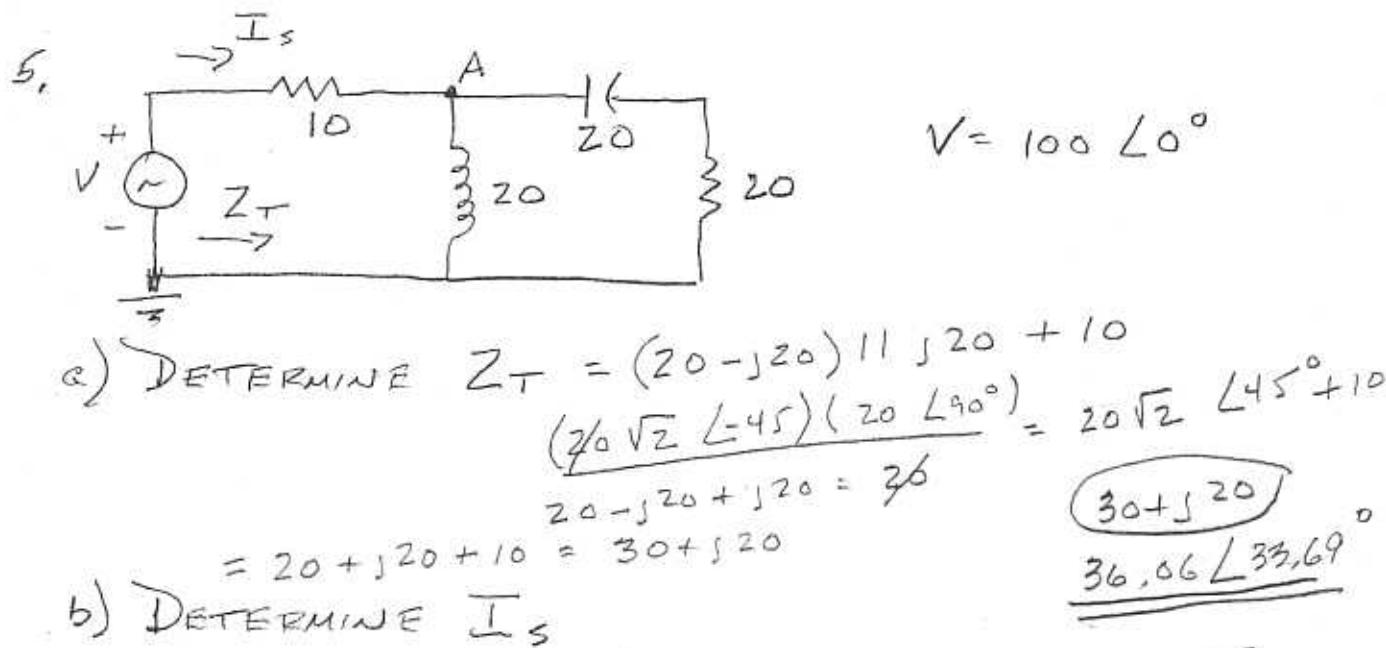

c) DETERMINE V_A

$$V_A = \frac{Z_{II}(V)}{Z_T} = \frac{(20\sqrt{2} \angle 45^\circ)(10 \angle 0^\circ)}{36.06 \angle -33.69^\circ}$$

$$= \underline{\underline{78.43 \angle 78.69^\circ \text{ Volts}}}$$


(1) EE-301 Review 3

Answers

1. $Z_T = 16 + j12 \quad V = 20 \angle 30^\circ$

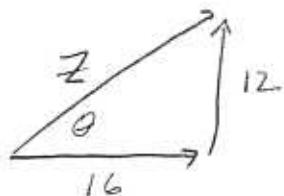A. $Z_T = 16 + j12$

$$Z = \sqrt{16^2 + 12^2} = \underline{\underline{20 \angle 36.9^\circ}}$$



$$Z = 20 \quad \theta = 36.9^\circ$$

B. $\underline{I} = \frac{V}{Z} = \frac{20 \angle 30^\circ}{20 \angle 36.9^\circ} = \underline{\underline{1A \angle -6.9^\circ}}$

C. $V = 20V \angle 30^\circ$


$$\begin{aligned} V(+ &)= 20\sqrt{2} \sin(\omega t + 30^\circ) \text{ Volts} \\ &= 28.28 \sin(\omega t + 30^\circ) \text{ Volts} \end{aligned}$$

$$\underline{I} = 1A \angle -6.9^\circ$$

$$\begin{aligned} I(+) &= (1)\sqrt{2} \sin(\omega t - 6.9^\circ) \text{ Amperes} \\ &= 1.414 \sin(\omega t - 6.9^\circ) \text{ Amperes} \end{aligned}$$

D. $S = \sqrt{I^*} = (20 \angle 30^\circ)(1 \angle +6.9^\circ)$
 $= 20 \angle 36.9^\circ \text{ Watts}$

Power

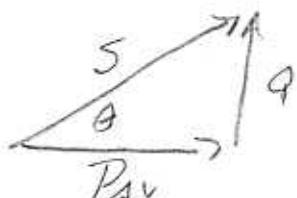

$$S = 20 \angle 36.9^\circ = \underline{\underline{20 \text{ Watts}}}$$

$$P_{AV} = 20 \cos 36.9^\circ$$

$$P = \underline{\underline{16 \text{ Watts}}}$$


$$Q = 20 \sin 36.9^\circ$$

$$Q = \underline{\underline{12 \text{ VAR}}}$$

$$F_P = \cos \theta = \underline{\underline{.80}}$$


(2) EE-301 Review B

ANSWERS

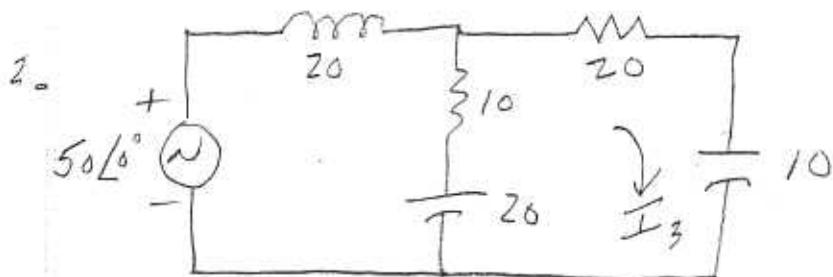

$$\begin{aligned}
 A \quad Z_T &= (Z_0 - j10) || (10 - j20) + j20 \\
 &= \frac{(22.36 \angle -26.57^\circ)(22.36 \angle 63.43^\circ)}{20 - j10 + 10 - j20} + j20 \\
 &= \frac{(22.36 \angle -26.57^\circ)(22.36 \angle -63.43^\circ)}{42.43 \angle -45^\circ} + j20 \\
 &= 11.78 \angle -45^\circ + j20 \\
 &= 8.33 - j8.33 + j20 = \underline{\underline{8.33 + j11.67}} \\
 &= \underline{\underline{14.34 \angle 54.48^\circ}}
 \end{aligned}$$
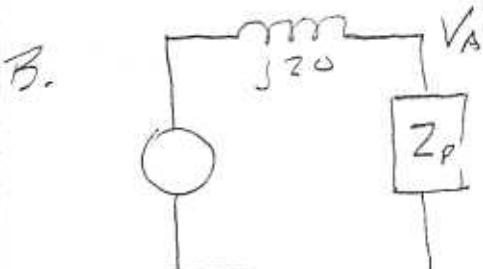
$$I = \frac{V}{Z_T} = \frac{50 \angle 0^\circ}{14.34 \angle 54.48^\circ} = \underline{\underline{3.49 A \angle -54.48^\circ}}$$



$$\begin{aligned}
 Z_p &= \text{Parallel Comb.} \\
 &= 11.78 \angle -45^\circ
 \end{aligned}$$

$$V_A = \frac{Z_p \times V_s}{Z_T} = \frac{11.78 \angle -45^\circ (50)}{14.34 \angle 54.48^\circ}$$

$$I_3 = \frac{V_A}{20 - j10} = \frac{41.07 \angle -99.48^\circ}{22.36 \angle -26.51^\circ} = 41.07 \angle -99.48^\circ$$

$$I_3 = 1.837 \angle -72.91^\circ$$

(3) EE-301 Review B

Answers

B CONT'D

$$V_{C2} = (I_3)(Z_{C2}) = (1.837 \angle -72.91^\circ)(10 \angle -90^\circ)$$
$$= \underline{18.37 \angle -162.91^\circ \text{ Volts}}$$

C. Power Factor

$$F_p = \cos \theta = \cos(54.48^\circ)$$
$$= \underline{\underline{.58}}$$


$\theta = +54.48^\circ$ so ELI
LAGGING (SEE I ALSO)

D. $X_C = 10 = 1/2\pi f C \Rightarrow 10 = 1/2\pi(10^4)(10)$


$$C = \frac{1}{2\pi(10^4)(10)} = .00159 \times 10^{-3}$$
$$= 1.59 \times 10^{-6} = \underline{\underline{1.59 \mu F}}$$

(4) EE-301 Review B Answers

3. LEFT SIDE DOES NOT APPLY

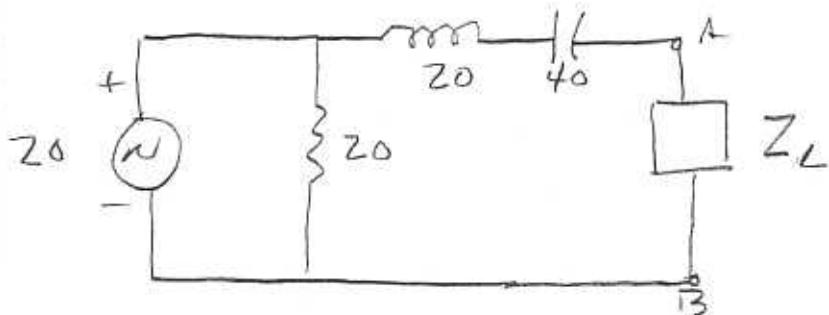


A) REMOVE LOAD. LOOK AT AB. SHORT SOURCE

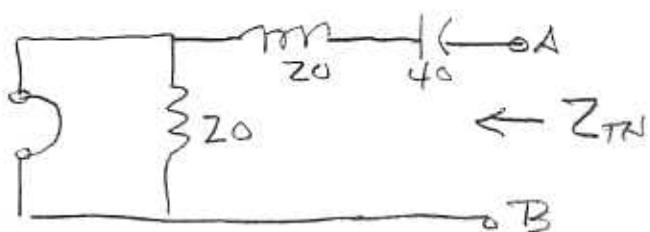

$$\begin{aligned} Z_{TH} &= (0 || 20) + j20 - j40 \\ &= 0 + j20 - j40 = -j20 = 20 \angle -90^\circ \end{aligned}$$

$$E_{TH} = E_{Z_0||} = E_{AB} = 20V \angle 0^\circ$$

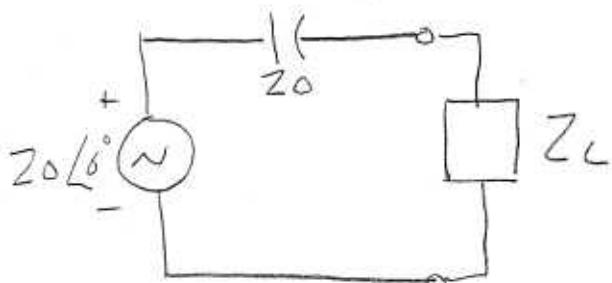

$$Z_L = Z_{TH}^* = 20 \angle +90^\circ = j20 = \text{INDUCTOR}$$

$$X_L = 20 \Omega$$

$$c) P_{MAX} = \frac{E_{TH}^2}{4R_{TH}} = 0 \quad \text{NO RESISTANCE}$$

ALL REACTIVE POWER

(5) EE-301 Review 3 Answers

4.

A) $V = 10V (\text{PEAK}) \angle 0^\circ$

$I = 5mA (\text{PEAK}) \angle +60^\circ$

$$V(+)= 10 \sin(\omega t + 0^\circ)$$


$$I(+)= 5 \times 10^{-3} \sin(\omega t + 60^\circ) \text{ or } 5mA \sin(\omega t + 60^\circ)$$

B) $V(\text{PNASOR}) = V_p / \sqrt{2} = 7.07V \angle 0^\circ$

$$I(\text{PNASOR}) = 3.54mA \angle +60^\circ$$

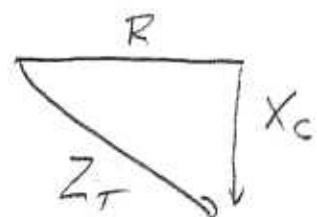c) $Z_T = \frac{V}{I} = \frac{7.07 \angle 0^\circ}{3.54 \times 10^{-3} \angle +60^\circ} = 2.0 \times 10^3 \angle -60^\circ$

$$= \underline{\underline{Z_K R \angle -60^\circ}}$$




D) E.L.I

LEADING Power Factor (see I \angle ANGLE)

6) EE-301 Review B

5.

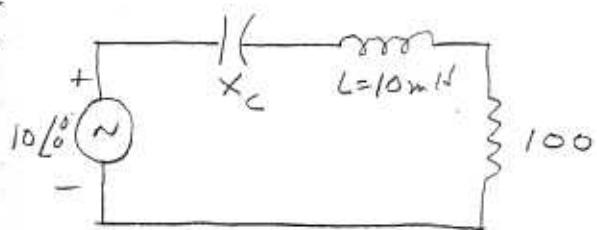


$$A) X_L = 2\pi f L = 2\pi \times 10 \times 10^{-3} (10 \times 10^3) = 628.3 \Omega$$

$$B) X_C = X_L = 628.3 \Omega$$

$$c) Q = X_L/R = 628.3/100 = 6.28$$

$$\text{BW} = \frac{f_s}{Q} = \frac{10 \text{ kHz}}{6.28} = 1.59 \text{ kHz}$$

D)

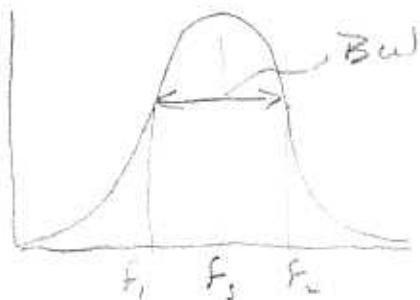

$$f_l = f_s - \text{BW}/2 = 10.0 \text{ kHz} - 745 \text{ kHz} = \underline{\underline{9.205 \text{ kHz}}}$$

$$f_h = f_s + \text{BW}/2 = \underline{\underline{10.795 \text{ kHz}}}$$