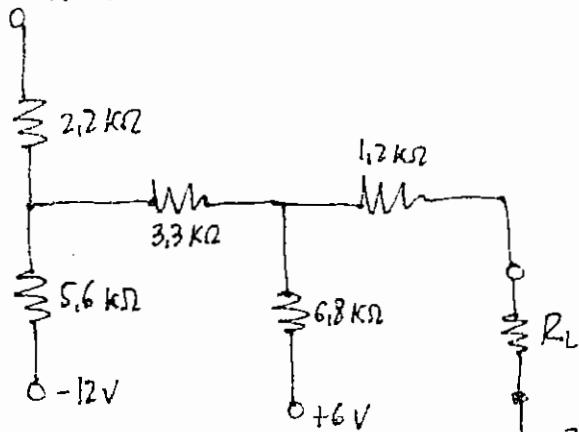



HW #13

9-17

+22V



\Rightarrow

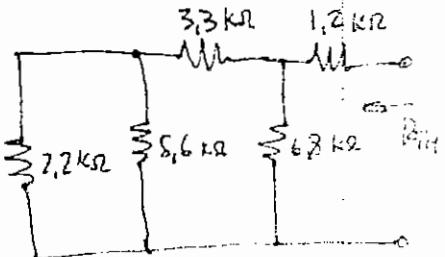

$$R_{TH} = \left[\left((2.2 \text{ k}\Omega \parallel 5.6 \text{ k}\Omega) + 3.3 \text{ k}\Omega \right) \parallel 6.8 \text{ k}\Omega \right] + 1.2 \text{ k}\Omega =$$


$$= \left[[1.58 + 3.3] \parallel 6.8 \right] + 1.2 \text{ k}\Omega = [4.88 \parallel 6.8] + 1.2 = 2.84 + 1.2 = 4.04 \text{ k}\Omega$$

$R_{TH} = 4.04 \text{ k}\Omega$

$E_{TH} \rightarrow$ Source Conversions

$$I_1 = \frac{22 \text{ V}}{2.2 \text{ k}\Omega} = 10 \text{ mA} \quad R = 2.2 \text{ k}\Omega$$

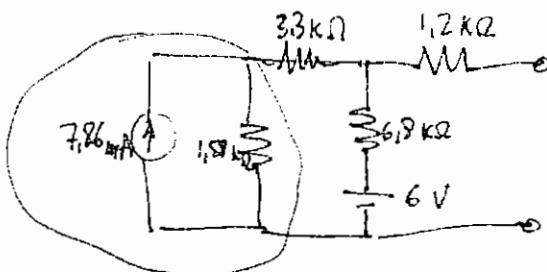
$$I_2 = \frac{12 \text{ V}}{5.6 \text{ k}\Omega} = 2.14 \text{ mA} \quad R = 5.6 \text{ k}\Omega$$



Combining parallel current sources

$$I_T = I_1 - I_2 = 10 \text{ mA} - 2.14 \text{ mA} = 7.86 \text{ mA}$$
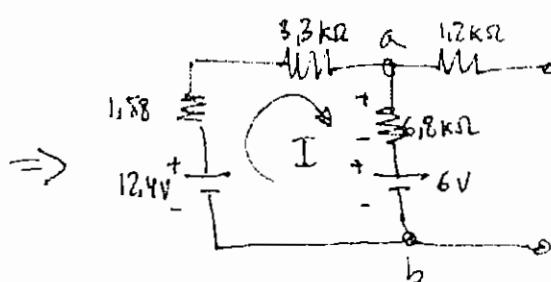
$$2.2 \text{ k}\Omega \parallel 5.6 \text{k}\Omega = 1.58 \text{ k}\Omega$$




Source Conversion

$$I = \frac{E_T}{R_T} = \frac{12.4 \text{ V} - 6 \text{ V}}{1.58 + 3.3 + 6.8} = 550 \mu\text{A}$$

$$V_{6.8} = I \cdot R = 550 \mu\text{A} \cdot 6.8 \text{ k}\Omega = 3.74 \text{ V}$$

$$E_{TH} = V_{ab} = V_{6.8} + E_6 = 3.74 \text{ V} + 6 \text{ V} = 9.74 \text{ V} = E_{TH}$$

9-30

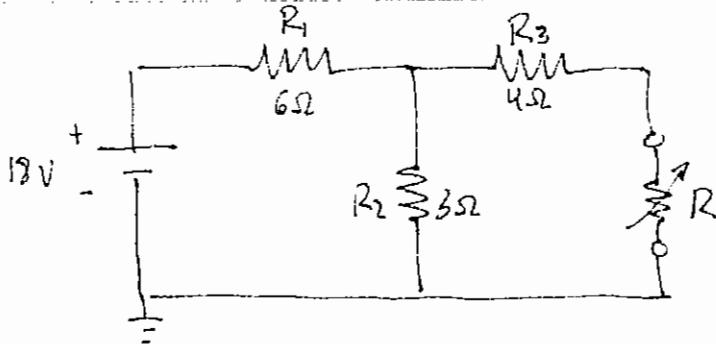

Max Power Transfer Condition $R = R_{TH}$

$$R_{TH} = R_3 + (R_1 \parallel R_2) = 6\Omega \quad \text{so} \quad \boxed{R = 6\Omega}$$

$$P_{max} = \frac{E_{TH}^2}{4R_{TH}} = \frac{6V^2}{4 \cdot 6} = \boxed{1.5W = P_{max}}$$


9-31

$R = R_{TH} = 2.18\Omega$ from problem 11

$$E_{TH} = 9.81V$$

$$P_{max} = \frac{E_{TH}^2}{4R_{TH}} = \frac{(9.81V)^2}{4 \cdot 2.18} = \boxed{11.06W = P_{max}}$$

9-35

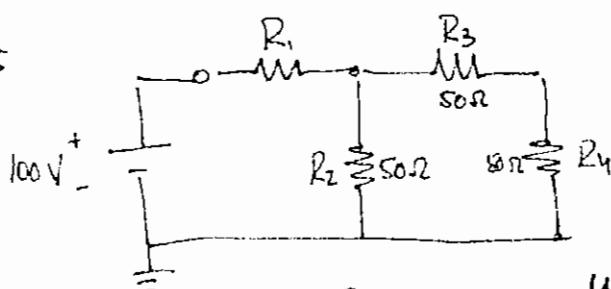

$R_1 ?$

$$E_{TH} = 100 \left(\frac{R_2}{R_1 + R_2} \right)$$

R_1 must be ≥ 0
 E_{TH} is max when $R_1=0$.

What about R_{TH} ?

$$R_{TH} = 50 + \left(\frac{1}{R_1} + \frac{1}{50} \right)^{-1}$$

As $R_1 \rightarrow 0$, $R_{TH} \rightarrow 0 \Rightarrow R_{TH} \rightarrow \text{minimum}$

If $R_1=0 \Rightarrow E_{TH}$ is a maximum and R_{TH} is a minimum \Rightarrow

$$\boxed{R_1 = 0\Omega}$$

$P_{max} = \frac{E_{TH}^2}{4R_{TH}}$ is max when $R_1 = 0\Omega$.


This solution works for this problem
but would likely fail for another problem.
See Next Page for How to solve it
every time.

9-35]

concept

Max Power to R_y occurs when
 $R_y = R_{TH}$ \Rightarrow find R_{TH} external to R_y
and set it equal to 50Ω to determine
 R_1 .

solution

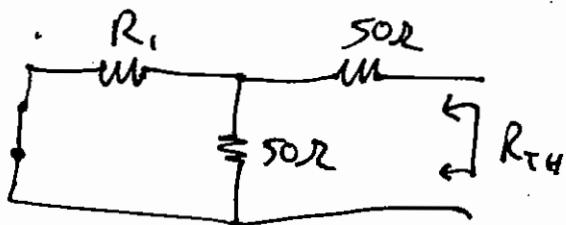

$$50\Omega = R_{TH} = 50\Omega + \left(\frac{1}{R_1} + \frac{1}{50} \right)^{-1}$$
$$0 = \left(\frac{1}{R_1} + \frac{1}{50} \right)^{-1}$$

Multiply
by 1

$$\left(\frac{R_1}{R_1} \right) (0) = \left(\frac{1}{\frac{1}{R_1} + \frac{1}{50}} \right) \frac{R_1}{R_1}$$

$$1 = \frac{R_1}{R_1}$$

Multiply
Both
sides
by $\left(1 + \frac{R_1}{50} \right)$

$$\left(1 + \frac{R_1}{50} \right) 0 = \frac{R_1}{\left(1 + \frac{R_1}{50} \right)} \left(1 + \frac{R_1}{50} \right)$$

$$0 = R_1$$