
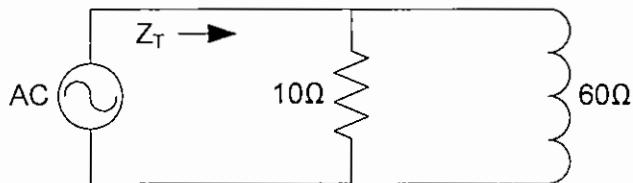


1) Given:


Find the total impedance for the given network and draw the impedance diagram.

$$Z_T = \left( \frac{1}{10\Omega} + \frac{1}{j60\Omega} \right)^{-1}$$
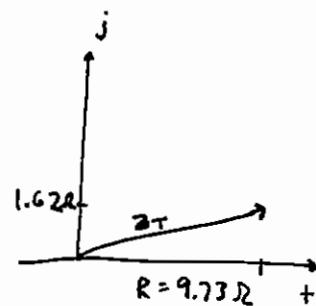
$$\begin{aligned} Z_T &= 9.87\Omega \angle 9.5^\circ \\ &= 9.73\Omega + j1.62\Omega \end{aligned}$$




2) Given:

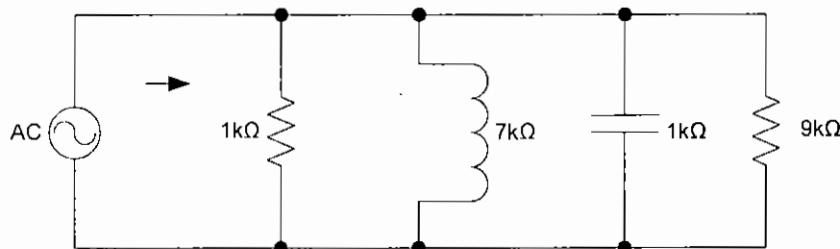
Find the total impedance for the given network and draw the impedance diagram.

$$Z_T = \left( \frac{1}{1000\Omega} + \frac{1}{j7000\Omega} + \frac{1}{-j1000\Omega} + \frac{1}{9000\Omega} \right)^{-1}$$
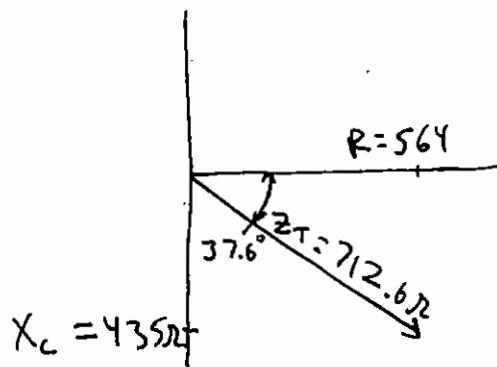
$$\begin{aligned} Z_T &= 712.6\Omega \angle -37.6^\circ \\ &= 564.2 - j435.3\Omega \end{aligned}$$




3) Given

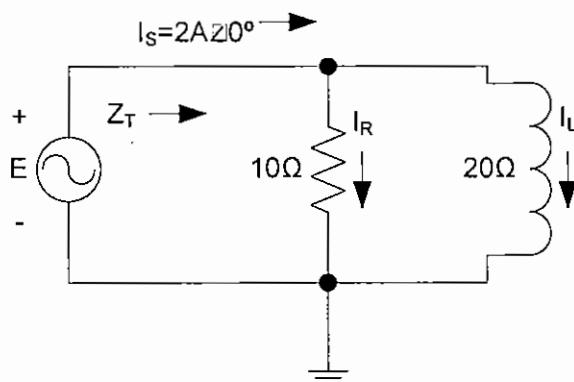a. Find the total impedance  $Z_T$  in polar form.

$$Z_T = \left( \frac{1}{10} + \frac{1}{j20} \right)^{-1} = 8.94 \Omega \angle 26.6^\circ$$

b. Draw the impedance diagram.


$$Z_T = 8 + j4 \Omega$$

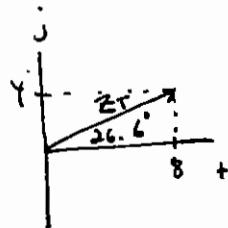c. Find the voltage  $E$  and the currents  $I_R$  and  $I_L$  in phasor form.

$$E = I_S Z_T = 2A \angle 0^\circ (8.94 \angle 26.6^\circ) = 17.9V \angle 26.6^\circ$$

$$I_R = \frac{E}{R} = \frac{17.9V \angle 26.6^\circ}{10} = 1.79A \angle 26.6^\circ$$

$$\text{KCL: } I_S = I_R + I_L \Rightarrow I_L = I_S - I_R = 2A \angle 0^\circ - 1.79A \angle 26.6^\circ = 0.894A \angle -63.4^\circ$$

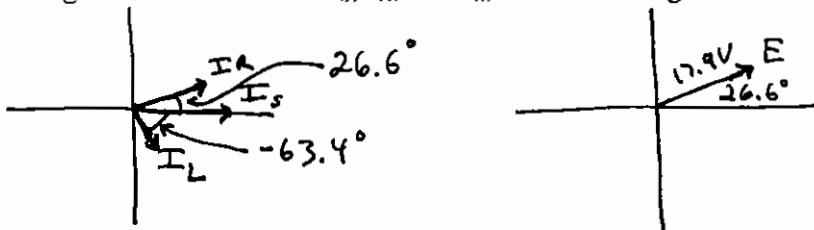d. Draw the phasor diagram of the currents  $I_S$ ,  $I_R$ , and  $I_L$ , and the voltage  $E$ .

e. Verify Kirchhoff's current law at one node.

$$I_L = \frac{E}{X_L} = \frac{17.9V \angle 26.6^\circ}{j20\Omega} = 0.895 \angle -63.4^\circ$$

KCL was used in part c for  $I_L$  thus using a different method (Ohm's Law) and getting the same answer verifies KCL was correct for this problem.


f. Find the average power delivered to the circuit.

$$P = EI \cos \theta_T = 17.9V(2A) \cos(26.6^\circ)$$

$P = 32W$

EE 301 HW#21  
AC Parallel

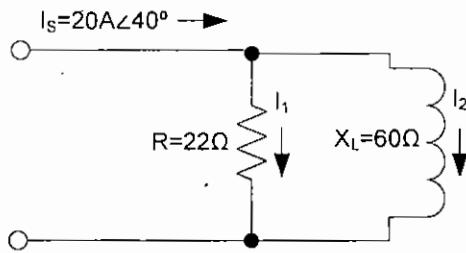- 4) Calculate the currents  $I_1$  and  $I_2$  in phasor form for each of the following circuits using the current divider rule.



$$Z_T = \left( \frac{1}{R} + \frac{1}{jX_L} \right)^{-1} = \left( \frac{1}{22} + \frac{1}{j60} \right)^{-1}$$



$$Z_T = 20.655 \angle 20.13^\circ$$

a)

$$I_1 = I_s \frac{Z_T}{Z_R}$$

$$= 20A \angle 40^\circ \frac{20.655 \angle 20.13^\circ}{22 \angle 0^\circ} = [18.8A \angle 60.1^\circ = I_1]$$
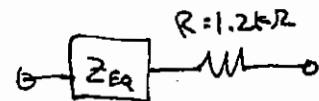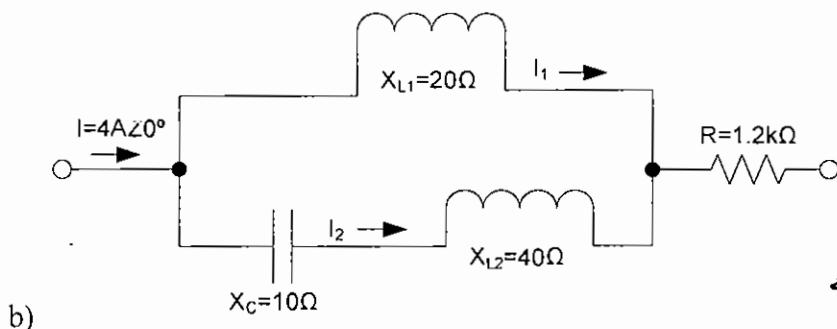
$$I_2 = I_s \frac{Z_T}{Z_L} = 20A \angle 40^\circ \frac{20.655 \angle 20.1^\circ}{60 \angle 90^\circ} = [6.89A \angle -30^\circ = I_2]$$



$$Z_{EQ} = \left( \frac{1}{j20} + \frac{1}{j40-j10} \right)^{-1} = 12\Omega \angle 90^\circ$$

$$I_1 = I \frac{Z_{EQ}}{Z_{L1}} = 4A \angle 0^\circ \frac{12\Omega \angle 90^\circ}{20\Omega \angle 90^\circ} = [2.4A \angle 0^\circ = I_1]$$

$$I_2 = I \frac{Z_{EQ}}{Z_{L2} + Z_C} = 4A \angle 0^\circ \frac{12\Omega \angle 90^\circ}{30\Omega \angle 90^\circ} = [1.6A \angle 0^\circ = I_2]$$