

## **ASYNCHRONOUS COUNTER DESIGN STEPS/PROCEDURES**

- a. Determine the # of FFs needed to support the counting sequence's highest #.

$$2^n - 1 \geq \text{Highest \#}$$

- b. Determine what states you want to toggle FROM → TO.

**Example:**

$$\begin{aligned} 0 &\rightarrow 5 \\ 000 &\rightarrow 101 \end{aligned}$$

- c. Build a truth Table.
- d. Simplify logic using a K-Map.
- e. Implement the design on the basic Asynchronous Counter Circuit.
- f. Draw the Timing Diagram (If Needed).