

## SYNCHRONOUS COUNTER DESIGN STEPS/PROCEDURES

1. Determine the # of FFs needed to support the counting sequence's highest #.

$$2^n - 1 \geq \text{Highest \#}$$

2. Build a State Transition Diagram. Be sure to include all states.
3. Build a State/Excitation Truth Table.
4. Simplify expressions for J and K inputs for each F/F on K-Maps.
5. Implement the Synchronous Counter/State Machine Circuit.
6. Draw the Timing Diagram (If Needed).

### RULES

	<u>J</u>	<u>K</u>
0 → 0	0	X
0 → 1	1	X
1 → 0	X	1
1 → 1	X	0