

EE331**Electrical Engineering I****EXAM II****Monday April 2nd, 2012**

This is a 50 minute exam. Please work quickly and quietly. Place your name below before beginning. There are 6 pages including this cover sheet. Please ensure that you have all 6 pages. Show as much work as practical to maximize partial credit. Eyes should remain on your own work. There is no sharing of calculators. **Do not discuss this exam until it is returned to you.** Please commence when advised.

Page	Points	Score
1		
2	16	
3	12	
4	20	
5	14	
6	14	
Total	76	


NAME: _____

SECTION: _____

Solution

Problem 1 - Warm up #1 (8 pts): Given that $v(t) = 20 \cdot \cos(377t + 10)$ V, and $i(t) = 15 \cdot \sin(377t + 80)$, plot the phasors (\tilde{I} and \tilde{V}) on the following diagram and answer the following questions.

$15 \cos(377t + 80 - 90)$

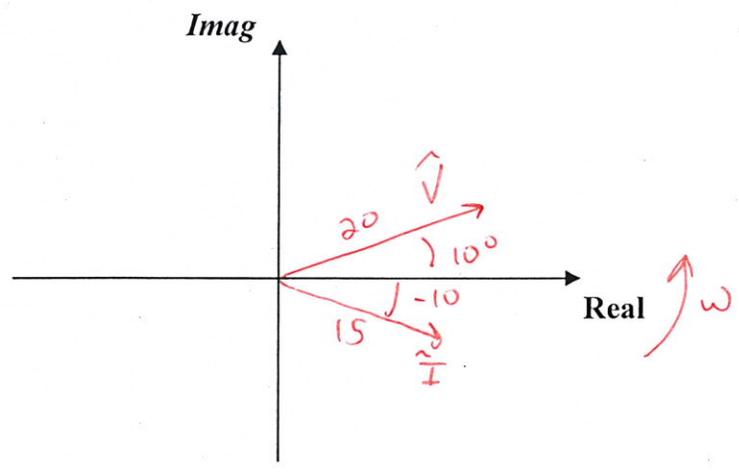


\tilde{I} leads / lags / is in phase with \tilde{V} (circle one)

Is this an overall inductive / capacitive / resistive circuit? (circle one)

ELI

Problem 2 (8 pts): Find $v_o(t)$.

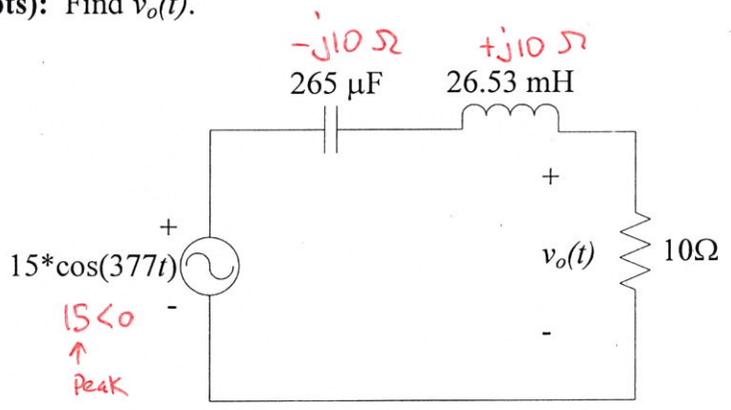

$v_o(t) = 15 \cos(377t)$

$\tilde{V}_o = \frac{15 \angle 0 \cdot 10 \angle 0}{10} = 15 \angle 0$

Bonus(2 pts):

- The current into a capacitor can change instantaneously. **True** / False (circle one)
- If the current through a 10 mH inductor increases from zero to 2 A, how much energy is stored in the inductor?

$\frac{1}{2} LI^2 = \frac{1}{2} \cdot 10 \cdot 10^{-3} \cdot 2^2 = 0.02 \text{ J}$

Problem 3: You are given a permanent magnet DC motor for use in an electric car that uses a 450 V battery. You run the following two tests:

Test 1: Apply 450 V_{DC} and you measure $I_a = 4$ A and $\omega = 200$ rad/s with no load

Test 2: Apply 450 V_{DC} and you measure $I_a = 300$ A and $\omega = 150$ rad/s with a load

a. (8 pts) Determine r_a , K_v , and T_{loss} .

Case 1: $V_A - I_a r_a - K_v \omega = 0$
 $450 - (4) \cdot r_a - K_v \cdot 200 = 0$

Case 2: $V_A - I_a r_a - K_v \omega = 0$
 $450 - (300) r_a - K_v \cdot 150 = 0$

Solve


$$\boxed{K_v = 2.24 \text{ V}\cdot\text{s}}$$

$$\boxed{r_a = 0.38 \Omega}$$

$$\Rightarrow T_{loss} + T_{load}^{\text{unloaded}} = K_v I_a = T_e$$

$$\boxed{T_{loss} = 2.24 \text{ V}\cdot\text{s} \cdot 4 \text{ A} = 8.96 \text{ N}\cdot\text{m}}$$

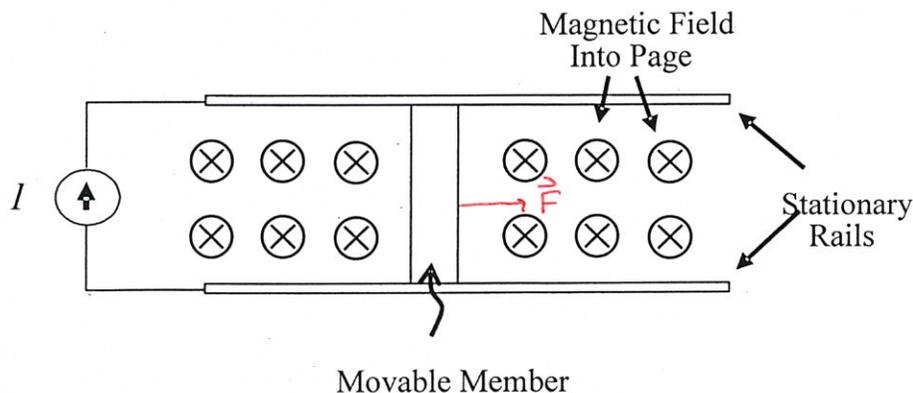Problem #4: Use the depiction of a linear DC motor below to answer the following questions.



TRUE FALSE (2pts) With the given current and magnetic field direction, the force on the movable member would be to the left.

TRUE FALSE (2pts) Greater acceleration can be generated if the stationary rails are lengthened.
 $F = ILB$


Bonus (2 pts): If the movable member's mass = 20 kg, its length = 1 m, $B = 10$ T, and $I = 1000$ A, how much time will it take to achieve a velocity = 500 m/s?

$$F = ILB = 1000 \text{ A} \cdot 1 \text{ m} \cdot 10 = 10,000 \text{ N} = ma$$

$$\Rightarrow a = \frac{10,000 \text{ N}}{20 \text{ kg}} = 500 \text{ m/s}^2 \Rightarrow v = \int a dt = at \Rightarrow \boxed{t = 1 \text{ second}}$$

Problem 5 (20 pts): Given the single phase AC circuit below where $V_{load} = 5 \angle 0$ V_{rms}, $f = 10$ kHz, $R_{sense} = 10 \Omega$, $R_L = 40 \Omega$, $L = 2$ mH, and $R_x = 100 \Omega$ compute the requested quantities:

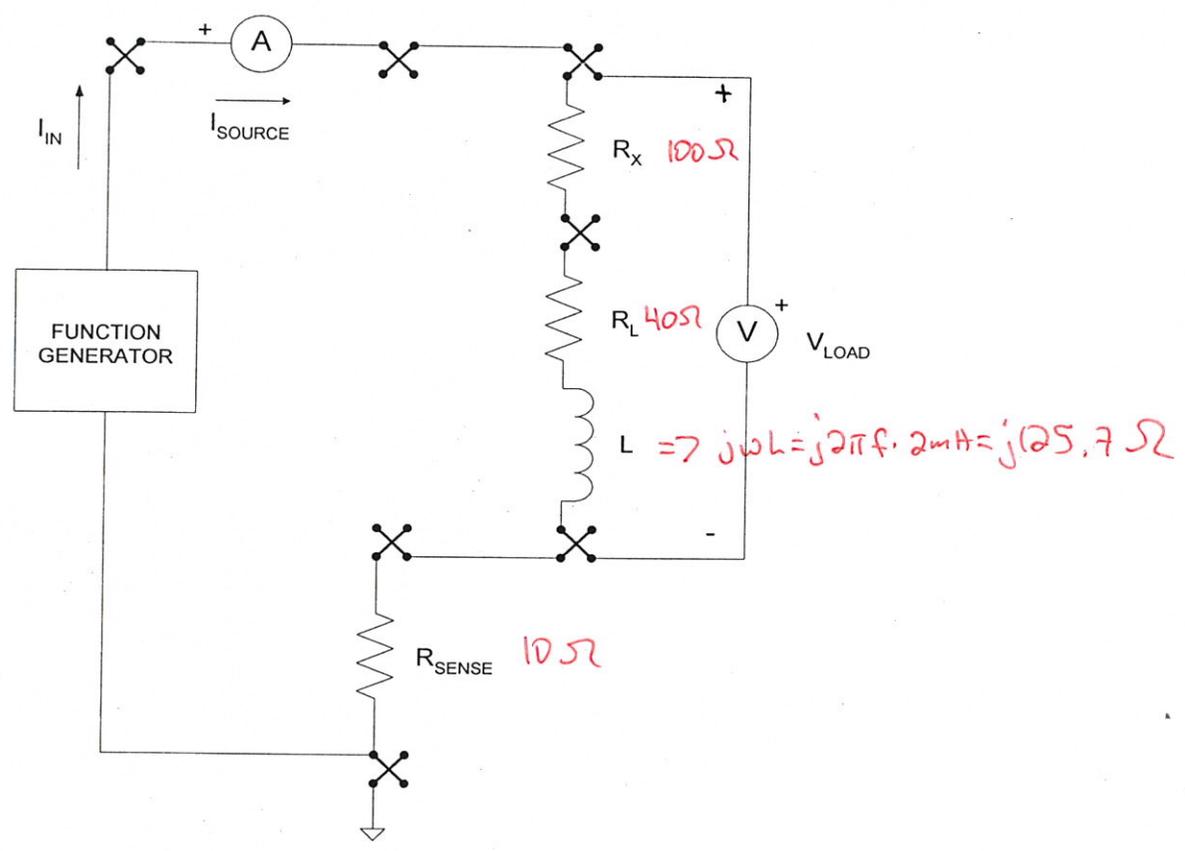***Note the load does not include R_{sense} ***



- $\hat{I}_{Load} = \frac{5 \angle 0}{140 + j125.7} = 0.0266 \angle -41.9^\circ$ A_{rms}
- $\hat{S}_{Load} = 5 \angle 0 \cdot 0.0266 \angle +41.9^\circ = 0.133 \angle 41.9^\circ$ VA = $99 + j88.8$ mVA

$Z_{Load} = \underline{140 + j125.7 \Omega}$

$I_{Load} = \underline{0.0266 \angle -41.9^\circ A_{RMS}}$


$S_{Load} = \underline{99 + j88.8 mVA}$

$P_{Load} = \underline{99 mW}$

$Q_{Load} = \underline{88.8 mVAR}$

Power Factor of Load = 0.74 Lagging

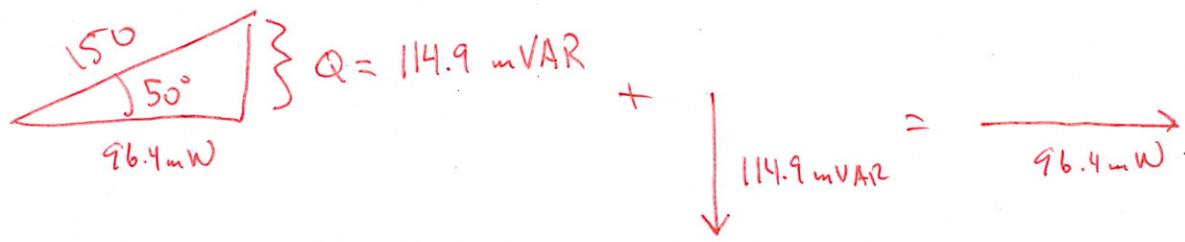Problem 6 (10 pts): Assuming that $\bar{S}_{Load} = 150 \angle 50^\circ \text{ mVA}$ for the previous problem (this may or may not be the case), determine the capacitance required to achieve a unity power factor.





$$Q_c = \frac{V^2}{|Z_c|} = \omega C V^2 \Rightarrow C = \frac{Q_c}{\omega V^2} = \frac{114.9}{(2\pi \cdot 10,000) \cdot 5^2} = \boxed{73.1 \text{ nF}}$$

Question (4 pts): Before the power factor correction, does the source voltage lead or lag the total current? By how much does the source voltage lead or lag?


ELI \Rightarrow Voltage leads by 50°
 $\theta_z > 0$, Inductive $\theta_z = \theta_v - \theta_i$

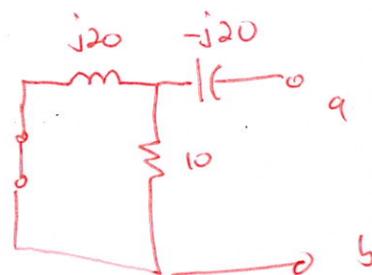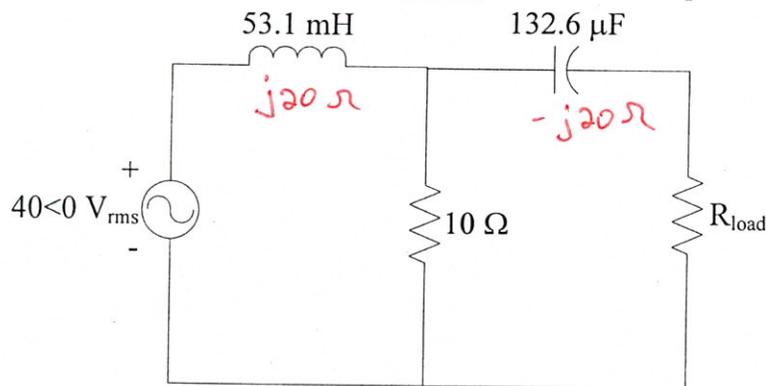Problem 7 (14 pts): Find and draw the Thevenin equivalent circuit for R_{load} assuming $f = 60$ Hz.



$$\bullet Z_{th} = -j20 + \underbrace{j20 // 10}_{8+j4} = 8 - j16 = 17.9 \angle -63.4^\circ$$
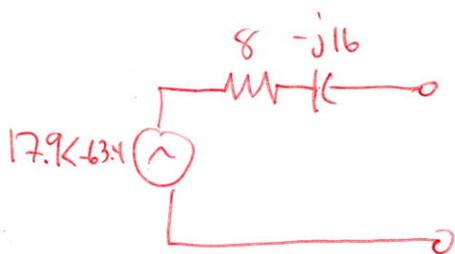
$$\bullet \hat{V}_{th} = \hat{V}_{oc} = \frac{40 \angle 0 \cdot 10 \angle 0}{10 + j20} = 17.9 \angle -63.4^\circ \text{ V}$$



Bonus Problem (2 pts): What should the load be (include specific component values, resistance, inductance, and capacitor values) for maximum power delivery?

$$Z_{th}^* = Z_{Load} = 8 + j16$$

max power

$$j\omega L \Rightarrow L = \frac{16}{377} = 42.4 \mu\text{H}$$