

EE331**Electrical Engineering I****EXAM II****Monday October 31st, 2011**


This is a 50 minute exam. Please work quickly and quietly. Place your name below before beginning. There are 6 pages including this cover sheet. Please ensure that you have all 6 pages. Show as much work as practical to maximize partial credit. Eyes should remain on your own work. There is no sharing of calculators. **Do not discuss this exam until it is returned to you.** Please commence when advised.

Page	Points	Score
1		
2	14	
3	14	
4	16	
5	20	
6	16	
Total	80	

NAME: _____ *Key*

SECTION: _____

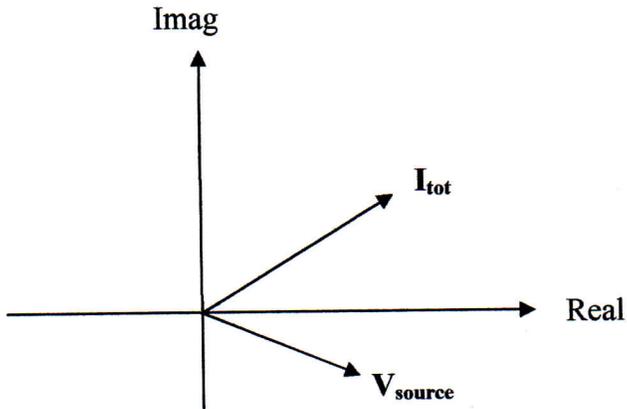Problem 1 - Warm up #1 (4 pts): Given the following phasor diagram,




I_{tot} **leads** / lags / is in phase with V_{source} (circle one)


Is this an overall **inductive** / **capacitive** circuit? (circle one)

ICE

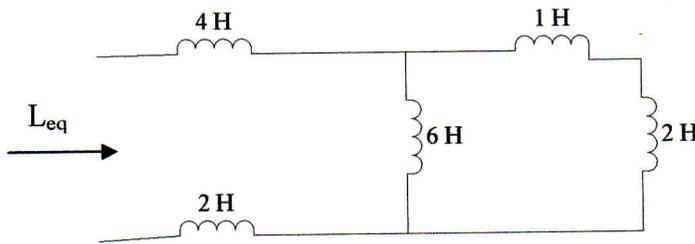Problem 2 (6 pts): Find the equivalent Inductance and Capacitance in the below circuits.



$L_{eq} = \underline{8H}$

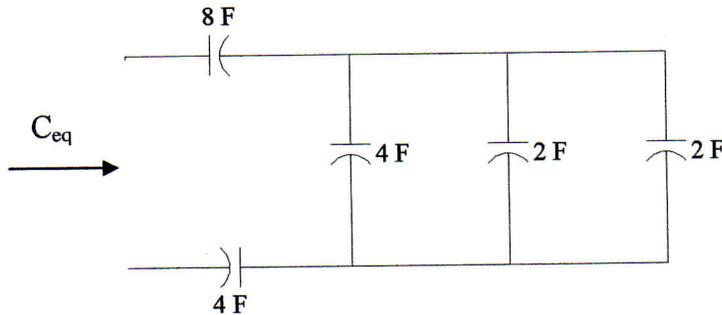

$C_{eq} = \underline{2F}$

Problem 3 (4 pts): Express $y(t)$ as a single cosine with the form, $A \cdot \cos(\omega \cdot t + \theta)$:

$y(t) = -10 \cdot \sin(377 \cdot t + 10) + 10 \cdot \cos(377 \cdot t + 100^\circ)$

$-10 \cos(377t - 80) + 10 \cos(377t + 100)$

$10 \cos(377t + 100) + 10 \cos(377t + 100)$

$y(t) = \underline{20 \cos(377t + 100)}$


Bonus (3 pts)

1) The general relationship between the magnetic flux density **B** and the magnetic field intensity **H** is given by $B = \mu H$. (fill in the blank)

2) The current through an inductor can change instantaneously. **True** / **False** (circle one)

3) Faraday's Law for the induced voltage in a loop is related to the magnetic flux, ϕ , by $\frac{\partial \phi}{\partial t}$.

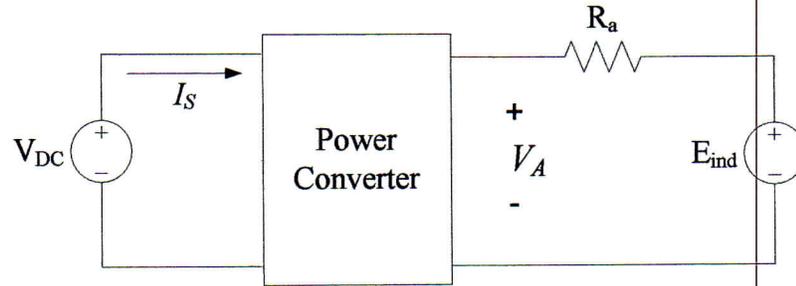Problem 4: A permanent magnet DC motor is controlled with a power converter with a constant DC supply voltage, $V_{DC} = 100$ V. The motor is characterized by, $K_v = 0.133$ V*s, and $R_a = 2$ Ω .



a. (8 pts) If the $T_{load} = 0.532$ N*m, T_{loss} is negligible, and the motor speed is equal to 1800 RPM compute V_A .

$$\bullet \omega = \frac{1800 \text{ rev}}{\text{min}} \cdot \frac{1 \text{ min}}{60 \text{ sec}} \cdot \frac{2\pi \text{ rad}}{1 \text{ rev}} = 188.5 \text{ rad/s}$$

$$\bullet E_{ind} = k_v \omega = 0.133 \text{ V}\cdot\text{s} \cdot 188.5 = 25.07 \text{ V}$$

$$\bullet T_{dev} = T_{load} + T_{loss} = 0.532 \text{ N}\cdot\text{m} = k_v I_a \Rightarrow I_a = 4 \text{ A}$$

$$\bullet \rightarrow V_A = E_{ind} + I_a \cdot R_a = 25.07 \text{ V} + 4 \cdot 2 \Omega = \boxed{33.1 \text{ V}}$$

b. (2 pts) What is the Duty Cycle?


$$D = \frac{33.1 \text{ V}}{100} = \boxed{0.331}$$

c. (4 pts) If the Power Converter is 96% efficient, what is the value of the source current, I_S ?


$$0.96 = \frac{V_A \cdot I_a}{V_{DC} \cdot I_S} = \frac{33.1 \text{ V} \cdot 4 \text{ A}}{100 \text{ V} \cdot I_S} \Rightarrow \boxed{I_S = 1.38 \text{ A}}$$

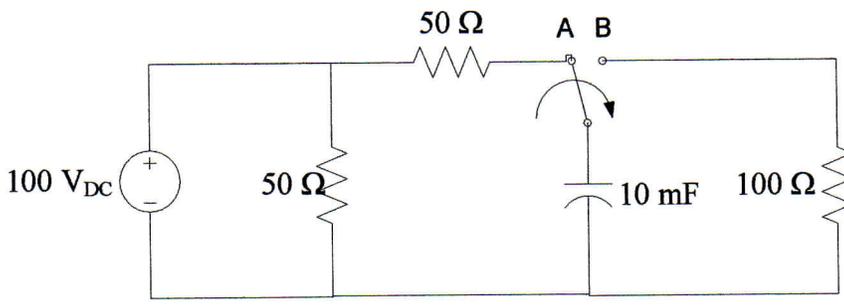Problem 5: The switch has been in position A for a long time. At $t = 0$, the switch is moved to position B.

- (10 pts) Write the mathematical expression for $v_C(t)$ and sketch $v_C(t)$ on the axis below for $t \geq 0$. Be sure to include values for the initial voltage, final voltage, and time constant.
- (6 pts) Write the mathematical expression for $i_C(t)$ and sketch $i_C(t)$ on the axis below for $t \geq 0$. Be sure to include values for the initial current, final current, and time constant.




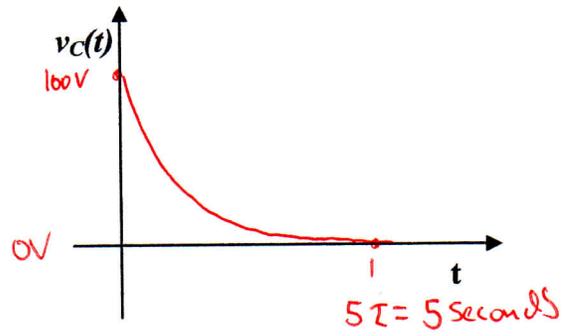① $V_C(t) = V_f + (V_i - V_f)e^{-t/\tau}$
 ② $V_i = 100V$
 $V_f = 0V$
 $\tau = R_{th}C = 100\Omega \cdot 10mF = 1Sec$




$v_C(t) = 100e^{-t}$

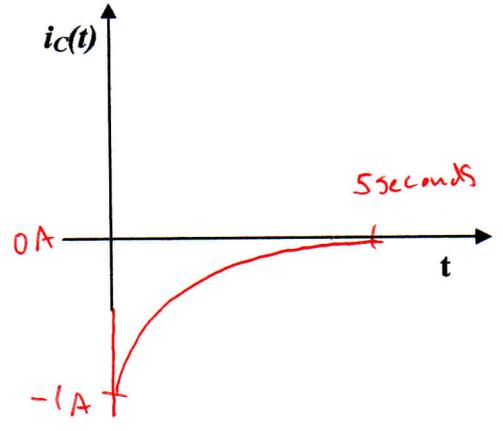$i_C(t) = C \frac{dv_C(t)}{dt} = 10mF \cdot (-100)e^{-t} = -e^{-t}$
 (Discharging)



$i_C(t) = -e^{-t}$

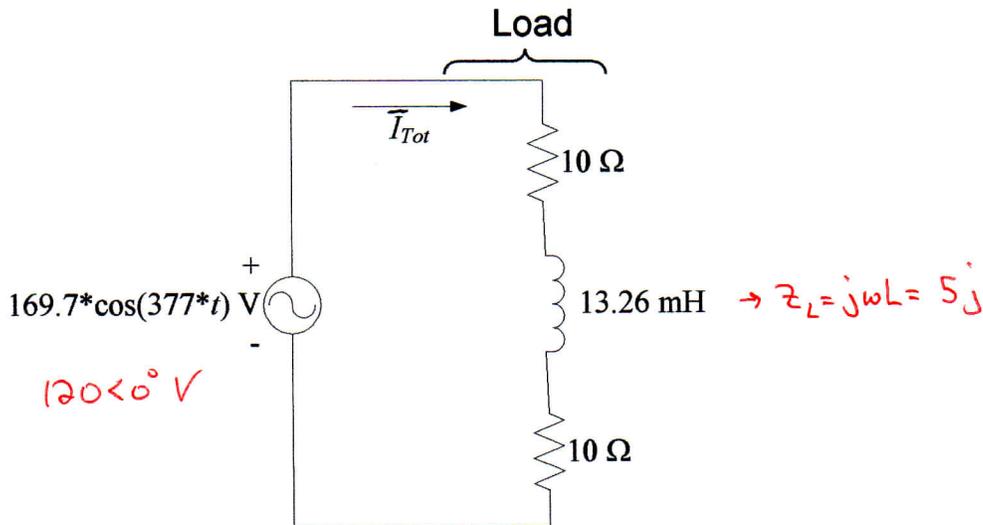Problem 6 (14 pts): Given the following single-phase AC circuit compute the following quantities below:



$$\hat{I}_{Tot} = \frac{120 \angle 0^\circ}{20.6 \angle 14^\circ} = 5.83 \angle -14^\circ$$

$$\hat{S}_{Tot} = \frac{|V|^2}{Z^*} = \frac{120^2}{20 - 5j} = 698.5 \angle 14^\circ = 677.6 + j169.4$$

$$\bar{Z}_{Tot} = \underline{20 + 5j = 20.6 \angle 14^\circ \Omega}$$

$$\bar{I}_{Tot} = \underline{5.83 \angle -14^\circ \text{ A}}$$

$$\bar{S}_{Tot} = \underline{677.6 + j169.4 \text{ VA}}$$

$$P_{Tot} = \underline{677.6 \text{ W}}$$

$$Q_{Tot} = \underline{169.4 \text{ VAR}}$$

$$\text{Power Factor} = \underline{0.97 \text{ LAGging}}$$

Question 1 (2 pts): The source voltage leads / lags / is in phase with the total current in the above circuit.

ELI

Problem 7 (6 pts): A capacitor, C = 31.2 μF, is placed in parallel with the Load above. Compute the new total complex power and power factor as seen by the source.

$$\bar{S}_{cap} = \frac{|V|^2}{Z^*} = 0 - j169.4 \text{ VA}$$


$$\hat{S}_{Tot} = \hat{S}_{Load} + \hat{S}_{cap} = 677.6 \text{ W}$$

$$Z_c = -j/\omega C = -85j \Omega$$

$$S_{Tot} = \underline{677.6 \text{ W}}$$

$$\text{Power Factor} = \underline{1.0}$$

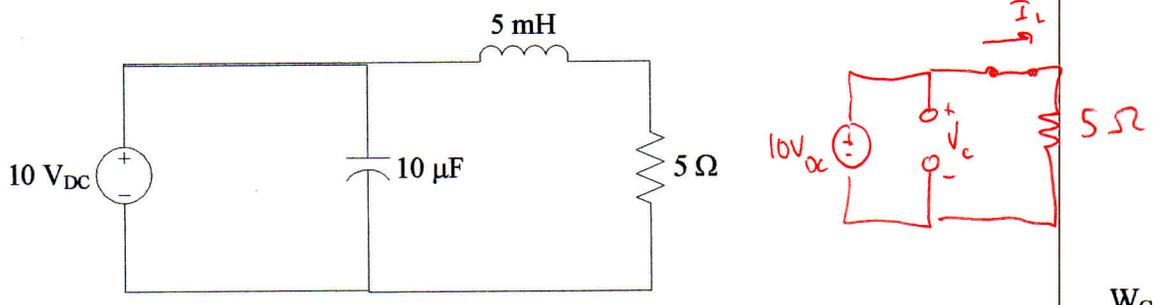Problem 8 (8 pts): Calculate the energy stored in the capacitor and inductor for the circuit below.




$$W_C = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 10 \mu F \cdot 10^2 =$$

$$W_L = \frac{1}{2} LI^2 = \frac{1}{2} \cdot 5 \text{ mH} \cdot 2^2 =$$

$$W_C = \underline{0.5 \text{ mJ}}$$

$$W_L = \underline{10 \text{ mJ}}$$

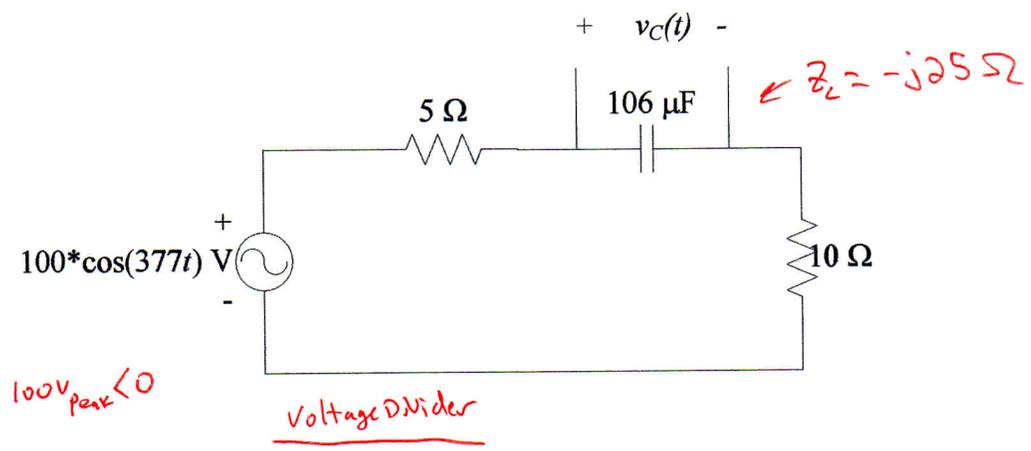Problem 9 (6 pts): Compute $v_C(t)$ for the circuit below



$$\hat{V}_C = \frac{100 V_{\text{Peak}} \angle 0^\circ \cdot (-j25)}{15 - 25j} = 85.7 \angle -31^\circ$$

V_{Peak}

$$v_C(t) = \underline{85.7 \cos(377t - 31^\circ) \text{ V}}$$

Question 2 (2 pts): What happens to $v_C(t)$ as the frequency of the source is increased?

$1/\omega C$ as $\omega \uparrow \Rightarrow |Z_C| \downarrow$ $|V_C(t)| \downarrow$ and $\theta \Rightarrow -90^\circ$

Bonus (1 pt): What type of filter is this circuit? Low pass / High pass (circle one)