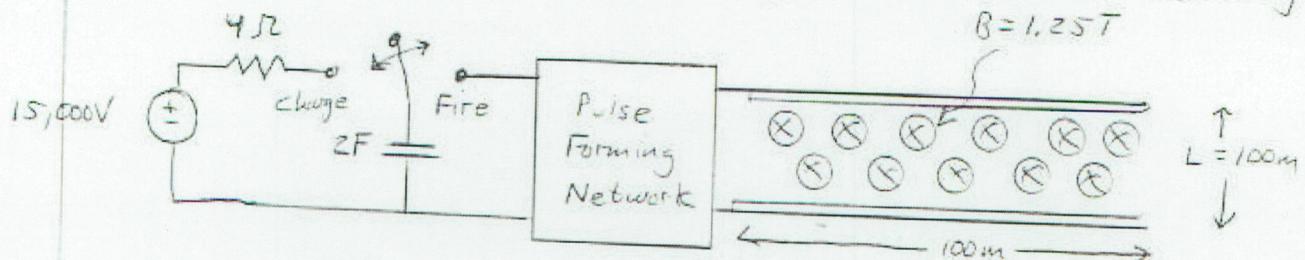


Problem 1 Given the linear motor aircraft launcher from lecture but this time assume that we have the capacitive energy storage system "up front" and that the pulse-forming network and rails are 50% efficient. The plane mass is 50,000kg.



(a) How long does it take for the capacitor bank to "Fully" charge? How much energy is stored?

$$\text{STEADY-STATE} = S \times T \quad T = RC = (4\Omega)(2F) = 8s$$

$$S(8s) = \underline{\underline{40s}}$$

(b) How much energy is available for launching and what is the terminal velocity?

$$W_{\text{STORED}} = \frac{1}{2} CV^2 = \frac{1}{2} (2F)(15000V)^2 = 225 \text{ MJ}$$

$$W_{\text{LAUNCH}} = 0.5 W_{\text{STORED}} = 0.5 (225 \text{ MJ}) = \underline{\underline{112.5 \text{ MJ}}}$$


$$\frac{1}{2} m v^2 = 112.5 \text{ MJ}$$

$$\frac{1}{2} (50,000 \text{ kg}) v^2 = 112.5 \text{ MJ}$$

$$v = 67.1 \text{ m/s}$$

(c) How much time does it take to launch?

Assume constant acceleration so that

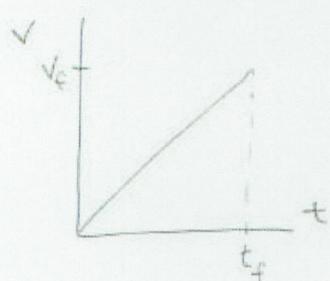

$$x = \frac{1}{2} v_f t_f$$

$$100\text{m} = \frac{1}{2} (67.1\text{m/s}) t_f$$

$$t_f = 2.98\text{s}$$

(d) What is the rail current?

$$F = B L I$$

$$F = m a$$

$$a = \frac{\Delta v}{\Delta t} = \frac{67.1\text{m/s}}{2.98\text{s}} = 22.52\text{m/s}^2$$

$$F = (50,000\text{kg})(22.52\text{m/s}^2) = 1.13\text{MN}$$


$$1.13\text{MN} = B L I = (1.25\text{T})(100\text{m}) I$$

$$I = 9000\text{A}$$

T F The back EMF is 15,000V upon takeoff

$$E = B L u = (1.25\text{T})(100\text{m})(67.1\text{m/s}) = 8.4\text{kV}$$

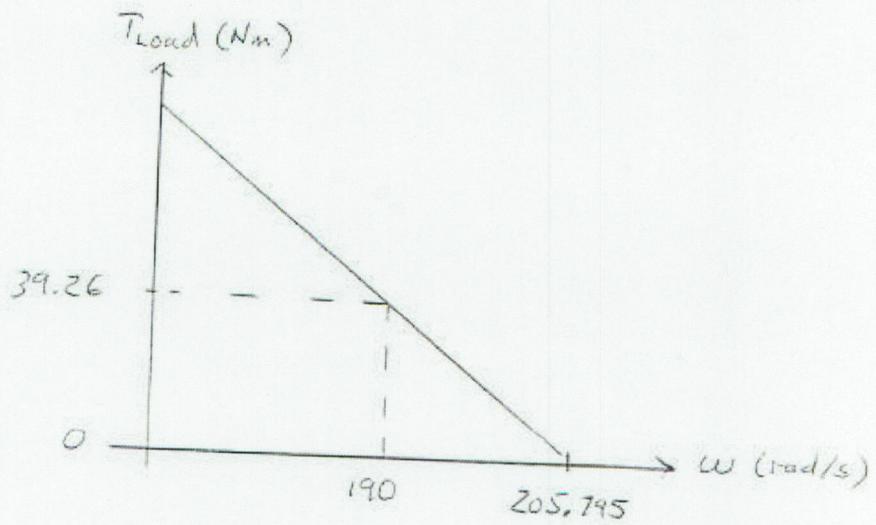Problem 2 The load torque on a permanent magnet DC motor is measured at different speeds so we assemble the following curve. The data is taken with $V_a = 120V$. The vendor reports that the nominal armature resistance is 0.1353Ω



(a) Assuming T_{loss} is constant, find K_v and T_{loss}

$$V_a = I_a R_a + K_v w \rightarrow I_a = \frac{V_a - K_v w}{R_a}$$

$$T_e = K_v I_a = \frac{K_v V_a}{R_a} - \frac{K_v^2 w}{R_a}$$

$$T_e = T_{loss} + T_{load}$$

$$T_{loss} + T_{load} = \frac{K_v V_a}{R_a} - \frac{K_v^2 w}{R_a}$$

$$T_{loss} + 39.26 \text{ N-m} = \frac{K_v (120V)}{0.1353 \Omega} - \frac{K_v^2 (190 \text{ rad/s})}{0.1353 \Omega}$$

$$T_{loss} + 0 \text{ N-m} = \frac{K_v (120V)}{0.1353 \Omega} - \frac{K_v^2 (205.795 \text{ rad/s})}{0.1353 \Omega}$$

$$T_{loss} = 2.81 \text{ N-m}$$

$$K_v = 0.58 \text{ V-s}$$

OR

Case 1 0.353Ω 205.795 rad/s

$$120V \rightarrow V_A - I_{aNL} R_a - K_V \omega_{NL} = 0$$

Case 2 0.353Ω 190 rad/s

$$120V \rightarrow V_A - I_{aL} R_a - K_V \omega_L = 0$$

3 Equations, 3 unknowns

$$K_V = 0.5799$$

$$I_{aNL} = 4.85A \Rightarrow$$

$$I_{aL} = 72.55A$$

$$T_{loss} = k_V I_{aNL} = 2.81 \text{ N.m}$$

$$T_{load} = K_V I_{aL} - K_V I_{aNL} = K_V (I_{aL} - I_{aNL}) = 39.26 \text{ N.m}$$

and $T_{loss} = K_V I_{aNL}$ \leftarrow Constant
 NOLOAD

(b) Find the motor efficiency when it operates at $\omega = 190 \text{ rad/s}$

$$\eta = \frac{P_{load}}{P_{in}} = \frac{T_{load} \omega}{P_{in}} =$$

$$P_{in} = V_a I_a$$

$$T_e = T_{load} + T_{loss} = 39.26 \text{ N.m} + 2.81 \text{ N.m} = 42.07 \text{ N.m}$$

$$T_e = K_V I_a \rightarrow I_a = \frac{42.07 \text{ N.m}}{0.58 \text{ N.m/A}} = 72.53 \text{ A}$$

$$\eta = \frac{T_{load} \omega}{V_a I_a} = \frac{(39.26 \text{ N.m})(190 \text{ rad/s})}{(120V)(72.53A)} = 85.7\%$$

T (F)


The armature of a rotating PM DC machine is stationary

The brushes of a PM DC machine connect to

(a) The armature

(b) The commutator

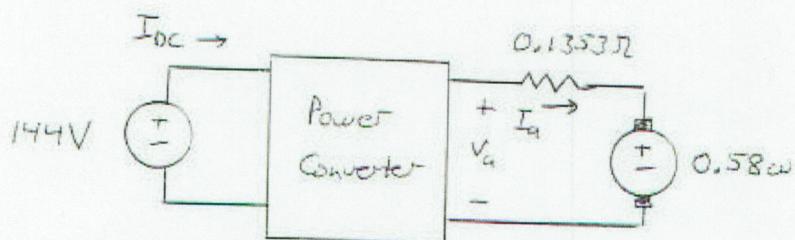Problem 3. Given the same motor from prob 2 is controlled with a power converter where the duty cycle is set for 0.6. The converter is 96% efficient and is supplied from a 144V battery bank. The load torque applied to the motor is governed by $T_{load} = 0.001\omega^2$



(a) Find the average armature voltage

$$\bar{V}_a = D V_{DC} = 0.6(144V) = \underline{\underline{86.4V}}$$

(b) Find the average armature current and rotor speed

$$\rightarrow V_a = I_a R_a + K_v \omega$$

$$K_v I_a = T_{LOAD} + T_{LOSS}$$

$$\rightarrow K_v I_a = 0.001\omega^2 + 2.81 \text{ N-m}$$

$$\begin{cases} 86.4V = I_a (0.1353 \Omega) + (0.58V \cdot s) \omega \\ (0.58 \text{ N-m/A}) I_a = 0.001\omega^2 + 2.81 \text{ N-m} \end{cases}$$

$$\boxed{I_a = 38.62 \text{ A}}$$


$$\boxed{\omega = 140 \text{ rad/s}}$$

(c) Find the average current supplied by the battery


$$\eta_{\text{conv}} = \frac{P_{\text{conv}, \text{out}}}{P_{\text{conv}, \text{in}}} = \frac{V_a I_a}{V_a I_{\text{DC}}} = \frac{(86.4 \text{ V})(38.62 \text{ A})}{(144 \text{ V}) I_{\text{DC}}} = 0.96$$

$$\boxed{I_{\text{DC}} = 24.14 \text{ A}}$$

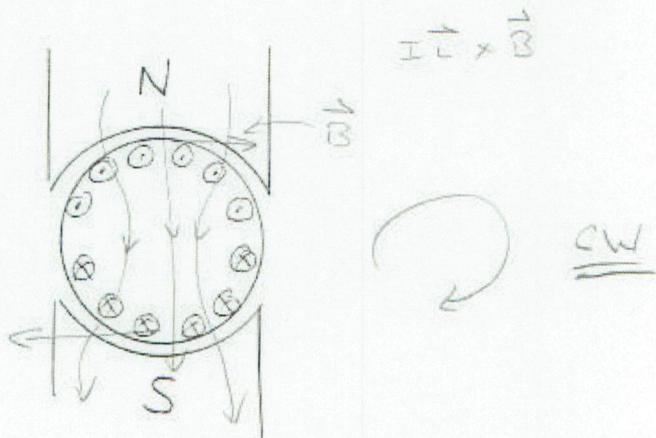Q. What direction will the armature turn if the current distribution is for motor operation?



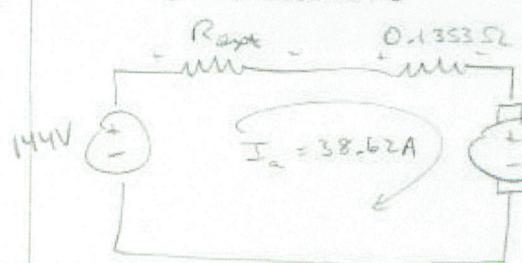
(d) If we attach external resistance (no converter) to control speed, what value is required to achieve $\omega = 140 \text{ rad/s}$?



$$\begin{aligned} \text{KVL: } & -144 \text{ V} + (38.62 \text{ A}) R_{\text{ext}} \\ & + (38.62 \text{ A})(0.1353 \Omega) \\ & + (0.58 \text{ V.s})(140 \text{ rad/s}) = 0 \end{aligned}$$

$$\boxed{R_{\text{ext}} = 1.5 \Omega}$$

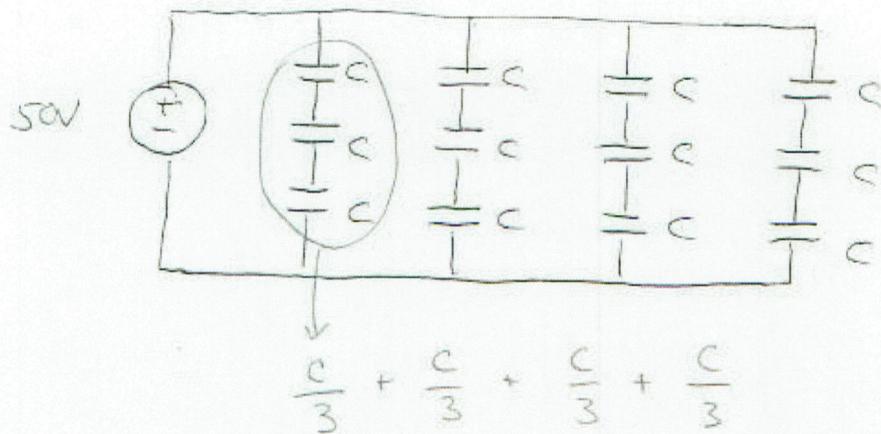Problem 4. What value of capacitance V is required to store 1000J of energy?





$$C_{eq} = \frac{4C}{3}$$

$$1000J = \frac{1}{2} C V^2$$

$$1000J = \frac{1}{2} \frac{4C}{3} (50V)^2$$

$$C = 600 \text{ mF}$$

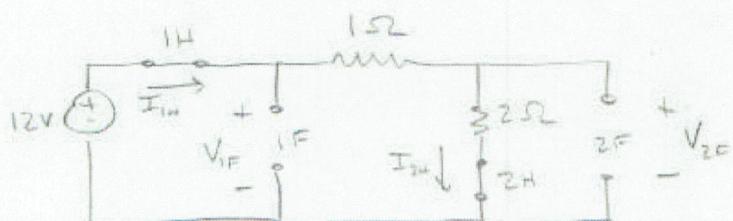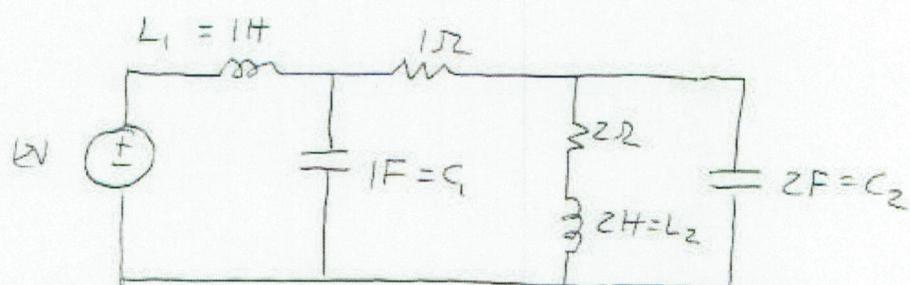Problem 5. Determine the steady-state energy stored in each component



$$V_{IF} = 12V$$

$$V_{2F} = \left(\frac{2\Omega}{2\Omega}\right) 12V = 8V$$

$$I_{1H} = \frac{12V}{3\Omega} = 4A$$

$$I_{2H} = I_{1H} = 4A$$

$$W_{1F} = \frac{1}{2}(1F)(12V)^2 = 72J$$


$$W_{2F} = \frac{1}{2}(2F)(8V)^2 = 64J$$

$$W_{1H} = \frac{1}{2}(1H)(4A)^2 = 8J$$


$$W_{2H} = \frac{1}{2}(2H)(4A)^2 = 16J$$

The instantaneous change of inductor
 (voltage, current, power) will cause a
 problem.

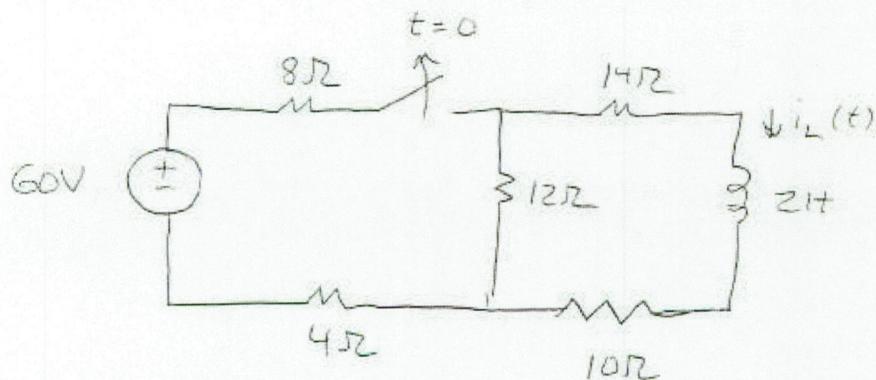Problem 6. Given the following circuit, Find $i_L(t)$ for $t \geq 0$



STEADY-STATE WITH SWITCH SHUT:

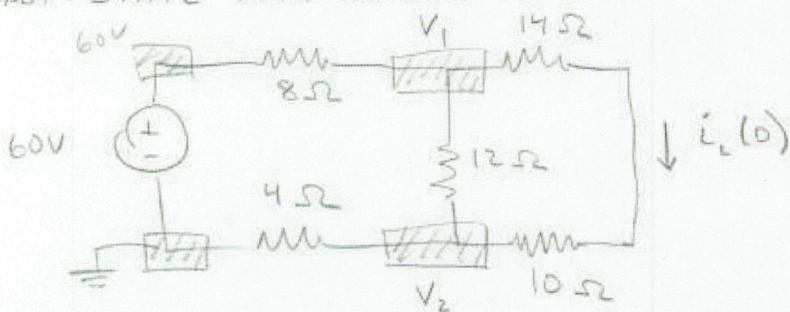

$$\left\{ \begin{array}{l} \frac{V_1 - 60V}{8\Omega} + \frac{V_1 - V_2}{12\Omega} + \frac{V_1 - V_2}{24\Omega} = 0 \\ \frac{V_2 - V_1}{24\Omega} + \frac{V_2 - V_1}{12\Omega} + \frac{V_2}{4\Omega} = 0 \end{array} \right.$$

$$V_1 = 36V \quad V_2 = 12V$$

$$i_L(0) = \frac{V_1 - V_2}{24\Omega} = \frac{36V - 12V}{24\Omega} = 1A$$

$$i_L(\infty) = 0A$$

$$\tau = \frac{L}{R_{Th}}$$

$$R_{Th} = 14\Omega + 12\Omega + 10\Omega = 36\Omega$$

$$\tau = \frac{2H}{36\Omega} = 55.6 \text{ ms}$$

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-t/\tau}$$

$$i_L(t) = (1A) e^{-t/55.6ms}$$

(b) At what time does the energy drop to 6.25% of its original value?

$$W_0 = \frac{1}{2} (2H) (1A)^2 = 1J$$

$$W_t = 0.0625 J = \frac{1}{2} (2H) i^2 \rightarrow i = 250 \text{ mA}$$

$$250 \text{ mA} = (1A) e^{-\frac{t}{55.6ms}}$$

$$-\frac{t}{55.6ms} = -1.386 \rightarrow t = 77.1 \text{ ms}$$


(c) When is the energy "fully" depleted?

$$t = 5 \times \pi = 5(55.6 \text{ ms}) = \underline{\underline{278 \text{ ms}}}$$

(d) If we reclosed the switch, how long for the current to charge up to $\frac{1}{2} A$?

$$i_i(0) = 0A \quad i_i(\infty) = 1A$$

$$T = \frac{L}{R_{Th}}$$

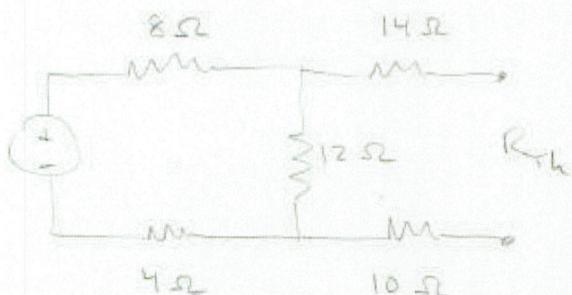

$$(8\Omega + 4\Omega) \parallel 12\Omega + 14\Omega + 10\Omega = R_{Th}$$

$$\underbrace{12\Omega}_{6\Omega} + 14\Omega + 10\Omega = \underline{\underline{30\Omega}}$$


$$T = \frac{2H}{30\Omega} = 66.7 \text{ ms}$$

$$i_i(t) = 1A \left(1 - e^{-\frac{t}{66.7 \text{ ms}}}\right) = 0.5A$$

$$e^{-\frac{t}{66.7 \text{ ms}}} = 0.5$$

$$-\frac{t}{66.7 \text{ ms}} = -0.693 \rightarrow \underline{\underline{t = 46.2 \text{ ms}}}$$

Problem 7 Given the following circuit

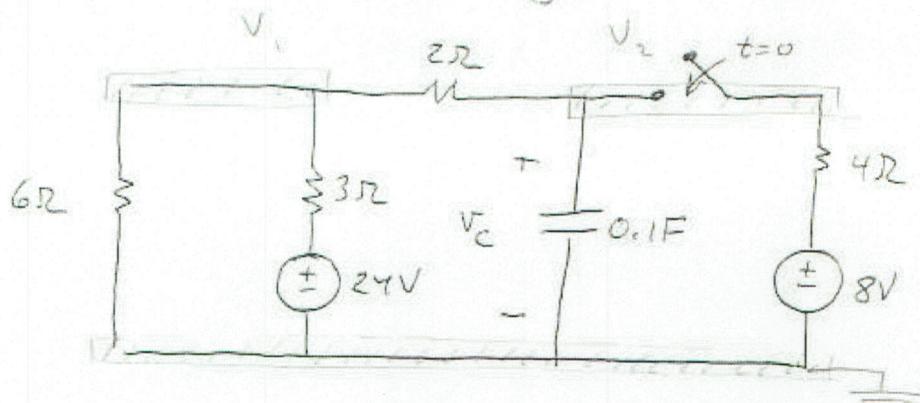


Find the expression for $v_c(t)$ for $t \geq 0$

$$v_c(0) = \left(\frac{6\Omega}{9\Omega}\right) 24V = 16V$$

$$\left. \begin{aligned} \frac{V_1}{6\Omega} + \frac{V_1 - 24V}{3\Omega} + \frac{V_1 - V_2}{2\Omega} &= 0 \\ \frac{V_2 - V_1}{2\Omega} + \frac{V_2 - 8V}{4\Omega} &= 0 \end{aligned} \right\} \quad \begin{aligned} V_1 &= 14V \\ V_2 &= 12V \end{aligned}$$

$$v_c(\infty) = V_2 = 12V$$

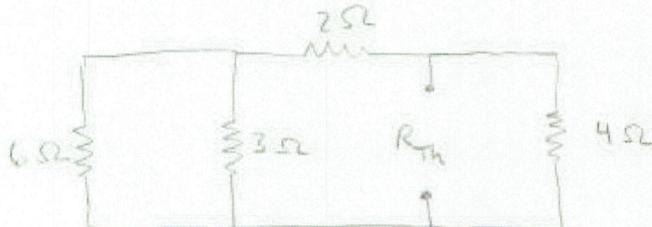

$$R_{th} = 4\Omega \parallel (2\Omega + 3\Omega \parallel 6\Omega)$$

$$= 4\Omega \parallel (2\Omega + 2\Omega)$$


$$R_{th} = \underbrace{4\Omega}_{2\Omega} \rightarrow \tau = R_{th}C = (2\Omega)(0.1F)$$

$$\tau = 0.2s$$

$$v_c(t) = 12V + (16V - 12V) e^{-\frac{t}{0.2s}}$$

$$v_c(t) = 12V + (4V) e^{-\frac{t}{0.2s}}$$

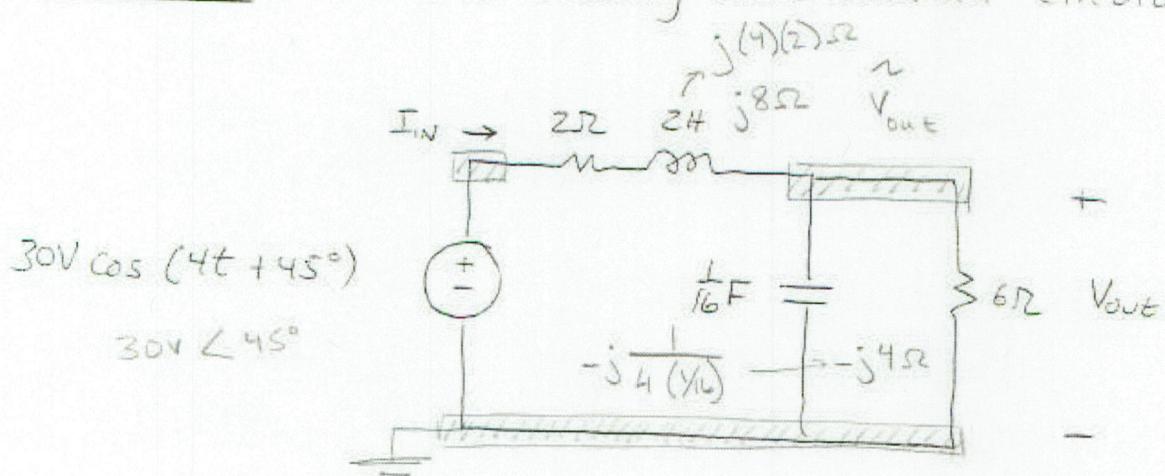Problem 8 Given the following time-domain circuit




(a) Find the steady-state expressions for V_{out} and I_{in}

$$\frac{\tilde{V}_{out} - 30V \angle 45^\circ}{2\Omega + j8\Omega} + \frac{\tilde{V}_{out}}{-j4\Omega} + \frac{\tilde{V}_{out}}{6\Omega} = 0$$

$$\boxed{\tilde{V}_{out} = 15.38 V \angle -65^\circ}$$

$$\tilde{I}_{in} = \frac{30V \angle 45^\circ - 15.38V \angle -65^\circ}{2\Omega + j8\Omega} = \boxed{4.62A \angle -8.7^\circ}$$

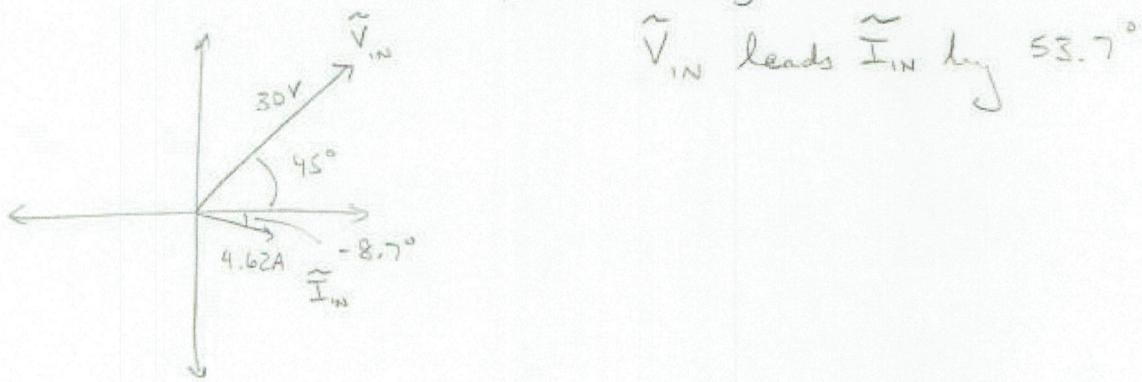
(b) Sketch the phasors \tilde{V}_{IN} and \tilde{I}_{IN} and state who leads whom and by what angle



(c) Find the circuit input impedance from your values


$$Z = \frac{\tilde{V}_{IN}}{\tilde{I}_{IN}} = \frac{30V \angle 45^\circ}{4.62A \angle -8.7^\circ} = \underline{6.49 \Omega \angle 53.7^\circ}$$

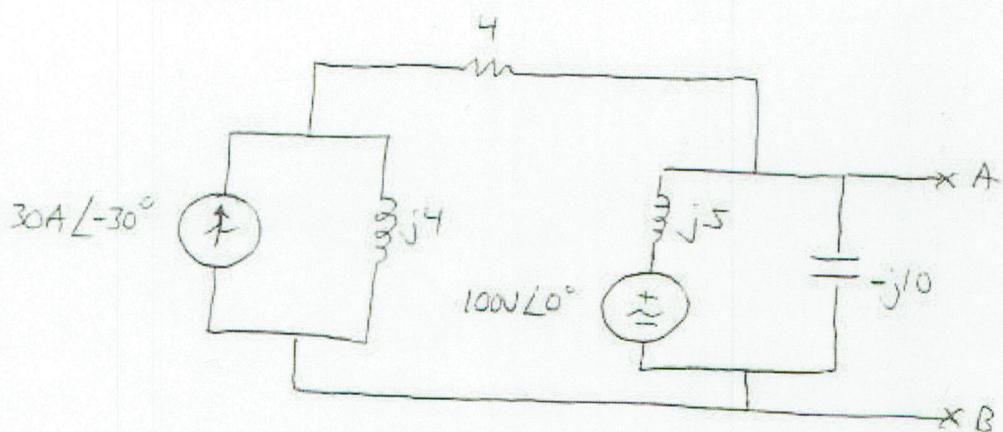Problem 9 Given the following frequency-domain circuit



Find the Thevenin Equivalent "seen" from terminals

A and B

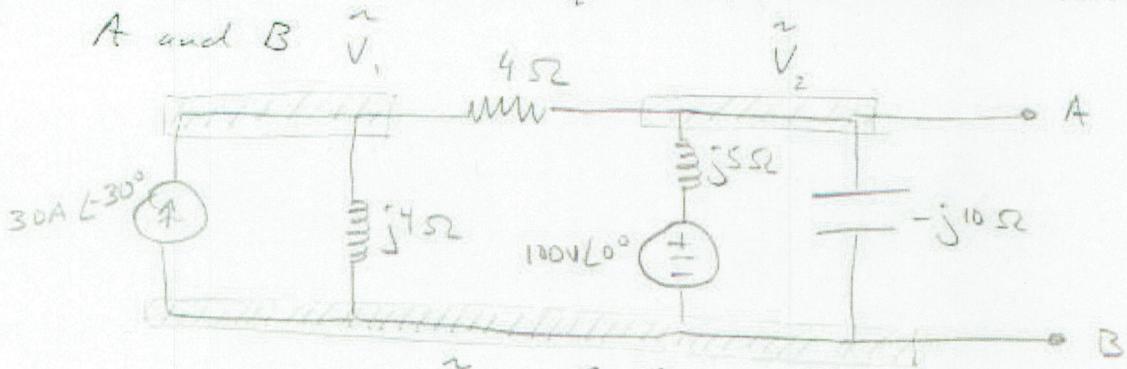

$$-(30A \angle -30^\circ) + \frac{\tilde{V}_1}{j4\Omega} + \frac{\tilde{V}_1 - \tilde{V}_2}{4\Omega} = 0$$

$$\tilde{V}_1 = 136.25V \angle 39.7^\circ$$

$$\frac{\tilde{V}_2 - \tilde{V}_1}{4\Omega} + \frac{\tilde{V}_2 - 100V \angle 0^\circ}{j5\Omega} + \frac{\tilde{V}_2}{-j10\Omega} = 0$$

$$\tilde{V}_2 = 97.55V \angle 25.6^\circ$$


$$= Z_{Th}$$

$$Z_{Th} = (-j10\Omega) \parallel (j5\Omega) \parallel (4\Omega + j4\Omega)$$

$$Z_{Th} = 3.89\Omega \angle 60.9^\circ$$

$$= 1.89\Omega + j3.4\Omega$$


97.55V L 25.6°

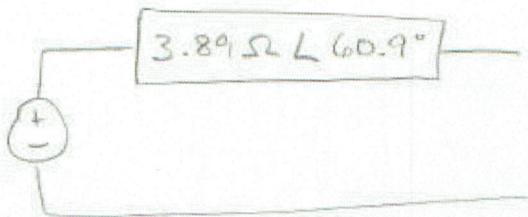

IF the source frequencies are 20rad/s, what capacitor do we need to attach to the Thévenin so that the voltage source and its current are in phase?

\tilde{V} in phase with \tilde{I} means impedance angle $\theta = 0^\circ$ or $X = 0$

$$\rightarrow -X_C = X_{Th}$$

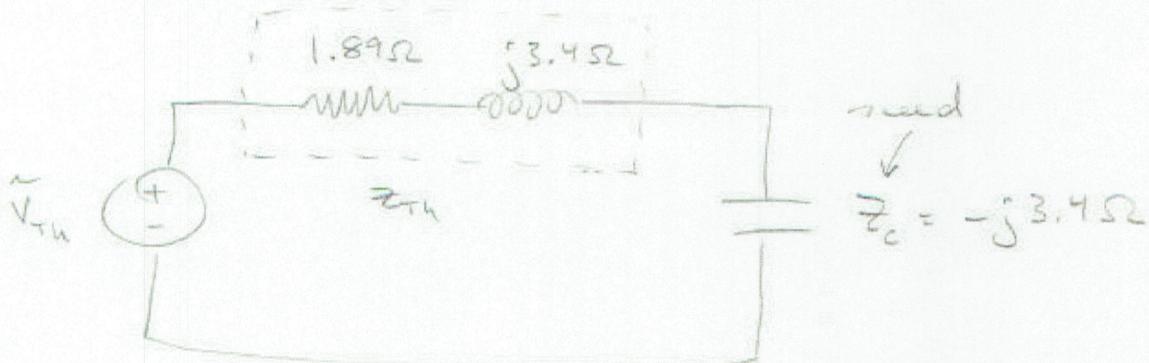


$$Z_c = -j \frac{1}{\omega C} \rightarrow \frac{1}{(20 \cdot \text{ad/s}) C} = 3.4 \Omega$$

$$C = 14.7 \text{ mF}$$

Problem 10 Given the following scope image

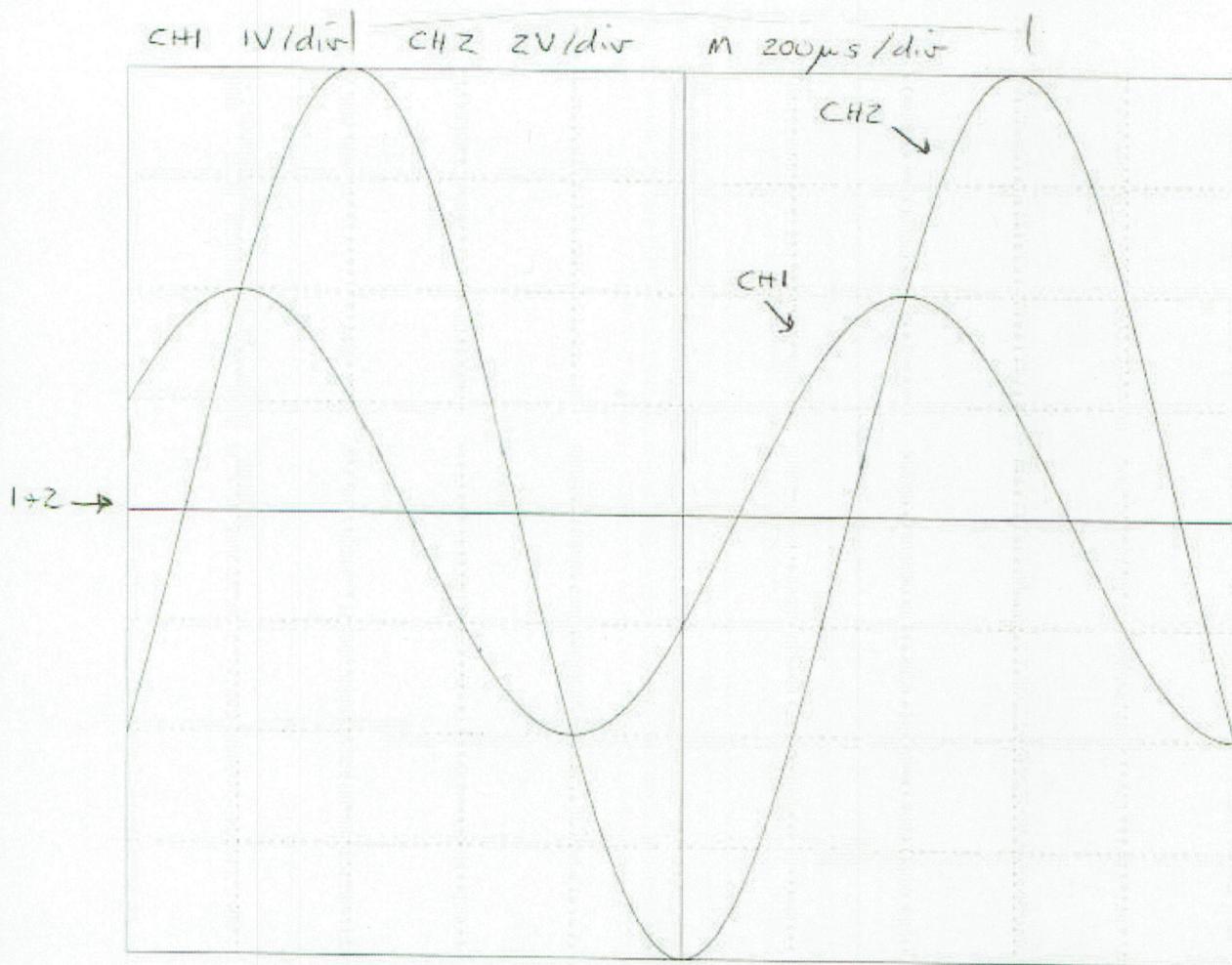a. Find the frequency (in Hz)

$$f = \frac{1}{T} = \frac{1}{6(200\mu s/div)} = \underline{\underline{833 \text{ Hz}}}$$



b. Who leads whom and by how much
CH1 leads CH2 by 1 div

$$\Delta\phi = \frac{\Delta t}{T} (360^\circ) = \frac{1 \text{ div}}{6 \text{ div}} (360^\circ) = \underline{\underline{60^\circ}}$$


c. RMS value of CH2 signal $V_p = 4 (2V/div) = 8V$
 $V_{rms} = \frac{8V}{\sqrt{2}} = \boxed{5.66V}$

Problem 11. Given the following scope image

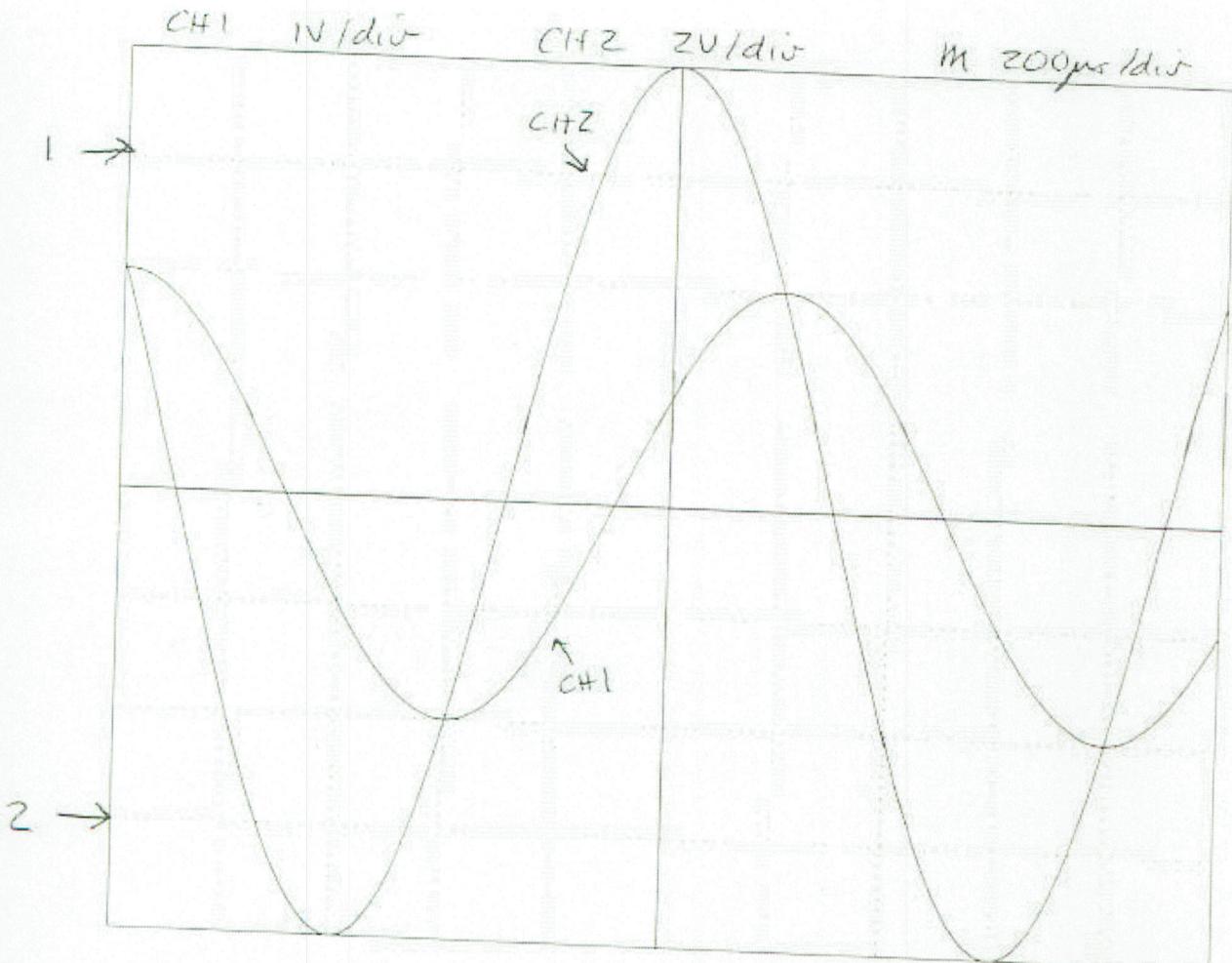- a. Determine the DC offset

$$\text{CH1} \rightarrow -3\text{div} (1\text{V/div}) = \underline{\underline{-3\text{V}}}$$

$$\text{CH2} \rightarrow +3\text{div} (2\text{V/div}) = \underline{\underline{6\text{V}}}$$



- b. IF we use the DMM VAC measure on CH1, what does it read?

$$\text{CH1 amplitude} = 2\text{div} (1\text{V/div}) = 2\text{V}$$

$$V_{\text{rms}} = \frac{2\text{V}}{\sqrt{2}} = \boxed{1.41\text{V}}$$

Topics

- Single-Phase AC Power


- Power Factor Correction

- Ideal Transformers

- Three-Phase Circuit Analysis

- Three-Phase Transformers

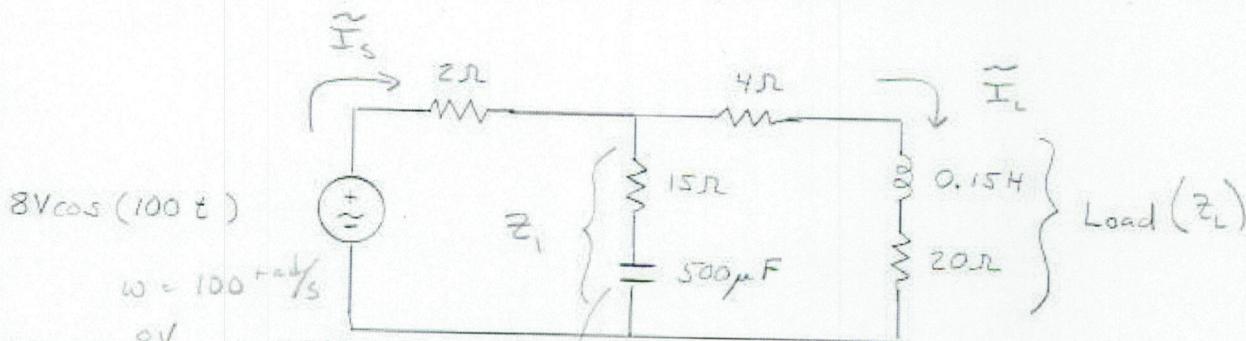ex. 1 Given the following circuit, Find the real and reactive power consumed by the load



$$8V \cos(100t)$$

$$\omega = 100 \text{ rad/s}$$

$$V_{rms} = \frac{8V}{\sqrt{2}} = 5.66V$$

$$Z_c = \frac{1}{(100 \text{ rad/s})(500 \mu\text{F})} L - 90^\circ = 20\Omega L - 90^\circ$$

$$Z_{0.15H} = (100 \text{ rad/s})(0.15H) L 90^\circ = 15\Omega L 90^\circ$$

$$Z_1 = 15\Omega + 20\Omega L - 90^\circ = 25\Omega L - 53.13^\circ$$

$$Z_2 = 20\Omega + 15\Omega L 90^\circ = 25\Omega L 36.87^\circ$$

alternate method: nodal analysis... see page 3

$$Z_{eq} = 2\Omega + Z_1 \parallel (4\Omega + Z_2)$$

$$= 2\Omega + (25\Omega L - 53.13^\circ) \parallel (4\Omega + 25\Omega L 36.87^\circ)$$

$$= 2\Omega + (25\Omega L - 53.13^\circ) \parallel (28.3\Omega L 32^\circ)$$

$$= 2\Omega + 18\Omega L - 13.82^\circ = 19.94\Omega L - 12.45^\circ$$

$$\tilde{I}_s = \frac{\tilde{V}_s}{\tilde{Z}_{eq}} = \frac{5.66V L 0^\circ}{19.94\Omega L - 12.45^\circ} = 0.284A L 12.45^\circ$$


Current divider to find \tilde{I}_L :

$$\tilde{I}_L = \left(\frac{\tilde{Z}_L}{\tilde{Z}_L + 4\Omega + \tilde{Z}_L} \right) \tilde{I}_s = \frac{25\Omega L - 53.13^\circ}{25\Omega L - 53.13^\circ + 4\Omega + 25\Omega L 36.87^\circ}$$

$$\tilde{I}_L = 180.6mA L - 33.37^\circ$$

$$P_L = I_L^2 R_L = (180.6mA)^2 (20\Omega) = 652.3\text{ mW}$$
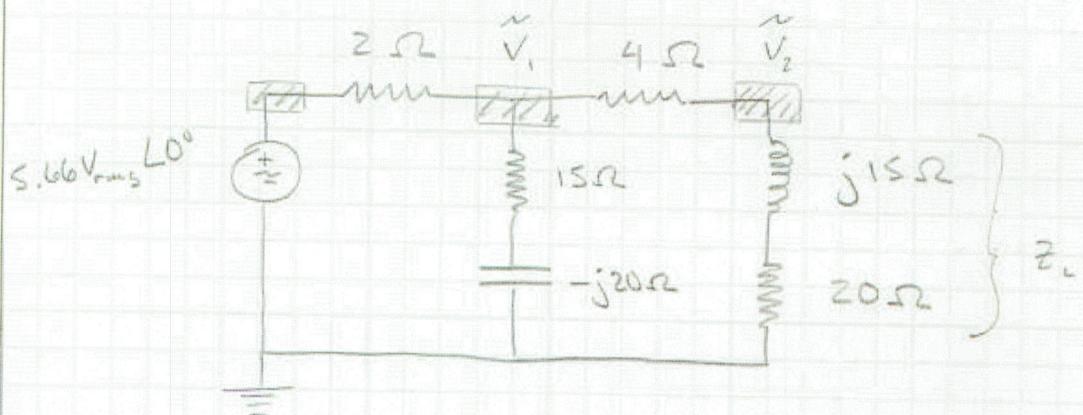
$$Q_L = I_L^2 X_L = (180.6mA)^2 (15\Omega) = 489.2\text{ mVAR}$$



$$\left\{ \begin{array}{l} \frac{\tilde{V}_1 - 5.66 \text{ V} \angle 0^\circ}{2\Omega} + \frac{\tilde{V}_1}{15\Omega - j20\Omega} + \frac{\tilde{V}_1 - \tilde{V}_2}{4\Omega} = 0 \\ \frac{\tilde{V}_2 - \tilde{V}_1}{4\Omega} + \frac{\tilde{V}_2}{20\Omega + j15\Omega} = 0 \end{array} \right.$$

$$\tilde{V}_1 = 5.11 \text{ V} \angle -1.37^\circ$$

$$\tilde{V}_2 = 4.51 \text{ V} \angle 3.5^\circ$$


$$\tilde{V}_{LOAD} = \tilde{V}_2 \quad \tilde{I}_{LOAD} = \frac{\tilde{V}_2}{Z_L} = \frac{4.51 \text{ V} \angle 3.5^\circ}{20\Omega + j15\Omega}$$

$$\tilde{I}_{LOAD} = 180.4 \text{ mA} \angle -33.4^\circ$$

$$P_L = I_L^2 R_{LOAD} = (180.4 \text{ mA})^2 (20\Omega) = 650.9 \text{ mW}$$

$$Q_L = I_L^2 X_{LOAD} = (180.4 \text{ mA})^2 (15\Omega) = 488.2 \text{ mVAR}$$

ex. 2 The follow R-L load consumes 800W

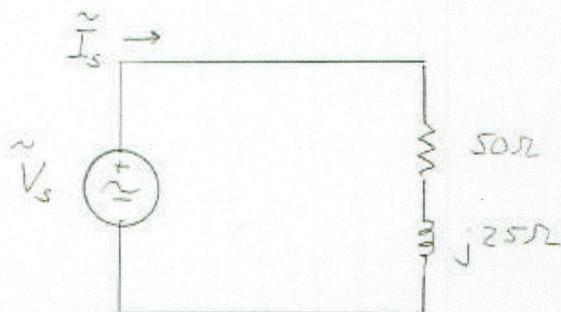

Determine \tilde{V}_s and \tilde{I}_s and the source apparent power


$$P = I^2 R \rightarrow 800W = \tilde{I}_s^2 (50\Omega)$$

$$\tilde{I}_s = 4A_{rms}$$

Traditionally choose \tilde{V}_s to be reference phasor;

$$\tilde{V}_s = V_s \angle 0^\circ \rightarrow \tilde{I}_s = I_s \angle -\Theta$$

where Θ is impedance angle given by:

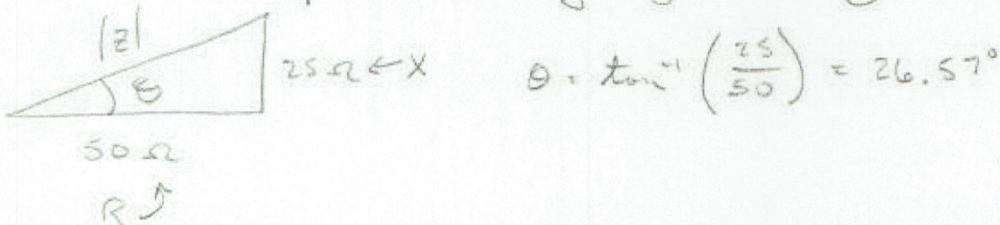

$$\text{so that } \boxed{\tilde{I}_s = 4A \angle -26.57^\circ} \quad (\text{rms})$$

$$\text{and } \tilde{V}_s = \tilde{I}_s Z = (4A \angle -26.57^\circ)(50\Omega + j25\Omega)$$

$$\boxed{\tilde{V}_s = 223.6V \angle 0^\circ}$$

\nwarrow rms


Ex. 3 For the previous circuit, if the source frequency is 60Hz, Find the capacitor required to power factor correct to unity.

$$\text{Find } Q : \quad Q = I^2 X = (4A)^2 (25\Omega) = 400 \text{ VAR}$$

$$C = \frac{Q}{\omega V^2} = \frac{400 \text{ VAR}}{(377 \text{ rad/s})(223.6 \text{ V})^2}$$

$$\boxed{C = 21.22 \mu\text{F}}$$

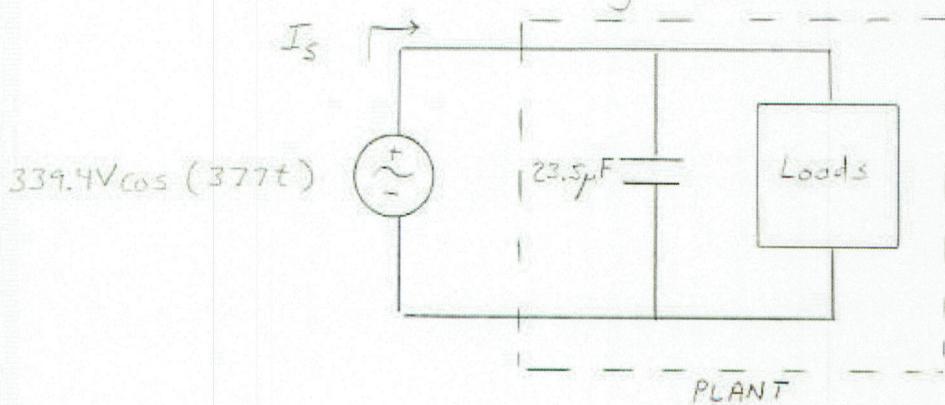ex. 4 Given the following system, if $I_s = 3.929A \cos(377t - 25.84^\circ)$



Find the power factor and real & reactive power of the load
make \tilde{V}_s and \tilde{I}_s rms phasors:

$$\tilde{V}_s = \frac{339.4V}{\sqrt{2}} = 240V_{rms} \quad \tilde{I}_s = \frac{3.929A}{\sqrt{2}} = 2.78A_{rms}$$

$$\tilde{V}_s = 240V_{rms} \angle 0^\circ \quad \tilde{I}_s = 2.78A_{rms} \angle -25.84^\circ$$

$\checkmark \leftarrow \text{design}$

$$S = \tilde{V}_s \tilde{I}_s^* = (240V \angle 0^\circ)(2.78A \angle 25.84^\circ)$$

$$S = 667.2 \text{VA} \angle 25.84^\circ$$

alternate method: Ps and Qs... see next page

$$S = S_{CAP} + S_{LOADS}$$

$$S_{CAP} = \frac{\tilde{V}_s^2}{Z_{CAP}} \quad Z_{CAP} = \frac{1}{\omega C} \angle -90^\circ = \frac{1}{(377 \text{rad/s})(22.5 \mu F)} \angle -90^\circ$$


$$Z_{CAP} = 112.87 \Omega \angle -90^\circ$$

$$S_{CAP} = \frac{(240V)^2}{112.87 \Omega \angle -90^\circ} = 510.3 \text{VA} \angle -90^\circ$$

$$667.2 \text{VA} \angle 25.84^\circ = 510.3 \text{VA} \angle -90^\circ + S_{LOADS}$$

$$S_{LOADS} = 160 \text{VA} \angle 53.15^\circ = 600W + j800 \text{VAR}$$
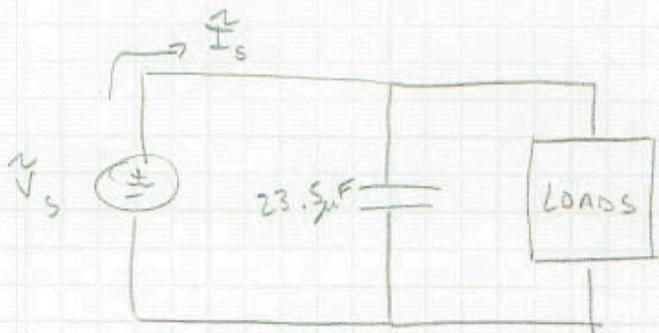
$$\text{pf} = \cos 53.15^\circ = 0.6 \text{ lagging}$$



$$\tilde{V}_s = 240 V_{rms} \angle 0^\circ \quad \tilde{I}_s = 2.78 A_{rms} \angle -25.84^\circ$$

$$Z_C = -\frac{j}{\omega C} = -\frac{j}{(377)(23.5 \mu F)} = -j112.87 \Omega$$

$$P_{TOTAL} = V_s I_s \cos \Theta_{TOTAL} \text{ where } \Theta = \phi_V - \phi_I$$

$$\Theta_{TOTAL} = 0^\circ - (-25.84^\circ)$$

$$\Theta_{TOTAL} = 25.84^\circ$$

$$P_{TOTAL} = (240V)(2.78A) \cos 25.84^\circ = 600.5W$$

$$Q_{TOTAL} = V_s I_s \sin \Theta_{TOTAL}$$

$$= (240V)(2.78A) \sin 25.84^\circ = 290.8 \text{ VAR}$$

$$P_{TOTAL} = P_{CAP} + P_{LOADS} \rightarrow P_{LOADS} = 600.5W$$

$$Q_{TOTAL} = Q_{CAP} + Q_{LOADS}$$

$$Q_{CAP} = \frac{V^2}{X_C} = \frac{(240V)^2}{-112.87\Omega} = -510.3 \text{ VAR}$$

$$290.8 \text{ VAR} = -510.3 \text{ VAR} + Q_{LOADS}$$

$$Q_{LOADS} = 801.1 \text{ VAR}$$

$$\Theta_{LOADS} = \tan^{-1} \left(\frac{801.1}{600.5} \right) = 53.1^\circ$$

$$\rho f = \cos \Theta_{LOADS} = \cos (53.1^\circ) = 0.6 \text{ lagging}$$

