

Q. What is the maximum current that a  $\frac{1}{2}W$ ,  $100\Omega$  resistor can carry?

$$P = I^2 R$$

$$0.5W = I^2 (100\Omega)$$

$$\boxed{I_{\max} = 70.7 \text{ mA}}$$


Q Suppose you must dissipate  $10W$  and require  $100\Omega$  of resistance, but you only have  $2W$  resistors. Suggest the minimal part solution will have to use at least 5 resistors, each dissipating the full rated  $2W$ . Can achieve  $100\Omega$  with 5 identical resistors by putting (5)  $20\Omega$  resistors in series or (5)  $500\Omega$  resistors in parallel.

Q. A 6V battery is rated for 7Ah,  
what resistance must be attached  
across it for the battery to last

$$5\text{hrs} ? \quad \frac{7\text{A}\cdot\text{hr}}{\text{I}} = 5\text{hr} \Rightarrow \text{I} = 1.4\text{A}$$


$$V = IR \rightarrow 6\text{V} = (1.4\text{A})R \rightarrow R = 4.29\Omega$$

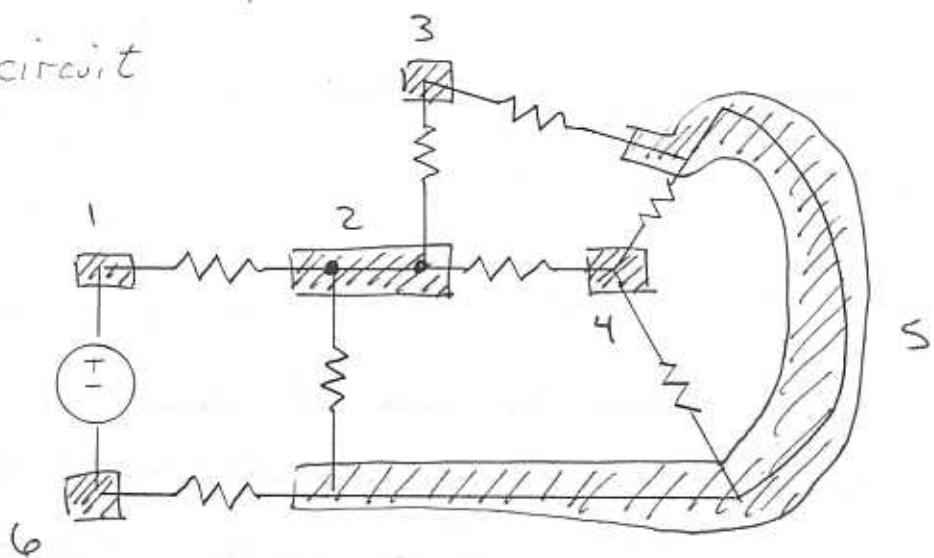Q. How many nodes are in the following circuit



[6]

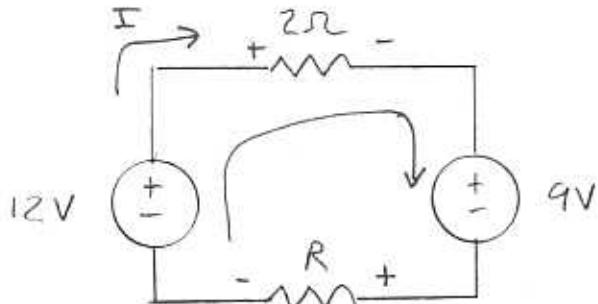Q What value of  $R$  will cause the  $2\Omega$  resistor to absorb  $1W$



Find  $V_{2\Omega}$ :

$$P = \frac{V^2}{R}$$

$$1W = \frac{V_{2\Omega}^2}{2\Omega}$$

$$V_{2\Omega} = 1.41V$$

$$\text{KVL: } -12V + V_{2\Omega} + 9V + V_R = 0$$

$$-12V + 1.41V + 9V + V_R = 0 \rightarrow V_R = 1.59V$$


Ohm's Law on  $2\Omega$  to find  $I$ :  $V = IR$

$$1.41V = I(2\Omega) \rightarrow I = 0.705A$$

Ohm's Law on  $R$ :

$$1.59V = (0.705A)R \rightarrow R = 2.26\Omega$$

Q.

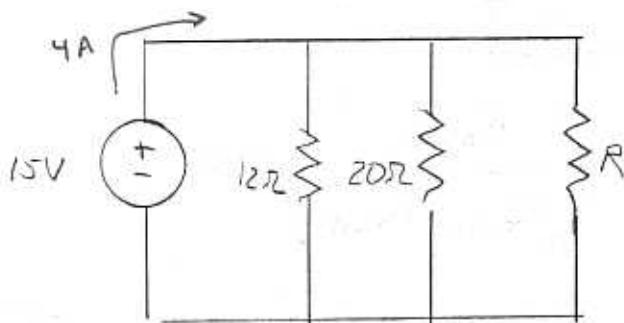

What  $R$  is required to have the supply source no more than  $4A$ ? What power does  $12\Omega$  absorb?

$$15V = (4A) R_{eq} \rightarrow R_{eq} = 3.75\Omega$$

$$12\Omega \parallel 20\Omega = 7.5\Omega$$

$$7.5\Omega \parallel R = \frac{(7.5)R}{7.5 + R} = 3.75\Omega$$

$$R = 7.5\Omega$$

$$P_{12\Omega} = \frac{V^2}{R}$$

$$P_{12\Omega} = \frac{(15V)^2}{12\Omega}$$

$$P_{12\Omega} = 18.75W$$


Q. If you have a 12V battery and a bulb rated for 5V at 0.1A, what series resistance is required and at what standard wattage ( $\frac{1}{8}W$ ,  $\frac{1}{4}W$ ,  $\frac{1}{2}W$ , 1W, 2W)

Bulb resistance :

$$V = IR_{\text{bulb}}$$

$$5V = (0.1A) R_{\text{bulb}}$$

$$R_{\text{bulb}} = 50\Omega$$

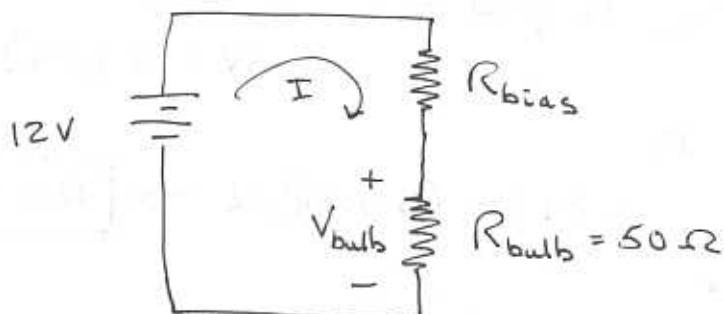


$$V_{\text{bulb}} = \left( \frac{R_{\text{bulb}}}{R_{\text{bias}} + R_{\text{bulb}}} \right) 12V$$

$$5V = \left( \frac{50\Omega}{R_{\text{bias}} + 50\Omega} \right) 12V \rightarrow R_{\text{bias}} = 70\Omega$$

$$\text{B} \quad I = \frac{12V}{120\Omega} = 0.1A$$

$$P_{\text{bias}} = I^2 R_{\text{bias}} = (0.1A)^2 (70\Omega) = 0.7W$$

$\Rightarrow$  1W resistor required

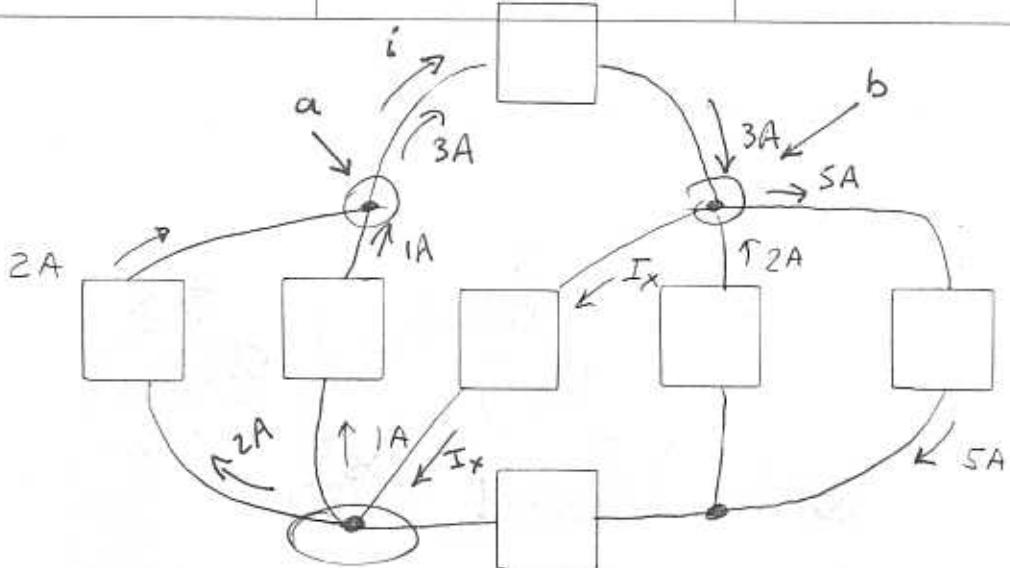


KCL @ a :  $2A + 1A = i$ ; KCL @ b:

Q. Find  $I_x$

$$I_x = 0A \quad 3A + 2A = I_x + 5A$$

~~KVL:  $V_1 - 5V + 3V = 0$~~

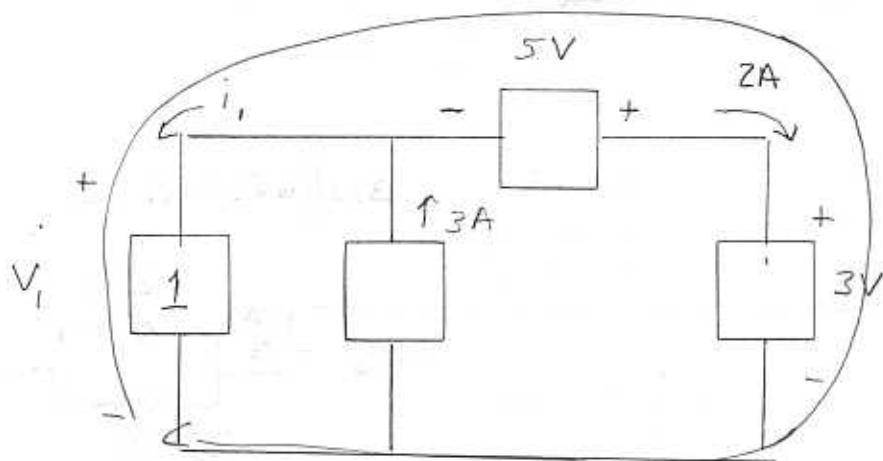Q. Find the power absorbed by component 1



KCL to find  $i_1$ :  $3A = i_1 + 2A \rightarrow i_1 = 1A$



KVL around outside to find  $V_1$ :

$$-V_1 - 5V + 3V = 0 \rightarrow V_1 = -2V$$

$$P = VI = (-2V)(1A) = -2W$$


Note: power absorbed is "-" because it is acting like a source

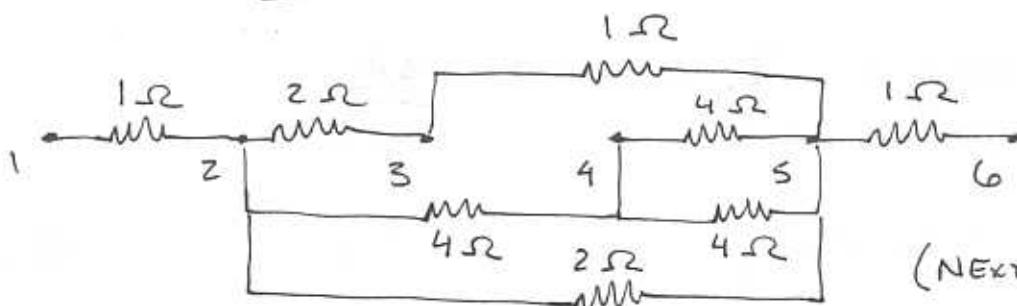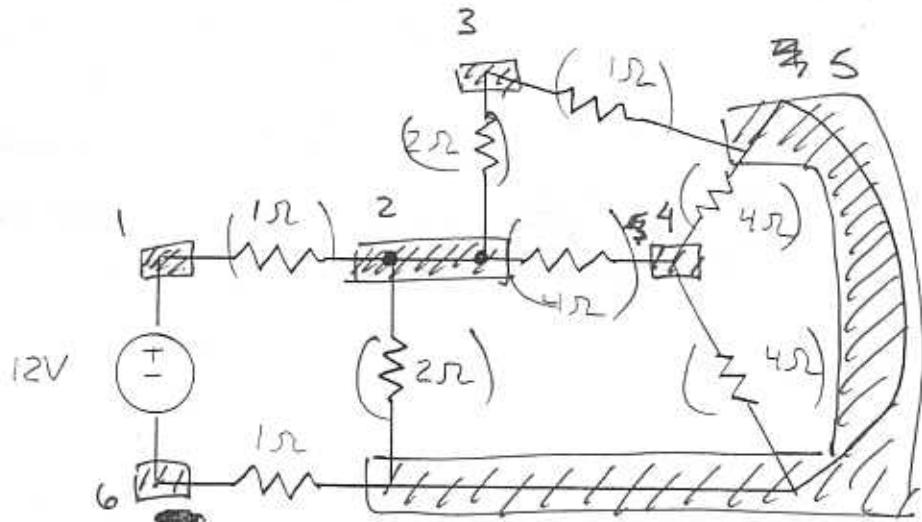Q. Find the equivalent resistance seen by the 12V source



(NEXT PAGE)


Q. Find  $R$  so that  $I_R = 4A$

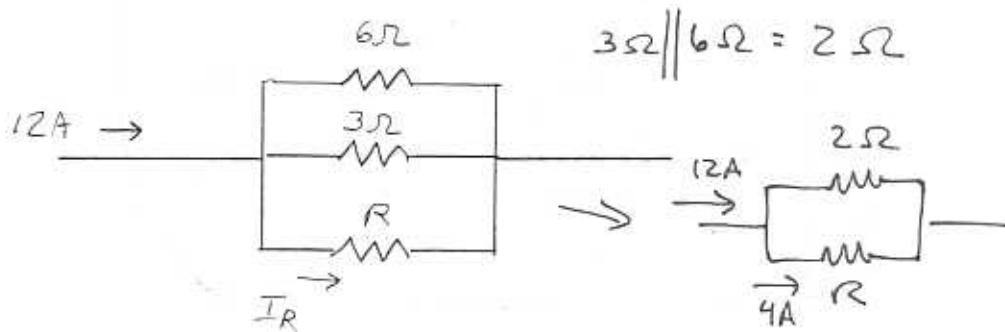


Current divider

$$I_R = \left( \frac{2\Omega}{R+2\Omega} \right) 12A = 4A$$

$$\boxed{R = 4\Omega}$$

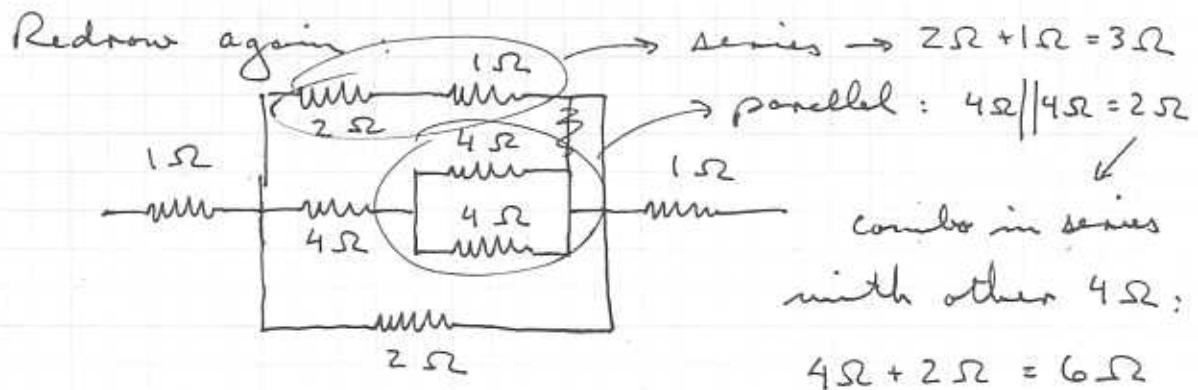


Now have:

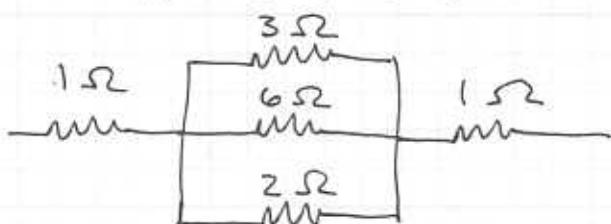

$$R_{eq} = 1\Omega + 3\Omega \parallel 6\Omega \parallel 2\Omega + 1\Omega$$

$$1\Omega + 1\Omega + 1\Omega = \boxed{3\Omega}$$

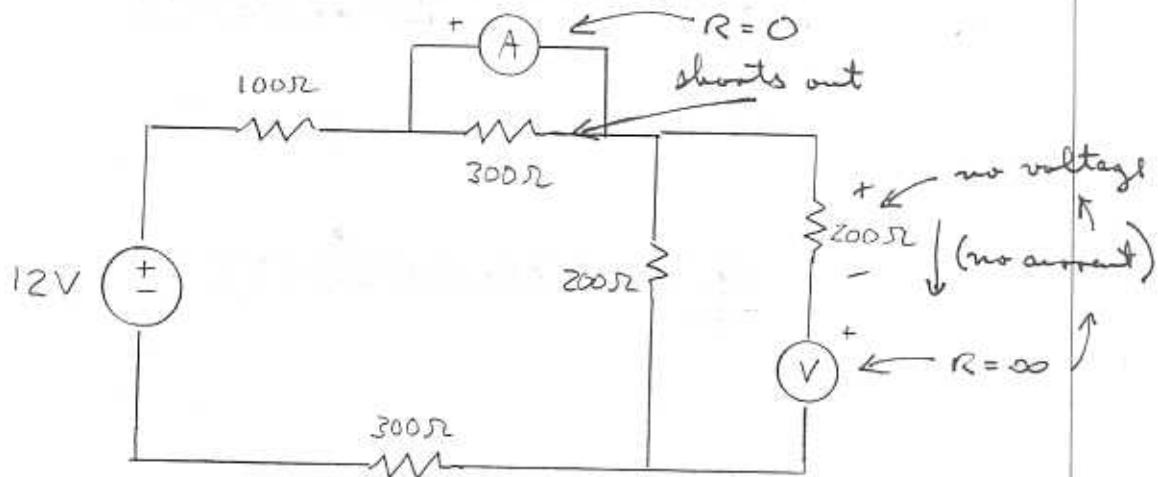Q. Consider ideal voltmeter and ammeter, what does each meter read?



effectively:


$$\text{I} = \frac{12V}{100\Omega + 200\Omega + 300\Omega}$$

$$\boxed{\text{I} = 20 \text{ mA}}$$

$$V_{200\Omega} = \left( \frac{200\Omega}{600\Omega} \right) 12V = \boxed{4V}$$


Q. If the ammeter has an internal resistance of  $10\Omega$  and the voltmeter is ideal, what does the voltmeter read?
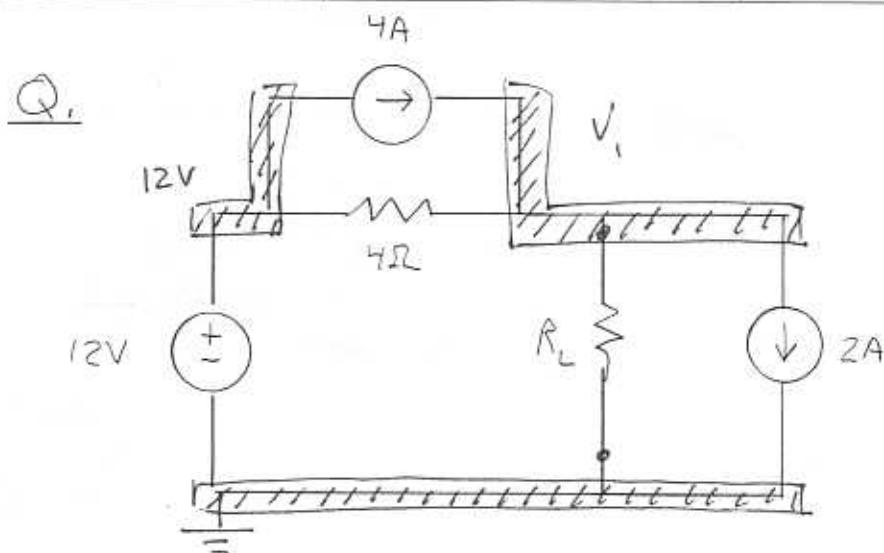
$$V_{40\Omega} = \left( \frac{40\Omega}{40\Omega + 10\Omega + 40\Omega} \right) 9V = \boxed{4V}$$




Find the Thevenin Equivalent seen by  $R_L$
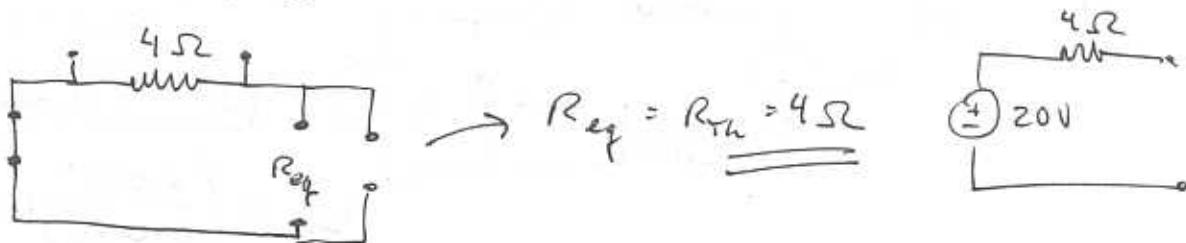
$$-4A + \frac{2V_1 - 12V}{4\Omega} + 2A = 0 \rightarrow V_1 = \underline{\underline{20V}} = V_{Th}$$



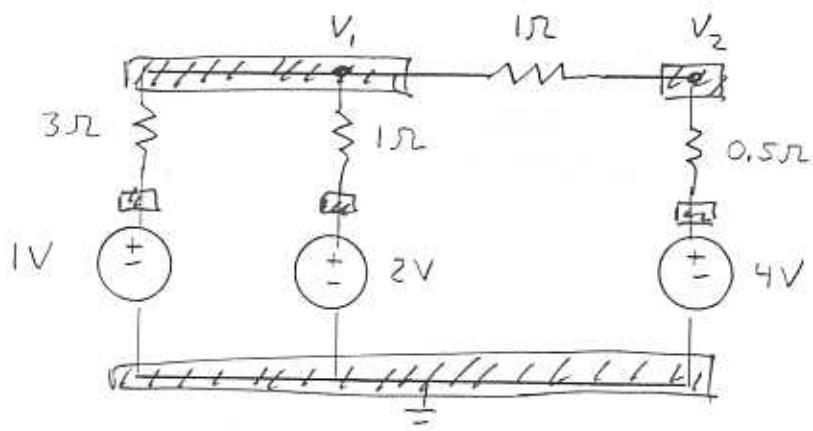Q. Determine node voltages  $V_1$  and  $V_2$



$$\frac{V_1 - 1V}{3\Omega} + \frac{V_1 - 2V}{1\Omega} + \frac{V_1 - V_2}{1\Omega} = 0$$


$$\frac{V_2 - V_1}{1\Omega} + \frac{V_2 - 4V}{0.5\Omega} = 0$$

$$V_1 = 2.5V$$

$$V_2 = 3.5V$$

Find  $i_1$  and  $i_2$ ,  $V_1$

Q.

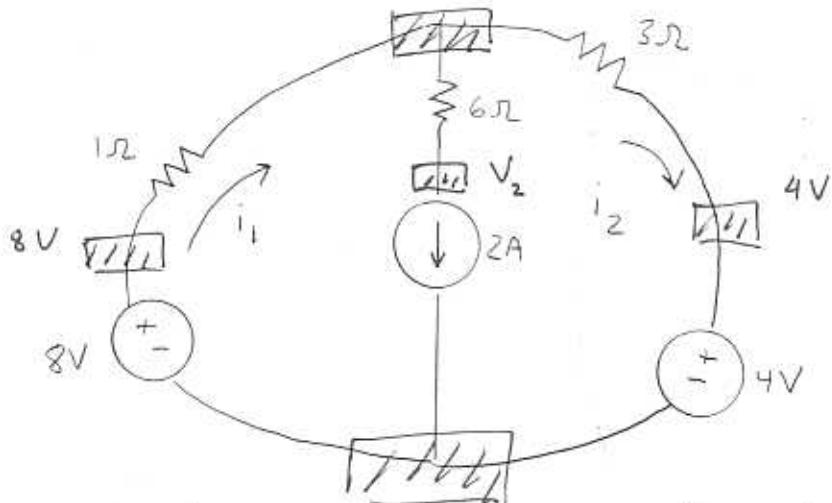


Use nodal to find  $V_1$ . Since we don't need  $V_2$  & we know that the current through the  $6\Omega$  resistor is  $2A$ , I'll use that instead of writing  $\frac{V_1 - V_2}{6\Omega}$

$$\frac{V_1 - 8V}{1\Omega} + 2A + \frac{V_1 - 4V}{3\Omega} = 0 \rightarrow V_1 = 5.5V$$

$$i_1 = \frac{8V - V_1}{1\Omega} = \frac{8V - 5.5V}{1\Omega} = \underline{\underline{2.5A}} \quad i_2 = \frac{V_1 - 4V}{3\Omega} = \frac{5.5V - 4V}{3\Omega} = \underline{\underline{0.5A}}$$

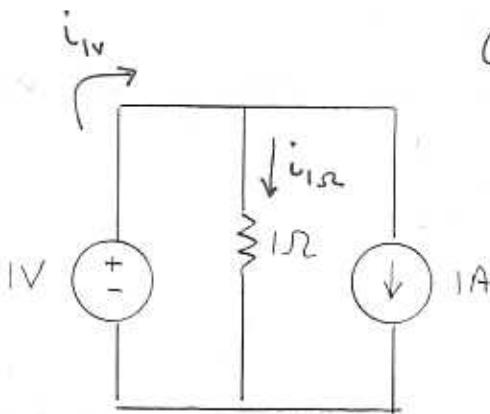Q. Find the power delivered by the  $1V$  source



Ohm's Law to find  $i_{1\Omega}$

$$1V = i_{1\Omega}(1\Omega)$$


$$i_{1\Omega} = 1A$$

KCL to find  $i_{1V}$


$$i_{1V} = i_{1\Omega} + 1A \\ = 1A + 1A = 2A$$

$$P_{1V} = (1V)(2A) = \boxed{2W}$$

Q. Find the Thevenin Equivalent at ab

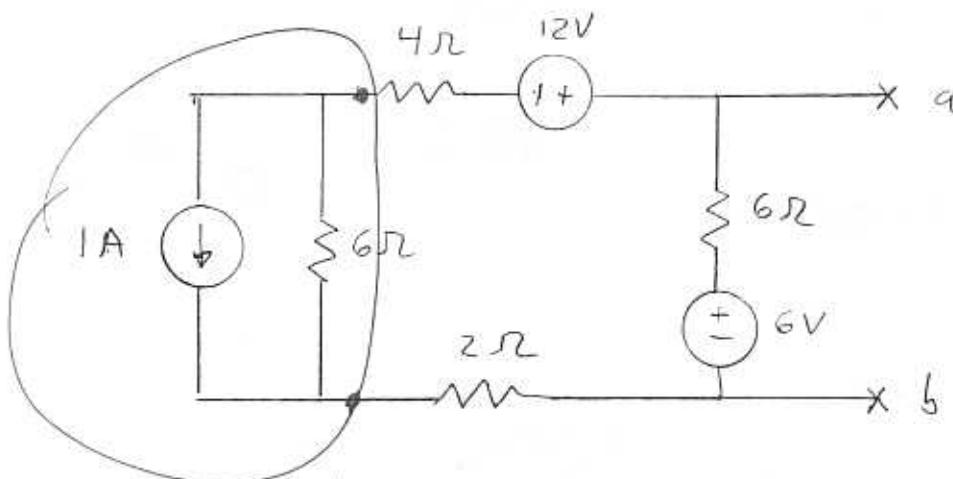

source transformation.

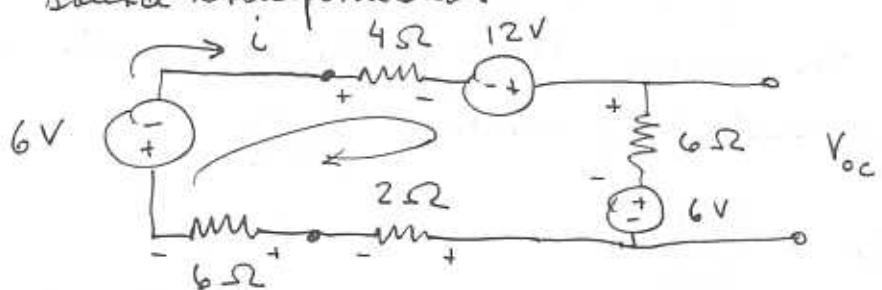



use KVL to find current i :

$$+6V + i(4\Omega) - 12V + i(6\Omega) + 6V + i(2\Omega) + i(6\Omega) = 0$$

$$\text{solve } \rightarrow i = 0$$


no current  $\rightarrow$  no voltage across resistors

$$\rightarrow \boxed{V_{oc} = 6V}$$

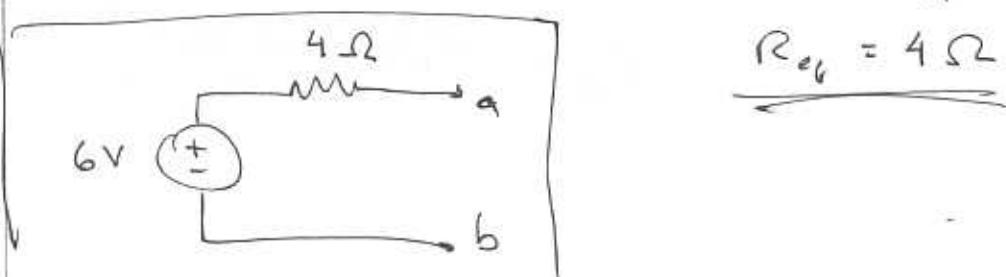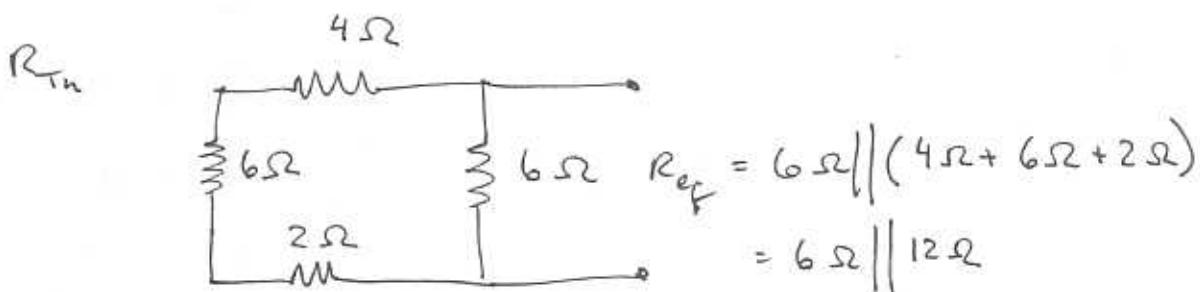


$$\boxed{R_{eq} = 4\Omega}$$

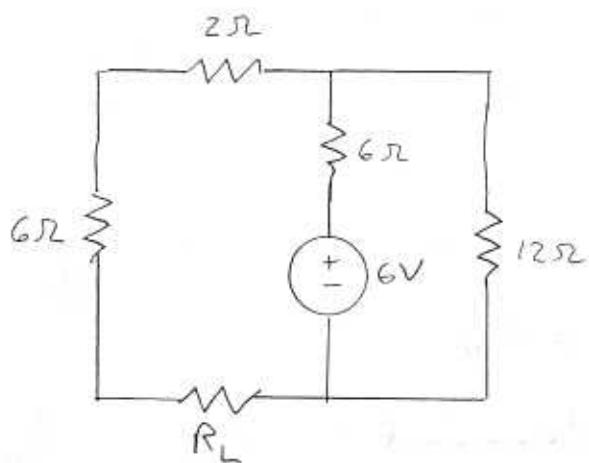Q. If  $R_L$  is chosen to give maximum power transfer, what is the maximum power transferred?



NEXT PAGE...

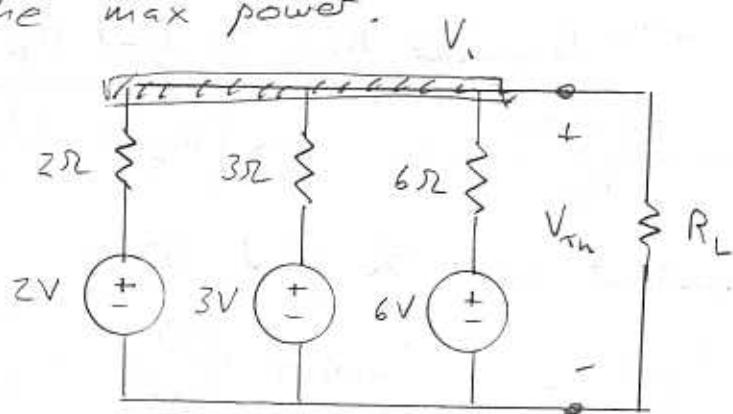Q. Find  $R_L$  for max power transfer and find the max power.



$$\frac{V_o - 2V}{2\Omega} + \frac{V_o - 3V}{3\Omega} + \frac{V_o - 6V}{6\Omega} = 0 \quad \text{NEXT PAGE}$$


$$V_o = 3V = V_{th}$$

$$R_{L,max} = 1\Omega$$

$$R_{th} = 2\Omega \parallel 3\Omega \parallel 6\Omega = 1\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(3V)^2}{4(1\Omega)} = 2.25W$$

Thevenize "as seen by"  $R_L$ :

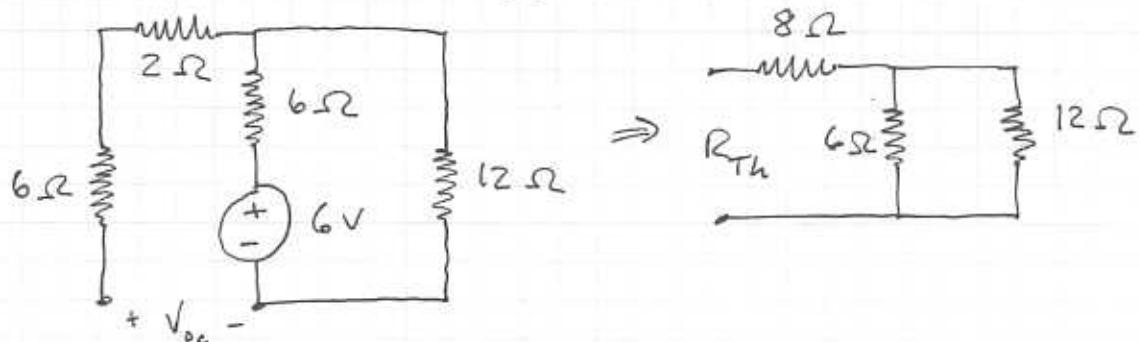

After removing  $R_L$ , no current through the "orphaned"  $2\Omega$  &  $6\Omega$  resistors

→ no voltage across them, so


$$V_{Th} = V_{oc} = V_{12\Omega}$$

$$V_{Th} = \left( \frac{12\Omega}{6\Omega + 12\Omega} \right) 6V = \underline{\underline{4V}}$$

$$\begin{aligned} R_{Th} &= 8\Omega + 6\Omega \parallel 12\Omega \\ &= 8\Omega + 4\Omega = 12\Omega \end{aligned}$$

$$P_{L,\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(4V)^2}{4(12\Omega)} = \boxed{0.333 W}$$

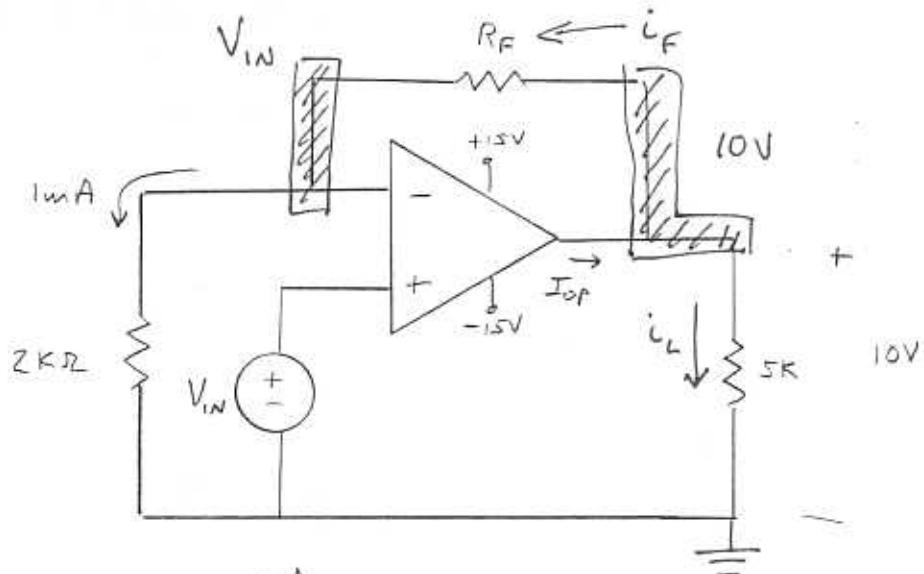Q. Given the following, find  $V_{IN}$ ,  $R_F$  and  $I_{op}$



$$v^+ = v^- = V_{IN}$$

KCL at “-” terminal :  $\frac{V_{IN}}{2k\Omega} + \frac{V_{IN} - 10V}{R_F} = 0$

Ohm's law across  $2k\Omega$  to find  $V_{IN}$  :

$$V_{IN} = (1mA)(2k\Omega) = \boxed{2V}$$


Plug into “-” terminal KCL to find  $R_F$  :

$$\frac{2V}{2k\Omega} + \frac{2V - 10V}{R_F} = 0 \rightarrow \boxed{R_F = 8k\Omega}$$

KCL at output node to find  $I_{op}$  :

$$I_{op} = i_F + i_L = 1mA + \frac{10V}{5k\Omega} = \boxed{3mA}$$


Q Find  $V_{out}$  and  $I_{op}$

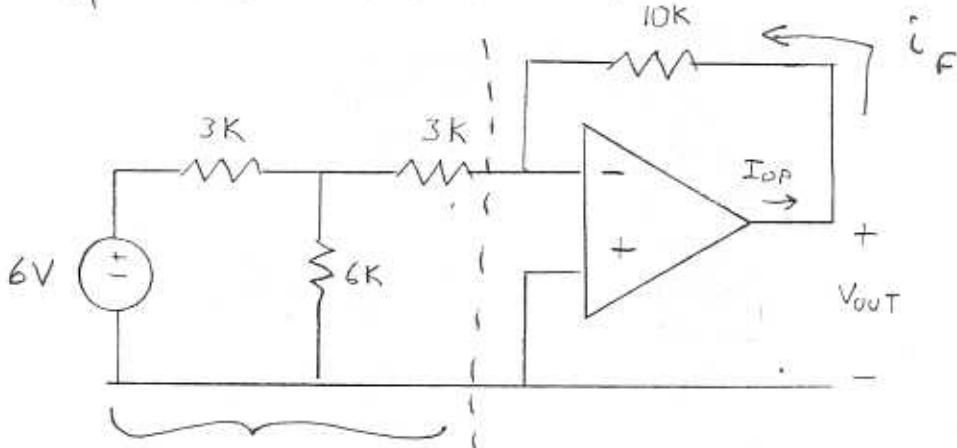

Thevenize to get conventional inverting amplifier

$$V_{Th} = \left( \frac{6k\Omega}{3k\Omega + 6k\Omega} \right) 6V = 4V$$
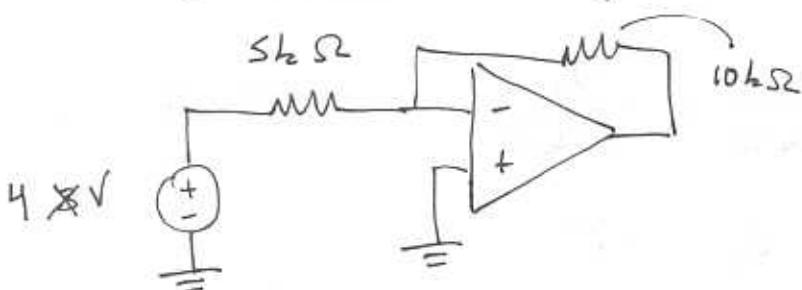
$$R_{Th} = 3k\Omega + 3k\Omega \parallel 6k\Omega = 5k\Omega$$




~~for  $V_o$~~

$$V_o = -\frac{R_F}{R_i} V_i = -\left(\frac{10k\Omega}{5k\Omega}\right) 4V = \boxed{-8V}$$

$$I_{op} = i_F = \frac{V_o}{R_F} = \frac{-8V}{10k\Omega} = \boxed{-0.8mA}$$

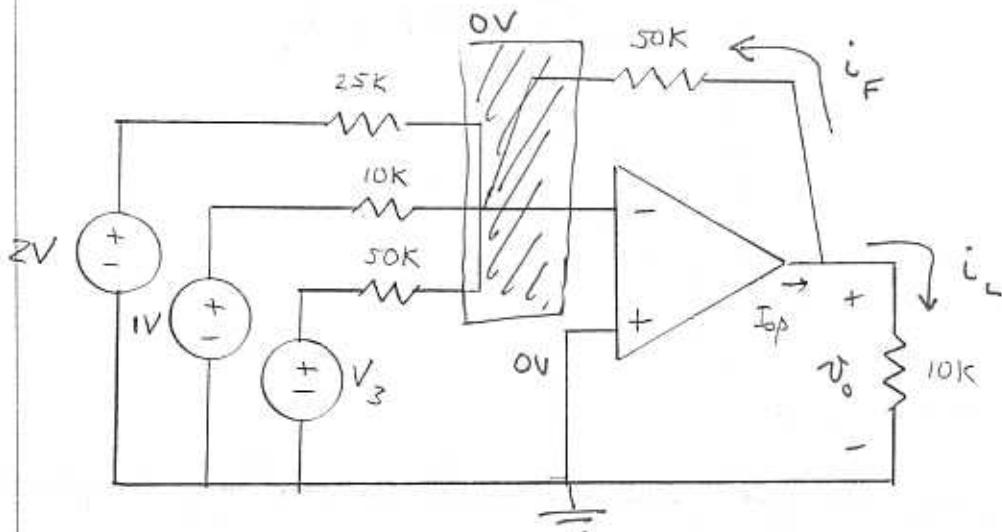Q. Find  $V_3$  so  $I_{op} = -0.72 \text{ mA}$



KCL at output node:  $I_{op} = i_F + i_L$

$$i_F = \frac{V_o - 0V}{50k\Omega} \quad i_L = \frac{V_o - 0V}{10k\Omega}$$

$$I_{op} = \frac{V_o}{50k\Omega} + \frac{V_o}{10k\Omega} = -0.72 \text{ mA}$$

$$V_o = -6V$$

Conventional summing amplifier topology:

$$V_o = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

$$-6V = - \left( \frac{50k\Omega}{25k\Omega} 2V + \frac{50k\Omega}{10k\Omega} 1V + \frac{50k\Omega}{50k\Omega} V_3 \right)$$

$$\Rightarrow V_3 = -3V$$