

Name: Key  
Section: \_\_\_\_\_

## EE331 Homework PS1 – fall 2012

### Problems from Alexander & Sadiku:

#### CH1

- 1.18 (Ans: -300W, 100W, 280W, -32W, -48W)

#### CH2

- 2.4 (Warm-up!)
- 2.12 (Ans:  $v_1 = 70\text{V}$ ,  $v_2 = 10\text{V}$ ,  $v_3 = 60\text{V}$ , use KVL)
- 2.26 (find the voltage across the parallel network using the data given for the  $16\Omega$  resistor and use that voltage to calculate the remaining currents) (Ans:  $i_x = 45\text{A}$ ,  $P_{total} = 22.4\text{W}$ )
- 2.34 (Ans:  $R_{eq} = 100\text{ Ohm}$ ,  $P_{tot} = 400\text{ W}$ )
- 2.41 (Ans: 16 Ohms)

### Additional Problems (Instructor Option):


- 2<sup>nd</sup> page of this Problem Set
- Any as assigned by instructor

## EE331 Homework PS1 – fall 2012

**1.15** When a car has a dead battery, it can often be started by connecting the battery from another car across its terminals. The positive terminals are connected together as are the negative terminals. The connection is illustrated in Fig. P1.15. Assume the current  $i$  in Fig. P1.15 is measured and found to be 30 A.

- Which car has the dead battery?
- If this connection is maintained for 1 min, how much energy is transferred to the dead battery?

Figure P1.15

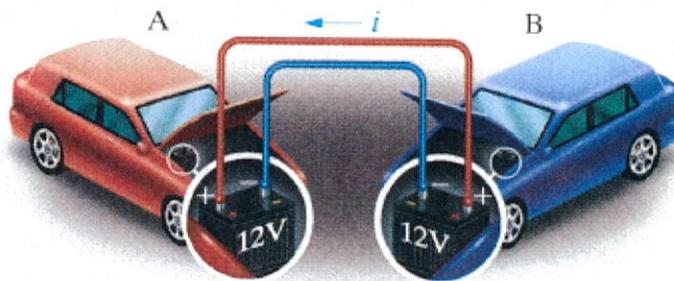

a) Current Flows into "A"

$$P = Vi = (30)(12) = 360 \text{ W}$$

↑  
(+) Power or Absorbing by "A"

∴ A is the Dead Battery

$$b) w(t) = \int_0^t p dx ; 1 \text{ min} = 60 \text{ sec}$$


$$w(60) = \int_0^{60} 360 dx$$

$$= 360(60 - 0)$$

Energy →  $w = 21,600 \text{ J}$

Figure 1.29

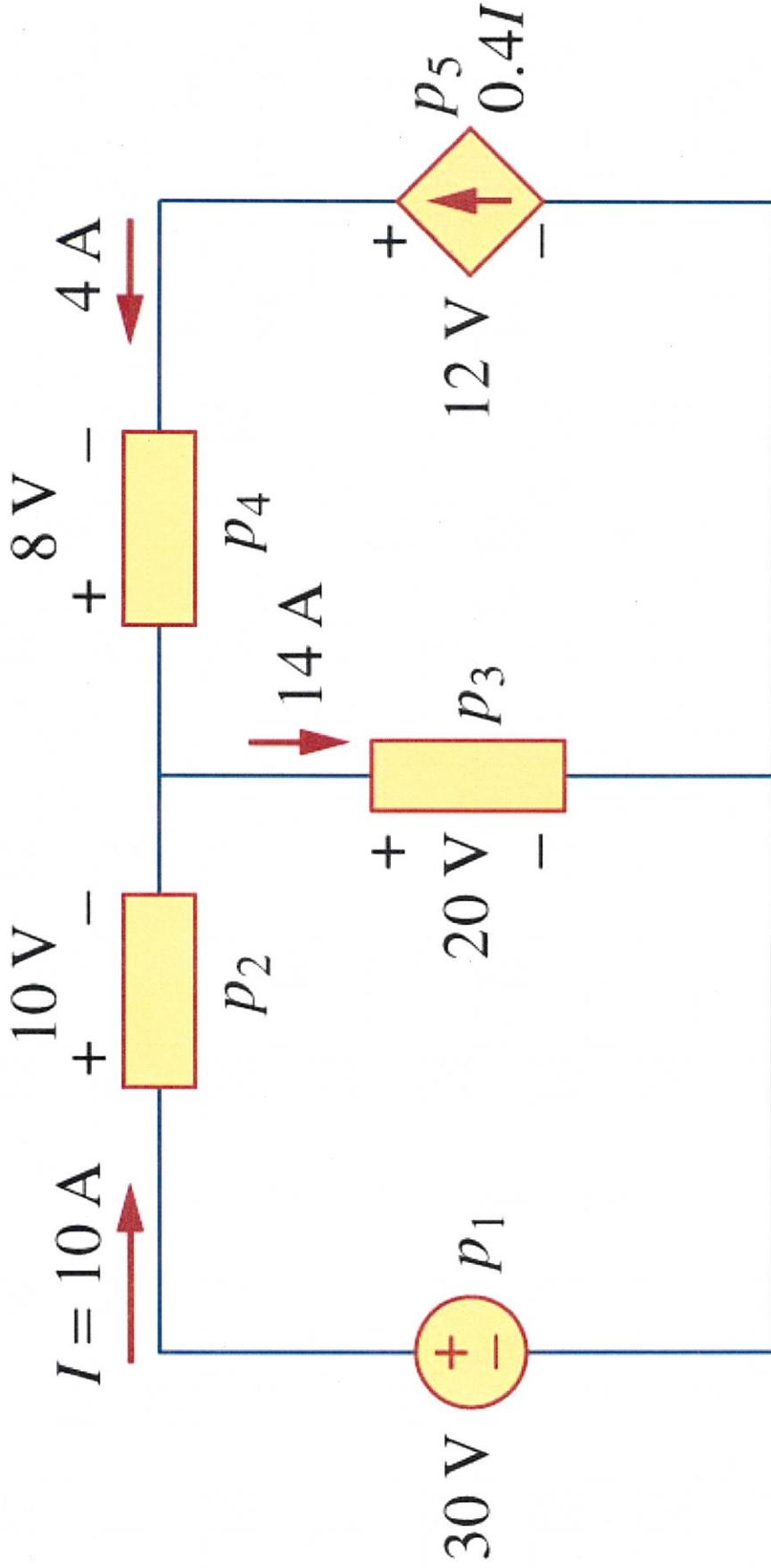Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



### Chapter 1, Solution 18

$$p^1 = 30(-10) = -300\text{ W}$$

$$p^2 = 10(10) = 100\text{ W}$$


$$p^3 = 20(14) = 280\text{ W}$$

$$p^4 = 8(-4) = -32\text{ W}$$

$$p^5 = 12(-4) = -48\text{ W}$$

Figure 2.68

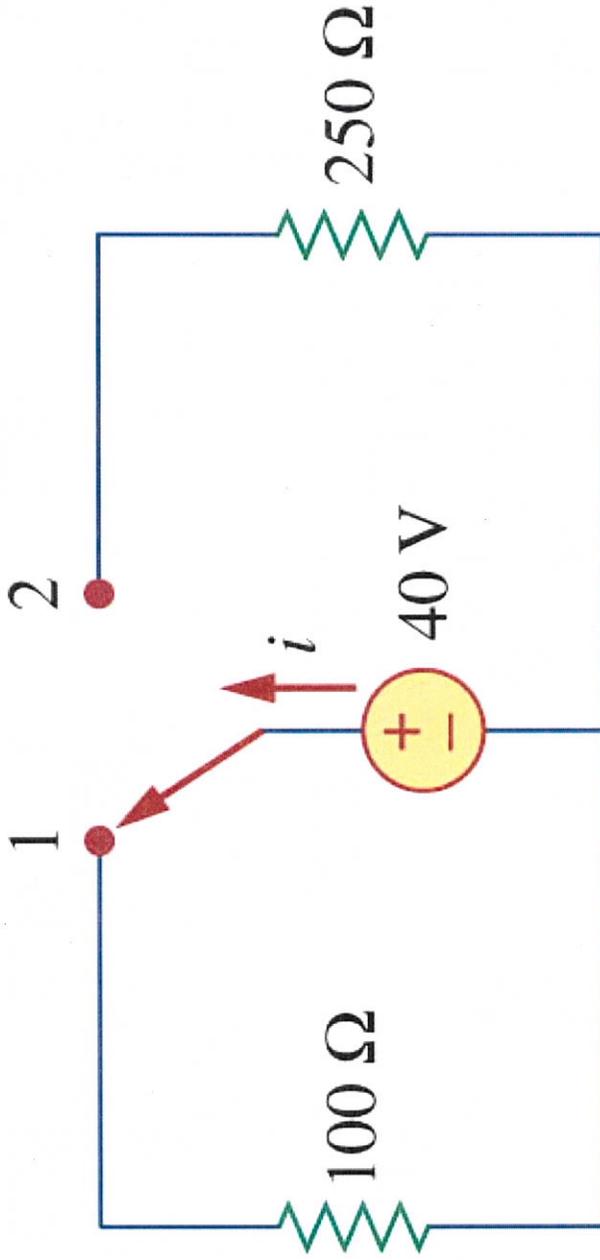Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




a.4

(a)  $i = 40/100 = 400 \text{ mA}$

(b)  $i = 40/250 = 160 \text{ mA}$

Chapter 2, Solution 12

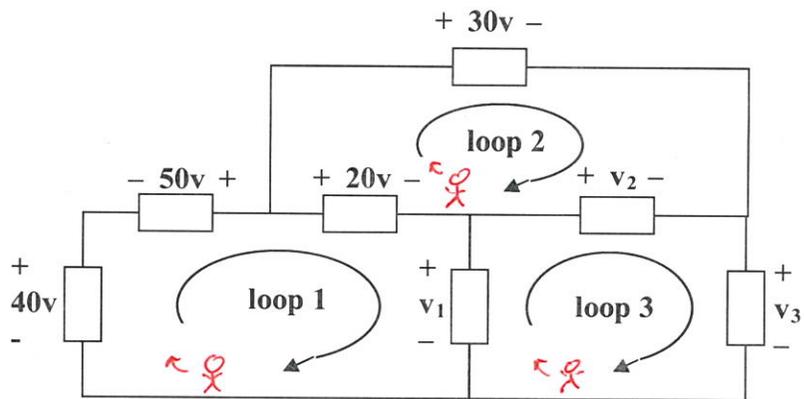

For loop 1,  $-40 - 50 + 20 + v_1 = 0$  or  $v_1 = 40 + 50 - 20 = 70 \text{ V}$

For loop 2,  $-20 + 30 - v_2 = 0$  or  $v_2 = 30 - 20 = 10 \text{ V}$

For loop 3,  $-v_1 + v_2 + v_3 = 0$  or  $v_3 = 70 - 10 = 60 \text{ V}$

### Chapter 2, Problem 26.

For the circuit in Fig. 2.90,  $i_o = 3$  A. Calculate  $i_x$  and the total power absorbed by the entire circuit.

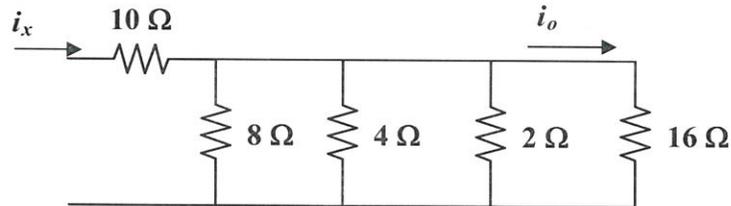


Figure 2.90  
For Prob. 2.26.

### Solution

If  $i_{16} = i_o = 3$  A, then  $v = 16 \times 3 = 48$  V and  $i_8 = 48/8 = 6$  A;  $i_4 = 48/4 = 12$  A; and  $i_2 = 48/2 = 24$  A.


Thus,

$$i_x = i_8 + i_4 + i_2 + i_{16} = 6 + 12 + 24 + 3 = 45 \text{ A}$$

$$\begin{aligned} p &= (45)^2 10 + (6)^2 8 + (12)^2 4 + (24)^2 2 + (3)^2 16 = 20,250 + 288 + 576 + 1152 + 144 \\ &= 20250 + 2106 = 22.356 \text{ kW}. \end{aligned}$$

Figure 2.98

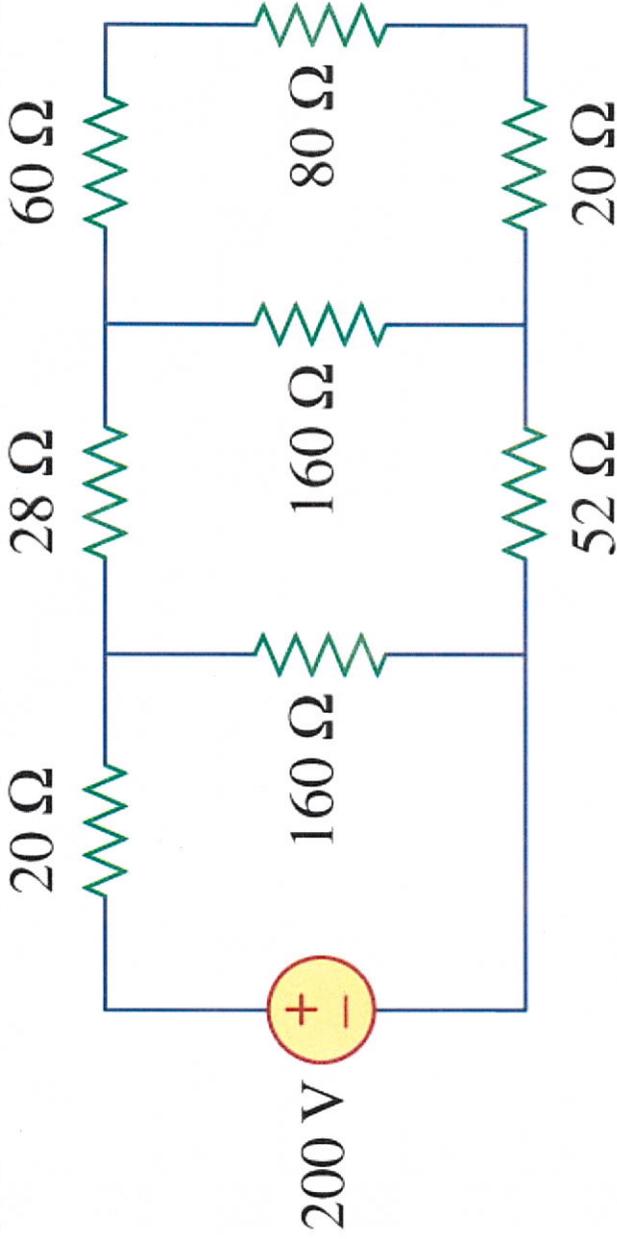Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



### Chapter 2, Solution 34

$$160 // (60 + 80 + 20) = 80 \Omega,$$


$$160 // (28 + 80 + 52) = 80 \Omega$$

$$R_{eq} = 20 + 80 = 100 \Omega$$

$$I = 200 / 100 = 2 \text{ A or } p = VI = 200 \times 2 = 400 \text{ W.}$$

Figure 2.105

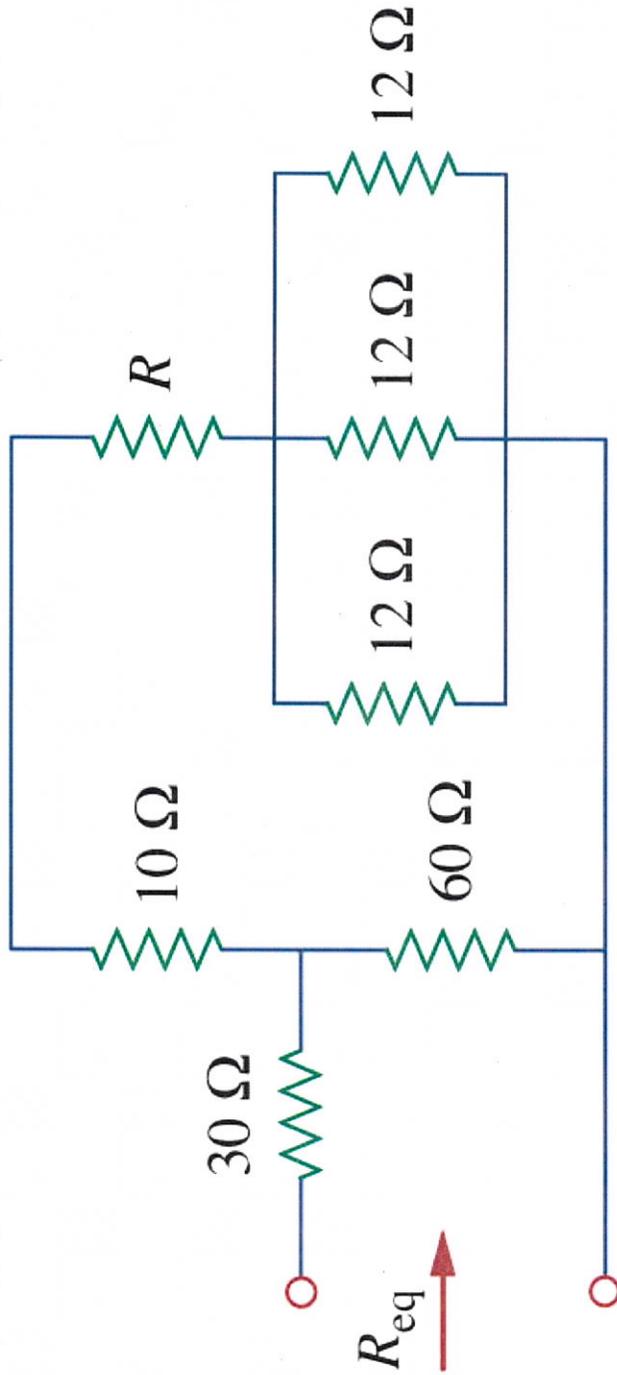Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Chapter 2, Solution 41

Let  $R_0$  = combination of three  $12\ \Omega$  resistors in parallel

$$\frac{1}{R_0} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12} \longrightarrow R_0 = 4$$

$$R_{eq} = 30 + 60 \parallel (10 + R_0 + R) = 30 + 60 \parallel (14 + R)$$

$$50 = 30 + \frac{60(14 + R)}{74 + R} \longrightarrow 74 + R = 42 + 3R$$

$$\text{or } R = 16\ \Omega$$