

## EE331 Homework PS2 – fall 2012

Problems from Alexander & Sadiku:


### CH2

- 2.19 – Warm up!
- 2.27
- 2.36 (maintain your intermediate resistor combination steps to help you get the output voltage using voltage divider and/or current divider) *Ans:*  $i = 0.2A$ ,  $V_o = 600mV$
- 2.39
- 2.67
- 2.74

Additional Problems (Instructor Option):

- 3.11 – Give Nodal Analysis a go!
- Any as assigned by instructor

Figure 2.83

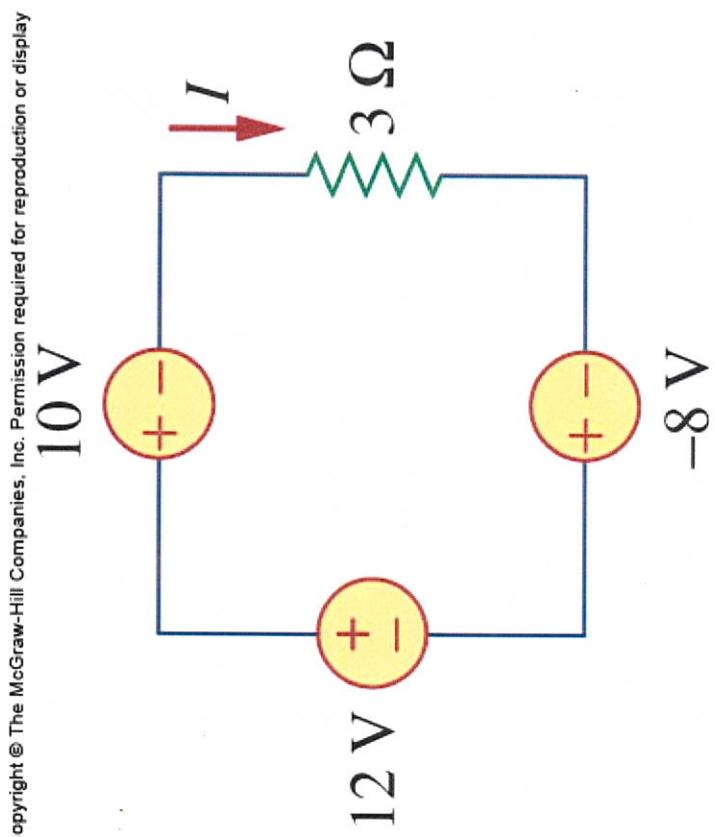

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

### Chapter 2, Solution 19

Applying KVL around the loop, we obtain

$$-(-8) - 12 + 10 + 3i = 0 \longrightarrow i = -2A$$

Power dissipated by the resistor:

$$P_{3\Omega} = i^2 R = 4(3) = 12W$$

Power supplied by the sources:

$$P_{12V} = 12 ((-2)) = -24W$$

$$P_{10V} = 10 (-(-2)) = 20W$$

$$P_{8V} = (-8)(-2) = 16W$$

**Chapter 2, Problem 27.**

Calculate  $I_o$  in the circuit of Fig. 2.91.

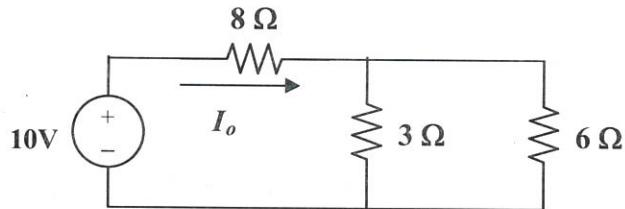


Figure 2.91  
For Prob. 2.27.


**Solution**

The 3-ohm resistor is in parallel with the 6-ohm resistor and can be replaced by a  $[(3 \times 6) / (3 + 6)] = 2$ -ohm resistor. Therefore,

$$I_o = 10 / (8 + 2) = 1 \text{ A.}$$

Figure 2.100

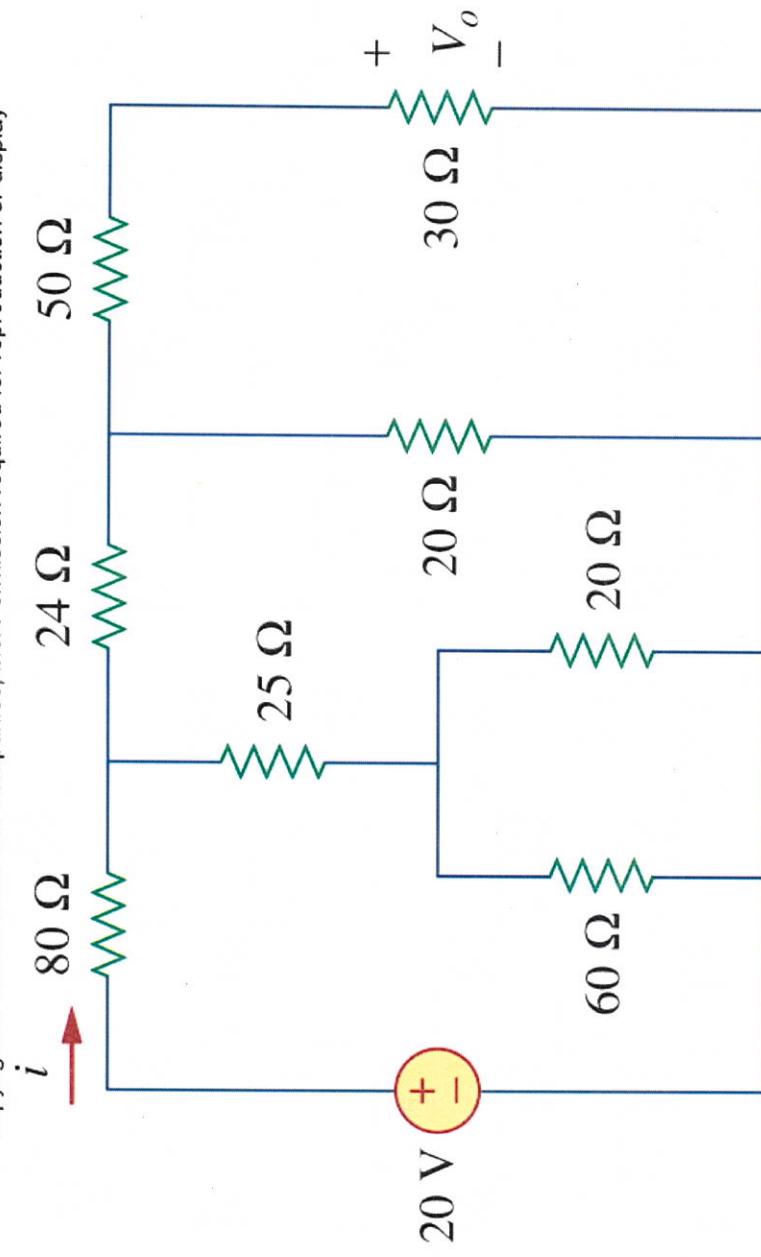Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



### Chapter 2, Solution 36

$$20//(30+50) = 16, \quad 24 + 16 = 40, \quad 60//20 = 15 \\ R_{eq} = 80 + (15+25)40 = 80+20 = 100 \Omega$$

$$i = 20/100 = 0.2 \text{ A}$$

If  $i_1$  is the current through the 24-Ω resistor and  $i_o$  is the current through the 50-Ω resistor, using current division gives

$$i_1 = [40/(40+40)]0.2 = 0.1 \text{ and } i_o = [20/(20+80)]0.1 = 0.02 \text{ A or}$$

$$V_o = 30i_o = 30 \times 0.02 = 600 \text{ mV.}$$

## Chapter 2, Problem 39.

Evaluate  $R_{eq}$  for each of the circuits shown in Fig. 2.103.

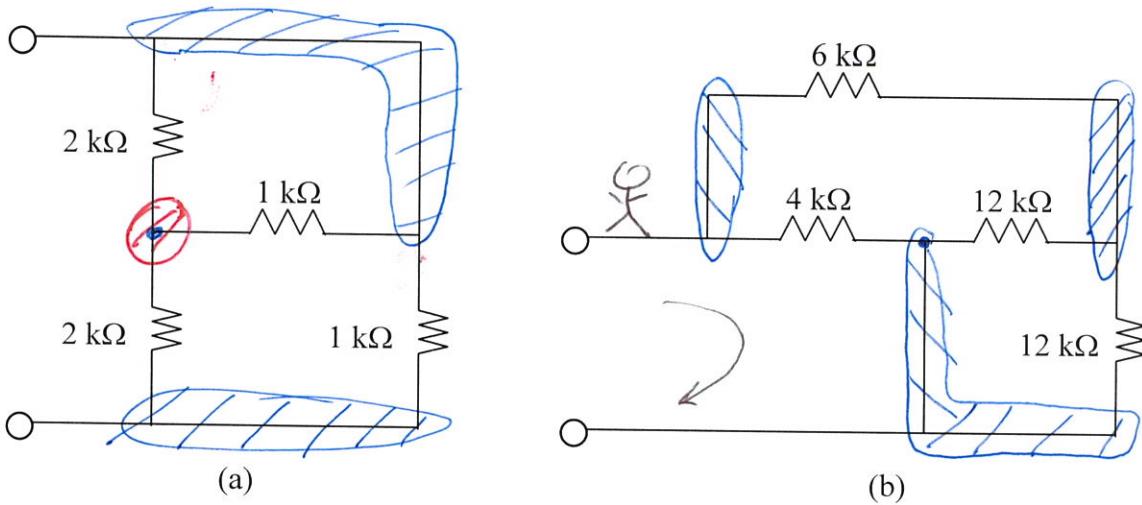



Figure 2.103 For Prob. 2.39.

$$\bullet R_{eq_a} = \left[ \left( 2k \parallel 1k \right) + 2k \right] \parallel 1k$$

$$= \left( \frac{2}{3}k + 2k \right) \parallel 1k$$

$$R_{eq_a} = 0.728k \Omega \approx 728\Omega$$

Could Re-draw - Can make easier

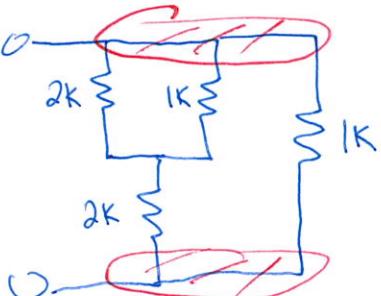


$$\bullet R_{eq_b} = 4k \parallel (6k + 12k \parallel 12k)$$

$$= 4k \parallel 12k$$

$$\boxed{R_{eq_b} = 3k \Omega}$$

Re-draw

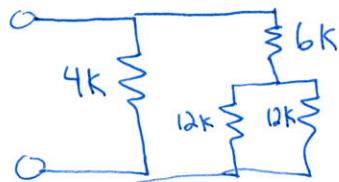


Chapter 2, Problem 67.

- (a) Obtain the voltage  $v_o$  in the circuit of Fig. 2.127(a)
- (b) Determine the voltage  $v'_o$  measured when a voltmeter with  $6\text{-k}\Omega$  internal resistance is connected as shown in Fig. 2.127(b)
- (c) The finite resistance of the meter introduces an error into the measurement. Calculate the percent error as

$$\left| \frac{v_o - v'_o}{v_o} \right| \times 100\%.$$

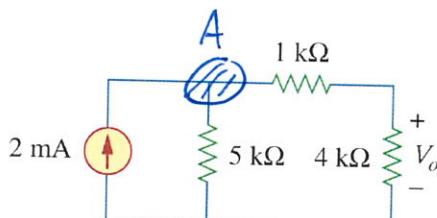- (d) Find the percent error if the internal resistance were  $36\text{k}\Omega$ .




(a)

$$a) R_{eq} = 5\text{k} \parallel (1\text{k} + 4\text{k}) = 2.5\text{k}\Omega$$

$$V_A = 2\text{mA} \cdot 2.5\text{k}\Omega = 5\text{V}$$
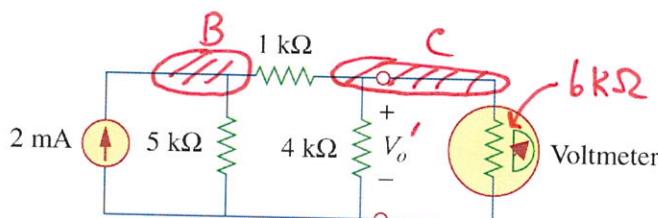
$$V_o = 5\text{V} \left( \frac{4\text{k}\Omega}{1\text{k}\Omega + 4\text{k}\Omega} \right) = 4\text{V}$$



$$(b) R_i = 4\text{k}\Omega \parallel 6\text{k}\Omega = 2.4\text{k}\Omega$$

$$R_s = 1\text{k}\Omega + 2.4\text{k}\Omega = 3.4\text{k}\Omega$$

$$R_{eq} = 5\text{k}\Omega \parallel 3.4\text{k}\Omega = 2.024\text{k}\Omega$$

$$b) V_B = 2\text{mA} \cdot 2.024\text{k}\Omega = 4.05\text{V}$$

$$V_C = V'_o = 4.05\text{V} \left( \frac{2.4\text{k}\Omega}{3.4\text{k}\Omega} \right)$$

$\uparrow$   
(Want)

$$V'_o = 2.86\text{V}$$

$$c) \left| \frac{4\text{V} - 2.86\text{V}}{4\text{V}} \right| \cdot 100\% = 28.5\%$$

$$d) R'_i = 4\text{k}\Omega \parallel 36\text{k}\Omega = 3.6\text{k}\Omega$$

$$R'_s = 4.6\text{k}\Omega \Rightarrow V'_B = 2\text{mA} \cdot 2.4\text{k}\Omega = 4.8\text{V}$$

$$R_{eq} = 2.4\text{k}\Omega$$

$$V'_C = V''_o = 4.8\text{V} \left( \frac{3.6\text{k}\Omega}{4.6\text{k}\Omega} \right) = 3.76\text{V}$$

$$\left| \frac{4\text{V} - 3.76\text{V}}{4\text{V}} \right| \cdot 100\% \approx 6\%$$

Nice Improvement!

**Chapter 2, Problem 74.**

The circuit in Fig. 2.134 is to control the speed of a motor such that the motor draws currents 5 A, 3 A, and 1 A when the switch is at high, medium, and low positions, respectively. The motor can be modeled as a load resistance of  $20 \text{ m}\Omega$ . Determine the series dropping resistances  $R_1$ ,  $R_2$ , and  $R_3$ .

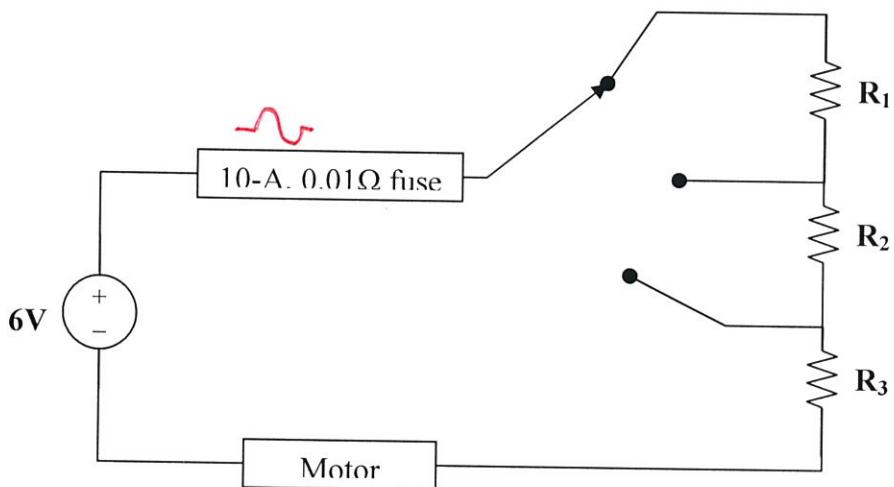


Figure 134

$$\text{High} - 6V = 5A \left( 0.01\Omega + R_3 + 0.02\Omega \right)$$

$$R_3 = 1.17\Omega$$

$$\text{MED.} - 6V = 3A \left( 0.01\Omega + (R_2 + R_3) + 0.02\Omega \right)$$

$$R_2 + R_3 = 1.97\Omega$$

$$R_2 = 0.8\Omega$$

$$\text{Low} - 6V = 1A \left( 0.01\Omega + (R_1 + R_2 + R_3) + 0.02\Omega \right)$$

$$R_1 + R_2 + R_3 = 5.97\Omega$$

$$R_1 = 4\Omega$$

### Chapter 3, Solution 11

Find  $V_o$  and the power absorbed by all the resistors in the circuit of Fig. 3.60.

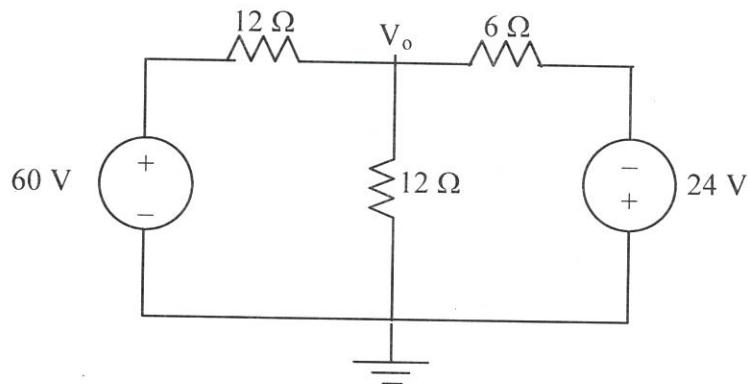


Figure 3.60  
For Prob. 3.11.

#### Solution

$$\text{At the top node, KCL produces } \frac{V_o - 60}{12} + \frac{V_o - 0}{12} + \frac{V_o - (-24)}{6} = 0$$

$$(1/3)V_o = 1 \text{ or } V_o = 3 \text{ V.}$$

$$P_{12\Omega} = (3 - 60)^2 / 12 = 293.9 \text{ W} \quad (\text{this is for the } 12 \Omega \text{ resistor in series with the } 60 \text{ V source})$$

~~293.9 W~~  
~~270.75 W~~

$$P_{12\Omega} = (V_o)^2 / 12 = 9 / 12 = 750 \text{ mW} \quad (\text{this is for the } 12 \Omega \text{ resistor connecting } V_o \text{ to ground})$$

$$P_{4\Omega} = (3 - (-24))^2 / 6 = 121.5 \text{ W.}$$