

EE331 Homework PS4 – fall 2012

Problems from Alexander & Sadiku:

CH5


- 5.8 – Warm up! *Ans:* a) -2V, b) -1V
- 5.13 (Remember your ideal Op Amp assumptions, equations 5.5 and 5.7) – A voltage divider works quite nicely to get this problem rolling.
- 5.21
- 5.27
- 5.37
- 5.47

Additional Problems (Instructor Option):

- Read page 196-197 in your text and solve Practice Problem 5.12 (on page 197)
- Any as assigned by instructor

Figure 5.47

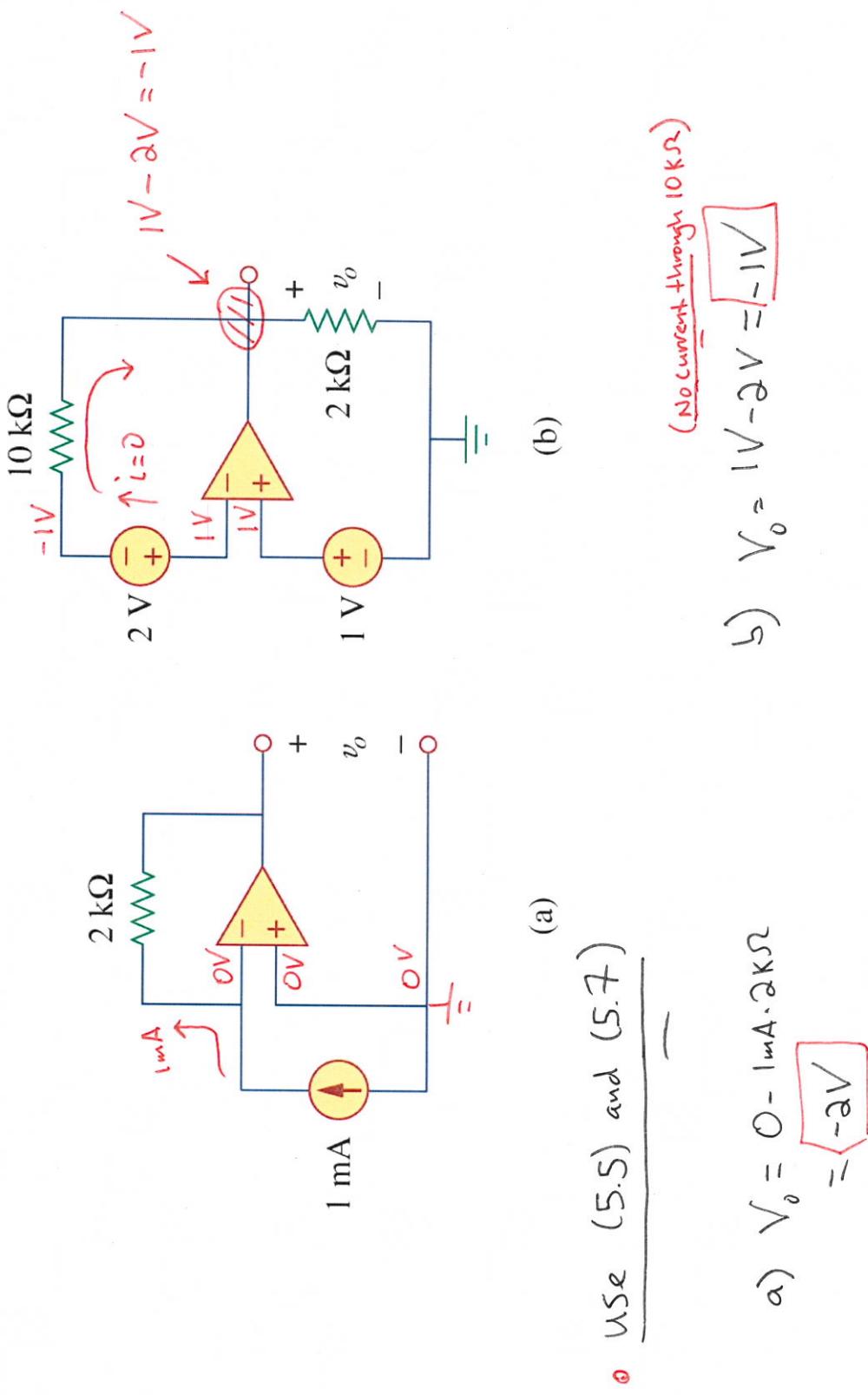Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Chapter 5, Problem 13

Find v_o and i_o in the circuit of Fig. 5.52.

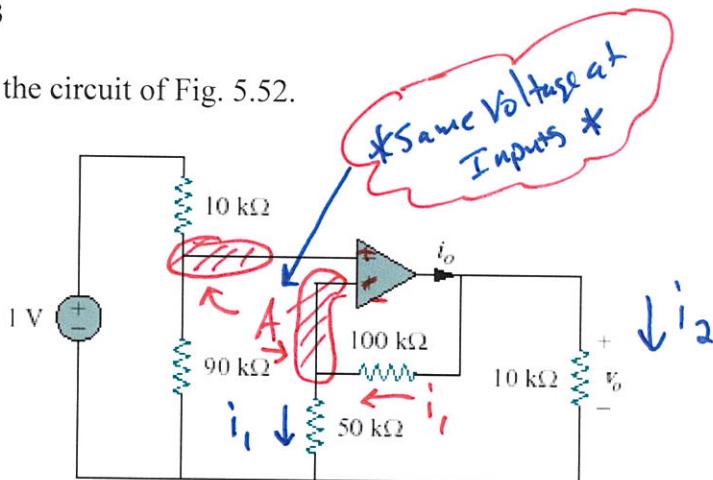


Figure 5.52 for Prob. 5.13

- Use Voltage Divider to find V_A

$$V_A = \frac{1V \cdot 90k\Omega}{(90k\Omega + 10k\Omega)} = 0.9V$$

- Now find i_1

$$i_1 = \frac{V_A}{50k\Omega} = 18mA$$

- $V_o = V_A + i_1 \cdot 100k\Omega = 2.7V$

(KCL) • $i_o = i_1 + i_2 = 18\mu A + \frac{2.7V}{10k\Omega} = 18\mu A + 0.27mA = 288\mu A$

Chapter 5, Problem 21.

Calculate v_o in the op amp circuit of Fig. 5.60.

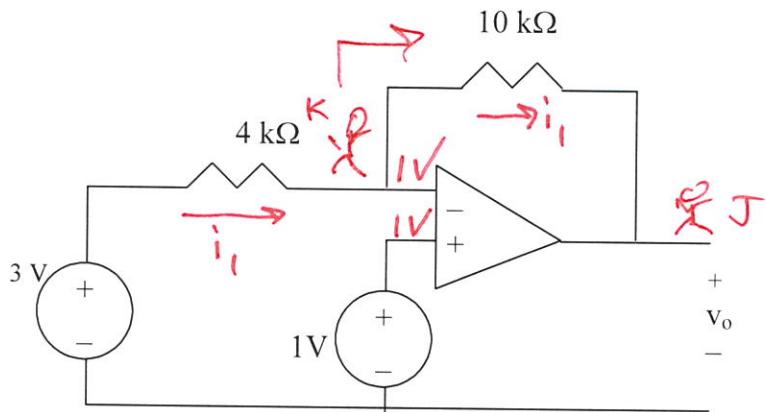


Figure 5.60 For Prob. 5.21.

- $i_1 = \frac{3V - 1V}{4k\Omega} = 0.5 \text{ mA}$

$$v_o = 1V - \underbrace{0.5 \text{ mA} \cdot 10k\Omega}_{I \cdot R} = \boxed{-4V}$$

Chapter 5, Problem 27.

Find v_o in the op amp circuit in Fig. 5.65.

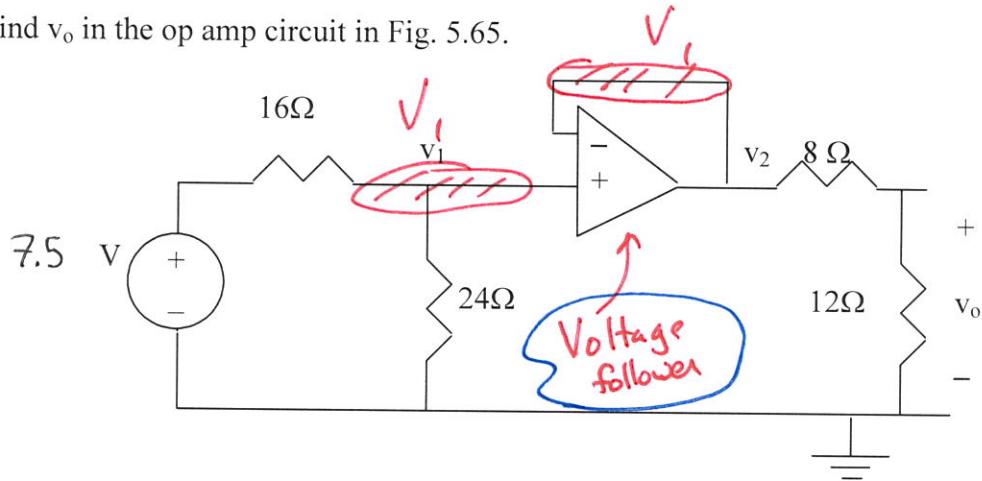


Figure 5.65 For Prob. 5.27.


$$\bullet V_1 = 7.5 \text{ V} \cdot \frac{24\Omega}{(16\Omega + 24\Omega)} = 4.5 \text{ V}$$

$$V_2 = V_1 \approx 4.5 \text{ V}$$

$$V_o = \frac{4.5 \text{ V} \cdot 12\Omega}{(8\Omega + 12\Omega)} = 2.7 \text{ V}$$

Figure 5.74

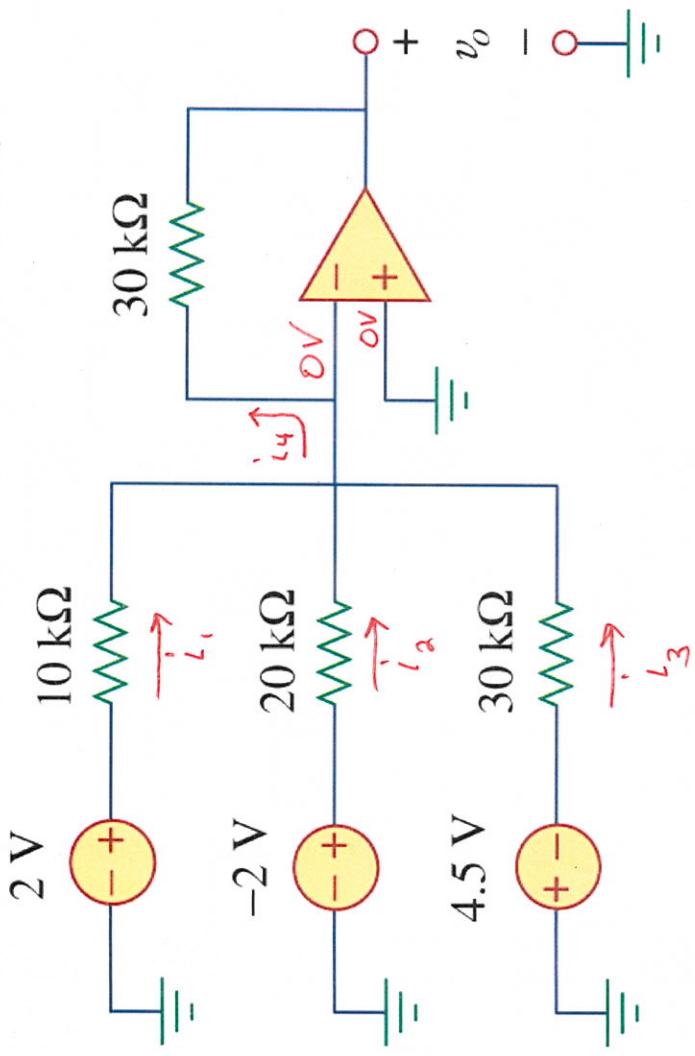Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$\begin{aligned} \bullet i_1 &= \frac{2V}{10k\Omega} = 0.2mA \\ \bullet i_2 &= -\frac{2V}{20k\Omega} = -0.1mA \\ \bullet i_3 &= -\frac{4.5V}{30k\Omega} = -0.15mA \end{aligned}$$

$$\begin{aligned} \Rightarrow i_4 &= -0.05mA \\ \Rightarrow V_o &= 0 + 0.05mA \cdot 30k\Omega = 1.5V \end{aligned}$$

Chapter 5, Problem 47.

The circuit in Fig. 5.79 is for a difference amplifier. Find v_o given that $v_1 = 1V$ and $v_2 = 2V$.

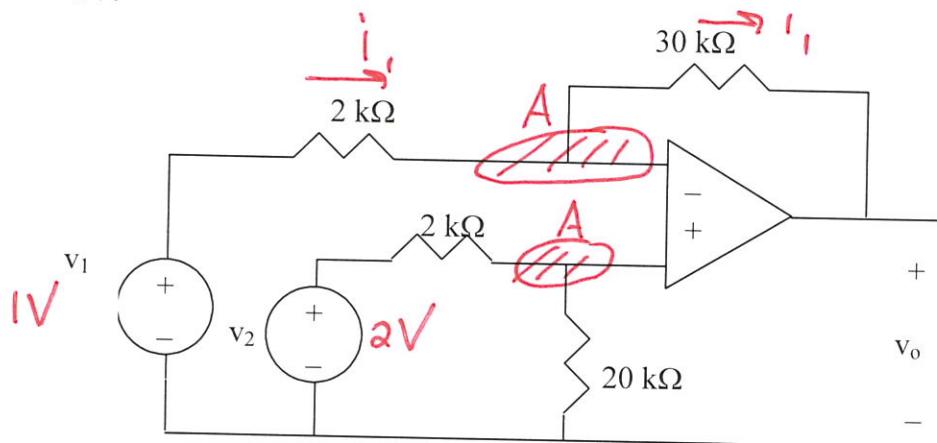


Figure 5.79 For Prob. 5.47.

$$\circ V_A = \frac{2V \cdot 20k\Omega}{(2k\Omega + 20k\Omega)} = 1.82V$$

$$\circ i_i = \frac{1V - 1.82V}{2k\Omega} = -410\mu A$$

$$\circ V_o = 1.82V + 410\mu A \cdot 30k\Omega = \boxed{14.1V}$$

(W_C = "current")

Digital to ANALOG Converter (Binary Weighted LADDER)

A three-bit DAC is shown in Fig. 5.37.

- Determine $|V_o|$ for $[V_1 V_2 V_3] = [010]$.
- Find $|V_o|$ if $[V_1 V_2 V_3] = [110]$.
- If $|V_o| = 1.25 \text{ V}$ is desired, what should be $[V_1 V_2 V_3]$?
- To get $|V_o| = 1.75 \text{ V}$, what should be $[V_1 V_2 V_3]$?

Answer: 0.5 V, 1.5 V, [101], [111].

Practice Problem 5.12

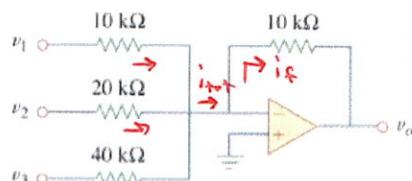


Figure 5.37

Three-bit DAC; for Practice Prob. 5.12.

$$(5.23) -V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 = R_f \left(\underbrace{\frac{V_1 - 0}{R_1}}_{10\text{k}\Omega} + \underbrace{\frac{V_2 - 0}{R_2}}_{20\text{k}\Omega} + \underbrace{\frac{V_3 - 0}{R_3}}_{40\text{k}\Omega} \right)$$

$$a) |V_o| = 0 + \frac{10\text{k}\Omega}{20\text{k}\Omega} \cdot 1\text{V} + 0 = 0.5\text{V}$$


$$b) |V_o| = \frac{10\text{k}\Omega}{10\text{k}\Omega} \cdot 1 + \frac{10\text{k}\Omega}{20\text{k}\Omega} \cdot 1\text{V} + 0 = 1.5\text{V}$$

$$c) 101 \rightarrow |V_o| = \frac{10\text{k}}{10\text{k}} \cdot 1 + 0 + \frac{10\text{k}}{40\text{k}} \cdot 1 = 1.25\text{V}$$

$$d) 111 \rightarrow |V_o| = \frac{10\text{k}}{10\text{k}} \cdot 1 + \frac{10\text{k}}{20\text{k}} \cdot 1 + \frac{10\text{k}}{40\text{k}} \cdot 1 = 1.75\text{V}$$


<u>Note</u>	<u>Output (V_o) V</u>
000	0
001	0.25
010	0.5
011	0.75
100	1.00
101	1.25
110	1.5
111	1.75

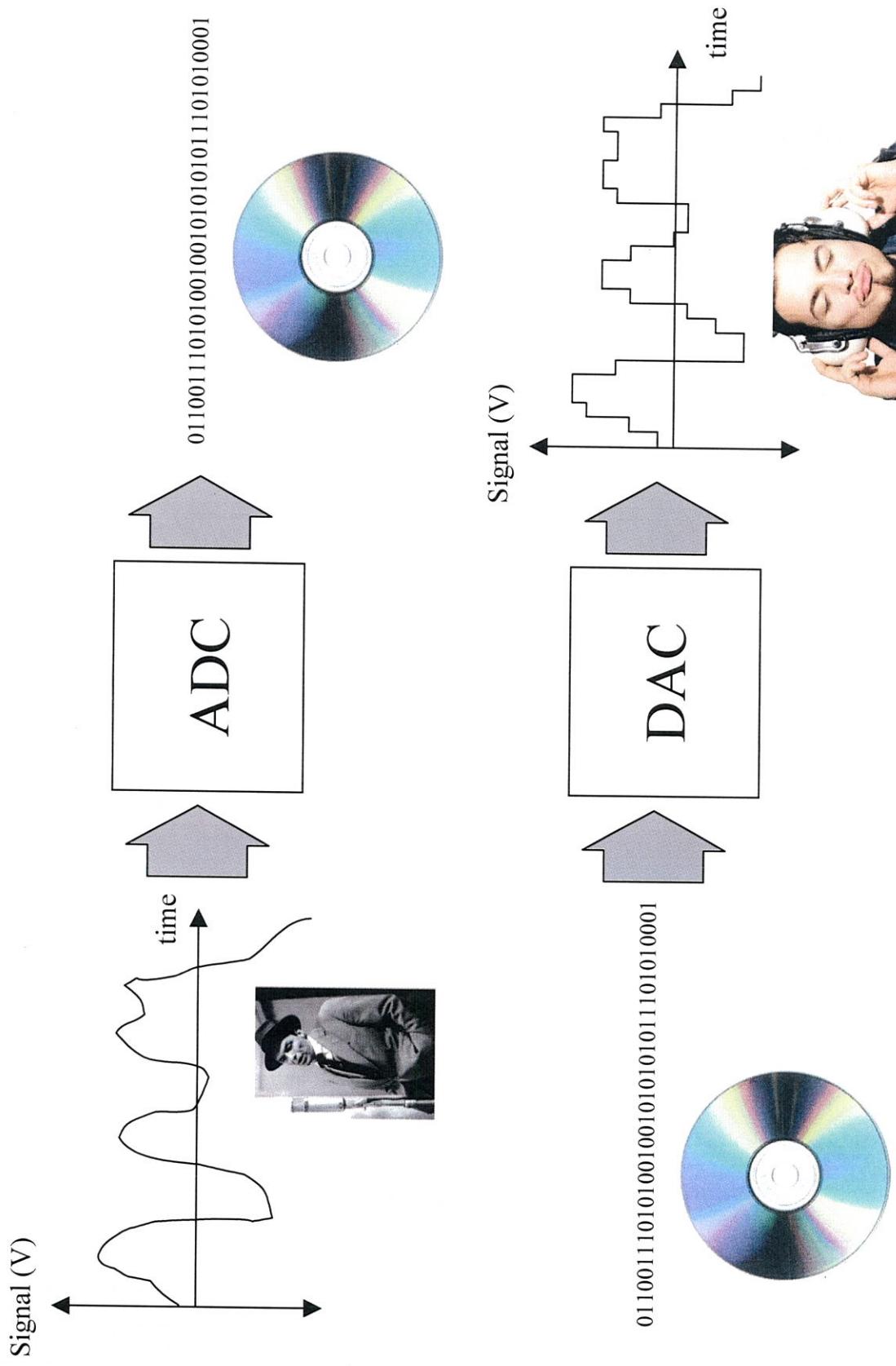* Summary / High Level
Look at Analog-to-Digital
and Digital-to-Analog (Next
3 Slides)



Analog to Digital (ADC)


Hambley pg. 316

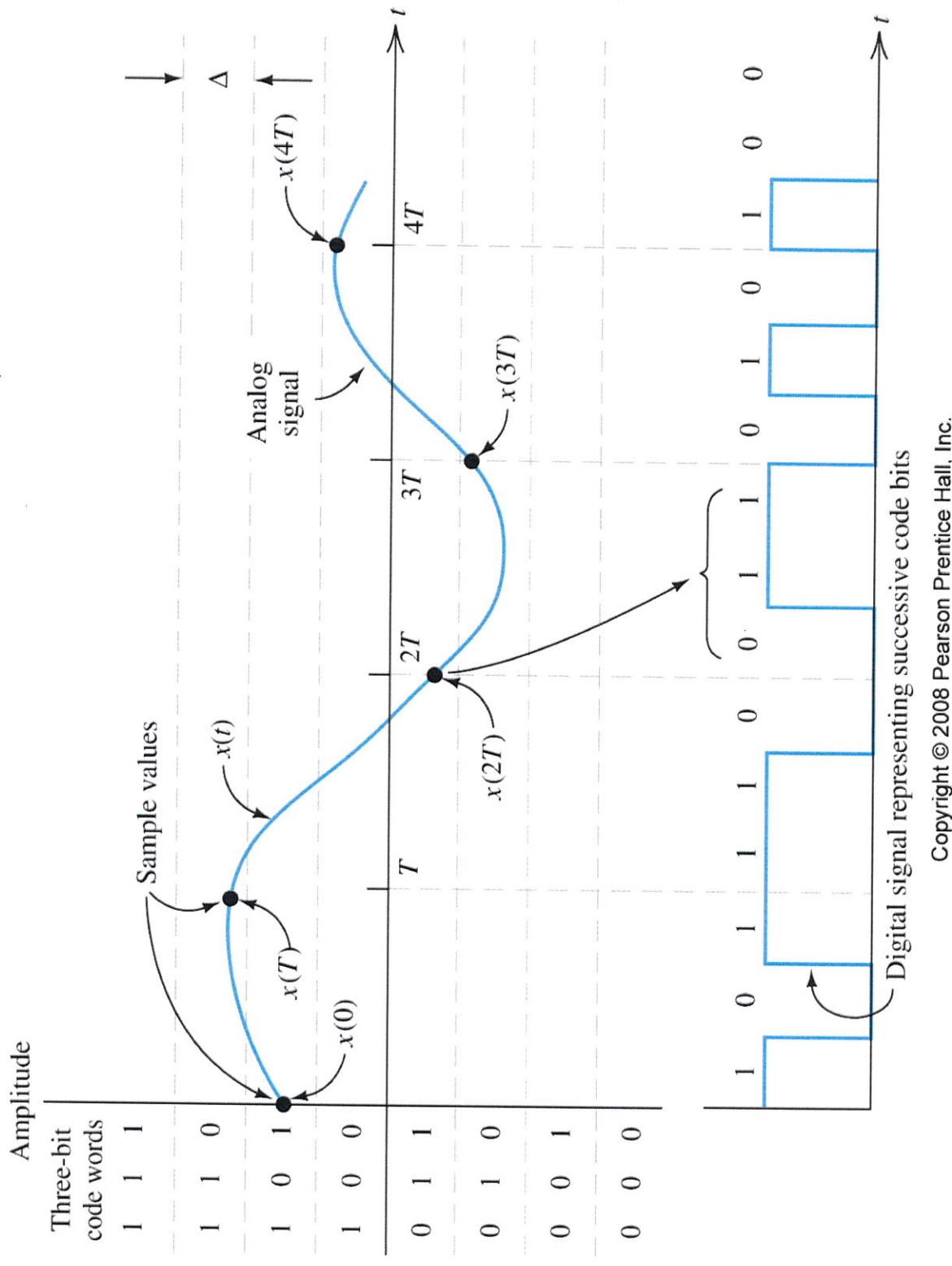

Copyright © 2008 Pearson Prentice Hall, Inc.

Digital to Analog (DAC)

Hambley pg. 316

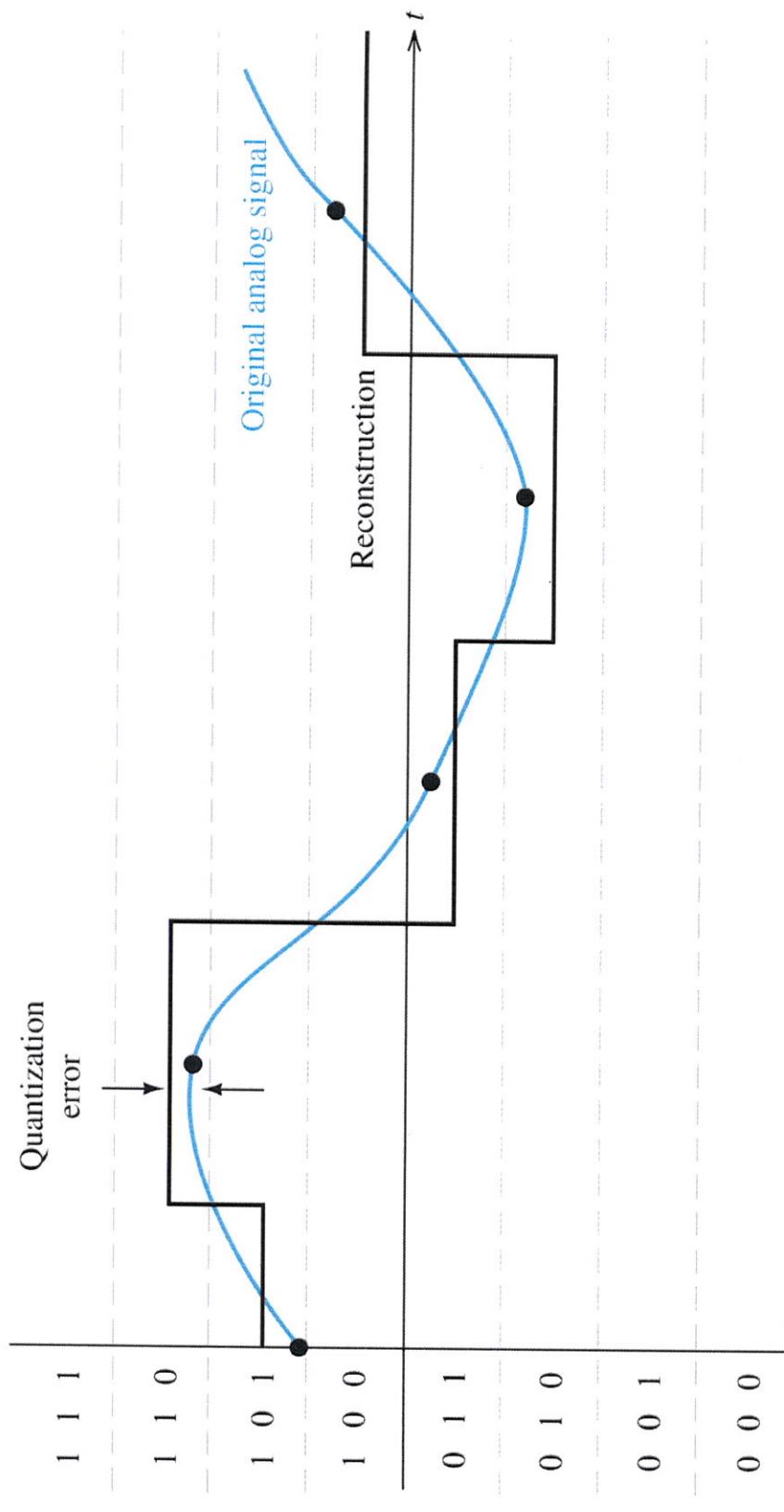

Copyright © 2008 Pearson Prentice Hall, Inc.