

EE331 Homework PS6 – fall 2012

Problems from Alexander & Sadiku:

CH6

- 6.13
- 6.20 (Ans: 1.333 microF)
- 6.46 ($i_L = 2A$, $W_L = 1J$, $W_C=0J$)

CH 7

- 7.40 (Just part a) – Also, graph the result – (Ans: 12V and $(4 + 8e^{-t/6}) V$)
- 7.56 – (hint: first find $i(t)$ through the inductor, then use the relationship from Chapter 6, equation 6.18 for inductors) – Ans: $v(t) = -4e^{-20t} V$

Additional Problems (Instructor Option):

- 6.74 (hint: read section 6.6.2 on pgs. 235-236) – What type of operation is accomplished?
- Any as assigned by instructor

Chapter 6, Problem 13.

Find the voltage across the capacitors in the circuit of Fig. 6.49 under dc conditions.


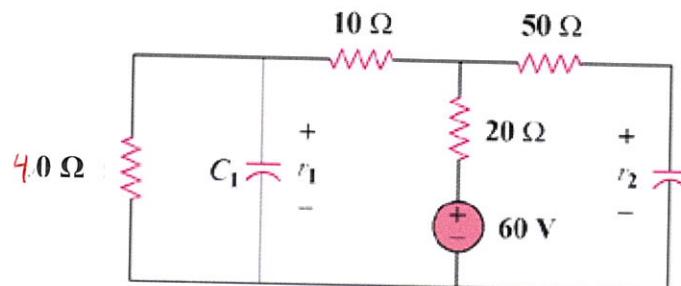


Figure 6.49

- Capacitors Look open to DC

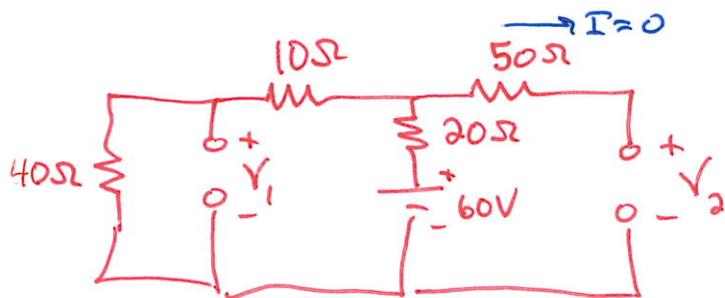

- Use Voltage Divider

$$V_1 = \frac{60V \cdot 40\Omega}{20\Omega + 10\Omega + 40\Omega} = 34.3V$$

$$V_2 = \frac{60V \cdot 50\Omega}{20\Omega + 10\Omega + 40\Omega} = 42.9V$$

Chapter 6, Problem 20.

Find the equivalent capacitance at terminals a-b of the circuit in Fig. 6.54.

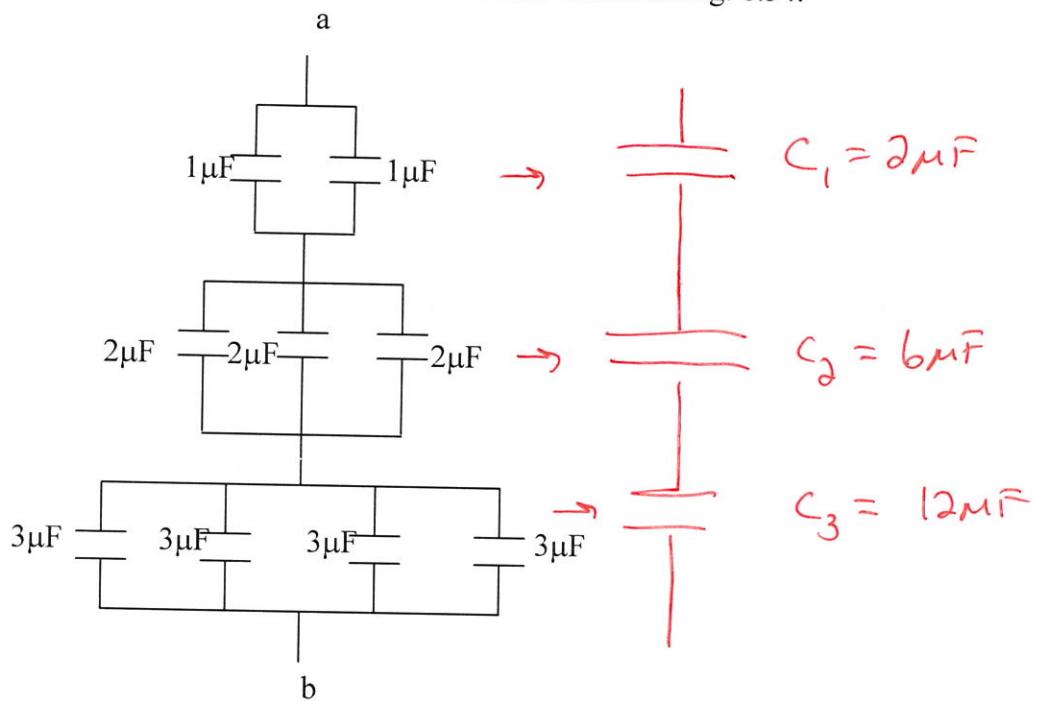


Figure 6.54 For Prob. 6.20.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \boxed{1.333 \mu F}$$

Chapter 6, Problem 46.

Find v_C , i_L , and the energy stored in the capacitor and inductor in the circuit of Fig. 6.69 under dc, steady-state, conditions.


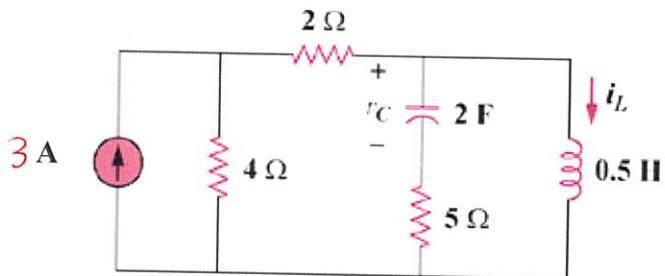


Figure 6.69

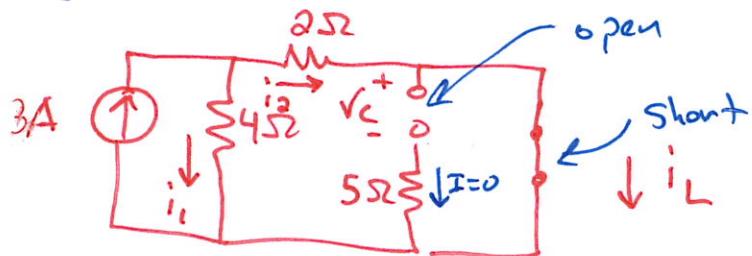* { Capacitor Looks like open
Inductor Looks like short



Current +
Divider $\Rightarrow i_1 = \frac{3A \cdot 2\Omega}{2\Omega + 4\Omega} = 1A$
(or could solve
Convert)

$$i_2 = i_L = 3A - 1A = 2A$$

or could get
w/current Divider
straight away.

- $W_L = \frac{1}{2} L i^2 = \frac{1}{2} \cdot (0.5H) \cdot (2A)^2 = \boxed{1J}$

- $W_C = \frac{1}{2} C V^2 = \frac{1}{2} \cdot (2F) \cdot (0V)^2 = \boxed{0J}$

No Voltage
Across as inductor
Shorted

Chapter 7, Problem 40.

Find the capacitor voltage for $t < 0$ and $t > 0$ for each of the circuits in Fig. 7.107.

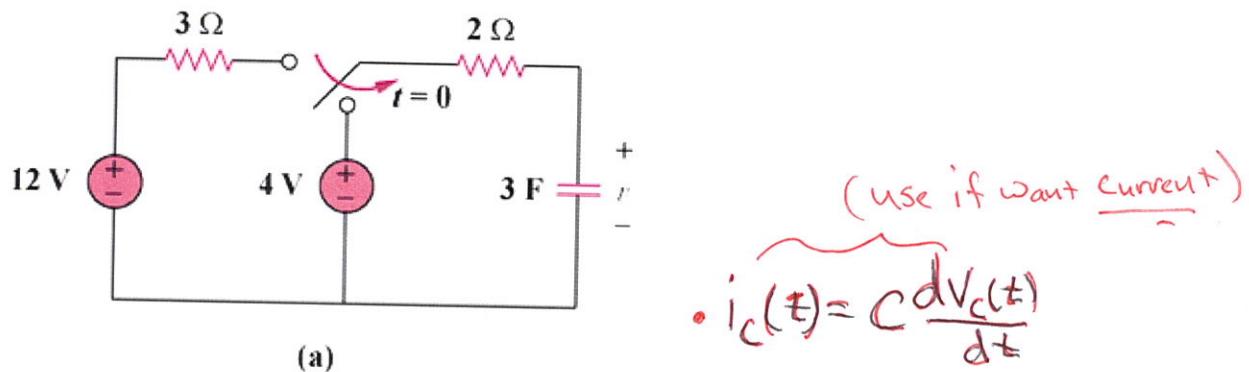


Figure 7.107


$$\underline{\text{Step 1}} \rightarrow V_C(t) = V_C(\infty) + [V_C(0) - V(\infty)] e^{-\frac{t}{\tau}}$$

$$\underline{\text{Step 2} \rightarrow 4} \Rightarrow V_C(\infty) = 4V$$

$$V_C(0^-) = V_C(0^+) \quad V_C(0) = 12V$$

$$\tau = R_{TH}C = (2\Omega) \cdot (3F) = 6 \text{ sec}$$
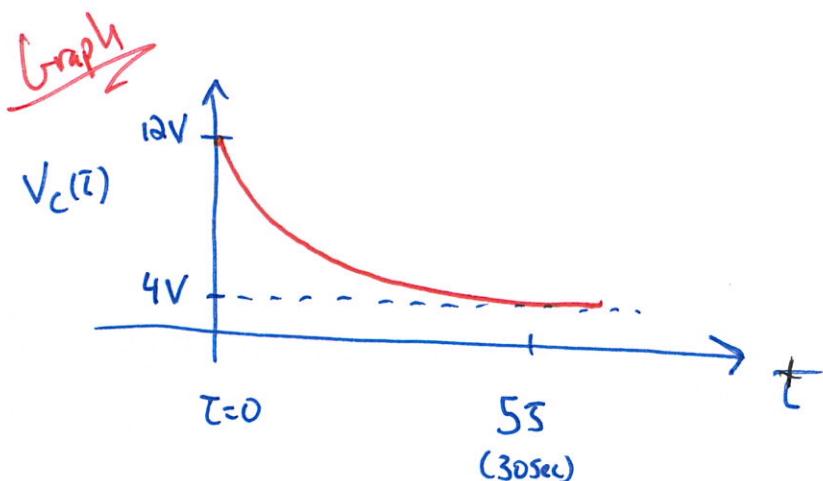
$$\underline{\text{Step 5}} \Rightarrow V_C(t) = \begin{cases} 4V + (8V)e^{-\frac{t}{6}} & \text{for } t > 0 \\ 12V & \text{for } t < 0 \end{cases}$$



Chapter 7, Problem 56.

For the network shown in Fig. 7.122, find $v(t)$ for $t > 0$.


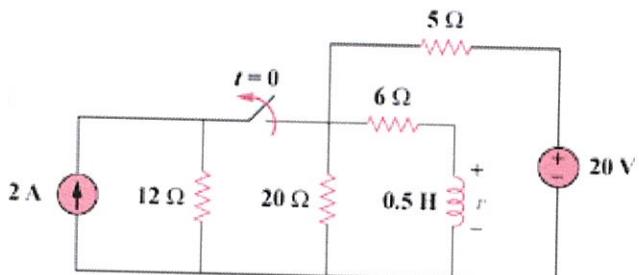


Figure 7.122 final initial

$$\text{Step 1} \rightarrow i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-\frac{t}{\tau}}$$

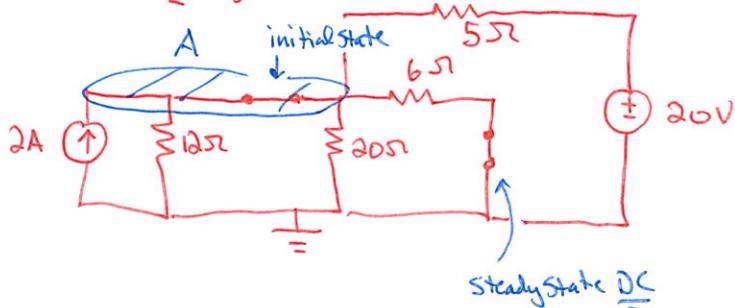
$$\text{Steps 2 to 4} \rightarrow i_L(0) \rightarrow \text{use Nodal}$$



$$-2A + \frac{V_A - 0}{12\Omega} + \frac{V_A - 0}{20\Omega} + \frac{V_A - 0}{6\Omega} + \frac{V_A - 20V}{5\Omega} = 0 \rightarrow V_A = 12V$$

$$\Rightarrow i_L(0) = \frac{V_A}{6} = 2A$$

$$i_L(\infty) \rightarrow$$

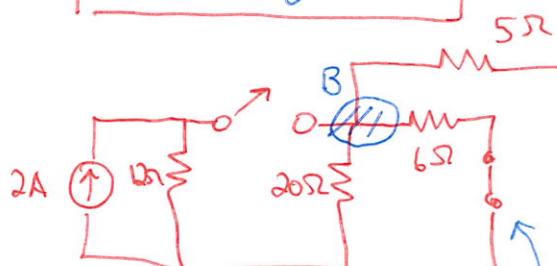

$$V_B = \frac{20V \cdot (20/6)}{(20/6) + 5} = 9.6V$$

$$i_L(\infty) = \frac{V_B}{6\Omega} = 1.6A$$

$$\rightarrow R_{eq} = 6 + 20/5 = 10\Omega$$

$$\zeta = \frac{L}{R_{TH}} = \frac{0.5H}{10\Omega} = 0.05$$

$$\text{Step 5} \rightarrow i_L(t) = 1.6 + (2 - 1.6) e^{-\frac{t}{0.05}} = 1.6 + 0.4 e^{-20t} A$$

$$= R_{TH}$$

$$\text{Final Answer} \rightarrow v(t) = L \frac{di}{dt} = \frac{1}{2} (0.4)(-20) e^{-20t} = -4 e^{-20t} V$$


Chapter 6, Solution 74.

$$RC = 0.01 \times 20 \times 10^{-3} \text{ sec}$$

$$v_o = -RC \frac{dv_i}{dt} = -0.2 \frac{dv}{dt} \text{ m sec}$$

$$v_o = \begin{cases} -2V, & 0 < t < 1 \\ 2V, & 1 < t < 3 \\ -2V, & 3 < t < 4 \end{cases}$$

Thus $v_o(t)$ is as sketched below:

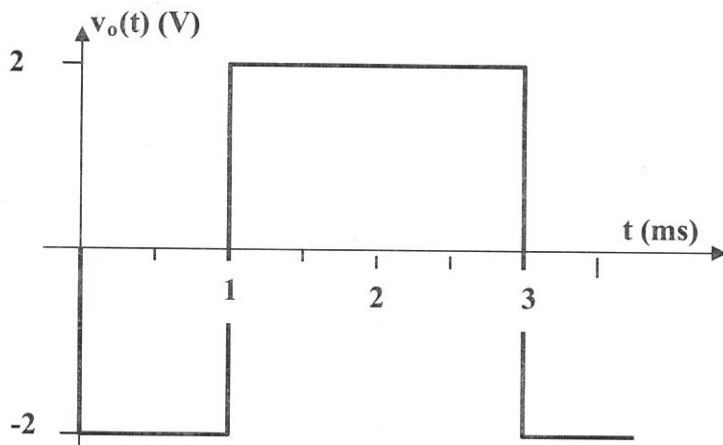

Differentiator