

Key
2

EE331 Homework PS7 – fall 2012

Problems from Alexander & Sadiku:

CH 9

- 9.1
- 9.3
- 9.8
- 9.30 (Ans: $2.5 \cdot \cos(60t+20)$ mA and $300 \cdot \cos(60t+110)$ mA)
- 9.35
- 9.44 (Ans: $960 \cdot \cos(200t - 7.96)$ mA)

CH 10

- 10.13 (Remember to use CSOLVE in calculator)


Other Problems:

- Pg. 2 and 3 of this Problem Set

Additional Problems (Instructor Option):

- Any as assigned by instructor

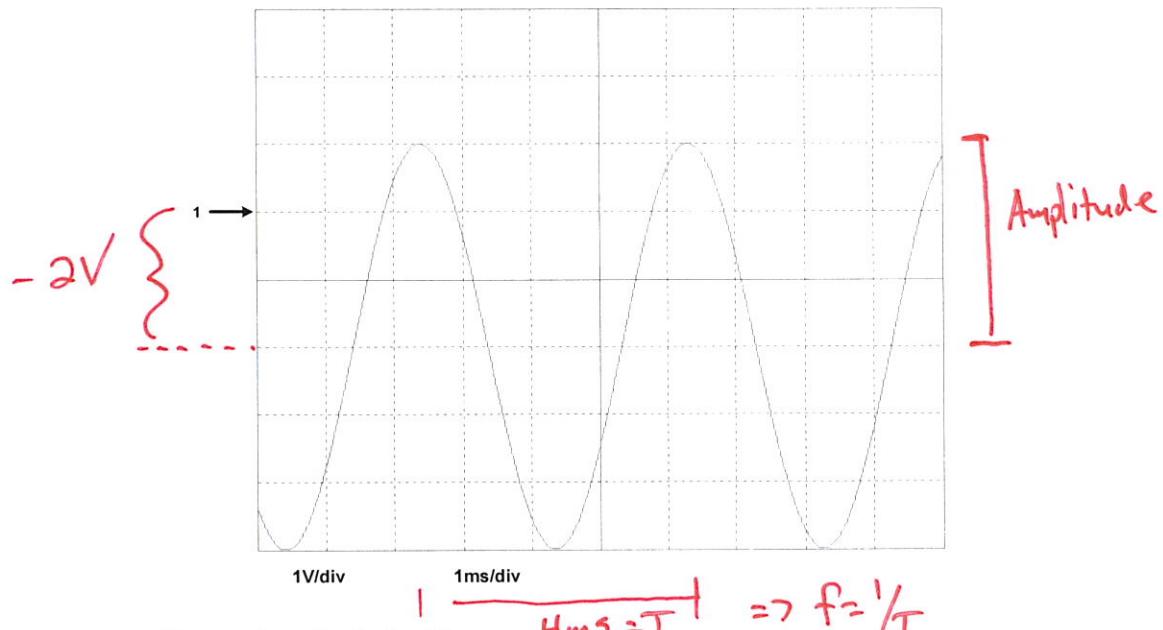Given the following scope image where the arrow indicates the ground level for CH1,




- Determine the DC offset
- Determine the frequency in Hz
- What is the RMS value of the sinusoidal part of the signal

a) $\boxed{-2V \text{ DC}}$

b) $4\text{ms} = T \Rightarrow \boxed{f = 1/T = 250 \text{ Hz}}$

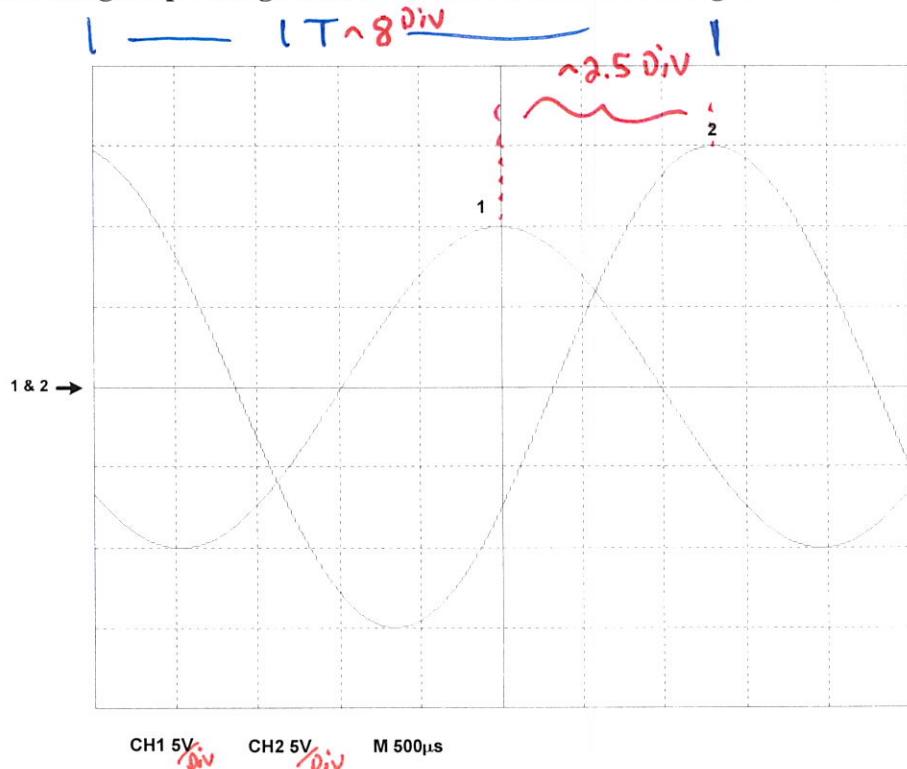c) $3V/\sqrt{2} = \boxed{2.12V}$

Given the following scope image where the arrow indicates the ground level for CH1 & CH2,



- a. Which signal leads which and by how many degrees?
- b. What is the RMS value of the signal on CH2?

a) 1 leads 2 $\Rightarrow 2.5 \text{ Div} \cdot \left(\frac{500 \mu s}{1 \text{ Div}} \right) = \boxed{1250 \mu s}$

$$\Rightarrow 1T = 8 \text{ Div} = 360^\circ$$

$$2.5 \text{ Div} / 8 \text{ Div} = \frac{x}{360^\circ} \Rightarrow \text{CH1 leads by } x \approx 112^\circ$$

b) $V_{rms} = \sqrt{\frac{1}{2}} = \boxed{10.6 V}$

Chapter 9, Problem 1.

Given the sinusoidal voltage $v(t) = 50 \cos(30t + 10^\circ)$ V, find: (a) the amplitude V_m , (b) the period T , (c) the frequency f , and (d) $v(t)$ at $t=10$ ms.

a) $V_m = 50$ V

b) $\omega = 2\pi f = 2\pi/T \Rightarrow T = \frac{2\pi}{\omega} = \frac{2\pi}{30} = 0.209$ sec

c) $f = \frac{30}{2\pi} = 4.77$ Hz

d) $V(10\text{ms}) = 50 \cdot \cos\left(30 \cdot \frac{\text{rad}}{5\text{sec}} \cdot 10\text{ms} \cdot \frac{360^\circ}{2\pi\text{rad}} + 10^\circ\right)$ V
= 44.5 ✓

Chapter 9, Solution 3.

(a) $10 \sin(\omega t + 30^\circ) = 10 \cos(\omega t + 30^\circ - 90^\circ) = 10\cos(\omega t - 60^\circ)$

(b) $-9 \sin(8t) = 9\cos(8t + 90^\circ)$

(c) $-20 \sin(\omega t + 45^\circ) = 20 \cos(\omega t + 45^\circ + 90^\circ) = 20\cos(\omega t + 135^\circ)$

(a) $10\cos(\omega t - 60^\circ)$, (b) $9\cos(8t + 90^\circ)$, (c) $20\cos(\omega t + 135^\circ)$

Chapter 9, Solution 8.


$$(a) \frac{60\angle 45^\circ}{7.5 - j10} + j2 = \frac{60\angle 45^\circ}{12.5\angle -53.13^\circ} + j2 \\ = 4.8\angle 98.13^\circ + j2 = -0.6788 + j4.752 + j2 \\ = \mathbf{-0.6788 + j6.752}$$

$$(b) (6-j8)(4+j2) = 24-j32+j12+16 = 40-j20 = 44.72\angle -26.57^\circ$$
$$\frac{32\angle -20^\circ}{(6-j8)(4+j2)} + \frac{20}{-10+j24} = \frac{32\angle -20^\circ}{44.72\angle -26.57^\circ} + \frac{20}{26\angle 112.62^\circ}$$
$$= 0.7156\angle 6.57^\circ + 0.7692\angle -112.62^\circ = 0.7109 + j0.08188 - 0.2958 - j0.71$$
$$= \mathbf{0.4151 - j0.6281}$$

$$(c) 20 + (16\angle -50^\circ)(13\angle 67.38^\circ) = 20 + 208\angle 17.38^\circ = 20 + 198.5 + j62.13$$
$$= \mathbf{218.5 + j62.13}$$

Chapter 9, Problem 30.

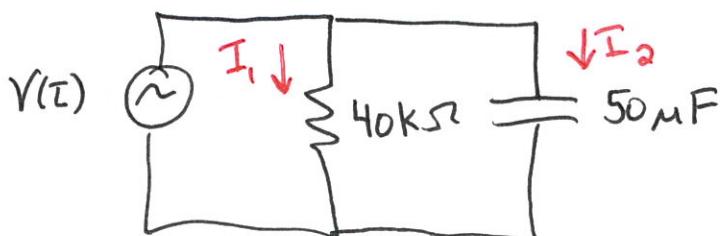If a voltage $v(t) = 100 \cos(60t + 20^\circ)$ V is applied to a parallel combination of a $40\text{-k}\Omega$ resistor and a $50\text{-}\mu\text{F}$ capacitor. Find the steady-state currents through the resistor and capacitor.



General Steps

- 1) Convert everything to phasors
- 2) Solve
- 3) Convert back to Time Domain

$$\bullet I_1 = \frac{\tilde{V}}{R} = \frac{100 < 20^\circ \text{ V}}{40\text{k}\Omega}$$

$$= 2.5\text{mA} < 20^\circ$$

$$\rightarrow \boxed{i_1(t) = 2.5\text{mA} \cos(60t + 20^\circ)}$$

$$\bullet I_2 = \frac{100 < 20^\circ \text{ V}}{333.3 < -90^\circ \Omega} \quad z_c = \frac{1}{\omega C j} = \frac{1}{60 \cdot 50\mu\text{F}} < -90^\circ = 333.3 < -90^\circ \Omega$$

$$= 300\text{mA} < 110^\circ$$

$$\rightarrow \boxed{i_2(t) = 300\text{mA} \cos(60t + 110^\circ)}$$

or if stay in time domain

$$\begin{aligned} \rightarrow i_2(t) &= C \frac{dV}{dt} = -50\mu\text{F} \cdot 100 \cdot 60 \cdot \sin(60t + 20^\circ) \\ &= -300\text{mA} \sin(60t + 20^\circ) \\ &= \boxed{300\text{mA} \cos(60t + 110^\circ)} \end{aligned}$$

Chapter 9, Problem 35.

Find current i in the circuit of Fig. 9.42, when $v_s(t) = 50 \cos 200t$ V.

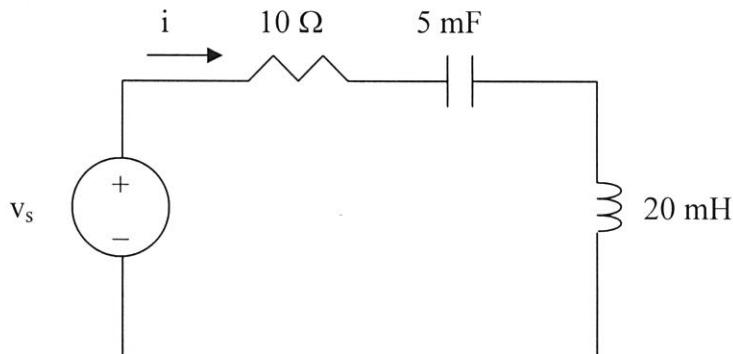



Figure 9.42 For Prob. 9.35.

Convert to phasor

$$\bullet Z_R = 10\Omega \angle 0^\circ, Z_C = \frac{1}{\omega C} \angle -90^\circ, Z_L = \omega L \angle 90^\circ \\ = 10\Omega \angle 0^\circ \qquad \qquad \qquad = 4\Omega \angle 90^\circ$$

Solve

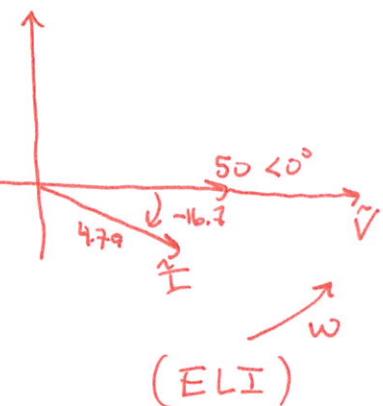
$$\bullet Z_{\text{Total}} = Z_R + Z_C + Z_L \\ = 10\Omega - 1\Omega j + 4\Omega j \\ = 10\Omega + 3\Omega j \\ = 10.44 \angle 16.7^\circ \Omega \leftarrow \text{(Overall Inductive!)} \quad \begin{array}{l} R \\ \downarrow M-m \\ (10+3j)\Omega \\ \uparrow L \end{array}$$



$$\bullet I = \frac{V_s}{Z_{\text{TOT}}} = \frac{50\sqrt{0^\circ}}{10.44 \angle 16.7^\circ \Omega} = 4.79 \angle -16.7^\circ A$$

$$\rightarrow i(I) = 4.79 \cos(200t - 16.7^\circ) A$$


Convert to time domain

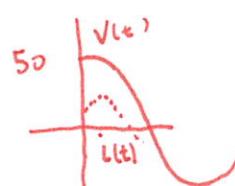

↳ shifted to Right, ∴ Voltage leads current (ELI)

Figure 9.51

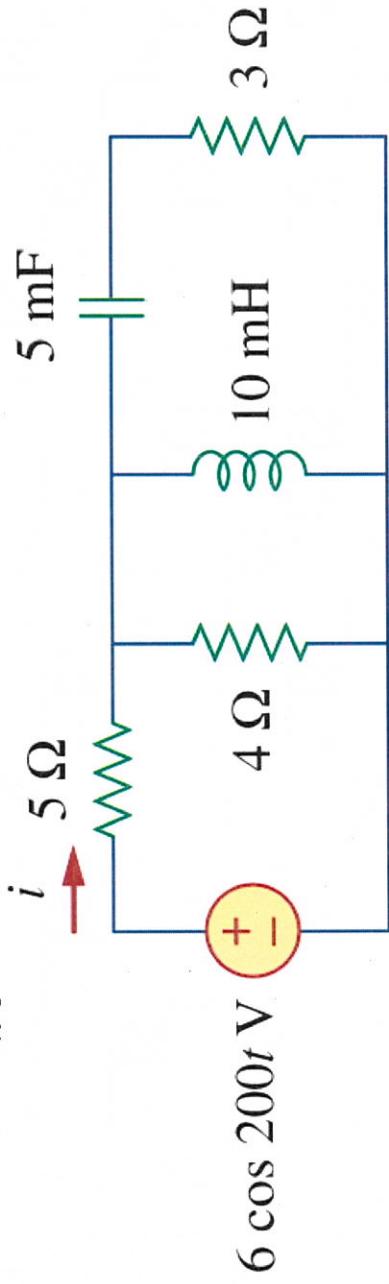Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Chapter 9, Solution 44.

$$\omega = 200$$

$$\begin{aligned}
 10 \text{ mH} &\longrightarrow j\omega L = j(200)(10 \times 10^{-3}) = j2 \\
 5 \text{ mF} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(200)(5 \times 10^{-3})} = -j \\
 Y &= \frac{1}{4} + \frac{1}{j2} + \frac{1}{3-j} = 0.25 - j0.5 + \frac{3+j}{10} = 0.55 - j0.4 \\
 Z &= \frac{1}{Y} = \frac{1}{0.55 - j0.4} = 1.1892 + j0.865 \\
 I &= \frac{6 \angle 0^\circ}{5 + Z} = \frac{6 \angle 0^\circ}{6.1892 + j0.865} = 0.96 \angle -7.956^\circ
 \end{aligned}$$

Thus,

$$i(t) = 960 \cos(200t - 7.956^\circ) \text{ mA}$$

Chapter 10, Problem 13.

Determine V_x (see Fig. 10.62), using any method of your choice.

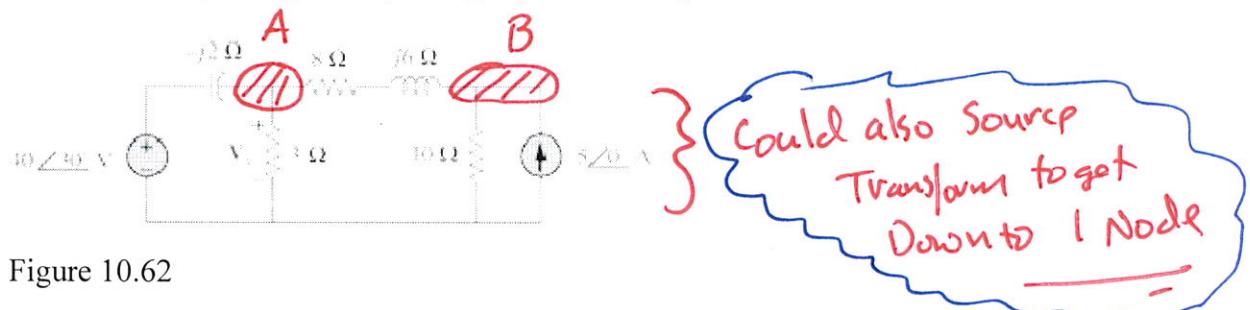


Figure 10.62

$$A: \frac{\tilde{V}_A - 40\angle 30^\circ}{-j2} + \frac{\tilde{V}_A - 0}{3\angle 0^\circ} + \frac{\tilde{V}_A - \tilde{V}_B}{8+6j} = 0$$

$$B: \frac{\tilde{V}_B - \tilde{V}_A}{8+6j} + \frac{\tilde{V}_B - 0}{10\angle 0^\circ} + (-5\angle 0^\circ) = 0$$


Solve $\Rightarrow \left\{ \begin{array}{l} \tilde{V}_A = \tilde{V}_x = 29.4\angle 62.9^\circ V \\ \tilde{V}_B = 40.8\angle 28^\circ V \end{array} \right.$

$$\tilde{V}_B = 40.8\angle 28^\circ V$$

OR

Chapter 10, Solution 13.

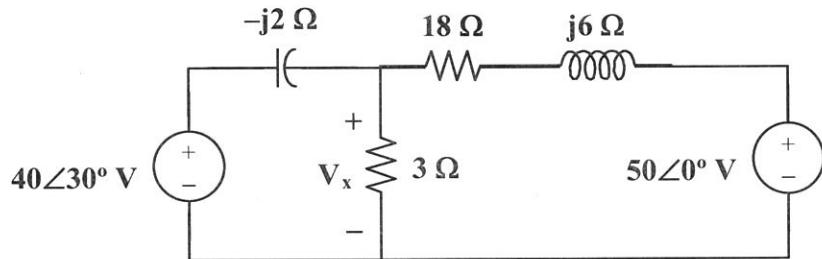Nodal analysis is the best approach to use on this problem. We can make our work easier by doing a source transformation on the right hand side of the circuit.



$$\frac{V_x - 40\angle 30^\circ}{-j2} + \frac{V_x}{3} + \frac{V_x - 50}{18 + j6} = 0$$

which leads to $V_x = 29.36\angle 62.88^\circ \text{ A}$.