

Name: \_\_\_\_\_  
Section: \_\_\_\_\_

Key

## EE331 Homework PS8 – fall 2012

**Problems from Alexander & Sadiku:**

**CH 10**

- 10.55 (*Just find the Thevenin for parts a and b*)

**CH 11**


- 11.2 (Ans:  $P_{avg}$  5 Ohm = 2.647 W, 0 W for inductor and capacitor, why?)
- 11.3
- 11.6 (Ans: 276.8 W)
- 11.9

**Additional Problems (Instructor Option):**


- Any as assigned by instructor

Chapter 10, Problem 55.

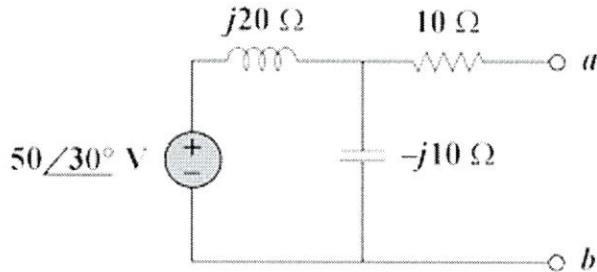Find the Thevenin and Norton equivalent circuits at terminals  $a-b$  for each of the circuits in Fig. 10.98.




(a)

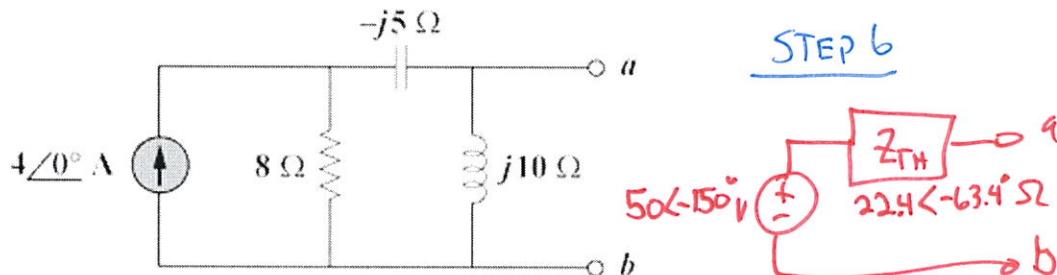

(b)

Figure 10.98

a) Steps 1 → 3

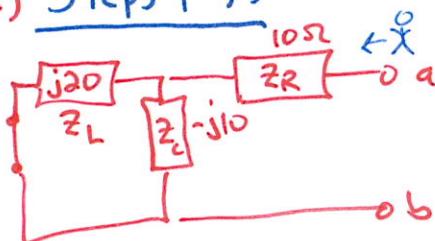


Step 4

$$\begin{aligned} Z_{TH} &= Z_R + Z_L \parallel Z_C \\ &= (10\Omega + j0) + \frac{(0+j20)(0-j10)}{(0+j20)+(0-j10)} \\ &= 10\Omega + (-j20) \end{aligned}$$


$$\boxed{Z_{TH} = 22.4 \angle -63.4^\circ \Omega}$$

Step 5

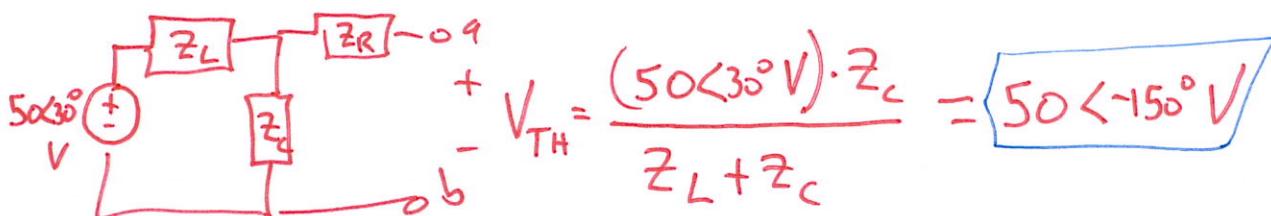

10-55 b

STEPS 1-3

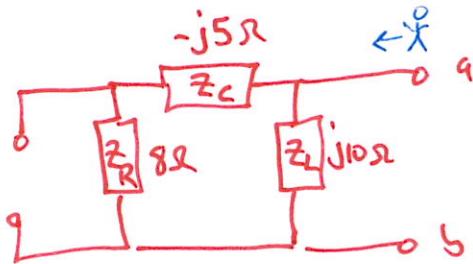


STEP 4

$$Z_{TH} = \frac{(Z_C + Z_R) // Z_L}{8\Omega - j5 + j10}$$

$$= \frac{(8-j5)\Omega \cdot (0+j10)\Omega}{8\Omega - j5 + j10}$$

$$Z_{TH} = 10 < 26^\circ \Omega$$

STEP 5

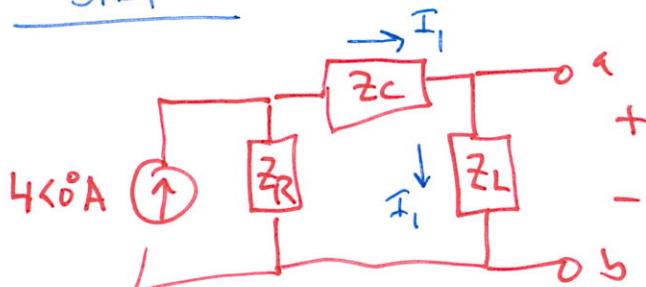

$$V_{TH} = I_1 \cdot Z_L$$

$$= 3.4 < -32^\circ \text{ A} \cdot (j10)$$

$$V_{TH} = 33.9 < 58^\circ \text{ V}$$

By Current Division

$$I_1 = \frac{4 < 0^\circ \text{ A} \cdot Z_R}{Z_R + Z_C + Z_L}$$

$$= \frac{4 < 0^\circ \text{ A} \cdot (8 + 0j)\Omega}{8\Omega - j5 + j10}$$


$$= 3.4 < -32^\circ \text{ A}$$

STEP 6



## Chapter 11, Solution 2.

Using current division,

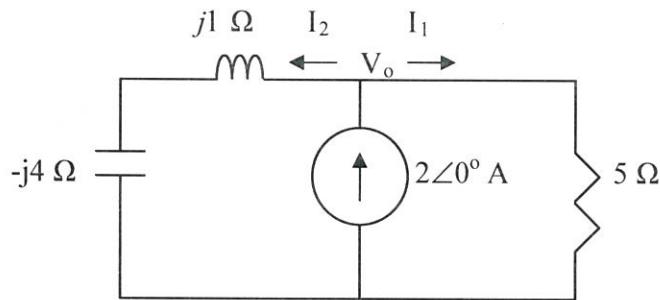

$$I_1 = \frac{j1 - j4}{5 + j1 - j4} (2) = \frac{-j6}{5 - j3}$$

$$I_2 = \frac{5}{5 + j1 - j4} (2) = \frac{10}{5 - j3}$$

For the inductor and capacitor, the average power is zero. For the resistor,


$$P = \frac{1}{2} |I_1|^2 R = \frac{1}{2} (1.029)^2 (5) = 2.647 \text{ W}$$

$$V_o = 5I_1 = -2.6471 - j4.4118$$

$$S = \frac{1}{2} V_o I^* = \frac{1}{2} (-2.6471 - j4.4118) x 2 = -2.6471 - j4.4118$$

Hence the average power supplied by the current source is **2.647 W**.

**Chapter 11, Solution 3.**

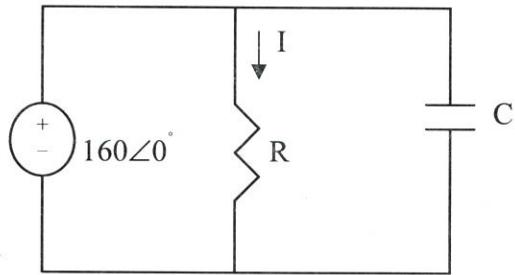

$$90 \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j90 \times 10^{-6} \times 2 \times 10^3} = -j5.5556$$

$$I = 160/60 = 2.667\text{A}$$

The average power delivered to the load is the same as the average power absorbed by the resistor which is


$$P_{\text{avg}} = 0.5|I|^2 60 = \mathbf{213.4 \text{ W.}}$$

### Chapter 11, Solution 6.

$$20 \text{ mH} \longrightarrow j\omega L = j10^3 \times 20 \times 10^{-3} = j20$$

$$40 \mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j10^3 \times 40 \times 10^{-6}} = -j25$$

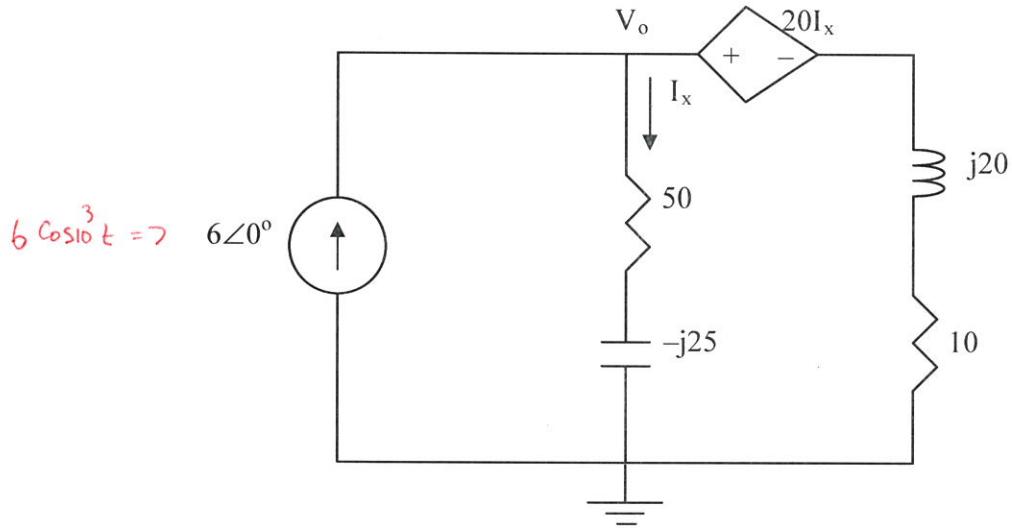We apply nodal analysis to the circuit below.



$$-6 + \frac{V_o - 20I_x}{10 + j20} + \frac{V_o - 0}{50 - j25} = 0$$

But  $I_x = \frac{V_o}{50 - j25}$ . Substituting this and solving for  $V_o$  leads

$$\left( \frac{1}{10 + j20} - \frac{20}{(10 + j20)(50 - j25)} + \frac{1}{50 - j25} \right) V_o = 6$$

$$\left( \frac{1}{22.36 \angle 63.43^\circ} - \frac{20}{(22.36 \angle 63.43^\circ)(55.9 \angle -26.57^\circ)} + \frac{1}{55.9 \angle -26.57^\circ} \right) V_o = 6$$

$$(0.02 - j0.04 - 0.012802 + j0.009598 + 0.016 + j0.008) V_o = 6$$

$$(0.0232 - j0.0224) V_o = 6 \text{ or } V_o = 6 / (0.03225 \angle -43.99^\circ) = 186.05 \angle 43.99^\circ \text{ volts.}$$


$$|I_x| = 186.05 / 55.9 = 3.328$$

We can now calculate the average power absorbed by the 50-Ω resistor.

$$P_{\text{avg}} = [(3.328)^2 / 2] \times 50 = 276.8 \text{ W.}$$

Figure 11.41

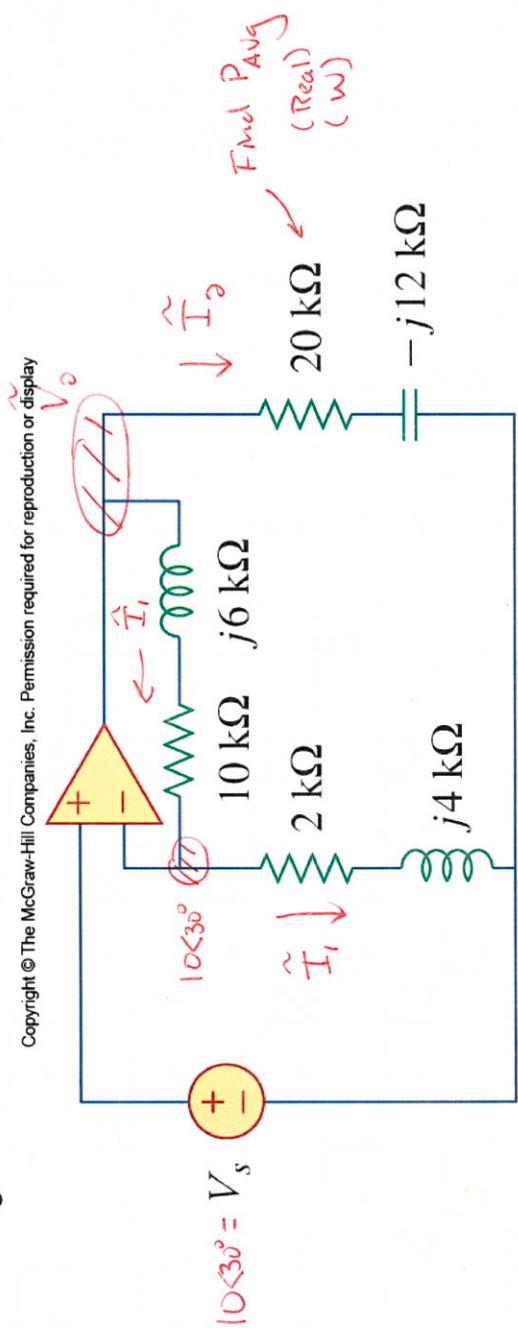Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\hat{I}_1 = \frac{10 < 30^\circ V}{(2 k\Omega + j4 k\Omega)} = 2.24 < -33.4 \text{ mA}$$


$$\begin{aligned} \hat{V}_o &= 10 < 30^\circ + \hat{I}_1 \cdot (10 k\Omega + j6 k\Omega) \\ &= 34.93 < 6.37^\circ \text{ V} \end{aligned}$$

$$\hat{I}_2 = 1.5 < 37.3^\circ \text{ mA}$$

(Assume Peak Value)

$$P_{AVG} = \frac{1}{2} \cdot (1.5)^2 \cdot 20 \text{ k}\Omega = 22.5 \text{ mW}$$

## Instantaneous & Average Power

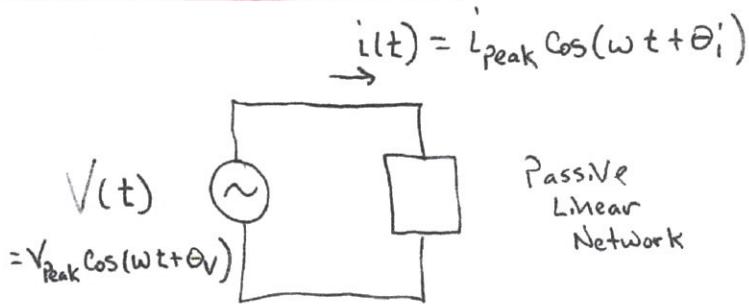

- $P(t) = V(t) \cdot i(t)$

$$= V_{\text{peak}} \cos(\omega t + \theta_V) \cdot i_{\text{peak}} \cos(\omega t + \theta_i)$$


$$= \frac{1}{2} V_{\text{peak}} i_{\text{peak}} [\cos(\cancel{\omega t + \theta_V - \omega t - \theta_i}) + \dots \\ \cos(2\omega t + \theta_V + \theta_i)]$$

$$\cos A \cdot \cos B = \frac{1}{2} \cos(A-B) + \frac{1}{2} \cos(A+B)$$

Instantaneous Power

$$\rightarrow P(t) = \frac{1}{2} V_{\text{peak}} i_{\text{peak}} [\underbrace{\cos(\theta_V - \theta_i)}_{\text{Constant}} + \underbrace{\cos(2\omega t + \theta_V + \theta_i)}_{\text{Averages to Zero}}]$$
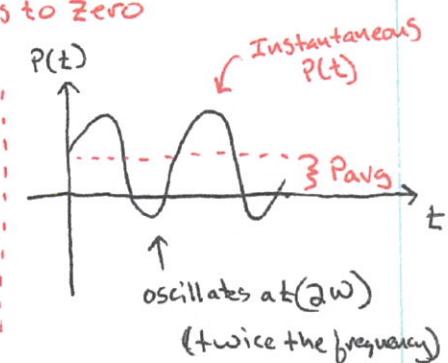
$$\begin{aligned} P_{\text{avg}} &= \frac{1}{2} V_{\text{peak}} i_{\text{peak}} \cdot \cos(\theta_V - \theta_i) \\ &\quad \text{--- } \theta_Z \leftarrow \text{Impedance Angle} \\ &= \frac{1}{2} (\sqrt{2} \cdot V_{\text{rms}})(\sqrt{2} i_{\text{rms}}) \cos(\theta_Z) \\ &= V_{\text{rms}} I_{\text{rms}} \cos \theta_Z \quad (\text{Watts}) \end{aligned}$$



### Notes

- Purely Resistive Load  $\rightarrow R + 0j = Z_R$

$$\theta_V = \theta_i, \therefore \theta_V - \theta_i = 0$$

$$\Rightarrow P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos(0^\circ) = V_{\text{rms}} I_{\text{rms}} = \frac{1}{2} V_{\text{peak}} I_{\text{peak}}$$

- Purely Reactive Load (Inductive or Capacitive)  $\rightarrow 0 + Xj = Z$


$$\theta_V - \theta_i = \pm 90^\circ$$

$$\Rightarrow P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos(\pm 90^\circ) = 0$$

No Avg. Power!  
(Sloshes Back and forth)
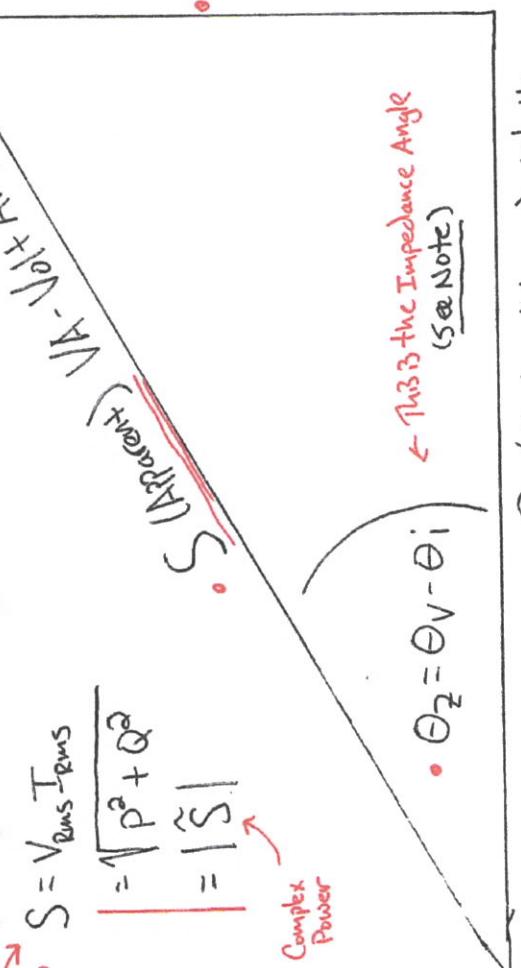
## Power TRIANGLE

\* No Tilda, No Angle, This is the Magnitude of Hypotenuse



\* VA - Volt Amps

$$\bullet \frac{V}{Z} = \frac{\tilde{V}}{\tilde{Z}} = \frac{V \angle \theta_V}{I \angle \theta_i} = \frac{V \angle \theta_V - \theta_i}{I \angle \theta_i} = \frac{V}{I} \angle \theta_2$$

Impedance Angle

•  $Q$  (Reactice or Imaginary) VAR - Volt Amps Reactive

$$\bullet \frac{V}{Z} = \frac{\tilde{V}}{\tilde{Z}} = \frac{V \angle \theta_V}{I \angle \theta_i} = \frac{V \angle \theta_V - \theta_i}{I \angle \theta_i} = \frac{V}{I} \angle \theta_2$$

$$\bullet P \text{ (Real or Average) Watts}$$

•  $P = S \cos \theta_2$

•  $= I_{\text{rms}} V_{\text{rms}} \cos \theta_2$

•  $= \frac{1}{2} I_{\text{peak}} V_{\text{peak}} \cos \theta_2$

•  $= \text{Real} [\tilde{S}]$

•  $\theta_2 = \theta_V - \theta_i$  ← This is the Impedance Angle

•  $Q$  (Reactice or Imaginary) VAR - Volt Amps Reactive

•  $Q = I_{\text{rms}} V_{\text{rms}} \sin \theta_2$

•  $= \frac{1}{2} I_{\text{peak}} V_{\text{peak}} \sin \theta_2$

•  $= S \sin \theta_2$

•  $= \text{Imaginary} (\tilde{S})$

• Putting it ALL Together with Complex Power

•  $\tilde{S} = \hat{V}_{\text{rms}} \hat{I}_{\text{rms}}$  ← Complex Conjugate

•  $= |S| \angle \theta_2$  ← Apparent Power

•  $= V_{\text{rms}} \angle \theta_V \cdot I_{\text{rms}} \angle \theta_i$

•  $= V_{\text{rms}} I_{\text{rms}} \angle \theta_V - \theta_i$  This is the Impedance Angle,  $\theta_2$

• Power Factor

•  $\text{PF} = \cos \theta_2 = \frac{P}{S}$

• For Purely Resistive Load,  $R + 0j = Z$

•  $\Rightarrow \theta_2 = 0^\circ$

•  $\Rightarrow \tilde{S} = V_{\text{rms}} I_{\text{rms}} \cos(0^\circ) + V_{\text{rms}} I_{\text{rms}} \sin(0^\circ) j$  (VA)

•  $= V_{\text{rms}} I_{\text{rms}} + 0j$  (VA or W)

•  $= S < 0^\circ$  VA or Watts & in this case as

•  $= \frac{1}{2} \cdot \hat{I}^* \hat{Z} = \frac{1}{2} \hat{I}^* \frac{V^2}{Z}$  ← Complex Conjugate

•  $= \frac{1}{2} \cdot \hat{V}^* \hat{Z} = \frac{1}{2} \hat{V}^* \frac{I^2}{Z}$  ← Complex Conjugate