

Name: _____ Key
Section: _____

EE331 Homework PS9 – fall 2012

Problems from Alexander & Sadiku:

CH 11 –

- 11.51
- 11.61
- 11.69
- 11.71
- 11.74 (ans: pf = 0.9 lagging, C = 5.74 mF)

Additional Problems (Instructor Option):

- 11.85
- Any as assigned by instructor

Chapter 11, Solution 51.

(a) $Z_T = 2 + (10 - j5) \parallel (8 + j6)$
 $Z_T = 2 + \frac{(10 - j5)(8 + j6)}{18 + j} = 2 + \frac{110 + j20}{18 + j}$
 $Z_T = 8.152 + j0.768 = 8.188 \angle 5.382^\circ$

$$\text{pf} = \cos(5.382^\circ) = 0.9956 \quad (\text{lagging})$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


(b) $S = \mathbf{V}\mathbf{I}^* = \frac{|\mathbf{V}|^2}{Z} = \frac{(16)^2}{(8.188 \angle -5.382^\circ)}$
 $S = 31.26 \angle 5.382^\circ$

P = S cos θ = 31.12 W

(c) Q = S sin θ = 2.932 VAR

(d) S = |S| = 31.26 VA

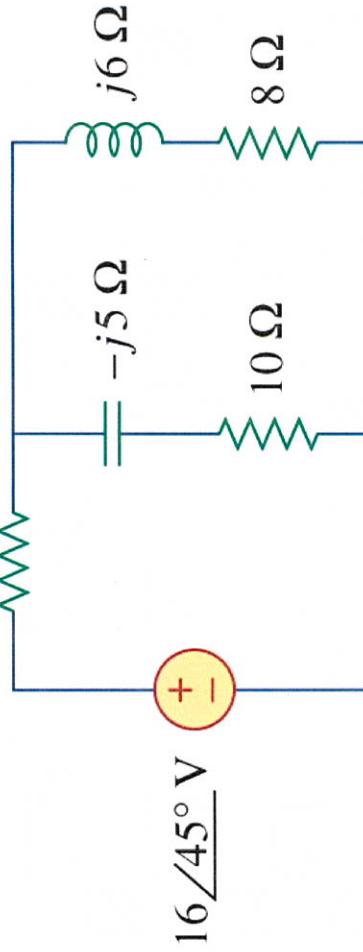
(e) S = 31.26 ∠ 5.382° = (31.12+j2.932) VA




- (a) 0.9956 (lagging), (b) 31.12 W, (c) 2.932 VAR, (d) 31.26 VA, (e) [31.12+j2.932] VA

Figure 11.80

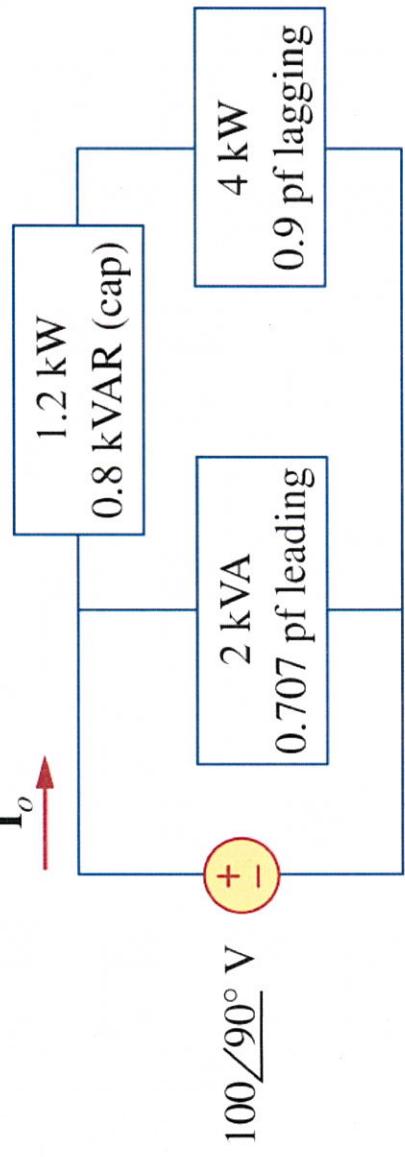
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



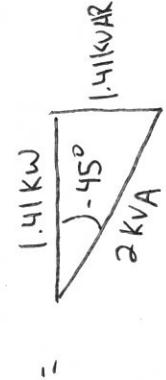
$$\hat{S}_{\text{tot}} = \hat{S}_1 + \hat{S}_2 + \hat{S}_3$$



$$= 1.41 \text{ kVA}$$

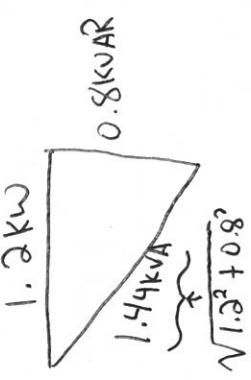


$$= 1.44 \text{ kVA}$$

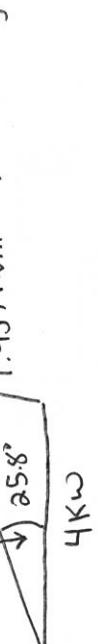

$$= 1.934 \text{ kVA}$$

$$= 6.61 \text{ kVA}$$

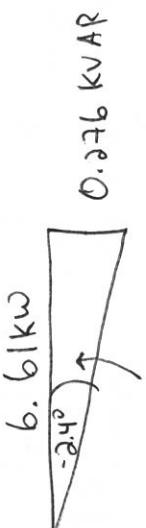

$$\tan^{-1}\left(\frac{0.376}{6.61}\right) = -2.4^\circ$$

$$\hat{S}_{\text{tot}} = 6.61 + j0.376 = 6.62 \angle -2.4^\circ \text{ kVA}$$

$$66.2 \angle -92.4^\circ \text{ A}$$

$$\hat{I} * = \frac{\hat{S}_{\text{tot}}}{\hat{V}_{\text{source}}} = \frac{6.62 \angle -2.4^\circ \text{ kVA}}{100 \angle 90^\circ \text{ V}} = 66.2 \angle -92.4^\circ \text{ A}$$

$$\Rightarrow \hat{I} = 66.2 \angle -92.4^\circ \text{ A}$$

Complex Conjugate

Chapter 11, Problem 69.

Refer to the circuit shown in Fig. 11.88.

- What is the power factor?
- What is the average power dissipated?
- What is the value of the capacitance that will give a unity power factor when connected to the load?

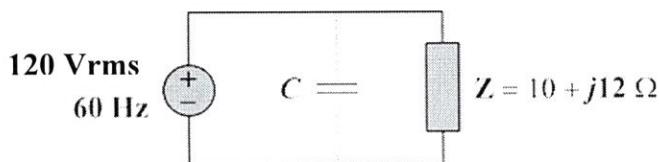


Figure 11.88

$$a) \quad Z = 10 + 12j = 15.6 \angle 50.2^\circ \Omega$$

$$\theta_Z = \theta_V - \theta_I$$


$$\rightarrow \text{pf} = \cos(\theta_Z) = 0.64 \text{ Lagging (ELI)}$$

$$b) \quad \text{1ST} \rightarrow \hat{S} = \frac{V_{\text{rms}}^2}{Z^*} = \frac{(120V)^2}{15.6 \angle -50.2^\circ} = 923.1 \angle 50.2^\circ \text{ VA}$$

↑ complex conjugate

$$\rightarrow P_{\text{AVG}} = 590.9 \text{ W}$$

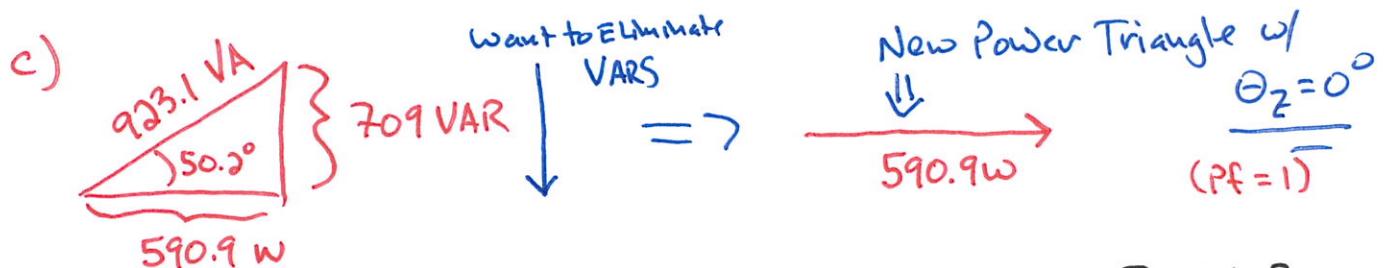or
 $\underbrace{590.9 + 709j}_{P_{\text{AVG}}} \text{ VA}$




$\therefore \text{NEED } -709 \text{ VAR to counter } +709 \text{ VAR}$

$$(11.60) \quad \rightarrow \quad Q = 709 \text{ VAR} = \frac{(120V)^2}{1/w_C} = \frac{(120V)^2}{(2\pi \cdot 60 \cdot C)}$$

$$\Rightarrow C = 130.6 \mu\text{F}$$

Chapter 11, Problem 71.

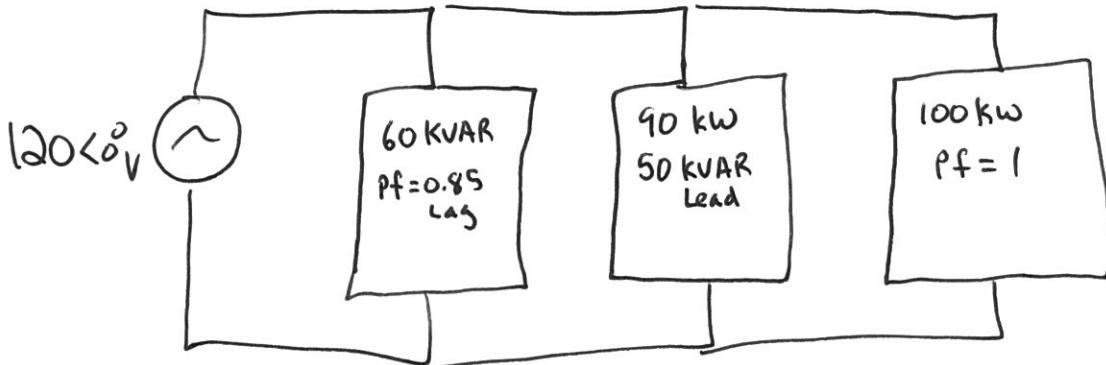Three loads are connected in parallel to a $120\angle 0^\circ$ V rms source. Load 1 absorbs 60 kVAR at $\text{pf} = 0.85$ lagging; load 2 absorbs 90 kW and 50 kVAR leading; and load 3 absorbs 100 kW at $\text{pf} = 1$. (a) Find the equivalent impedance. (b) Calculate the power factor of the parallel combination. (c) Determine the current supplied by the source.




151 USE Summation of Power Triangles

Load: #1 #2 #3



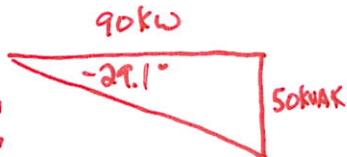
$$\begin{aligned} \bullet \cos^{-1}(0.85) &= 31.8^\circ \\ \uparrow & \text{as Inductive (ELI)} \\ \bullet P &= \frac{60 \text{ kVAR}}{\tan 31.8^\circ} = 96.8 \text{ kW} \end{aligned}$$



$$\bullet \theta_2 = \tan^{-1}\left(\frac{-50}{90}\right) = -29.1^\circ$$


3

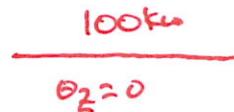

$$\bullet \theta_3 = 0^\circ$$

Total

$$(60 - 50) = 10 \text{ kW}$$

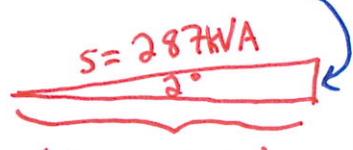

$$\begin{aligned} S &= 287 \text{ kVA} \\ (96.8 + 90 + 100) &= 286.8 \text{ kW} \end{aligned}$$

$$\bullet \theta_2 = \tan^{-1}\left(\frac{10}{286.8}\right) = 2^\circ$$

$$\bullet S = \sqrt{286.8^2 + 10^2} = 286.97 \text{ kVA}$$

$$\bullet \tilde{S} = 287 \angle 2^\circ \text{ kVA}$$

$$\text{a) } \tilde{S} = \frac{|V_{\text{rms}}|^2}{Z^*} \Rightarrow Z^* = \frac{(120V)^2}{287 \angle 2^\circ \text{ kVA}} = 50.2 \angle -2^\circ \text{ m}\Omega$$

$$\therefore Z = 50.2 \angle -2^\circ \text{ m}\Omega$$

$$\text{b) } \text{pf} = \cos \theta_2 = \cos(2^\circ) = 0.9994 \text{ Lagging}$$

$$\text{c) } \tilde{I}_{\text{source}} = \frac{\tilde{V}_{\text{source}}}{Z} = \frac{120V \angle 0^\circ}{50.2 \angle -2^\circ \text{ m}\Omega} = 2390.4 \angle -2^\circ \text{ A}$$

Chapter 11, Problem 74.

A 120-V rms 60-Hz source supplies two loads connected in parallel, as shown in Fig. 11.89.

- Find the power factor of the parallel combination.
- Calculate the value of the capacitance connected in parallel that will raise the power factor to unity.


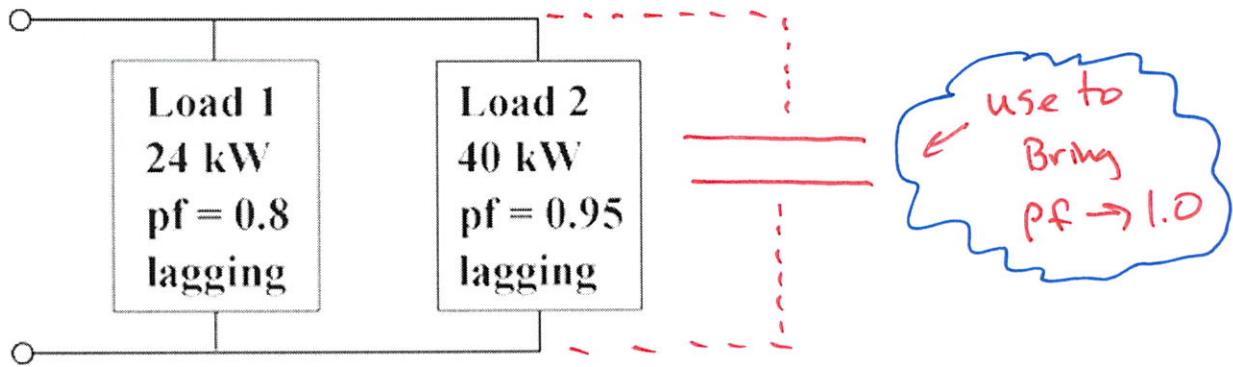


Figure 11.89

USE Summation of Power Triangles


LOAD: #1

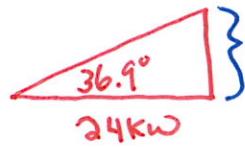

$$\bullet \Theta_2 = \cos^{-1}(0.8) = 36.9^\circ$$


↑
ELI → Inductive

#2

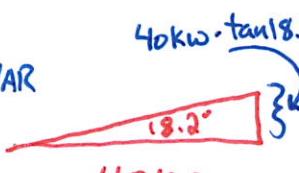

$$\bullet \Theta_2 = \cos^{-1}(0.95) = 18.2^\circ$$

Total

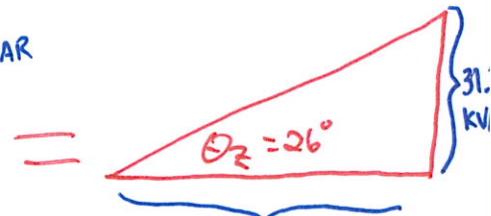

$$24\text{ kW} + 40\text{ kW} = 64\text{ kW}$$

$$\bullet \Theta_2 = \tan^{-1}\left(\frac{31.2}{64}\right) = 26^\circ$$

a) $\boxed{\text{pf} = \cos \Theta_2_{\text{Total}} = 0.9 \text{ LAGGING}}$

b) Want Final Power Triangle \rightarrow $\frac{\Theta_2 = 0^\circ}{64\text{ kW}} \rightarrow \boxed{0 \text{ VARS}}$

(11.60)
in book

Need to cancel with $31.2 \text{ kVAR} = \frac{V_{\text{rms}}^2}{|Z_C|} = \frac{(120\text{V})^2}{\frac{1}{(2\pi \cdot 60) \cdot C}}$ $\Rightarrow \boxed{C = 5.74 \mu\text{F}}$

Chapter 11, Problem 85.

A regular household system of a single-phase three-wire allows the operation of both 120-V and 240-V, 60-Hz appliances. The household circuit is modeled as shown in Fig. 11.96. Calculate: (a) the currents \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_n , (b) the total complex power supplied, (c) the overall power factor of the circuit.

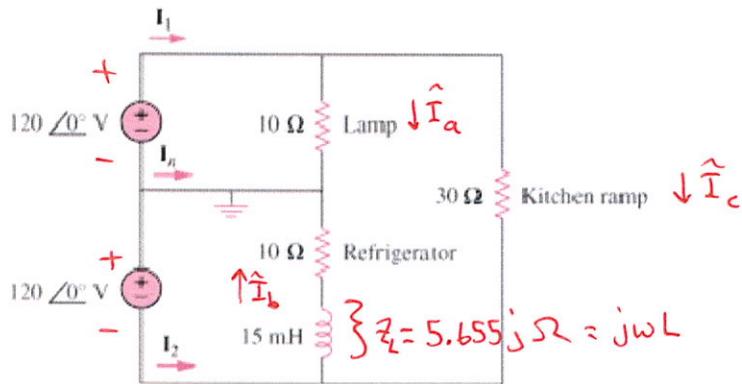


Figure 11.96

$$\begin{aligned} \bullet \hat{\mathbf{I}}_a &= \frac{120V\angle 0^\circ - 0V}{10\Omega} = 12\angle 0^\circ A \\ \bullet \hat{\mathbf{I}}_b &= \frac{-120V\angle 0^\circ - 0V}{10 + 5.655j\Omega} = -10.45\angle -29.5^\circ A \\ \bullet \hat{\mathbf{I}}_c &= \frac{120\angle 0^\circ - 120\angle 0^\circ}{30} = 8\angle 0^\circ A \end{aligned}$$


a)

$$\begin{aligned} \bullet \hat{\mathbf{I}}_1 &= \hat{\mathbf{I}}_a + \hat{\mathbf{I}}_c = 20\angle 0^\circ A \\ \bullet \hat{\mathbf{I}}_2 &= \hat{\mathbf{I}}_b - \hat{\mathbf{I}}_c = 17.85\angle 163.2^\circ A \\ \bullet \hat{\mathbf{I}}_n &= -\hat{\mathbf{I}}_a - \hat{\mathbf{I}}_b = 5.91\angle -119.4^\circ A \end{aligned}$$

$$\begin{aligned} b) \quad \hat{S}_{TOT} &= \hat{S}_{Lamp} + \hat{S}_{Refrigerator} + \hat{S}_{KR} = \hat{\mathbf{I}}_a^* \cdot 120\angle 0^\circ + \hat{\mathbf{I}}_b^* \cdot (-120\angle 0^\circ) + \hat{\mathbf{I}}_c^* \cdot 240\angle 0^\circ \\ &= 1440\angle 0^\circ + 1254\angle 29.5^\circ + 1920\angle 0^\circ \\ &= 4494.1\angle 7.9^\circ \text{ VA} \end{aligned}$$

$$c) \quad \langle \text{P.F.} = \cos(7.9^\circ) \rangle = 0.9905 \text{ Lagging}$$

Instantaneous & Average Power

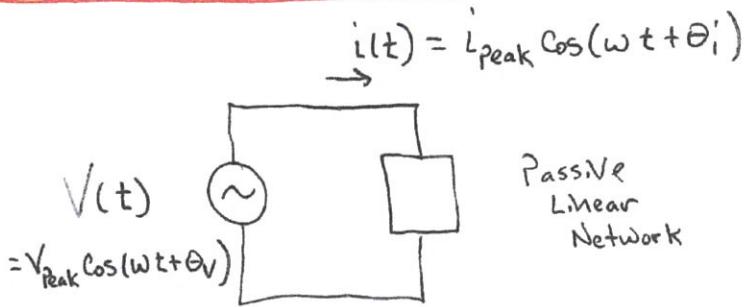

- $P(t) = V(t) \cdot i(t)$

$$= V_{\text{peak}} \cos(\omega t + \theta_V) \cdot i_{\text{peak}} \cos(\omega t + \theta_i)$$

$$= \frac{1}{2} V_{\text{peak}} \cdot i_{\text{peak}} \left[\cos(\cancel{\omega t + \theta_V - \omega t - \theta_i}) + \dots \right. \\ \left. \cos(2\omega t + \theta_V + \theta_i) \right]$$


$$\cos A \cdot \cos B = \frac{1}{2} \cos(A-B) + \frac{1}{2} \cos(A+B)$$

Instantaneous Power

- $P(t) = \frac{1}{2} V_{\text{peak}} \cdot i_{\text{peak}} \left[\cos(\theta_V - \theta_i) + \cos(2\omega t + \theta_V + \theta_i) \right]$

Constant

Averages to Zero

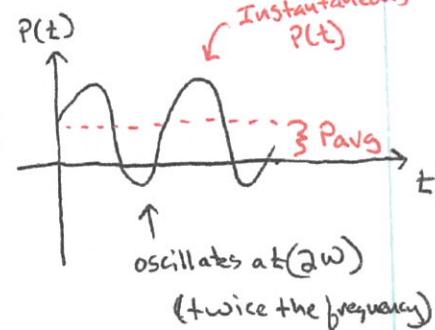

Notes

- Purely Resistive Load $\rightarrow R + 0j = Z_R$

$$\theta_V = \theta_i, \therefore \theta_V - \theta_i = 0$$

$$\Rightarrow P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos(0^\circ) = V_{\text{rms}} I_{\text{rms}} = \frac{1}{2} V_{\text{peak}} I_{\text{peak}}$$

- Purely Reactive Load (Inductive or Capacitive) $\rightarrow 0 + Xj = Z$

$$\theta_V - \theta_i = \pm 90^\circ$$

$$\Rightarrow P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos(\pm 90^\circ) = 0$$


No Avg. Power!
(Sloshes Back and Forth)

Power TRIANGLE

* no Tilda, No Angle, This is the magnitude of the tension

$$\bullet S = V_{\text{Rms}} I_{\text{Rms}} = \sqrt{P^2 + Q^2} = |\hat{S}|$$

Complex Power

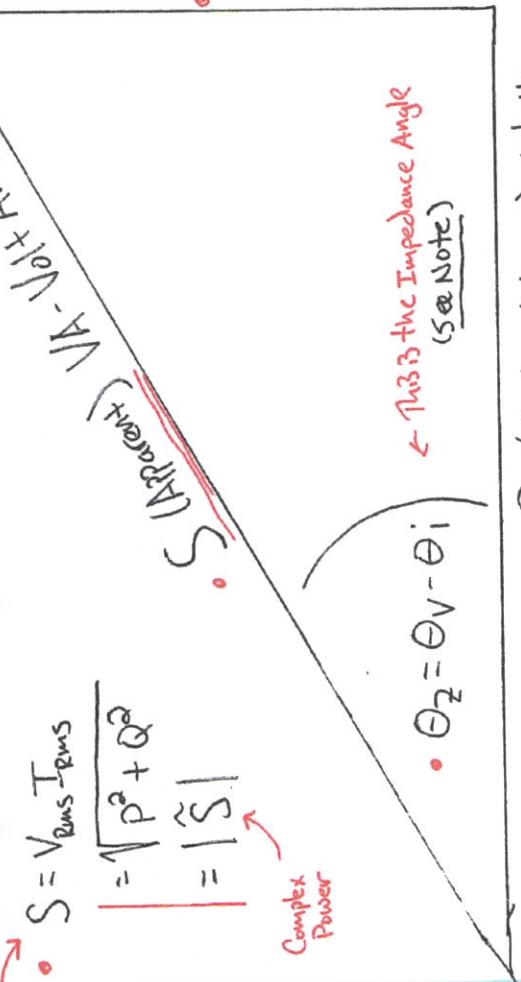

* Note
• $\frac{V}{Z} = \frac{\tilde{V}}{\tilde{Z}} = \frac{V \angle \Theta_V}{I \angle \Theta_i} = \frac{V}{I} \angle \Theta_V - \Theta_i = \frac{V}{I} < \Theta_V - \Theta_i$

Impedance Angle

$$• \frac{V}{Z} = \frac{\tilde{V}}{\tilde{Z}} = \frac{V \angle \Theta_V}{I \angle \Theta_i} = \frac{V}{I} < \Theta_V - \Theta_i = \frac{V}{I} < \Theta_2$$

• Q (Reactive or Imaginary) VARs Reactive

$$\begin{aligned} Q &= I_{\text{Rms}} V_{\text{Rms}} \sin \Theta_2 \\ &= \frac{1}{2} I_{\text{Peak}} V_{\text{Peak}} \sin \Theta_2 \\ &= S \sin \Theta_2 \\ &= \text{Imaginary}(\hat{S}) \end{aligned}$$

$$\begin{aligned} * \text{ Note} \\ • \frac{V}{Z} = \frac{\tilde{V}}{\tilde{Z}} = \frac{V \angle \Theta_V}{I \angle \Theta_i} = \frac{V}{I} < \Theta_V - \Theta_i = \frac{V}{I} < \Theta_2 \end{aligned}$$

• Q (Reactive or Imaginary) VARs Reactive

$$\begin{aligned} P &= S \cos \Theta_2 \\ &= I_{\text{Rms}} V_{\text{Rms}} \cos \Theta_2 \\ &= \frac{1}{2} I_{\text{Peak}} V_{\text{Peak}} \cos \Theta_2 \\ &= \text{Real}[\hat{S}] \end{aligned}$$

$$\begin{aligned} \bullet \hat{S} &= \hat{V}_{\text{Rms}} \hat{I}_{\text{Rms}} \\ &\quad \xrightarrow{\text{Putting it All Together with Complex Power}} \text{Complex Power} \\ &\quad \xrightarrow{\text{Complex Conjugate}} \hat{S}^* < \Theta_2 = S < \Theta_2 \end{aligned}$$

$$\begin{aligned} &= V_{\text{Rms}} < \Theta_V \cdot I_{\text{Rms}} < \Theta_i \\ &= V_{\text{Rms}} I_{\text{Rms}} < \Theta_V - \Theta_i \end{aligned}$$

$$\begin{aligned} &= V_{\text{Rms}} I_{\text{Rms}} \cos \Theta_2 + V_{\text{Rms}} I_{\text{Rms}} \sin \Theta_2 \cdot j \end{aligned}$$

$$\begin{aligned} &= P + Q \cdot j \\ &= S \cos \Theta_2 + S \sin \Theta_2 \cdot j \end{aligned}$$

$$\begin{aligned} &= \frac{1}{2} \hat{I}^* \hat{Z}^2 = \frac{1}{2} \hat{V}^2 \hat{Z}^* \\ &= \frac{1}{2} \hat{V}^* \hat{Z}^* = \frac{1}{2} \hat{V}^2 \hat{Z} \end{aligned}$$

Complex Conjugate
 $\Rightarrow +\Theta_2$ for $S < \Theta_2$

$$= \frac{1}{2} \hat{V}^2 \hat{Z}$$

This is the Impedance Angle, Θ_2

$$= S < \Theta_2 \text{ or Watts} \leftarrow \text{in this case as no Reactive portion}$$

• P (Real or Average) Watts

• $\Theta_2 = \Theta_V - \Theta_i$ (See Note)

• $\hat{S} = \hat{V}_{\text{Rms}} \hat{I}_{\text{Rms}}$

• $P = S \cos \Theta_2$
Polar Form
Rectangular Form

• $\text{PF} = \cos \Theta_2 = P/S$

• For Purely Resistive Load, $R+0j = Z$
 $\Rightarrow \Theta_2 = 0^\circ$

• $\hat{S} = V_{\text{Rms}} I_{\text{Rms}} \cos(0^\circ) + V_{\text{Rms}} I_{\text{Rms}} \sin(0^\circ) \cdot j$
 $\hat{S} = V_{\text{Rms}} I_{\text{Rms}} + 0j$
 $= S < 0^\circ \text{ VA or W}$