
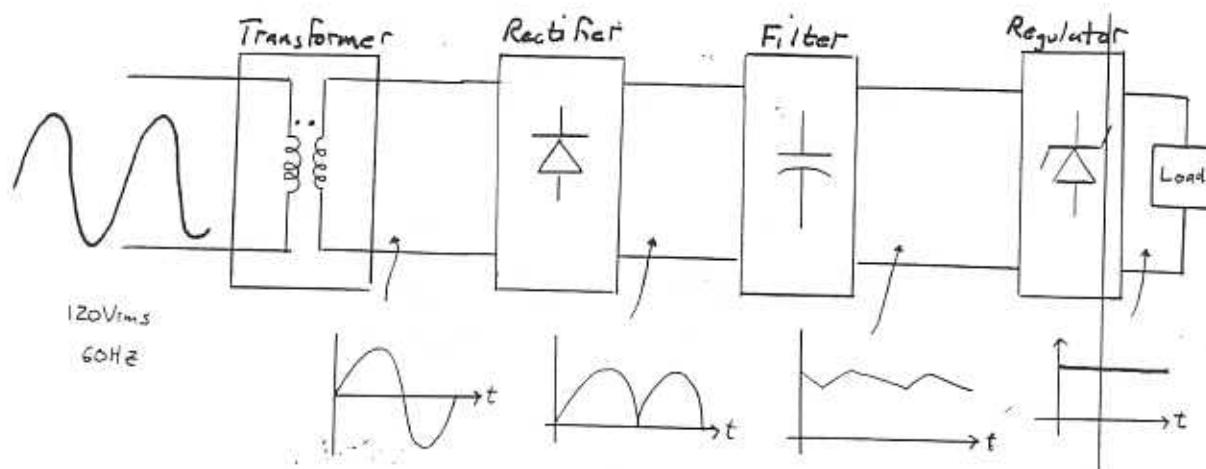


Recap from last time

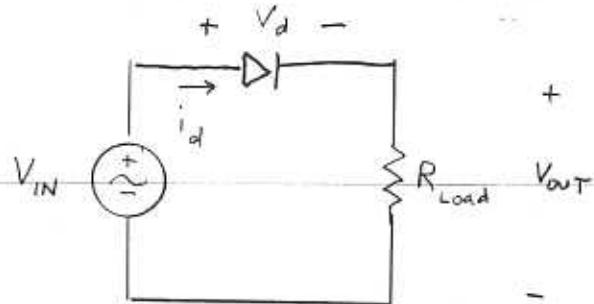(*) Most electronic equipment require a conversion from AC to DC



(*) The simplest structure of rectifier is the half-wave rectifier




which contains a diode, which for its simplest model is governed by

Forward Biased : "ON" $V_d \approx 0$ $i_d > 0$

Reverse Biased : "OFF" $i_d \approx 0$ $V_d < 0$

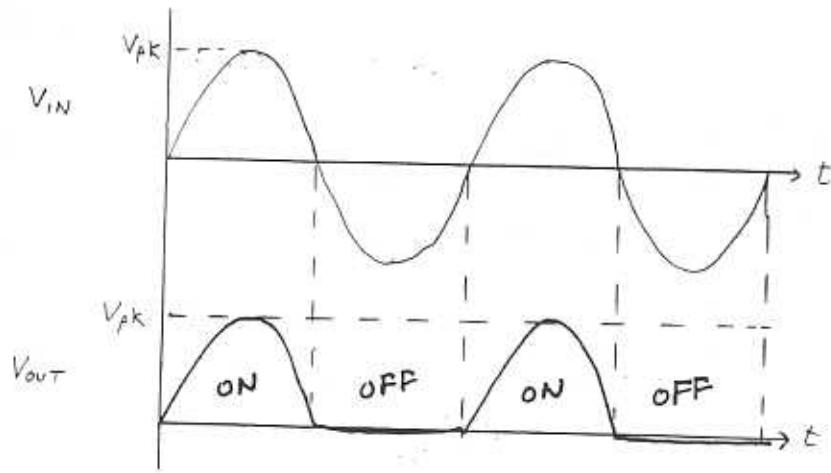(*) Upon assuming a "state" and performing circuit analysis
then testing our assumption, we found



which we then used to find the average and RMS values

$$V_{\text{out,ave}} = \frac{V_{\text{pk}}}{\pi} \quad V_{\text{out,RMS}} = \frac{V_{\text{pk}}}{2}$$

(*) Finally, we asserted that those values would be influenced by two real-world phenomena: diode voltage drop and the output resistance of the transformer so we would use


$$V_{\text{pk}} = (V_{\text{ses,pk,NL}} - 0.7) \frac{R_{\text{Load}}}{R_{\text{Load}} + R_{\text{TRAN}}}$$

where $0.7V$: assumed diode ON-state voltage drop


R_{TRAN} : assumed output resistance of the transformer

Full-Wave Rectifier

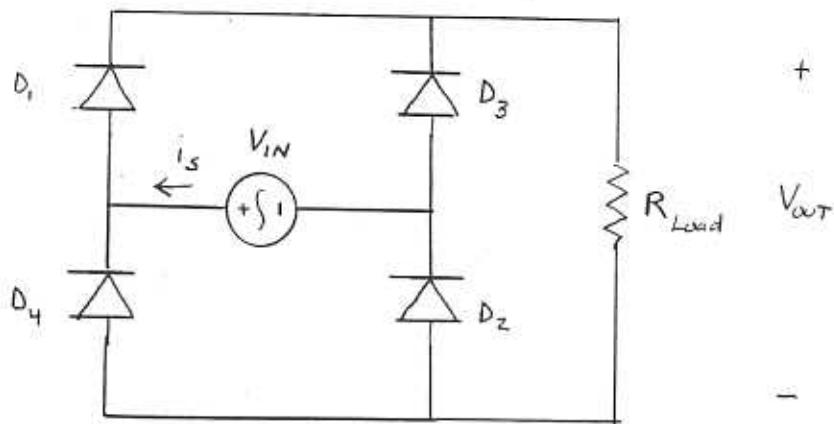(*) We next want to consider a way to reduce the output voltage ripple and increase the average value. Consider the following topology




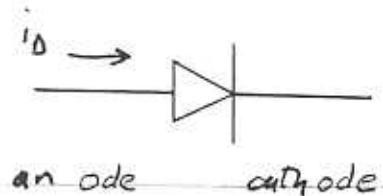Since the diode only conducts current from anode to cathode




we have 2 possible paths from the source (and have a complete path)


i_S positive

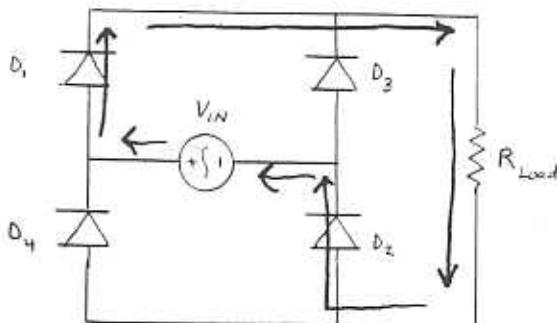

i_S negative

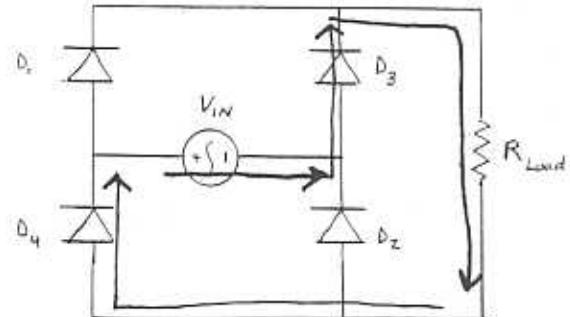

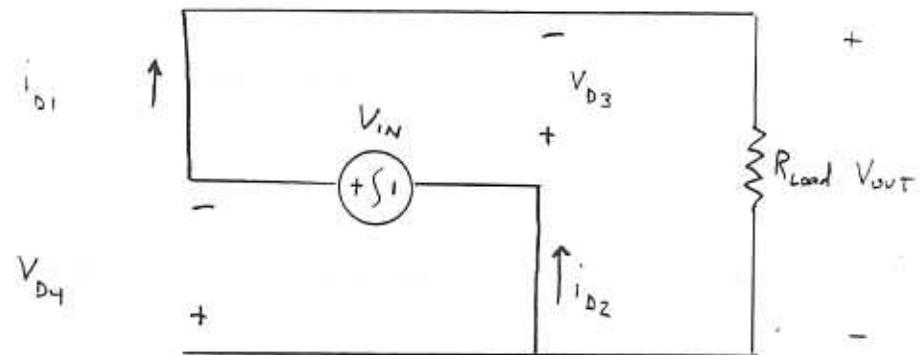Step 1: Assume D_1 and D_2 are "ON" and D_3 and D_4 are "OFF"




- KVL Demands : $V_{out} = V_{in}$

- Further : $V_{D4} = V_{D3} = -V_{in}$

- Ohm's Law Asserts : $i_{D1} = i_{D2} = \frac{V_{in}}{R_{load}}$

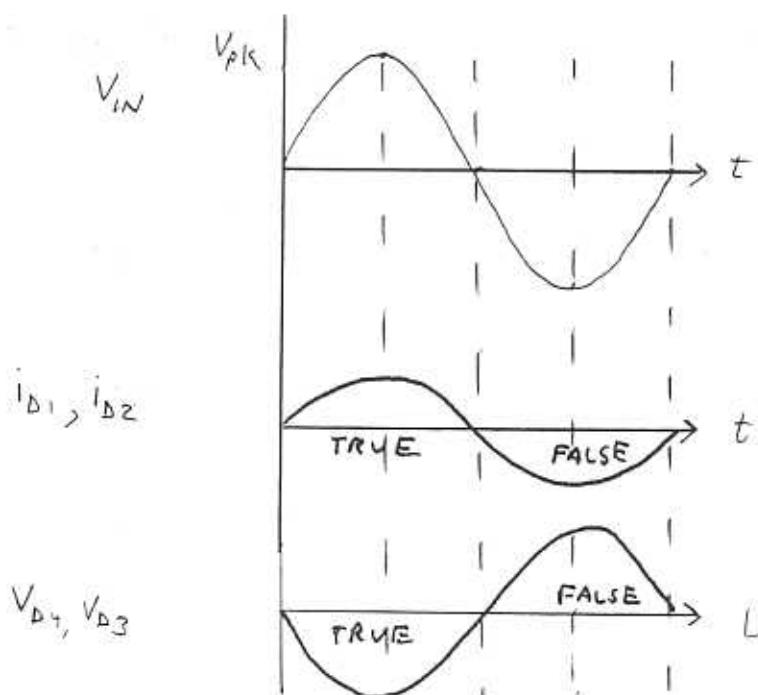
- IF we assume $V_{in} = V_{pk} \sin \omega t$



(*) The assumption on the status (D_1, D_2 ON D_3, D_4 OFF)
is TRUE if $i_{D_1} = i_{D_2} > 0$ AND $V_{D_3} = V_{D_4} < 0$
and FALSE otherwise

→ Thus our assumption is TRUE for the positive half cycle

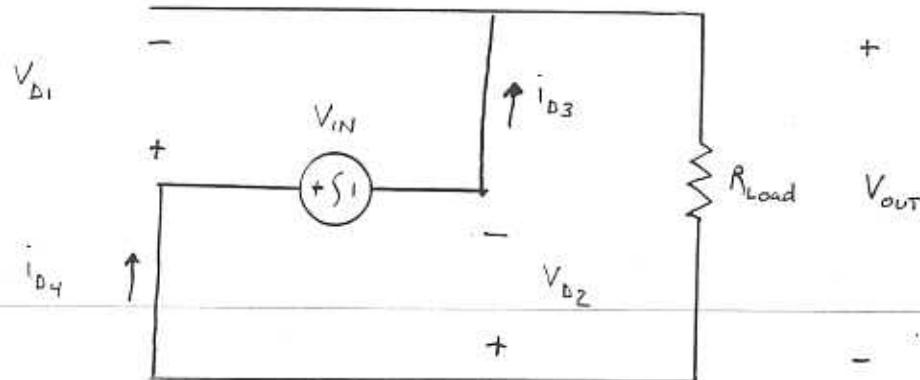Step 2: Assume D_3 and D_4 are "ON" and
 D_1 and D_2 are "OFF"




- KVL Demands : $V_{OUT} = -V_{IN}$

- And : $V_{D_1} = V_{D_2} = V_{IN}$

- Ohm's Law Gives : $i_{D_3} = i_{D_4} = \frac{-V_{IN}}{R_{Load}}$

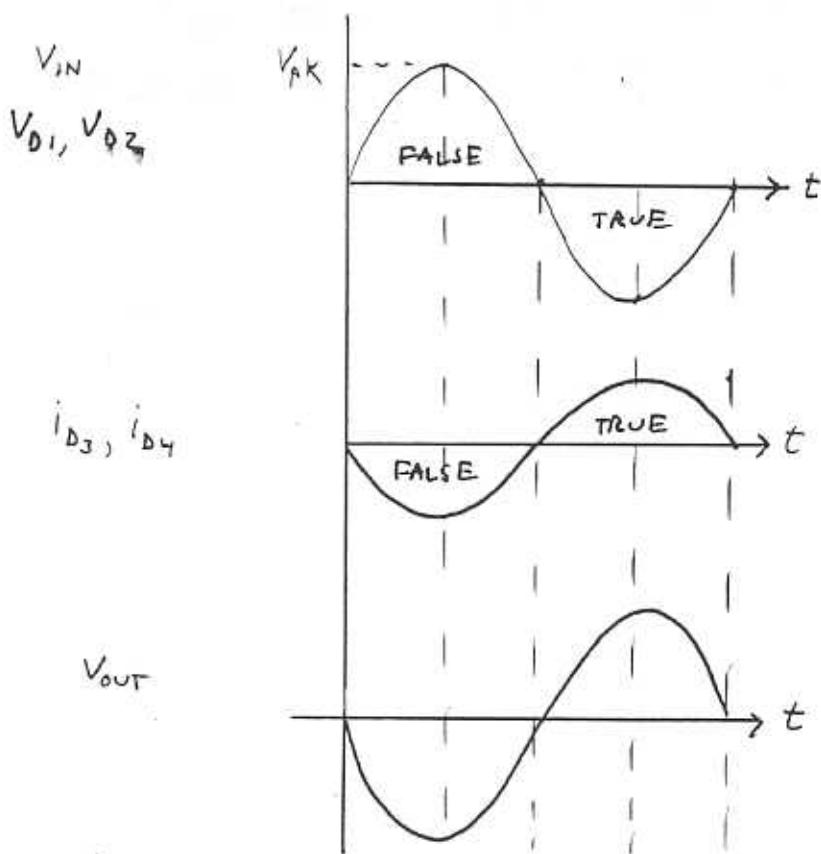- With $V_{IN} = V_{PK} \sin \omega t$, sketching




(*) The assumption of the status (D_3, D_4 ON D_1, D_2 OFF)

is TRUE if $i_{D3} = i_{D4} > 0$ AND $V_{D1} = V_{D2} < 0$

and FALSE otherwise

→ Thus our assumption is TRUE for the negative half cycle

Step 3 Recover V_{OUT}

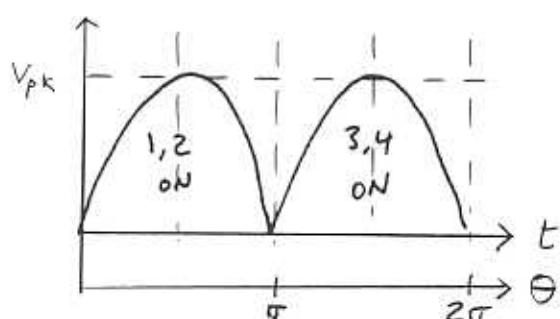

(*) We can now determine the AVERAGE and RMS values as we did for the half-wave rectifier:

$$V_{\text{out,ave}} = \frac{1}{\pi} \left[\int_0^{\pi} V_{\text{pk}} \sin \theta \, d\theta \right] = \frac{2 V_{\text{pk}}}{\pi}$$

$$V_{\text{out,RMS}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_{\text{out}})^2 \, d\theta} = \frac{V_{\text{pk}}}{\sqrt{2}}$$

since squaring V_{out} gives the same waveform as squaring V_{in} and thus it must have the same RMS value!

(*) The average power delivered to the load resistance is found as

$$P_{\text{load,ave}} = \frac{V_{\text{out,RMS}}^2}{R_{\text{load}}}$$

(*) To account for non-ideal effects, we must modify V_{pk} but this time we have 2 diode drops so

$$V_{\text{pk}} = (V_{\text{sec,pk,NL}} - 1.4V) \frac{R_{\text{load}}}{R_{\text{load}} + R_{\text{diode}}}$$

Ex. Suppose you wish to deliver 2W to a 2Ω load through a transformer with a 2Ω output resistance, determine the No-Load RMS value of the transformer secondary assuming a Full-wave rectifier is used

$$\rightarrow V_{\text{out,RMS}} = \sqrt{P_{\text{load,ave}} R_{\text{load}}} = 6.325V$$

$$\rightarrow V_{\text{pk}} = \sqrt{2} V_{\text{out,RMS}} = 8.944V$$


$$\rightarrow V_{\text{sec,pk,NL}} = \frac{20+2}{20} (V_{\text{pk}}) + 1.4V = 11.23V$$

$$\rightarrow V_{\text{sec,RMS,NL}} = \frac{V_{\text{sec,pk,NL}}}{\sqrt{2}} = 7.95V$$


(*) Many loads require "smoother" output voltage and will not operate properly without it. Thus, we need to filter the output -- with the simplest example being a capacitor

Filtering


(*) Half-Wave Rectifier

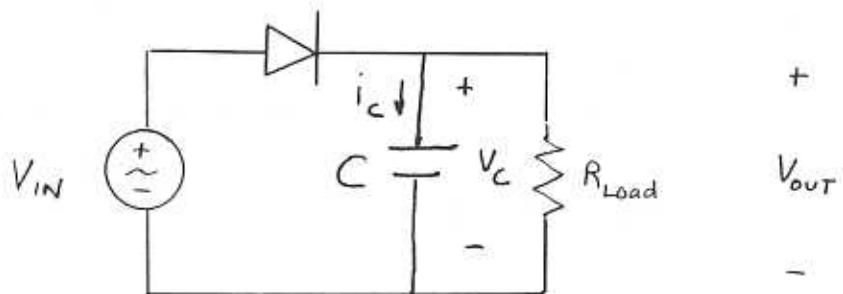

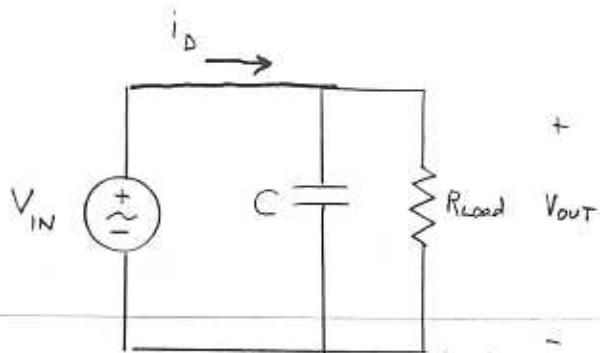Assuming an "ideal" diode, the circuit has two possible states



DIODE ON

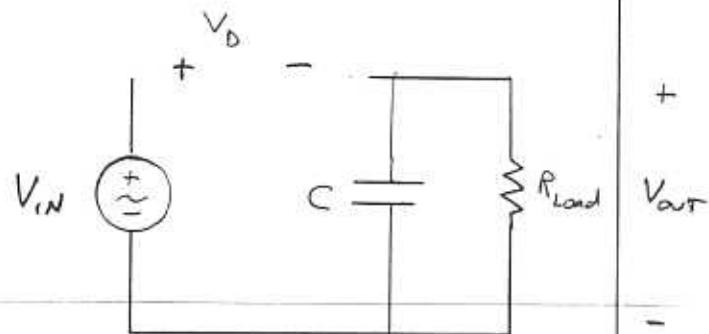

DIODE OFF


→ Capacitor charging

$$\rightarrow V_{OUT} = V_{IN}$$

→ Capacitor discharging

$$\rightarrow V_{OUT} = V_C$$

"Basic Idea"

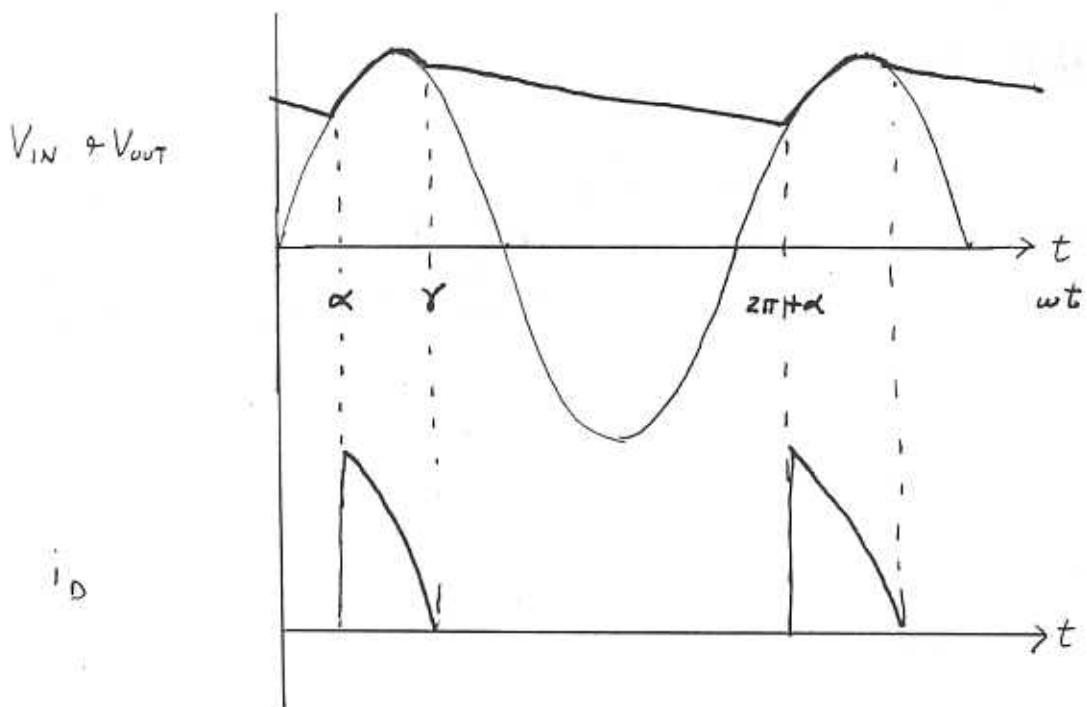


"The Analysis"

Define: α as angle at which diode starts to conduct

Define: γ as angle at which diode stops conducting

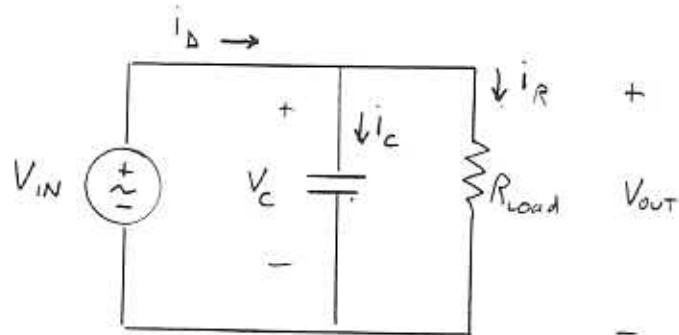Step 1 Analyze the circuit when the diode is assumed "ON" and find when $i_d \geq 0$



(*) The components are in parallel and if we let

$$V_{IN} = V_{pk} \sin \omega t = V_{pk} \sin \theta, \text{ then}$$

$$i_R = \frac{V_{IN}}{R_{load}} = \frac{V_{pk}}{R_{load}} \sin \omega t$$

$$i_C = C \frac{dV_C}{dt} = C \frac{d}{dt} [V_{pk} \sin \omega t] = V_{pk} \omega C \cos \omega t$$

Then KCL demands that

$$i_D = i_C + i_R$$

which we can add using phasors to get

$$i_D = V_{pk} \sqrt{(\omega C)^2 + (R_{load})^{-2}} \sin [\omega t + \tan^{-1}(\omega R_{load} C)]$$

The diode conducts until this current goes to zero.

Setting

$$i_D = 0 \rightarrow \sin [\omega t + \tan^{-1}(\omega R_{load} C)] = 0$$

which occurs when


$$\omega t + \tan^{-1}(\omega R_{load} C) = 0, \pi, 2\pi$$

But we defined $\omega t = \gamma$
at this point

So we find based on the Figure on page 32-10

$$\gamma = \pi - \tan^{-1}(\omega R_{load} C)$$

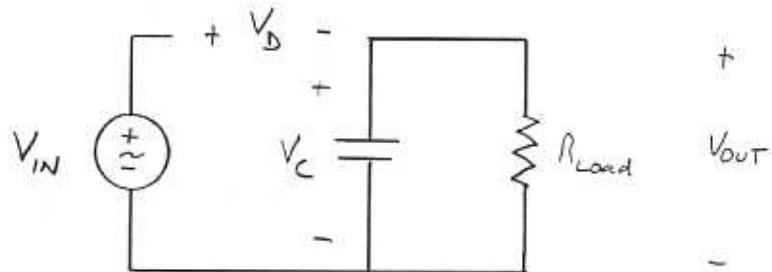Step 2 Analyze the circuit when the diode is assumed "OFF" and find when $V_D < 0$



(*) Since the diode turns off at $\omega t = \gamma$, at that point $V_{IN} = V_C = V_{pk} \sin(\gamma)$ and that voltage cannot change instantaneously and must be the starting point for this circuit.

$$V_I = V_{pk} \sin \gamma$$

(*) The capacitor voltage will exponentially decay, governed by

$$- \left(\frac{t - t_\gamma}{RC} \right)$$

$$V_C = V_I e$$


or in terms of angles

$$- \left(\frac{\theta - \gamma}{\omega RC} \right)$$

$$V_C = V_I e$$

(*) The diode voltage is given by

$$V_D = V_{IN} - V_C$$

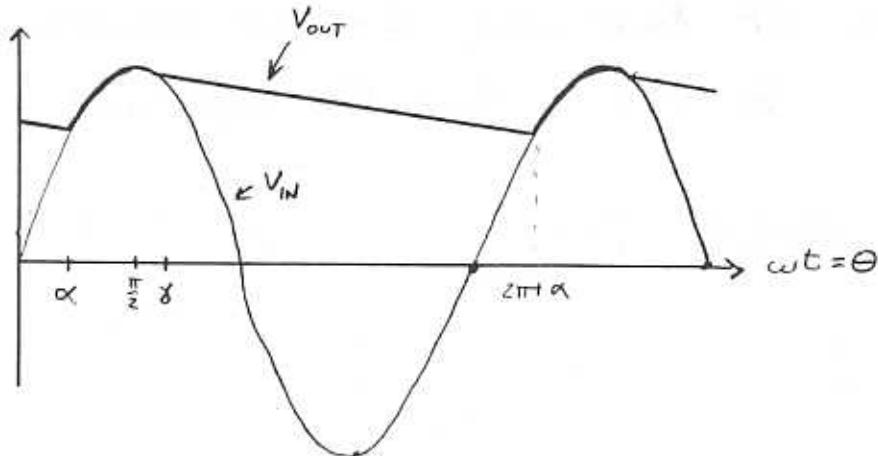

(*) The diode conducts until $V_D = 0$ when $\theta = 2\pi + \alpha$

$$V_D = V_{pk} \sin(2\pi + \alpha) - V_{pk} \sin(\gamma) C - \left(\frac{e^{i\theta + \alpha} - 1}{\omega R_{load} C} \right) = 0$$

even with γ known, this is a non-linear equation that is transcendental (multiple solutions)
(Fortunately our calculator solves it!)

Step 3 Once we know γ and α , we can find the capacitor ripple by

$$\Delta V_{out} = V_{pk} - V_{pk} \sin \alpha$$

and the average value is very close to

$$V_{out, ave} = V_{pk} - \frac{\Delta V_{out}}{2}$$

or

$$V_{out, ave} = (V_{pk} + V_{pk} \sin \alpha)/2$$

ex. IF $R_{load} = 500\Omega$, $C = 100\mu F$, $\omega = 377 \text{ rad/s}$ and $V_{pk} = 15V$, Find the ripple and average voltage

Step 1 Evaluate $\omega R_{load} C = 18.85 \text{ rad}$

Step 2 Find γ

$$\gamma = \pi - \tan^{-1}(\omega R_{load} C) = 1.62 \text{ rad}$$

1.51779

Step 3 Find α

$$\sin(\alpha) - \sin(\gamma) e^{-\left(\frac{2\pi + \alpha - \gamma}{\omega R_{load} C}\right)} = 0$$

Make sure to have MODE \rightarrow ANGLE \rightarrow RADIAN

$$\alpha = 0.843 \text{ rad}$$

Step 4 Find ΔV_{out} and $V_{out,ave}$

$$\Delta V_{out} = V_{pk} - V_{pk} \sin \alpha = 3.85V$$

$$V_{out,ave} = 15 - \frac{3.85}{2} = 13.07V$$