
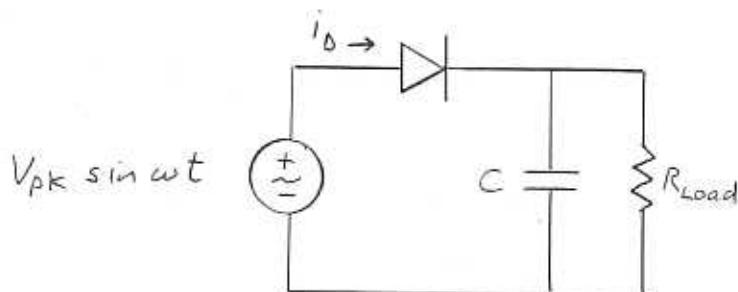


FILTERING SIMPLIFICATION

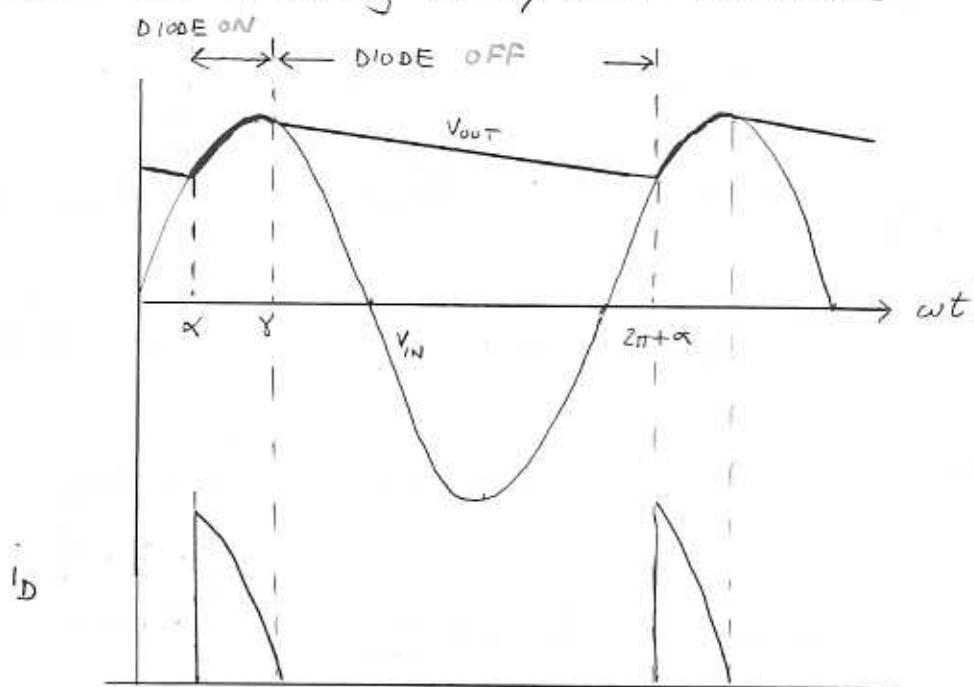(*) For the half-wave rectifier with capacitor filter



we found the following steady-state waveforms



we determined

- $\gamma = \pi - \tan^{-1}(\omega R_{load} C)$
- $\sin \alpha - \sin(\gamma) e^{-\left(\frac{2\pi + \omega - \gamma}{\omega R_{load} C}\right)} = 0$
- $\Delta V_{out} = V_{pk} - V_{pk} \sin \alpha$
- $V_{out,ave} = V_{pk} - \frac{\Delta V_{out}}{2}$

(*) These are cumbersome equations to design a filter!

Assumptions:

1. $\omega R_{\text{load}} C$ is typically big

2. Such that $\gamma \approx \pi - \frac{\pi}{2} \approx \frac{\pi}{2}$

3. If the diode does not conduct much,
then $\alpha \approx \frac{\pi}{2}$

When the diode is OFF (Fig 33-1), the output voltage is given by

$$V_{\text{out}} = (V_{pk} \sin \gamma) e^{-\left(\frac{\theta - \gamma}{\omega R_{\text{load}} C}\right)} \quad \gamma < \theta < 2\pi + \alpha$$

which hits its minimum value at $\theta = 2\pi + \alpha$

(*) Using the above assumptions, we find

$$V_{\text{out}, \text{min}} = V_{pk} \sin\left(\frac{\pi}{2}\right) e^{-\left(\frac{2\pi + \frac{\pi}{2} - \frac{\pi}{2}}{\omega R_{\text{load}} C}\right)} = V_{pk} e^{-\frac{2\pi}{\omega R_{\text{load}} C}}$$

$$(\omega R_{\text{load}} C \gg 4\pi)$$

This can be approximated by its Taylor expansion as

$$V_{\text{out}, \text{min}} \approx V_{pk} \left[1 - \frac{2\pi}{\omega R_{\text{load}} C} \right]$$

(*) The ripple is then approximated as

$$\Delta V_{\text{out}} = V_{\text{pk}} - V_{\text{out,min}} = V_{\text{pk}} \frac{2\pi}{w R_{\text{load}} C}$$

But with $w = 2\pi F$, we substitute and simplify

$$\Delta V_{\text{out}} = \frac{V_{\text{pk}}}{F R_{\text{load}} C}$$

Finally the average value is found to be

$$V_{\text{out,ave}} = V_{\text{pk}} - \frac{\Delta V_{\text{out}}}{2}$$

(*) Which gives us a couple of good "design" equations

Note 1 : The ripple is largest when R_{load} is smallest

Note 2 : The average voltage decreases with R_{load} small

Note 3 : The ripple can be made small by making C big

Ex. 1 Suppose R_{load} varies between 50Ω and 250Ω

The input voltage is 60Hz and we desire the minimum ^{average} output voltage to be 12V and the maximum ripple is 4V . Find the required C and V_{pk}

Recall

$$\Delta V_{out} \approx \frac{V_{pk}}{FR_{load} C}$$

$$V_{out,ave} \approx V_{pk} \left[1 - \frac{1}{2FR_{load} C} \right]$$

(*) Note $\Delta V_{out,max}$ occurs when $R_{load} = 50\Omega$

$V_{out,ave,min}$ occurs when $R_{load} = 250\Omega$

(*) To eliminate having to know V_{pk} form

$$\frac{\Delta V_{out,max}}{V_{out,ave,min}} = \frac{\frac{1}{FR_{load,min} C}}{\frac{2FR_{load,min} C - 1}{2FR_{load,min} C}}$$

or

$$\frac{\Delta V_{out,max}}{V_{out,ave,min}} = \frac{2}{2FR_{load,min} C - 1}$$

substituting

$$\frac{4\text{V}}{12\text{V}} = \frac{2}{2(60)(50)C - 1}$$

and solving for C gives $C = 116.7 \mu F$

which is a fair amount of capacitance!

(*) We can then solve for V_{pk} using -

$$\Delta V_{out,max} = \frac{V_{pk}}{f R_{load,min} C}$$

$$4V = \frac{V_{pk}}{60(50)(116.7 \mu F)}$$


giving

$$V_{pk} = 14V$$


Q. For a varying load, how can we minimize the ripple across the load and maintain the average voltage constant?

→ we need to know more!

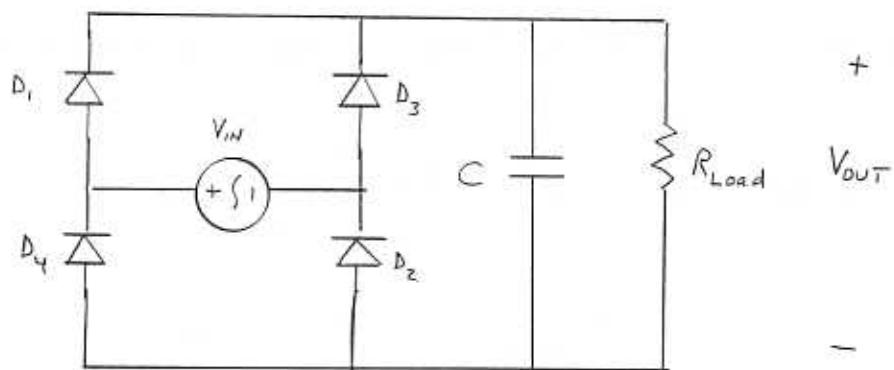FULL-WAVE RECTIFIER WITH CAPACITOR FILTER



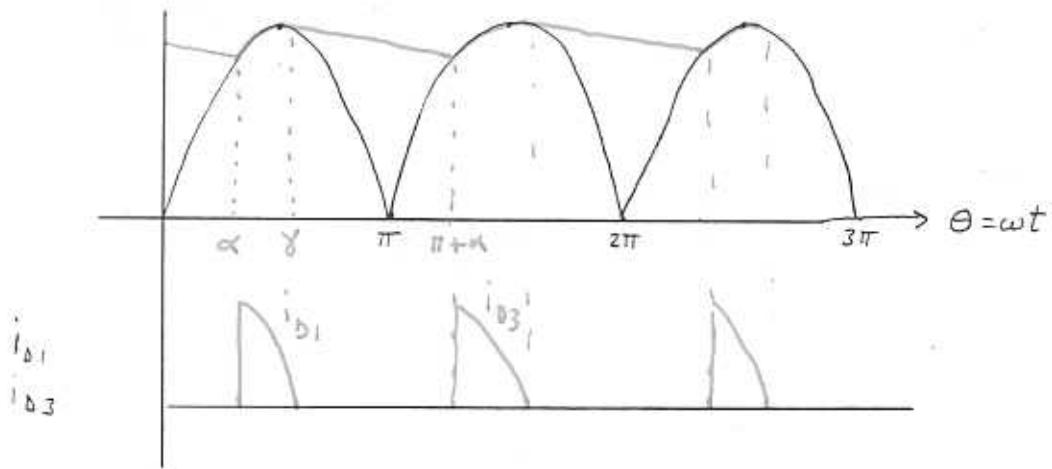(*) The resultant steady-state waveforms appear as follows



(*) The analysis follows as before (shown in the Appendix) with the following approximate results

$$\Delta V_{\text{out}} \approx \frac{V_{\text{pk}}}{2fR_{\text{load}}C}$$

$$V_{\text{out,ave}} \approx V_{\text{pk}} - \frac{\Delta V_{\text{out}}}{2}$$

$$V_{\text{out,ave}} \approx V_{\text{pk}} \left[\frac{4fR_{\text{load}}C - 1}{4fR_{\text{load}}C} \right]$$

and following some algebra

$$\frac{\Delta V_{out}}{V_{out,ave}} \approx \frac{2}{4fR_{load}C - 1}$$

(*) We notice that the ripple is reduced by a factor of 2 from the half-wave case, meaning less capacitance is required.

ex. 2 R_{load} varies between 50Ω and 250Ω . The input voltage is 60Hz. We want the minimum average output voltage to be 12V and the maximum ripple to be 4V. Find the required C and V_{pk}

→ $\Delta V_{out,max}$ occurs when $R_{load} = 50\Omega$

→ $V_{out,ave,min}$ occurs when $R_{load} = 250\Omega$

$$\frac{\Delta V_{out}}{V_{out,ave}} = \frac{4V}{12V} = \frac{2}{4(60)(50)C - 1}$$

solving for C gives

$$C = 583 \mu F$$

Substituting back into the ripple formula yields

$$\Delta V_{\text{out, max}} = \frac{V_{pk}}{2 F R_{\text{load, min}} C}$$

$$4V = \frac{V_{pk}}{Z(60)(50)(583 \times 10^{-6})}$$

which solves as $V_{pk} = 14V$

Note: to size the required secondary voltage of the transformer, you would need to account for diode drops and transformer output resistance!