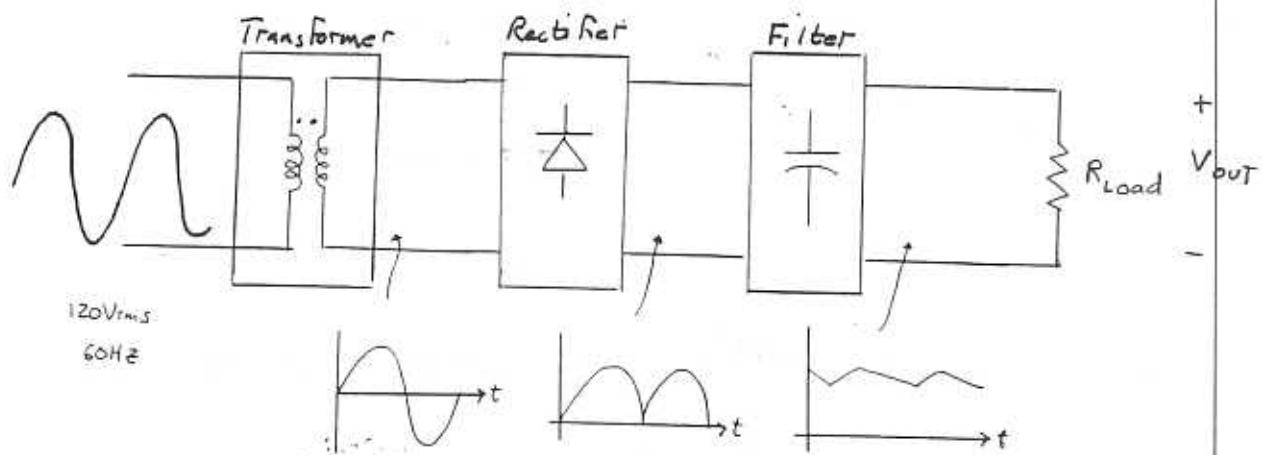


ZENER DIODE REGULATORS

(*) Thus far we have shown how to produce pulsating DC with a rectifier than how to reduce the ripple with a capacitor filter




However, many electronic loads require a more precise value of DC with even less ripple \rightarrow so we need to add a regulator


(*) The simplest (though not always the most practical) regulator is a specially-designed diode called a Zener diode.

HOW A ZENER DIODE WORKS

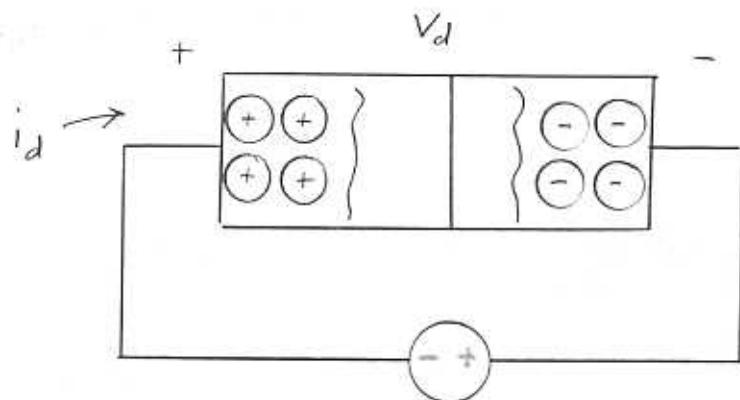
(*) Consider our "cartoon" picture of a diode with a reverse bias applied



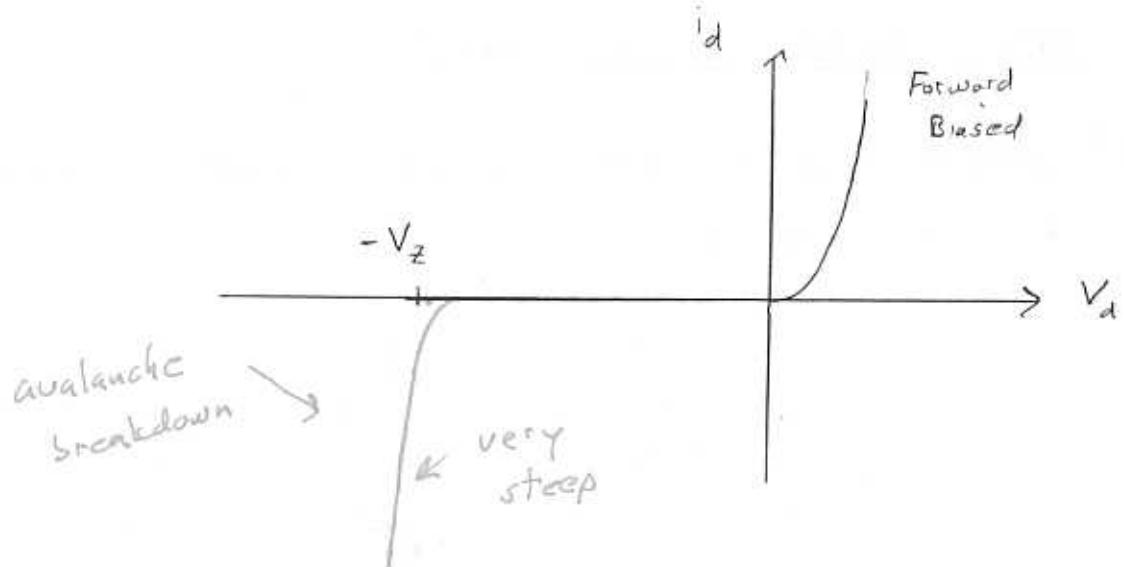- An electric field exists due to the charge separation
- For a large enough reverse voltage applied, the field is strong enough to ionize additional carriers
- Those carriers bump into other atoms, imparting energy, and ionizing them
- This "avalanche" of carriers leads to a reverse current flowing through the zener diode



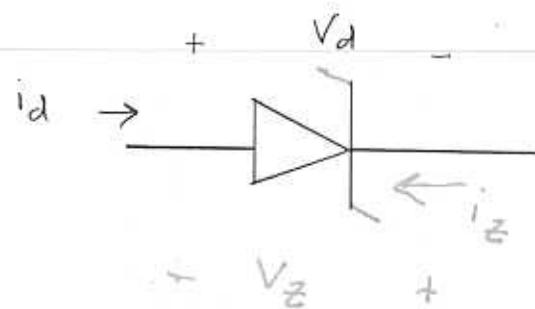
(*) The zener breakdown voltage V_z is a function of the doping of the p- and n-type material. Zener diodes can be manufactured to provide specific values of V_z . We differentiate it from a "regular Joe" diode by the circuit symbol



However since we normally operate it with reverse current and voltage, we relabel with i_z


ZENER DIODE AS REGULATOR

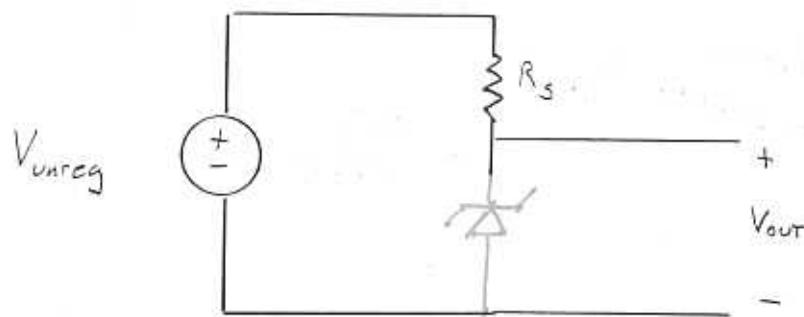- (*) Consider that we place a zener diode in the following circuit




Then based on the i-v characteristic, current will flow if $V_{unreg} > V_z$. Then $V_{out} = V_z$

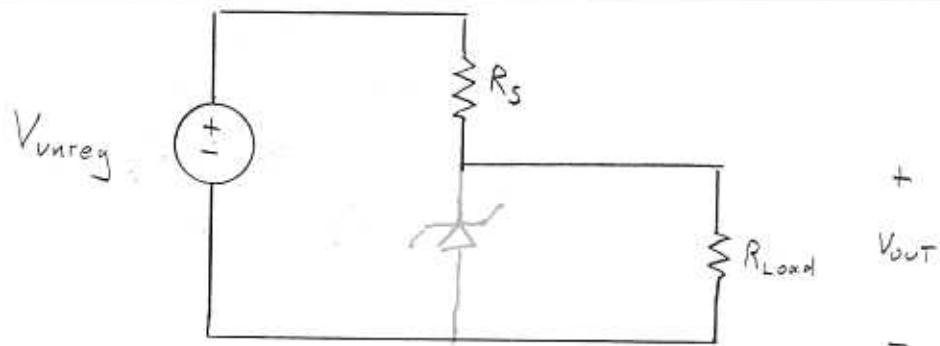- (*) If we next attach a load resistance



- Q How do we determine if the zener diode is in breakdown or not?

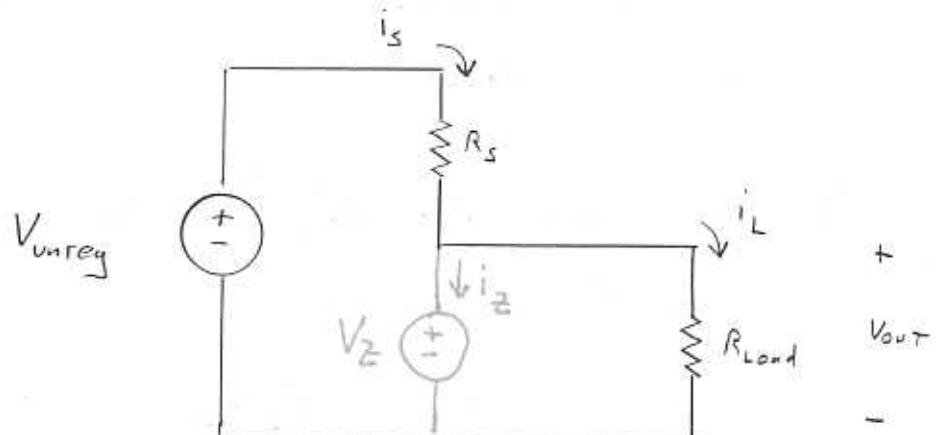A. Assume that it IS and replace it by a source voltage with value V_Z



Circuit analysis (think nodal) tells us that

$$\rightarrow i_L = \frac{V_Z}{R_{\text{load}}}$$

$$\rightarrow i_S = \frac{V_{\text{unreg}} - V_Z}{R_s}$$

and Finally KCL yields

$$\rightarrow i_Z = i_S - i_L$$

substituting


$$i_Z = \frac{V_{\text{unreg}} - V_Z}{R_s} - \frac{V_Z}{R_{\text{load}}}$$

(*) Two factors restrict the zener current :

(1) We need enough V_d to be beyond the zener "knee"

(2) We avoid too big i_d to exceed the thermal limitations \rightarrow

$$\rho_z = V_z i_z$$

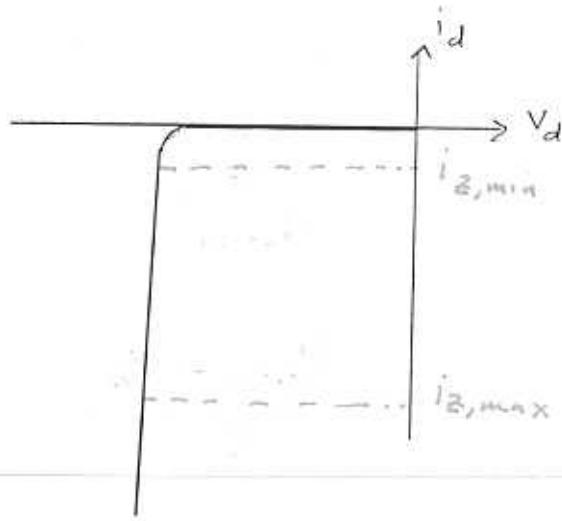


(*) Let's use the following rules of thumb to set values to each ^{safety}

$$i_{z,\max} = 0.8 \frac{\rho_z}{V_z}$$

$$i_{z,\min} = \frac{i_{z,\max}}{50}$$

(*) This will guide us in our selection of V_{bias} & R_s

HOW TO CHOOSE V_{UNREG} & R_s

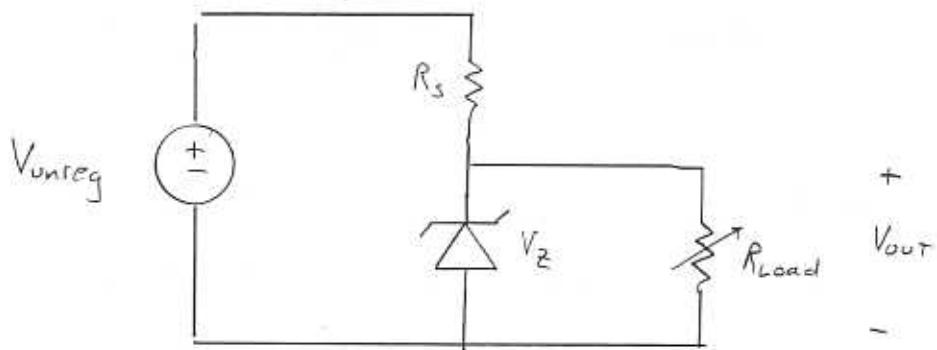

PROBLEM : (1) V_z set by desired V_{out} (^{what we want})

(2) V_{unreg} will vary between a peak
and a minimum value

(3) R_{load} varies from an open circuit
to some minimum value
(our loads turning ON & OFF)

→ We need to keep the zener in breakdown
and not blown up

$$\text{Returning to } i_z = \left(\frac{V_{unreg} - V_z}{R_s} \right) - \frac{V_z}{R_{load}}$$

- The max current occurs when

$$i_{z,\max} = \frac{V_{unreg,\max} - V_z}{R_s} - \frac{V_z}{R_{load,\min}}$$

- The min current occurs when

$$i_{z,\min} = \frac{V_{unreg,\min} - V_Z}{R_S} - \frac{V_Z}{R_{load,\min}}$$

where

$$R_{load,\min} < R_{load} < R_{load,\max}$$

- (*) This gives us 2 equations in 3 unknowns (R_S , $V_{unreg,\max}$ and $V_{unreg,\min}$). Let's probe this flexibility with an example.

ex. Suppose you choose a 0.5W, 9V zener diode for a load application where $300\Omega < R_{load} < \infty$. Determine the range of V_{unreg} for $R_S = 20\Omega$, 100Ω , 500Ω

Step 1: Establish target values for $i_{z,\min}$ and $i_{z,\max}$

$$i_{z,\max} = 0.8 \frac{P_Z}{V_Z} = 0.8 \frac{0.5W}{9V} = 44.4mA$$

$$i_{z,\min} = \frac{i_{z,\max}}{50} = 0.89mA$$

Step 2a For $R_s = 20\Omega$

$$i_{z,\min} = .89mA = \frac{V_{unreg,min} - V_z}{R_s} - \frac{V_z}{R_{load,min}} \leftarrow 300\Omega$$

$$i_{z,\max} = 44.4mA = \frac{V_{unreg,max} - V_z}{R_s} - \frac{V_z}{R_{load,max}} \leftarrow \infty$$

yields

$$V_{unreg,min} = 9.62V$$

$$V_{unreg,max} = 9.89V$$

Step 2b Repeating for $R_s = 100\Omega$ and $R_s = 500\Omega$

$$\underline{R_s = 100\Omega}$$

$$\underline{R_s = 500\Omega}$$

$$V_{unreg,min} = 12.09V$$

$$V_{unreg,min} = 24.45V$$

$$V_{unreg,max} = 13.44V$$

$$V_{unreg,max} = 31.2V$$

Step 3 What about the max power dissipated in R_s ?

$$P_{R_s,\max} = \frac{(V_{unreg,max} - V_z)^2}{R_s}$$

$$\underline{20\Omega}$$

$$\underline{100\Omega}$$

$$\underline{500\Omega}$$

$$P_{R_s,\max}$$

$$.04W$$

$$.197W$$

$$.985W$$

- If we desire smaller ripple for V_{outreg} , we need more capacitance.
- If we accept higher ripple, we need higher voltage levels and more dissipation in the resistance R_s .