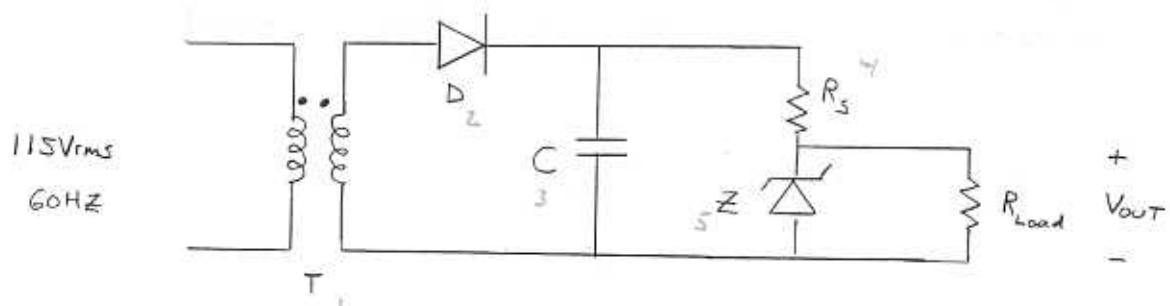


POWER SUPPLY DESIGN

(*) We can at best "tease" the topic -- especially since the zener regulator would most likely be replaced by either

1. Linear IC voltage regulator
2. Switchmode voltage regulator

(*) In our most basic topology



we have 5 components to specify. If we assume that our INPUT is wall-outlet power (115Vrms at 60Hz), then the starting point is what we want

DESIRED OUTPUT : $V_{out,min} < V_{out} < V_{out,max}$

For $R_{load,min} < R_{load} < R_{load,max}$

with the load voltage variation being as small as possible

MAIN COMPONENT SPECIFICATIONS1. Transformer

- Rated Primary Voltage
- Rated Secondary Voltage
- Rated Secondary Current
(or apparent power)

2. Rectifier Diode

- Blocking voltage (Peak Inverse Voltage)
- Average current

3. Capacitor

(Electrolytic)

↑
big values

- Rated Working Voltage
- Value
- Rated Ripple current

4. Resistor

- Value
- Power


5. Zener Diode

- Zener voltage
- Power

(*) Let's assume that our goal is to create a 6.1 V reference voltage where the attached load is anticipated to vary between $250 \Omega < R_{\text{load}} < \infty$. The starting point is choosing the transformer

Step 1: Choosing the transformer secondary voltage

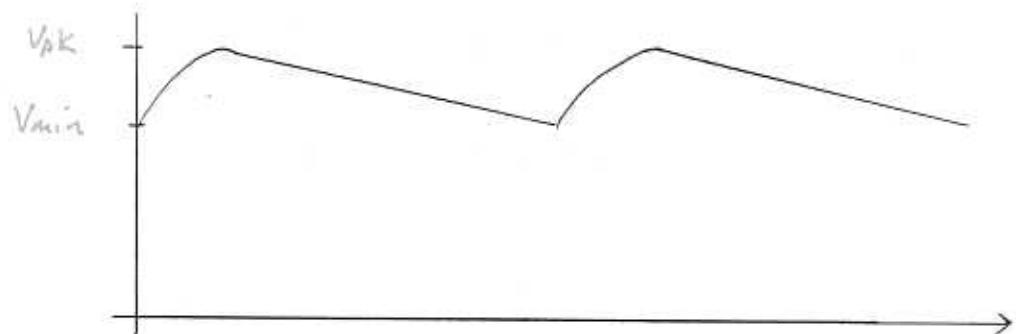(*) Recall, the filtered half-wave rectifier voltage will appear as follows



where

$$V_{pk} \approx (V_{sec,pk,NL} - 0.7 \text{ V}) \frac{R_{load}}{R_{load} + R_{TRAN}}$$

With the zener regulator in the circuit, we no longer simply have an R_{load} value to use here. Further, we generally don't know R_{TRAN} a priori, so let's ballpark this ratio as 0.96.

- (*) The transformer secondary voltages are given in RMS and are no-load values
- (*) We know that we need $V_{min} > 6.1 \text{ V}$ and $V_{pk} > V_{min}$ with the difference related to the amount of capacitance

Transformer

Rated Voltage (secondary)	Rated Current (secondary)	(Digikey) Cost	V_{pk}
12V	250mA	\$3.60	15.62
11V	270mA	\$3.60	14.26
10V	250mA	\$11.44	12.90
9V	330mA	\$3.60	11.55
8V	300mA	\$10.27	10.19
7V	230mA	\$2.98	8.83

(*) Let's choose the 115V / 10 V transformer as our first design swipe

Step 2: Specify the zener diode

(*) We find a 6.1V zener diode rated for 0.5W
Thus


$$i_{z,\max} = 0.8 \frac{P_z}{V_z} = 0.8 \frac{0.5}{6.1} = 65.5 \text{ mA}$$

$$i_{z,\min} \approx \frac{i_{z,\max}}{50} = \frac{65.5 \text{ mA}}{50} = 1.31 \text{ mA}$$

Step 3: Specify R_s

(*) Recall from last time that
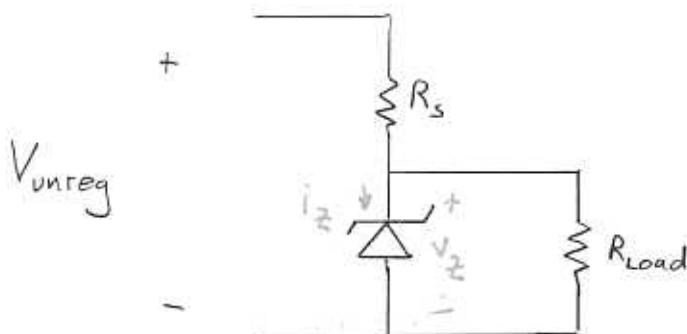
$$i_{z,\max} = \frac{(V_{unreg,max} - V_z)}{R_s} - \frac{V_z}{R_{load,\max}}$$



so

$$i_{z,\max} = 65.5 \text{ mA} = \frac{12.9 - 6.1V}{R_s} - \frac{6.1V}{\infty}$$

$$\text{solving for } R_s = 103.8 \Omega$$

This is not a standard value so we might choose $R_s = 120 \Omega$

$$(*) \text{ To get the max power } P_{R_s,\max} = \frac{(V_{unreg,max} - V_z)^2}{R_s}$$

which in our case gives 0.385 W and so we would choose at least a 0.5 W resistor

(*) We can now calculate the minimum capacitor voltage to ensure that the zener diode stays in breakdown

Recall

$$I_{Z,\min} = \frac{V_{unreg,\min} - V_Z}{R_S} - \frac{V_Z}{R_{load,\min}}$$

Substituting gives

$$1.31 \text{ mA} = \frac{V_{unreg,\min} - 6.1V}{120} - \frac{6.1V}{250}$$

which yields $V_{unreg,\min} = 9.1852$ ($> 6.1V$ ok)


(*) Therefore

$$9.1852V < V_C < 12.9V$$


and so our capacitor must achieve a peak-to-peak ripple of no more than 3.71 V, so let's be conservative and choose $\Delta V = 3V$

Step 4 : Establish the capacitance

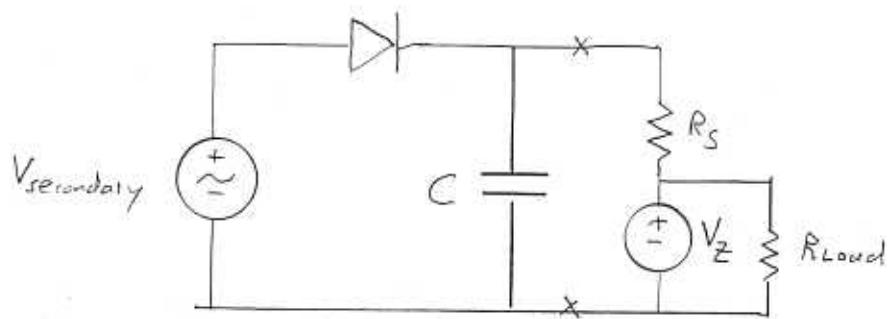
(*) When the zener is in breakdown, the circuit can be modeled as



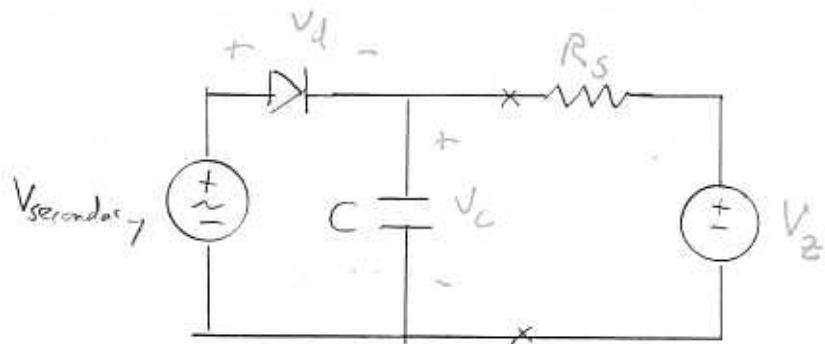The Thevenin Circuit "seen" to the right of the capacitor is



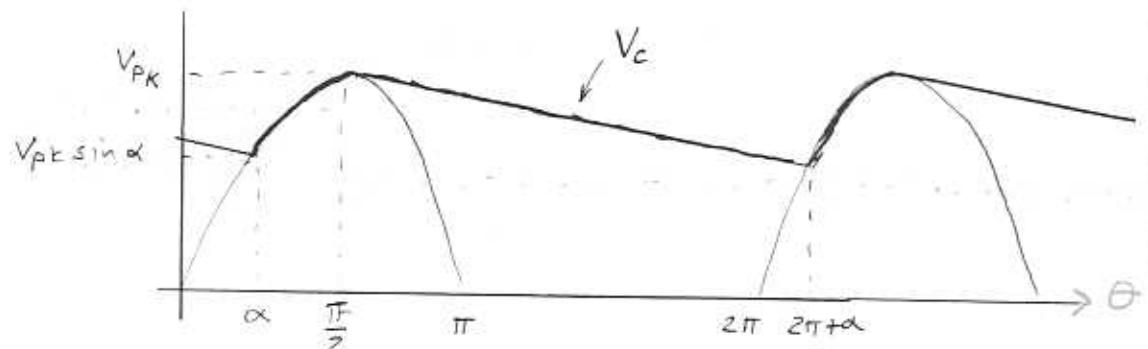(*) To simplify our life, consider that the diode conducts until $\theta = \pi/2$




(*) The diode remains OFF until

$$V_d = V_{\text{secondary}} - V_c > 0$$

where

$$- \frac{(0 - \pi_2)}{\omega r}$$

$$V_c = V_F + (V_I - V_F) e$$

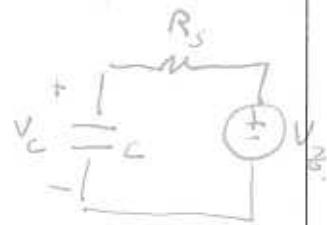

in which

$$V_I = V_{pk} \sin \frac{\pi}{2} = V_{pk} \quad V_F = V_z \quad r = R_s C$$

so

$$V_{pk} \sin(2\pi + \alpha) - V_z - (V_{pk} - V_z) e^{-\frac{(2\pi + \alpha - \pi_2)}{\omega R_s C}} = 0$$

once we know α , it follows (Figure Pg 35-7)

$$\Delta V = V_{pk} - V_{pk} \sin \alpha$$

(*) so let's work this problem in reverse.

Assume we want $\Delta V = 3V$, thus

$$\sin \alpha = \frac{12.9 - 3}{12.9} \rightarrow \alpha = 0.8748 \text{ rad}$$

substituting into the equation above gives

$$- \frac{(1.2\pi + 0.8748)}{377(120)C}$$

$$12.9 \sin(0.8748) - 6.1 - (12.9 - 6.1) e^{-\frac{377(120)C}{1.2\pi + 0.8748}} = 0$$

which has an analytical solution of

$$C = 212 \mu F$$

(*) This is not a standard value so choose

$$C = 220 \mu F$$

Step 5: Housekeeping

- a. We must also specify the rated capacitor voltage. A good rule of thumb is that it should be at least 20% higher than $V_{unreg, max}$

so $V_{crat} > 1.2 \times 12.9V = 15.48V$

/ too close


standard capacitor ratings are 16V, 25V, 63V, 100V

$220 \mu F$

25V \$0.3 per

63V \$0.64 per

100V \$1.74 per

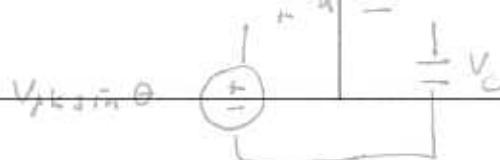

35-10

b. Rectifier Diode

(*) When the diode is OFF the max voltage it "sees" is

$$V_{d,\max} \approx -V_{pk} - V_{unreg,max}$$

In our case

$$V_{d,\max} \approx -12.9V - 12.9V = -25.8V$$

The rated voltage should be 20 % higher or 31 V. A standard voltage value is 50V

(*) The capacitor carries zero average current in the steady state so

$$i_{D,\text{ave}} = i_{R_s,\text{ave}}$$

where

$$i_{R_s,\text{ave}} \approx \frac{\left(V_{unreg,\max} + V_{unreg,\min} \right)}{2} - \frac{V_Z}{R_S}$$

$$i_{R_s,\text{ave}} \approx \frac{(12.9V + 9.19V)/2 - 6.1V}{120} = 41.2mA$$

a standard rated diode current is 1A

C. Transformer secondary current

(*) This rms value should be about twice the average diode current. In our case, $\sim 83\text{mA}$. Anything higher (which our transformer is) is fine!

Final Comments

(*) An actual power supply will need

- fuse protection
- input cord
- output terminals
- enclosure
- mounting board

but this gets us in the game! A "better" design would incorporate a linear voltage regulator. IF we need high efficiency, we go to a switchmode regulator.