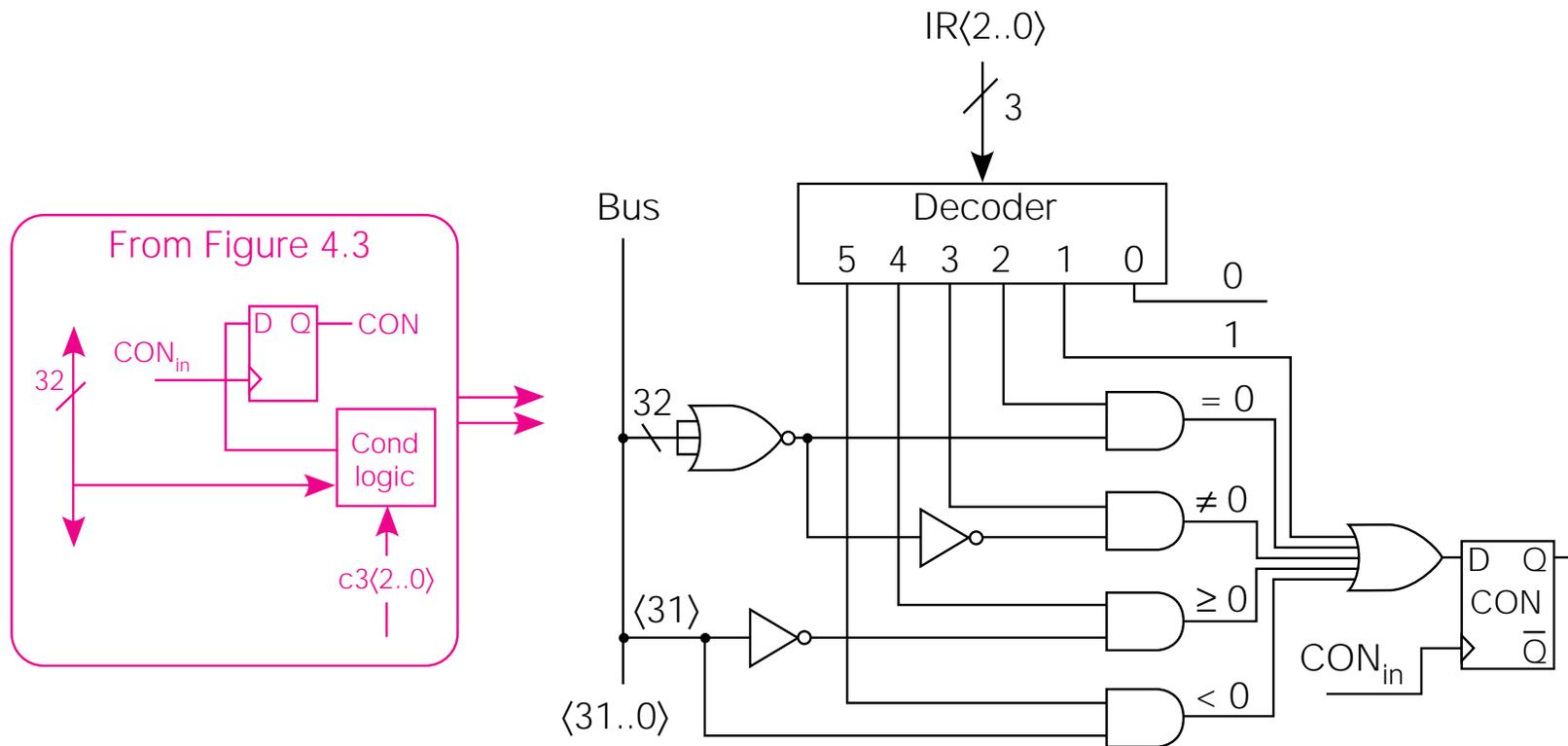


Fig 4.9 Computation of the Conditional Value CON



- **NOR gate does = 0 test of R[rc] on bus**